
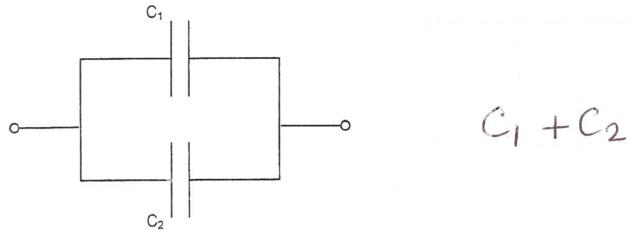


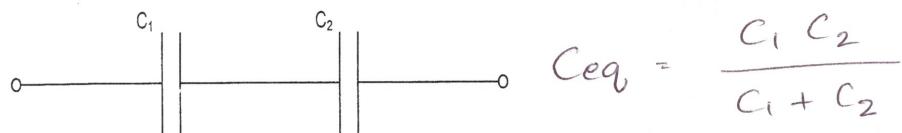
ECE 53A Fall 2007, Midterm 3, November 27, 2007, Name SOLUTIONS  
 1. Find the equivalent capacitance between the two terminals in each of the three networks.



$$C_1 + C_2$$




$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

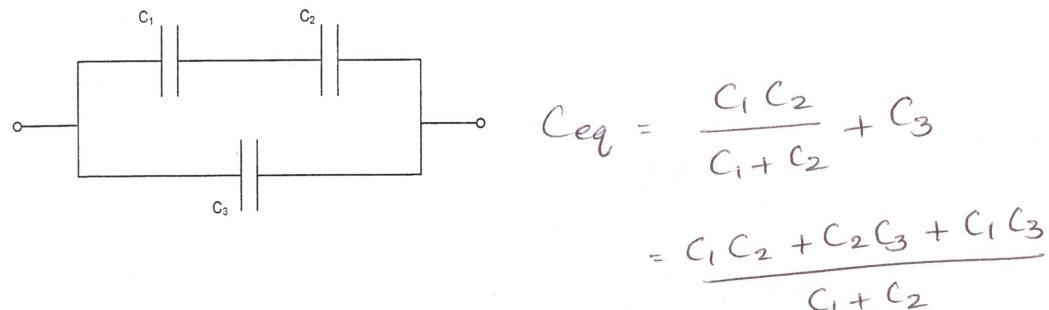

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} + C_3$$

$$= \frac{C_1 C_2 + C_2 C_3 + C_1 C_3}{C_1 + C_2}$$

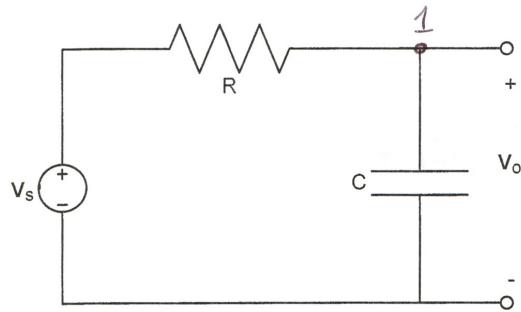2. In the following circuit, the voltage source  $v_s$  is a step function  $u(t)$ , i.e.  $u(t)=0$  for  $t<0$ ,  $u(t)=1$  for  $t\geq 0$ . At time  $t=0$ , output voltage  $v_o=0$ . Derive the function  $v_o(t)$  for  $t\geq 0$ .



Using KCL at node 1,

$$\frac{v_s - v_o}{R} = C \frac{dv_o}{dt}$$

$$CR \frac{dv_o}{dt} + v_o = v_s$$

$$\therefore v_o = v_s (1 - e^{-t/CR}) = 1 (1 - e^{-t/CR}), \text{ when } t \geq 0$$

=====

Method 2

$$v_o = b(1 - e^{-t/a})$$




$$v_o = v_s$$

$$a = \frac{R}{C}$$

$$a = CR$$

$$\therefore v_o = v_s (1 - e^{-t/CR})$$

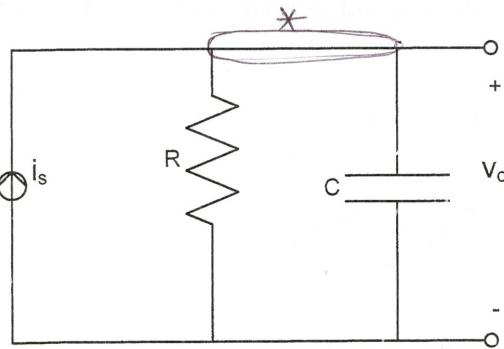3. In the following circuit, the current source  $i_s$  is a step function  $u(t)$ , i.e.  $u(t)=0$  for  $t<0$ ,  $u(t)=1$  for  $t\geq 0$ . At time  $t=0$ , output voltage  $v_o=0$ . Derive the function  $v_o(t)$  for  $t\geq 0$ .



Applying KCL at node \*,

$$i_s = \frac{v_o}{R} + C \frac{dv_o}{dt}$$

$$i_s R = v_o + CR \frac{dv_o}{dt}$$

$$\therefore v_o = i_s R (1 - e^{-t/CR}), \text{ when } t \geq 0$$

$$= R (1 - e^{-t/CR}) \because \text{when } t \geq 0, i_s = 1A$$

### Method 2


$$b = i_s R \quad i_s$$

$$a = RC$$

$$\therefore v_o = i_s R (1 - e^{-t/CR})$$

$$= R (1 - e^{-t/CR})$$

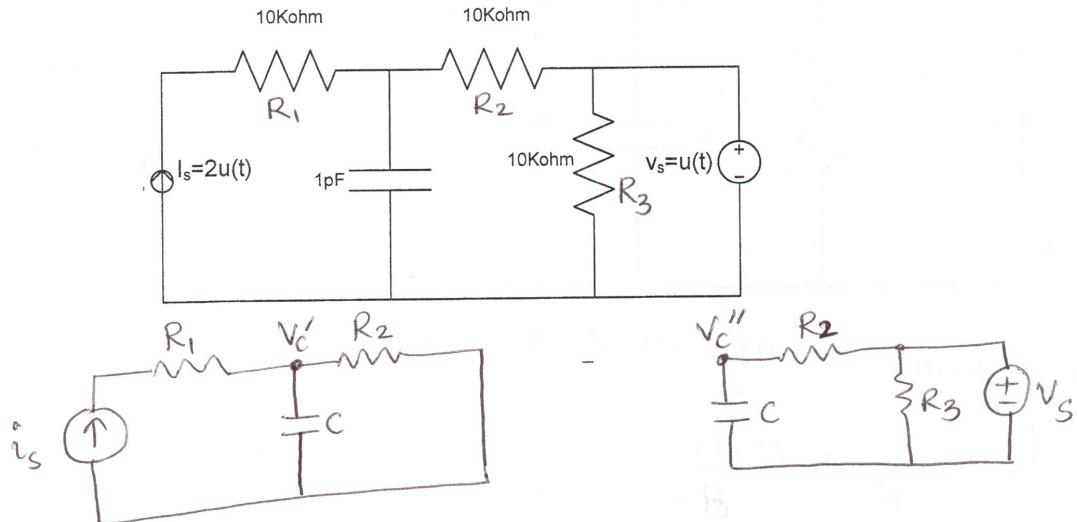4. In the following circuit, the voltage source  $v_s = u(t)$ , the current source  $i_s = 2u(t)$ , where  $u(t)$  is a step function, i.e.  $u(t) = 0$  for  $t < 0$ ,  $u(t) = 1$  for  $t \geq 0$ . Initially, the voltage across the capacitor is reset, i.e.  $v_c = 0$ . Find an expression of capacitor voltage  $v_c(t)$  for  $t \geq 0$ .



$$C \frac{dv'_c}{dt} + \frac{v'_c}{R_2} = i_s \rightarrow \textcircled{1} \quad C \frac{dv''_c}{dt} = \frac{v_s - v''_c}{R_2} \rightarrow \textcircled{2}$$

$\textcircled{1} + \textcircled{2}$  (superposition principle)


$$C \left( \frac{dv'_c}{dt} + \frac{dv''_c}{dt} \right) + \frac{v'_c}{R_2} = i_s + \frac{v_s}{R_2} - \frac{v''_c}{R_2}$$

$$C \frac{dV_c}{dt} + \frac{V_c}{R_2} = i_s + \frac{V_s}{R_2} \quad \left( \text{because } \frac{dv'_c}{dt} + \frac{dv''_c}{dt} = \frac{d(V_c' + V_c'')}{dt} \right)$$

$$CR_2 \frac{dV_c}{dt} + V_c = i_s R_2 + V_s$$

$$\Rightarrow V_c = (i_s R_2 + V_s) \left( 1 - e^{-t/(CR_2)} \right) = (20 \text{ kV} + 1 \text{ V}) \left( 1 - \underline{\underline{e^{-t/10 \text{ ns}}}} \right)$$

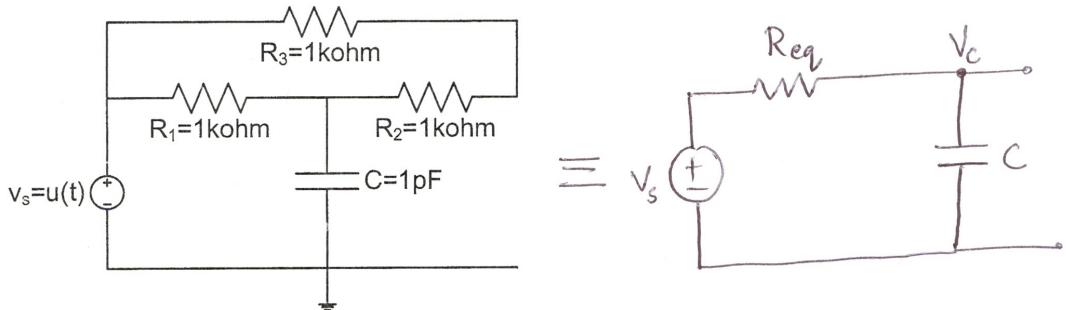5. Given a RC-network shown below, the voltage source  $v_s = u(t)$  is a step input, i.e.  $u(t) = 0$  for  $t < 0$ ,  $u(t) = 1$  for  $t \geq 0$ .



a. Derive the differential equation for the capacitor voltage,  $v_c(t)$ , given the initial condition that  $v_c(0) = 0\text{V}$ .

$$R_{eq} = (R_2 + R_3) \parallel R_1 = \frac{2\text{k}\Omega \times 1\text{k}\Omega}{3\text{k}\Omega} = \frac{2}{3}\text{k}\Omega$$

$$\frac{v_s - v_c}{R_{eq}} = C \frac{dv_c}{dt} \Rightarrow C R_{eq} \frac{dv_c}{dt} + v_c = v_s$$

$$\left(\frac{2}{3} \times 10^{-9}\right) \frac{dv_c}{dt} + v_c = 1$$

b. Solve for capacitor voltage  $v_c(t)$ . What is the time constant for this network?

$$\begin{aligned} v_c(t) &= v_s \left(1 - e^{-t/\tau}\right) \\ &= 1 \left(1 - e^{-t/(2/3 \times 10^{-9})}\right) \text{ V} \end{aligned}$$

$$\text{Time constant, } \tau = \frac{2}{3} \text{ ns}$$