

CSE 141 – Computer Architecture Spring 2005

Lecture 6 Single Cycle CPU Part 1 April 13, 2005

Pramod V. Argade

CSE141: Introduction to Computer Architecture

Instructor: Pramod V. Argade (p2argade@cs.ucsd.edu)
Office Hour:
Mon. 5:00 - 6:00 PM (AP&M 5218)

TAs:

Baris Arslan: barslan@cs.ucsd.edu
Chris Roedel: croedel@cs.ucsd.edu
Raid Ayoub: rayoub@cs.ucsd.edu
Leo Porter: leporter@cs.ucsd.edu

Textbook: Computer Organization & Design
The Hardware Software Interface, 3rd Edition.
Authors: Patterson and Hennessy

Web-page: <http://www.cse.ucsd.edu/classes/sp05/cse141>

Announcements

- **Reading Assignment**

- Chapter 3. Arithmetic for Computers
Sections B6, In More Depth 3.23, 3.4 - 3.8
- Chapter 5. The Processor: Datapath and Control
Sections 5.1 - 5.3, Appendix B7 - B11

- **Homework 2: Due Mon., April 18 in class**

- 3.13, 3.18, 3.19, 3.27, 3.30, 3.35, 3.38
 Multiply -11×-10 using Booth's algorithm and 5-bit 2-complement representation of multiplicand and multiplier.
 5.1

- **Quiz**

When: Mon., April 18th, First 10 minutes of the class


Topic: Arithmetic for Computers, Chapter 3 **Need:** Paper, pen

Course Schedule

Lecture #	Date	Day	Lecture Topic	Quiz Topic	Homework Due
1	3/28	Monday	Introduction, Ch. 1	-	-
2	3/30	Wednesday	Performance, Ch. 4	-	-
3	4/4	Monday	ISA, Ch. 2	Performance	#1
4	4/6	Wednesday	Arithmetic, Ch. 3	-	-
5	4/11	Monday	Arithmetic, Ch. 3	ISA	#2
6	4/13	Wednesday	Single cycle CPU, Ch. 5	-	-
7	4/18	Monday	Single cycle CPU, Ch. 5	Arithmetic	#3
8	4/20	Wednesday	Multi-cycle CPU, Ch. 5	-	-
9	4/25	Monday	Multi-cycle CPU, Ch. 5	Single Cycle CPU	#4
10	4/27	Wednesday	Review for the Midterm	-	-
	5/2	Monday	Mid-term Exam	-	-
11	5/4	Wednesday	Exceptions, Ch. 5 and Pipelining, Ch. 6	-	-
12	5/9	Monday	Pipelining, Ch. 6	-	-
13	5/11	Wednesday	Data and control hazards, Ch. 6	-	-
14	5/16	Monday	Data and control hazards, Ch. 6	Pipeline Hazards	#5
15	5/18	Wednesday	Memory & cache design, Ch. 7	-	-
16	5/23	Monday	Memory & cache design, Ch. 7	Cache	#6
17	5/25	Wednesday	Virtual Memory & cache design, Ch. 7	-	-
No Class	5/30	Monday	Memorial Day Holiday	-	-
18	6/1	Wednesday	Course Review	-	-
	6/10	Friday	Final Exam	-	-


Datapath and Control Design

 - The Five Classic Components of a Computer




Two Types of Logic Components

 - Combinational
 - Elements that operate on data values
 - Produces same output if given same inputs




 - State Elements
 - Contains internal storage
 - May produce different output if given same inputs
 - Clock is used to determine when a state element(s) should be written



Clock


 
- Clock is a free running signal
 - Fixed cycle time (period)
 - Frequency = $1/(\text{cycle time})$
 - Duty Cycle: $(\% \text{ high})/(\% \text{ low})$, e.g. 50/50 Duty Cycle below
 - Jitter: Uncertainty/wobble in rising or falling edge



Storage Elements



D Latch

  - Two inputs:
 - the data value to be stored (D)
 - the clock signal (C) indicating when to read & store D
- Two outputs:
 - the value of the internal state (Q) and its complement




Falling edge triggered D flip-flop

- Output changes only on the clock edge

  


Edge-triggered Clocking

 - Values stored in the machine are updated on a clock edge
 - The clock edge can be either rising or falling



- By default a state element is written every clock edge
 - An explicit write control signal is required otherwise.
- Edge triggered methodology allows, in the same clock cycle to:
 - read the contents of a register
 - send the value through some combinational logic, and
 - write the contents of the same or another register
- Possible to have the same state element as input and output


CPU: Clocking

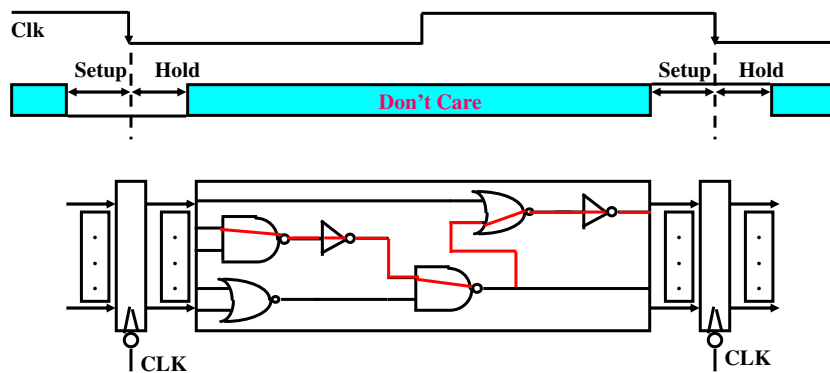

- All storage elements are clocked by the same clock edge


Register: A Storage Element

 - Similar to the D Flip Flop except
 - N-bit input and output
 - Write Enable input
- Write Enable:
 - 0: Data Out will not change
 - 1: Data Out will become Data In (on the clock edge)



Register File

 - Register File consists of (32) registers:
 - Two 32-bit output busses: busA and busB
 - One 32-bit input bus: busW
- Register is selected by:
 - RA selects the register to put on busA
 - RB selects the register to put on busB
 - RW selects the register to be written via busW when Write Enable is 1
- Clock input (CLK)



Memory

- Memory


- One input bus: Data In
- One output bus: Data Out

- Memory word is selected by:


- Address selects the word to put on Data Out
- Write Enable = 1: address selects the memory word to be written via the Data In bus

- Clock input (CLK)

 - The CLK input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:
 - > Address valid => Data Out valid after "access time."



Basic 4 x 2 Static RAM

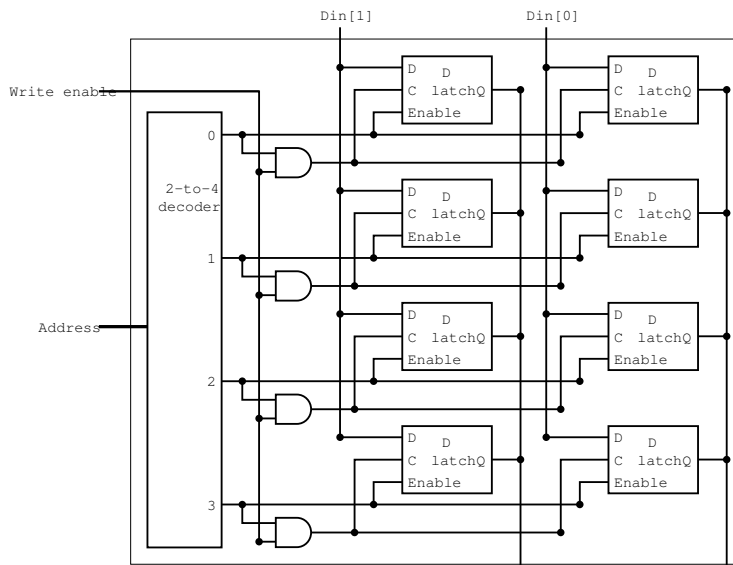

Register Transfer Language (RTL)

- Mechanism for describing the movement and manipulation of data between storage elements.
- Example:
 - $R[rd] \leftarrow R[rs] + R[rt]$
 - $PC \leftarrow PC + 4$
 - $R[rt] \leftarrow Mem[R[rs] + immediate]$


A Simple Implementation of MIPS CPU

- Simplified to contain only:
 - Memory-reference instructions: lw, sw
 - Arithmetic-logical instructions: add, sub, and, or, slt
 - Control flow instructions: beq, j
- Execution Time = Instructions * CPI * Cycle Time
- Processor design (datapath and control) will determine:
 - Clock cycle time
 - Clock cycles per instruction
- We will design a single cycle processor:
 - Advantage: One clock cycle per instruction
 - Disadvantage: long cycle time

Arithmetic Instructions (R-Type)

- ADD, SUB, AND, OR, SLT
- Example

add rd, rs, rt

 


Load/Store Instructions (I-Type)

- LW, SW
- Examples


lw rt, rs, imm16

sw rt, rs, imm16

 


Branch (I-Type)

- Beq
- Example
beq rs, rt, imm16

 


Jump (J-Type)

- J
- Example
J Label

 

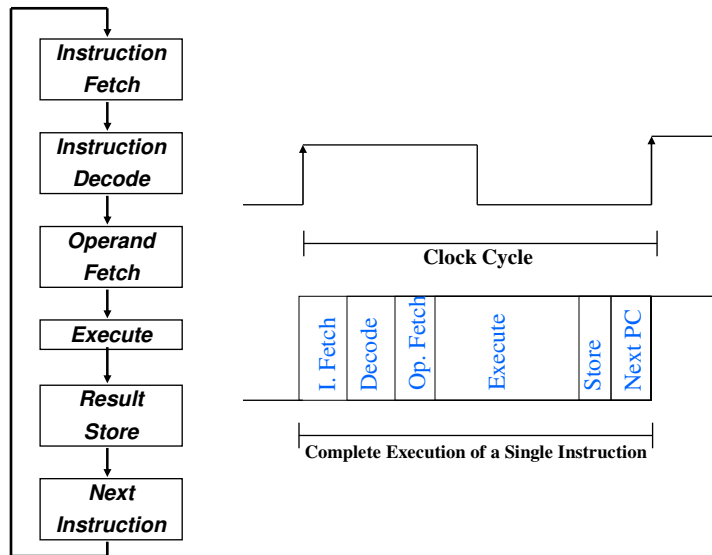Single Cycle Implementation \Rightarrow Datapath and Control




Components Required to implement the ISA

- Next PC generation
 - Add 4 or extended 16-bit immediate to PC
- Memory
 - Instruction read
 - Data read/write
- Registers (32 x 32-bit)
 - Read register r_s
 - Read register r_t
 - Write register r_t or r_d
- Sign extend immediate operand
- ALU to operate on the operands


Datapath

- Abstract / Simplified View:

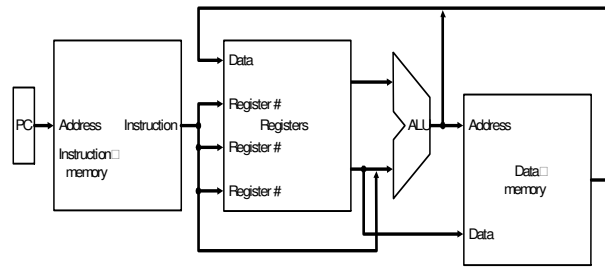



CPU: Instruction Fetch

 - RTL version of the instruction fetch step:
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump: $\text{PC} \leftarrow \text{“something else”}$



CPU: Register-Register Operations (Add, Subtract etc.)

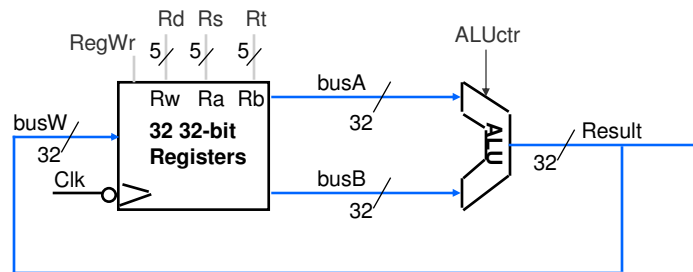 - $R[rd] \leftarrow R[rs] \text{ op } R[rt]$ Example: `addU rd, rs, rt`
 - Ra, Rb, and Rw come from instruction's rs, rt, and rd fields
 - ALUctr and RegWr: control logic after decoding the instruction





Pramod Argade

UCSD CSE 141, Spring 2005

Slide 6-25

CPU: Load Operations

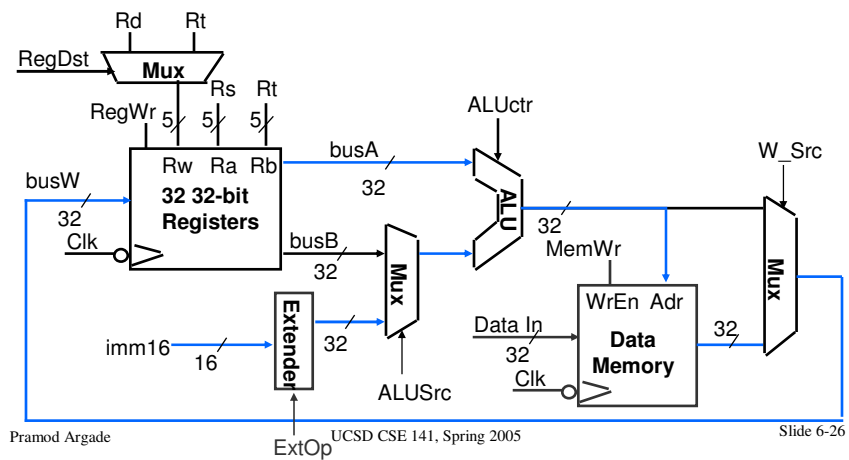 - $R[rt] \leftarrow \text{Mem}[R[rs] + \text{SignExt}[\text{imm16}]]$ Example: `lw rt, rs, imm16`





Pramod Argade

UCSD CSE 141, Spring 2005

Slide 6-26



CPU: Store Operations

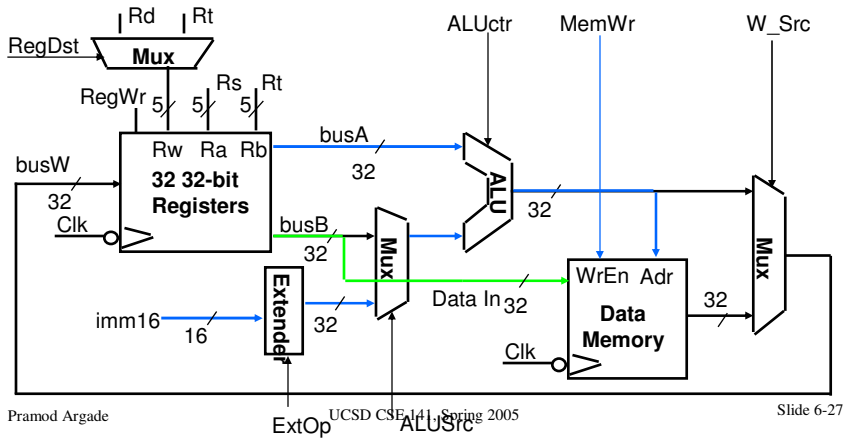 - $\text{Mem}[\text{R}[\text{rs}] + \text{SignExt}[\text{imm16}]] \leftarrow \text{R}[\text{rt}]$ Example: `sw rt, rs, imm16`



CPU: Datapath for Branching

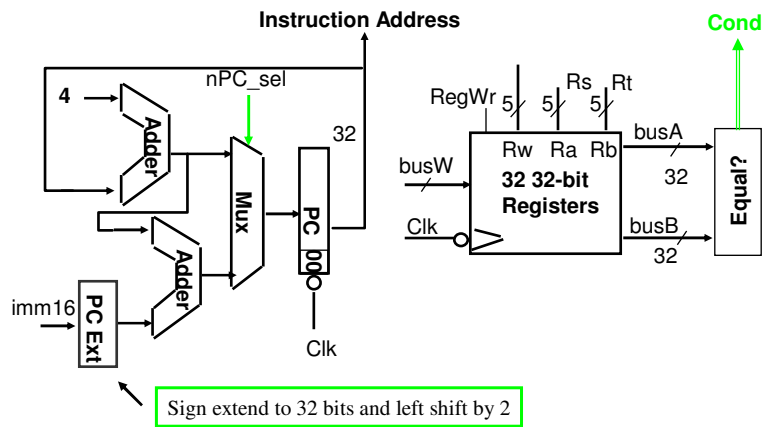 - `beq rs, rt, imm16` Datapath generates condition (equal)




CPU: Binary arithmetic for PC

- In theory, the PC is a 32-bit byte address into the instruction memory:
 - Sequential operation: $PC\langle 31:0 \rangle = PC\langle 31:0 \rangle + 4$
 - Branch operation: $PC\langle 31:0 \rangle = PC\langle 31:0 \rangle + 4 + \text{SignExt}[\text{Imm16}] * 4$
- The magic number “4” always comes up because:
 - The 32-bit PC is a byte address
 - And all our instructions are 4 bytes (32 bits) long
- In other words:
 - The 2 LSBs of the 32-bit PC are always zeros
 - There is no reason to have hardware to keep the 2 LSBs
- In practice, we can simplify the hardware by using a 30-bit $PC\langle 31:2 \rangle$:
 - Sequential operation: $PC\langle 31:2 \rangle = PC\langle 31:2 \rangle + 1$
 - Branch operation: $PC\langle 31:2 \rangle = PC\langle 31:2 \rangle + 1 + \text{SignExt}[\text{Imm16}]$
 - In either case: Instruction Memory Address = $PC\langle 31:2 \rangle$ concat “00”

Single Cycle Implementation

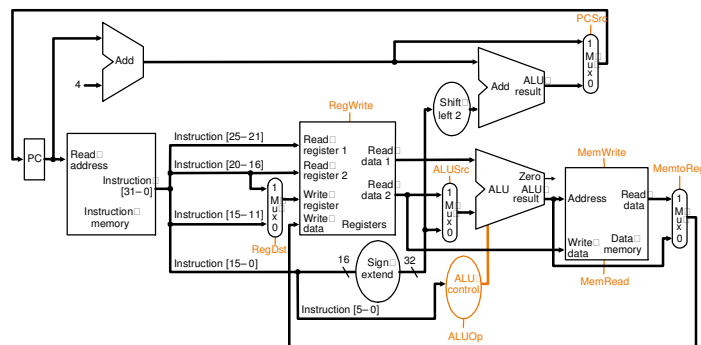- Putting it all together
 - Supports Arithmetic, Load/Store and Branch instructions



Announcements

- **Reading Assignment**

- Chapter 3. Arithmetic for Computers
Sections B6, In More Depth 3.23, 3.4 - 3.8
- Chapter 5. The Processor: Datapath and Control
Sections 5.1 - 5.3, Appendix B7 - B11

- **Homework 2: Due Mon., April 18 in class**

3.13, 3.18, 3.19, 3.27, 3.30, 3.35, 3.38

Multiply -11×-10 using Booth's algorithm and 5-bit 2-complement representation of multiplicand and multiplier.

5.1,

- **Quiz**

When: Mon., April 18th, First 10 minutes of the class

Topic: Arithmetic for Computers, Chapter 3 **Need:** Paper, pen