

First Name:

Last Name:


PID:

4. (10 points)


An FSM is defined by the following state transition table.

Present State $Q_1 Q_0$	Next state		Output Z
	$W=0$ $Q_1^+ Q_0^+$	$W=1$ $Q_1^+ Q_0^+$	
00	10	11	0
01	00	00	0
10	10	00	0
11	10	00	1

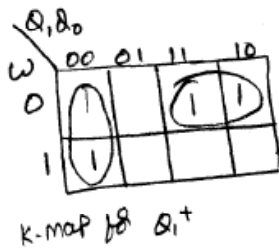(a) Derive the next state and output equations.


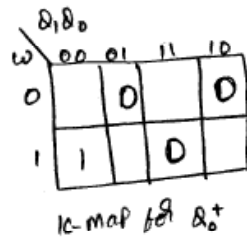
$$Q_1^+ = \bar{Q}_1 \bar{Q}_0 + Q_1 \bar{W}$$



$$Q_0^+ = \bar{Q}_1 \bar{Q}_0 W$$

→ Since this is a Moore machine, output depends only on current state


$$Z = \underline{\underline{Q_1 Q_0}}$$

First Name:

Last Name:

PID:

5. Consider the following state diagram:

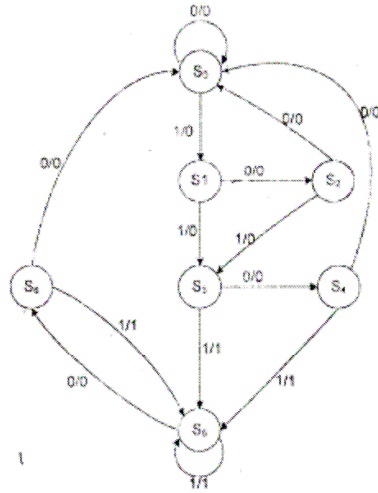

(a) Fill out the blanks in the state table

Present State	Next State		Output Y	
	A = 0	A = 1	A = 0	A = 1
S ₀	S ₀	S ₁	0	0
S ₁	S ₂	S ₃	0	0
S ₂	S ₀	S ₃	0	0
S ₃	S ₄	S ₅	0	1
S ₄	S ₀	S ₅	0	1
S ₅	S ₆	S ₅	0	1
S ₆	S ₀	S ₅	0	1

First Name: _____

Last Name: _____

PID: _____

(b) Label the rows and columns with states, and then fill the implication table.

S_1	S_0-S_2 S_1-S_3					
S_2	S_0-S_0 S_1-S_3	S_2-S_0 S_3-S_3				
S_3	X	X	X			
S_4	X	X	X	S_4-S_0 S_5-S_5		
S_5	X	X	X	S_4-S_6 S_5-S_5	S_0-S_6 S_5-S_5	
S_6	X	X	X	S_4-S_0 S_5-S_5	S_0-S_0 S_5-S_5	S_0-S_6 S_5-S_5
	S_0	S_1	S_2	S_3	S_4	S_5

(c) List all the original states, grouped into maximal classes of compatibility. Use only as many groups as necessary

$g_0 = \underline{S_0 /}$

$g_1 = \underline{S_1 /}$

$g_2 = \underline{S_2 /}$

$g_3 = \underline{\{S_3, S_5\} /}$

$g_4 = \underline{\{S_4, S_6\} /}$

$g_5 = \underline{\quad /}$

$g_6 = \underline{\quad /}$

First Name:

Last Name:


PID:

(d) Show the minimized state transition and output table. Fill in only as many rows of the table as necessary.


Present State	Next State		Output Y	
	A = 0	A = 1	A = 0	A = 1
g_0	g_0	g_1	0	0
g_1	g_2	g_3	0	0
g_2	g_0	g_3	0	0
g_3	g_4	g_3	0	1
g_4	g_0	g_3	0	1
g_5				
g_6				

First Name: _____ Last Name: _____ PID: _____

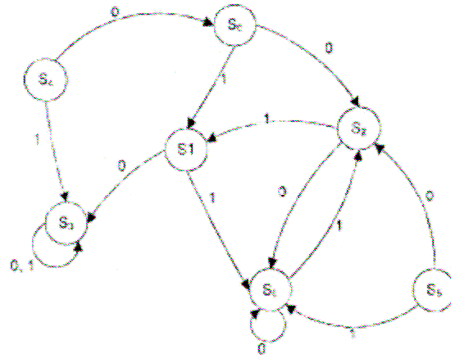6. Consider the finite state machine shown below.



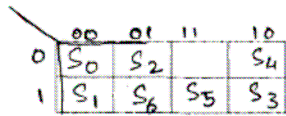Implement a state assignment using the minimum bit-change heuristic. Show your result in both K-map and the table.



State Name	Assignment		
	Q_2	Q_1	Q_0
S_0	0	0	0
S_1	0	0	1
S_2	0	1	0
S_3	1	0	1
S_4	1	0	0
S_5	1	1	0
S_6	0	1	1

