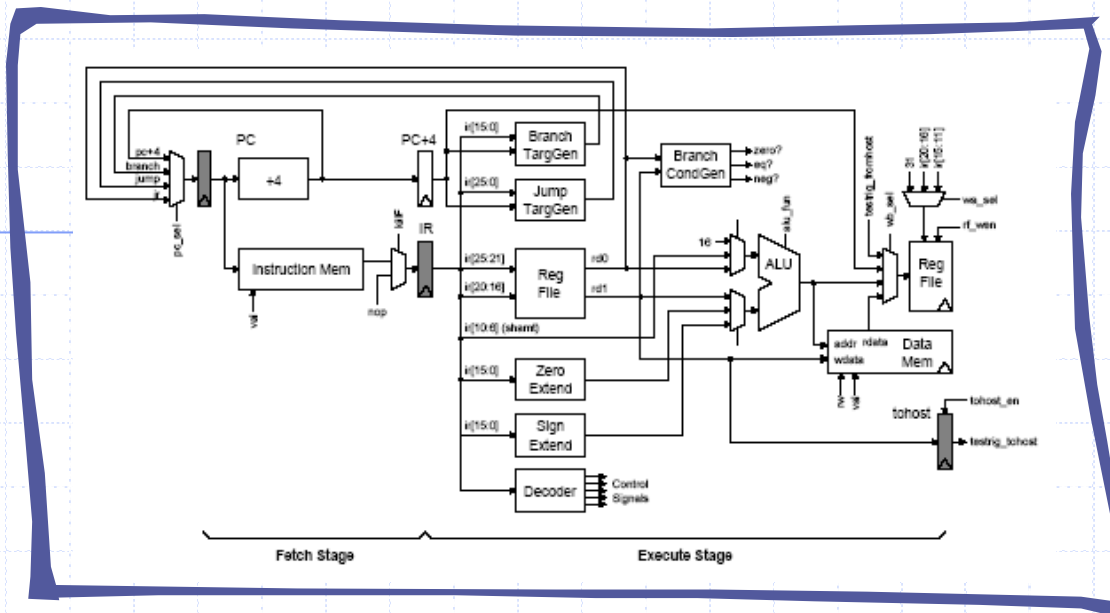


# Verilog 2 - Design Examples



6.375 Complex Digital Systems  
Arvind  
February 9, 2009

Courtesy of Arvind <http://csg.csail.mit.edu/6.375/>

# Verilog can be used at several levels

High-Level Behavioral



Register Transfer Level



Gate Level

*A common approach is to use C/C++ for initial behavioral modeling, and for building test rigs*

automatic tools to synthesize a low-level gate-level model

# Writing synthesizable Verilog: Combinational logic

- ◆ Use continuous assignments (**assign**)

```
assign C_in = B_out + 1;
```

- ◆ Use **always@(\*)** blocks with blocking assignments (=)

```
always @(*)  
begin  
    out = 2'd0;  
    if (in1 == 1)  
        out = 2'd1;  
    else if (in2 == 1)  
        out = 2'd2;  
end
```

**always blocks allow more expressive control structures, though not all will synthesize**

**default**

- ◆ Every variable should have a default value to avoid inadvertent introduction of latches
- ◆ Do not assign the same variable from more than one always block – ill defined semantics

# Writing synthesizable Verilog: Sequential logic

- ◆ Use `always @(posedge clk)` and non-blocking assignments (`<=`)


```
always @(posedge clk )  
    C_out <= C_in;
```

- ◆ Use only positive-edge triggered flip-flops for state
- ◆ Do not assign the same variable from more than one `always` block – ill defined semantics
- ◆ Do not mix blocking and non-blocking assignments
- ◆ Only leaf modules should have functionality; use higher-level modules only for wiring together sub-modules
 
# An example

```
wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @( posedge clk )
begin
    A_out <= A_in;
    B_out <= A_out + 1;
    C_out <= B_out + 1;
end
```



The order of non-blocking assignments does not matter!

The effect of non-blocking assignments is not visible until the end of the "simulation tick"

# Another way

```
wire A_in, B_in, C_in;  
reg  A_out, B_out, C_out;
```

```
always @( posedge clk )  
begin
```

```
    A_out <= A_in;
```


```
    B_out <= B_in;
```

```
    C_out <= C_in;
```

```
end
```

```
assign B_in = A_out + 1;
```

```
assign C_in = B_out + 1;
```

 


**B\_in and C\_in are  
evaluated as needed**
 
# An example: Some wrong solutions

```
wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @( posedge clk )
begin
    A_out <= A_in;
    B_out <= B_in;
    C_out <= C_in;
    assign B_in = A_out + 1;
    assign C_in = B_out + 1;
end
```



Syntactically illegal

# Another style – multiple always blocks

```
wire A_in, B_in, C_in;  
reg  A_out, B_out, C_out;
```


```
always @( posedge clk )  
    A_out <= A_in;
```

```
assign B_in = A_out + 1;
```

```
always @( posedge clk )  
    B_out <= B_in;
```

```
assign C_in = B_out + 1;
```
 
```
always @( posedge clk )  
    C_out <= C_in;
```



Does it have the same functionality?

*Yes. But why?*

Need to understand something about Verilog execution semantics

# Yet another style – blocking assignments

```
wire A_in, B_in, C_in;  
reg A_out, B_out, C_out;
```

```
always @(posedge clk)  
begin
```

```
1 A_out = A_in;
```


```
3 B_out = B_in;
```

```
5 C_out = C_in;
```

```
end
```


```
2 assign B_in = A_out + 1;
```

```
4 assign C_in = B_out + 1;
```

 

Does it have the same functionality?

*Not even close!*

 

# Verilog execution semantics

- Driven by simulation
- Explained using event queues

# Execution semantics of Verilog - 1

```
wire A_in, B_in, C_in;  
reg A_out, B_out, C_out;
```


```
always @(posedge clk )  
  A_out <= A_in;
```

```
assign B_in = A_out + 1;
```

```
always @(posedge clk )  
  B_out <= B_in;
```

```
assign C_in = B_out + 1;
```
 
```
always @(posedge clk )  
  C_out <= C_in;
```



On clock edge all those events which are sensitive to the clock are added to the active event queue in any order!

# Execution semantics of Verilog - 2

```
wire A_in, B_in, C_in;  
reg A_out, B_out, C_out;
```

```
always @(posedge clk )  
    A_out <= A_in;
```



```
assign B_in = A_out + 1;
```



```
always @(posedge clk )  
    B_out <= B_in;
```




```
assign C_in = B_out + 1;
```



```
always @(posedge clk )  
    C_out <= C_in;
```



Active Event Queue

 

A evaluates and as a consequence 1 is added to the event queue

# Execution semantics of Verilog -3

```
wire A_in, B_in, C_in;  
reg A_out, B_out, C_out;
```

```
always @(posedge clk )  
    A_out <= A_in;
```



```
assign B_in = A_out + 1;
```



```
always @(posedge clk )  
    B_out <= B_in;
```




```
assign C_in = B_out + 1;
```



```
always @(posedge clk )  
    C_out <= C_in;
```



Active Event Queue

 

Event queue is emptied before we go to next clock cycle

# Non-blocking assignment

- ◆ Within a “simulation tick” all RHS variables are read first and all the LHS variables are updated together at the end of the tick
- ◆ Consequently, two event queues have to be maintained – one keeps the computations to be performed while the other keeps the variables to be updated

# Non-blocking assignments require two event queues

```
wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;
```

```
always @(posedge clk)
  A_out <= A_in;
```

A

```
assign B_in = A_out + 1;
```

1

```
always @(posedge clk)
  B_out <= B_in;
```

B


```
assign C_in = B_out + 1;
```

2


```
always @(posedge clk)
  C_out <= C_in;
```

C

Active Event Queue

 


Non-Blocking Queue

 

Variables in RHS of always blocks are not updated until all inputs (e.g. LHS + dependencies) are evaluated
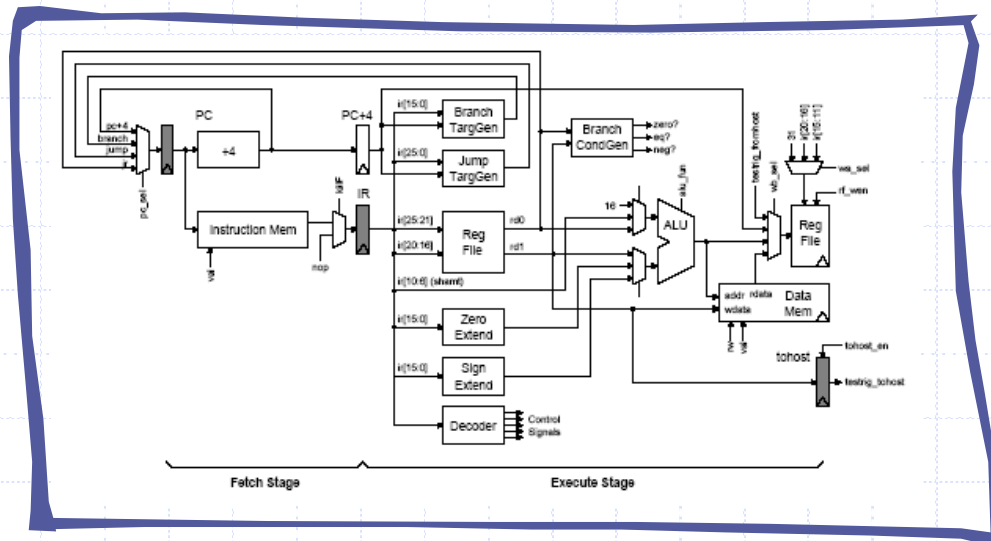
# Verilog Design Examples

- ◆ Greatest Common Divisor
- ◆ Unpipelined SMIPSV1 processor



Courtesy of Arvind <http://csg.csail.mit.edu/6.375/>

# GCD in C

```
int GCD( int inA, int inB)
{
    int done = 0;
    int A = inA;
    int B = inB;
    while ( !done )
    {
        if ( A < B )
        {
            swap = A;
            A = B;
            B = swap;
        }
        else if ( B != 0 )
            A = A - B;
        else
            done = 1;
    }
    return A;
}
```

Such a GCD description can be easily written in Behavioral Verilog

It can be simulated but it will have nothing to do with hardware, i.e. it won't synthesize.

# Behavioral GCD in Verilog

```
module GCD_behav#( parameter W = 16 )
( input  [W-1:0] inA, inB,
  output [W-1:0] out );
reg [W-1:0] A, B, out, swap;
integer done;
always @(*)
begin
  done = 0; A = inA; B = inB;
  while ( !done )
  begin
    if ( A < B )
      swap = A;
      A = B; B = swap;
    else if ( B != 0 )
      A = A - B;
    else
      done = 1;
  end
  out = A; end endmodule
```

User sets the input operands and checks the output; the answer will appear immediately, like a combinational circuit

Note data dependent loop, "done"

# Deriving an RTL model for GCD

```
module gcdGCDUnit_behav#( parameter W = 16 )
( input  [W-1:0] inA, inB,
  output [W-1:0] out );
reg [W-1:0] A, B, out, swap;
integer done;
always @(*)
begin
  done = 0; A = inA; B = inB;
  while ( !done )
  begin
    if ( A < B )
      swap = A;
      A = B; B = swap;
    else if ( B != 0 )
      A = A - B;
    else
      done = 1;
  end
  out = A; end endmodule
```

What does the RTL implementation need?


State

Less-Than Comparator


Equal Comparator

Subtractor
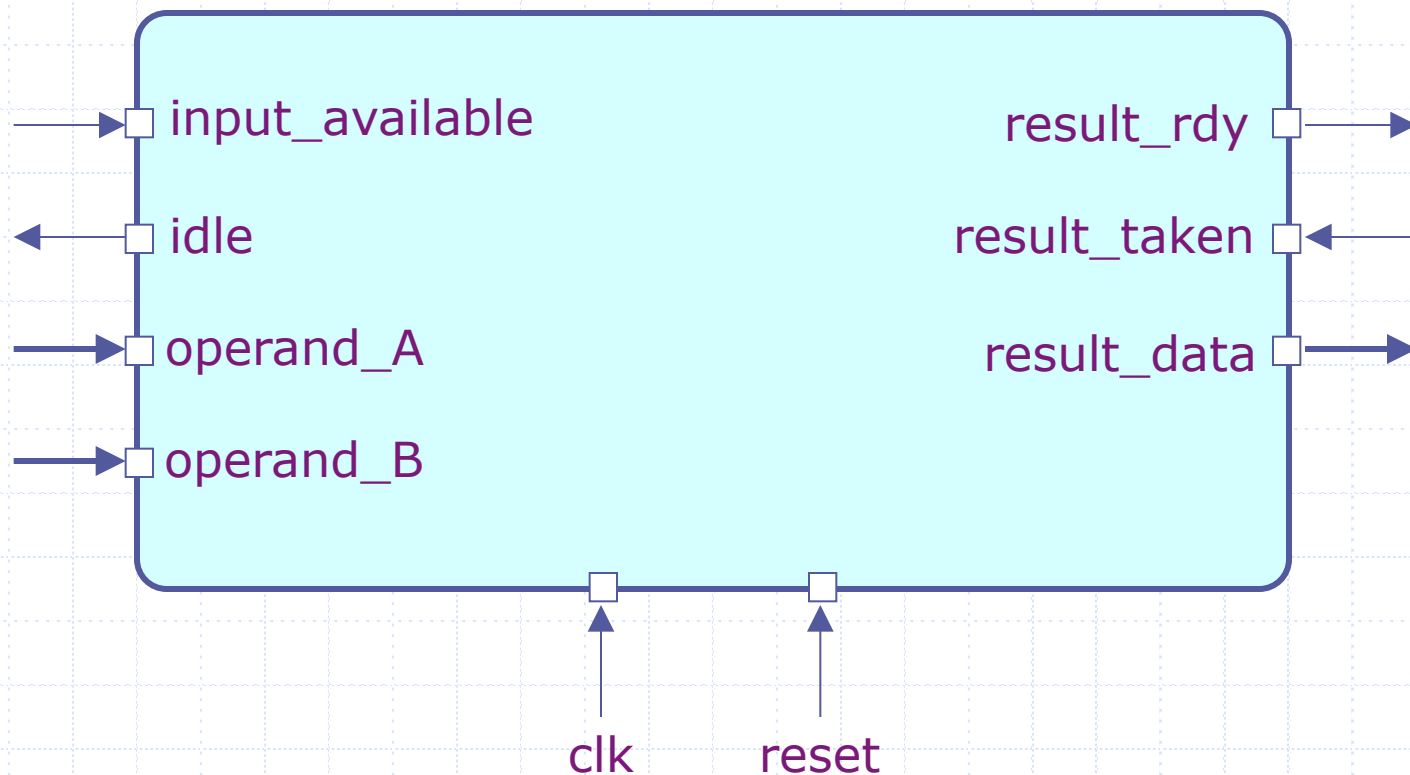
# Step 1: Design an appropriate port interface


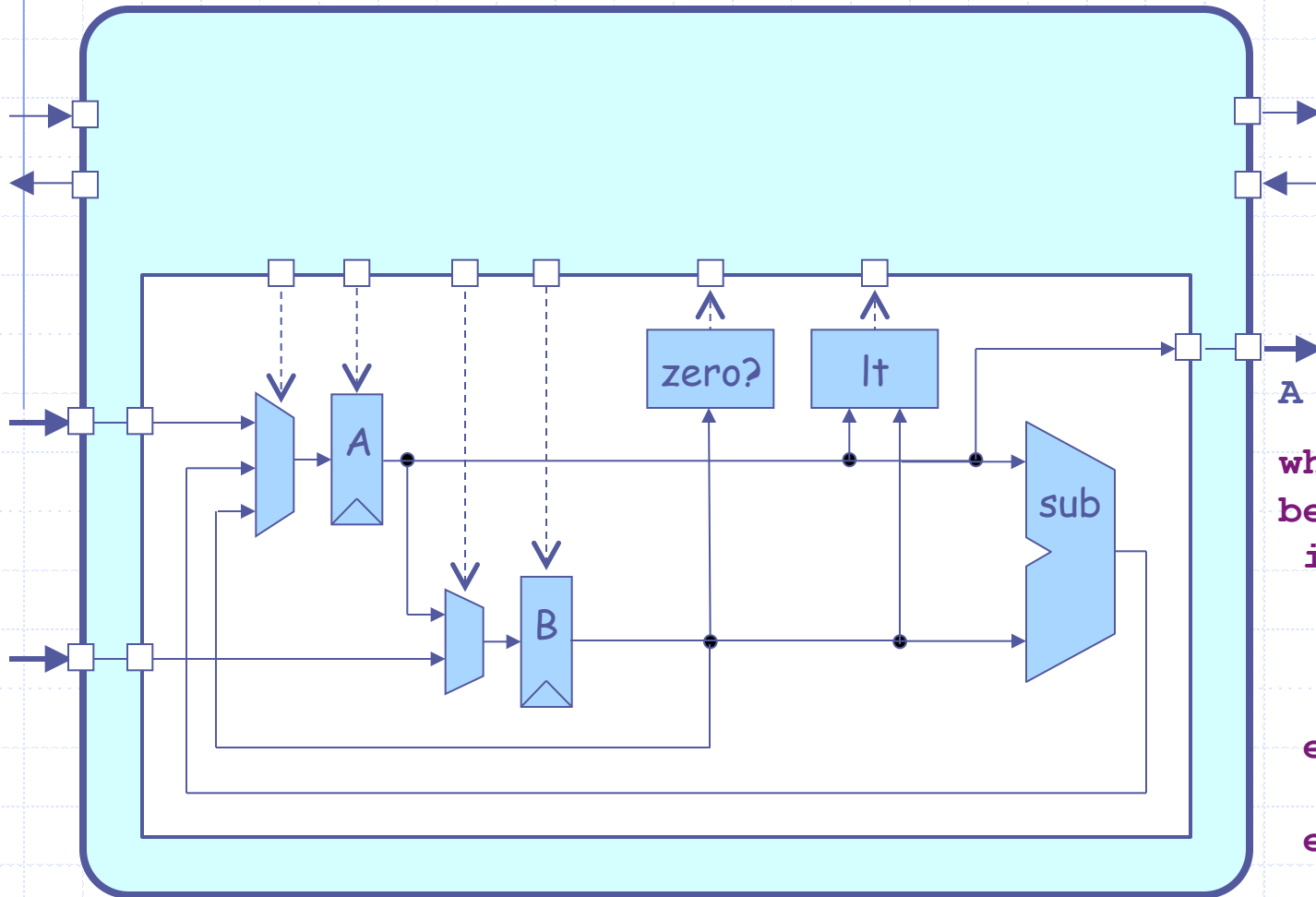
# Step 2: Design a datapath which has the functional units



```
A = inA; B = inB;
```

```
while ( !done )  
begin  
  if ( A < B )  
    swap = A;  
    A = B;  
    B = swap;  
  else if ( B != 0 )  
    A = A - B;  
  else  
    done = 1;
```


```
End
```

```
Y = A;
```

```
L03-21
```
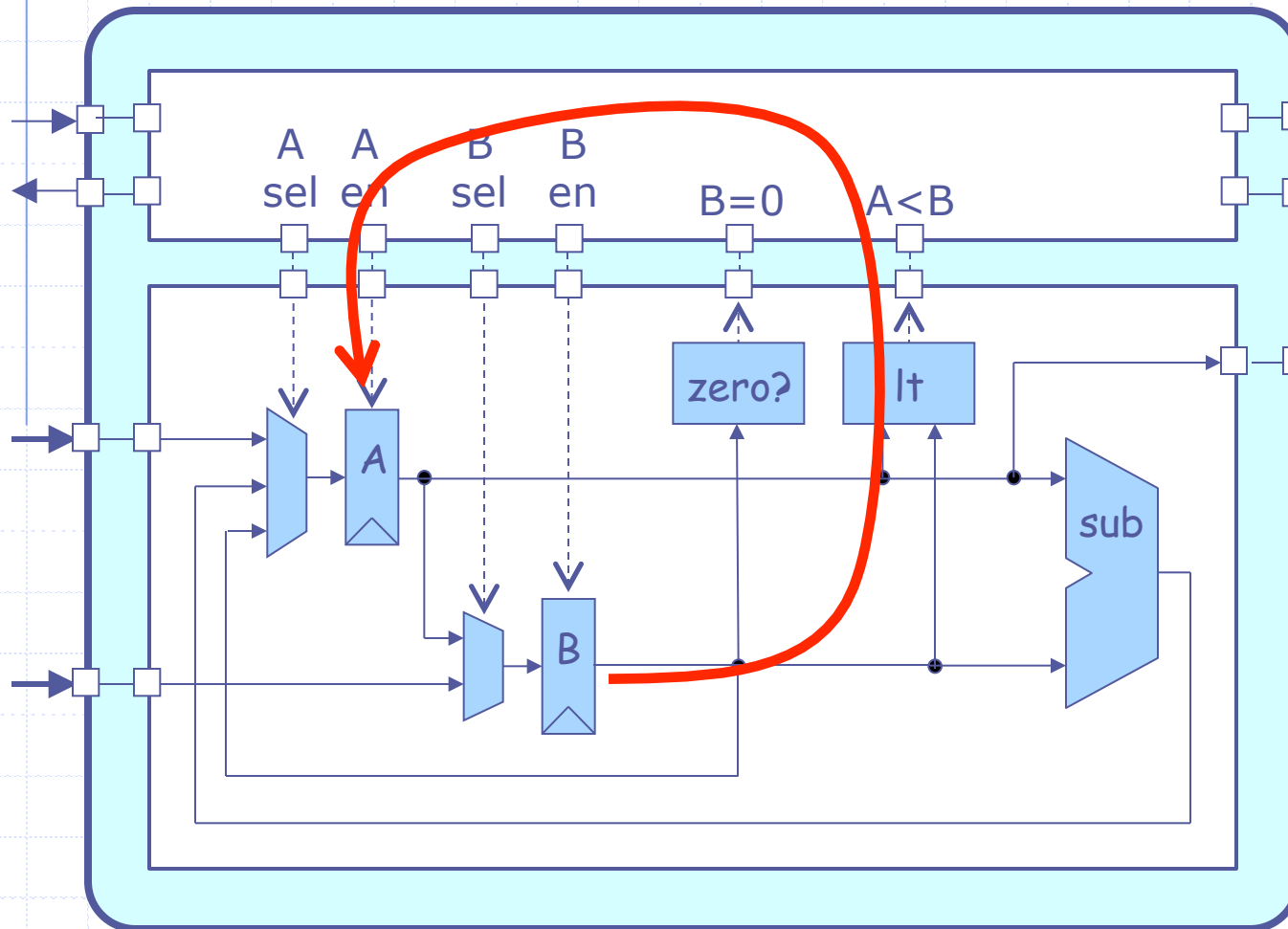
# Step 3: Add the control unit to sequence the datapath

Control unit should be designed to be either busy or waiting for input or waiting for output to be picked up



```

A = inA; B = inB;
while ( !done )
begin
  if ( A < B )
    swap = A;
    A = B;
    B = swap;
  else if ( B != 0 )
    A = A - B;
  else
    done = 1;

```

End  
Y = A; L03-22

# Datapath module interface

```
module GCDdatapath#( parameter W = 16 )
```

```
( input      clk,
```

```
  // Data signals
```

```
  input  [W-1:0] operand_A,
```

```
  input  [W-1:0] operand_B,
```

```
  output [W-1:0] result_data,
```

```
  // Control signals (ctrl->dpath)
```

```
  input      A_en,
```

```
  input      B_en,
```

```
  input  [1:0] A_sel,
```

```
  input      B_sel,
```

```
  // Control signals (dpath->ctrl)
```


```
  output      B_zero,
```

```
  output      A_lt_B
```

```
);
```

February 9, 2009

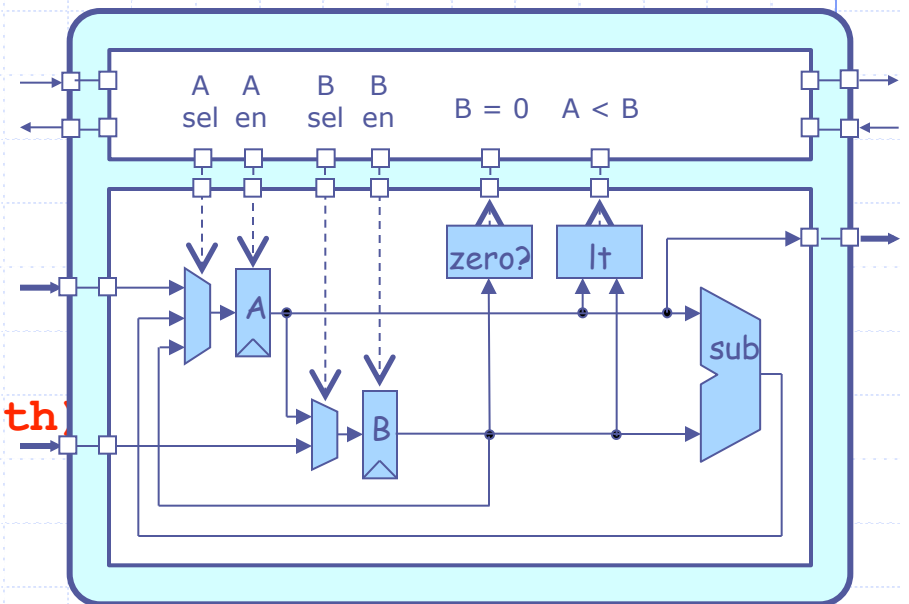Courtesy of Arvind <http://csg.csail.mit.edu/6.375/>



L03-23


# Connect the modules

```
wire [W-1:0] B;  
wire [W-1:0] sub_out;  
wire [W-1:0] A_out;
```

```
vcMux3#(W) A_mux  
( .in0 (operand_A) ,  
  .in1 (B) ,  
  .in2 (sub_out) ,  
  .sel (A_sel) ,  
  .out (A_out) );
```

```
wire [W-1:0] A;
```
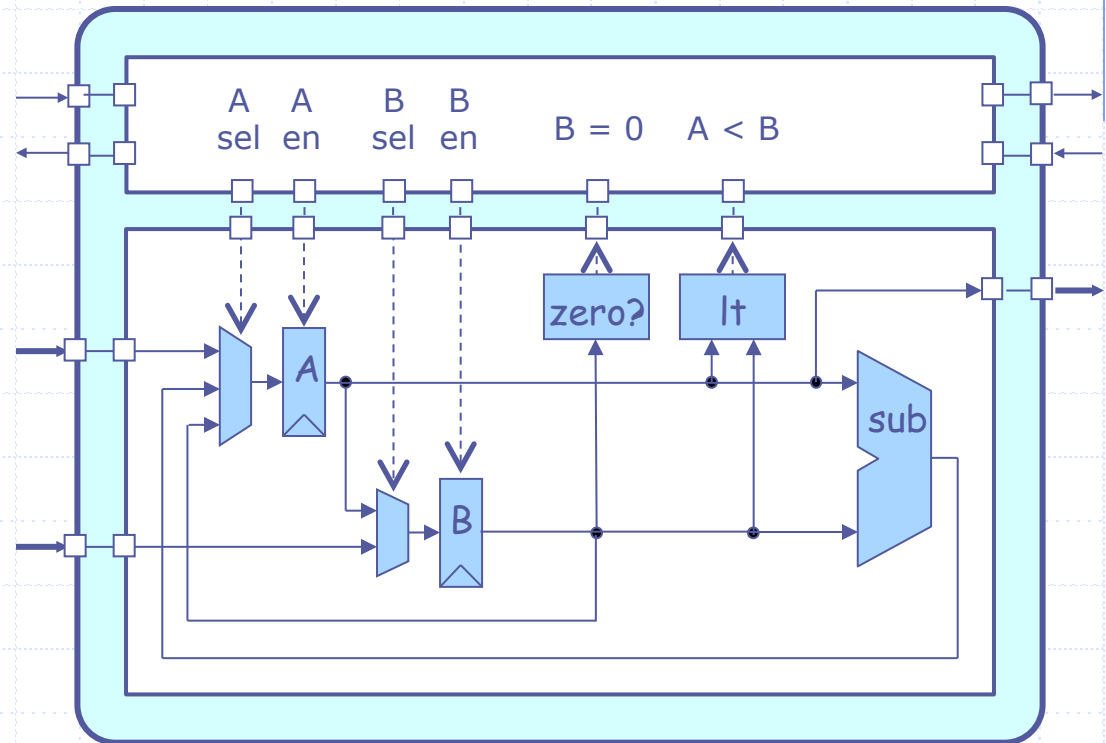
```
vcEDFF_pf#(W) A_pf  
( .clk (clk) ,  
  .en_p (A_en) ,  
  .d_p (A_out) ,  
  .q_np (A) );
```



Courtesy of Arvind <http://csg.csail.mit.edu/6.375/>

# Connect the modules ...

```
wire [W-1:0] B;
wire [W-1:0] sub_out;
wire [W-1:0] A_out;

vcMux3#(W) A_mux
( .in0 (operand_A),
  .in1 (B),
  .in2 (sub_out),
  .sel (A_sel),
  .out (A_out) );

wire [W-1:0] A;
vcEDFF_pf#(W) A_pf
( .clk (clk),
  .en_p (A_en),
  .d_p (A_out),
  .q_np (A) );

vcMux2#(W) B_mux
( .in0 (operand_B),
  .in1 (A),
  .sel (B_sel),
  .out (B_out) );


vcEDFF_pf#(W) B_pf
( .clk (clk),
  .en_p (B_en),
  .d_p (B_out),
  .q_np (B) );

assign B_zero = (B==0);
assign A_lt_B = (A < B);
assign sub_out = A - B;
assign result_data = A;
```

Using explicit state helps eliminate issues with non-blocking assignments

Continuous assignment combinational logic is fine
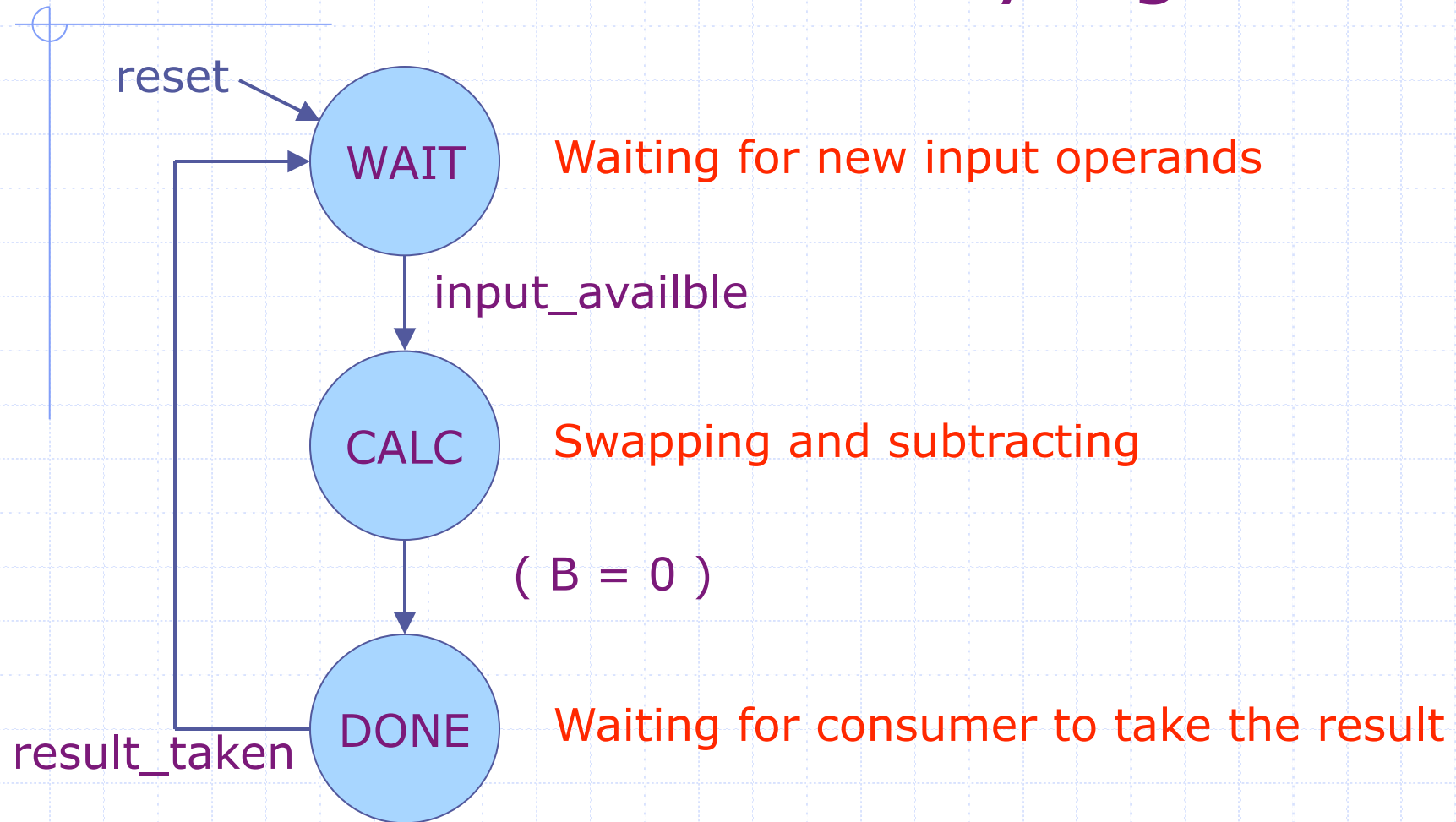
# Control unit requires a **state machine** for valid/ready signals



# Implementing the control logic FSM in Verilog

```
localparam WAIT = 2'd0;  
localparam CALC = 2'd1;  
localparam DONE = 2'd2;
```

Localparams are not really parameters at all. They are scoped constants.

```
reg [1:0] state_next;  
wire [1:0] state;
```

```
vcRDFP_pf#(2,WAIT)  
state_pf  
( .clk (clk),  
  .reset_p (reset),  
  .d_p (state_next),  
  .q_np (state) );
```

Explicit state in the control logic is also a good idea!

# Control signals for the FSM

```
reg [6:0] cs;
always @(*)
begin
    //Default control signals
    A_sel    = A_SEL_X;
    A_en     = 1'b0;
    B_sel    = B_SEL_X;
    B_en     = 1'b0;
    input_available = 1'b0;
    result_rdy = 1'b0;
    case ( state )
        WAIT :
            ...
        CALC :
            ...
        DONE :
            ...
    endcase
end

WAIT: begin
    A_sel    = A_SEL_IN;
    A_en     = 1'b1;
    B_sel    = B_SEL_IN;
    B_en     = 1'b1;
    input_available = 1'b1;
end


CALC: if ( A_lt_B )
    A_sel = A_SEL_B;
    A_en  = 1'b1;
    B_sel = B_SEL_A;
    B_en  = 1'b1;
else if ( !B_zero )
    A_sel = A_SEL_SUB;
    A_en  = 1'b1;
end

DONE: result_rdy = 1'b1;
```
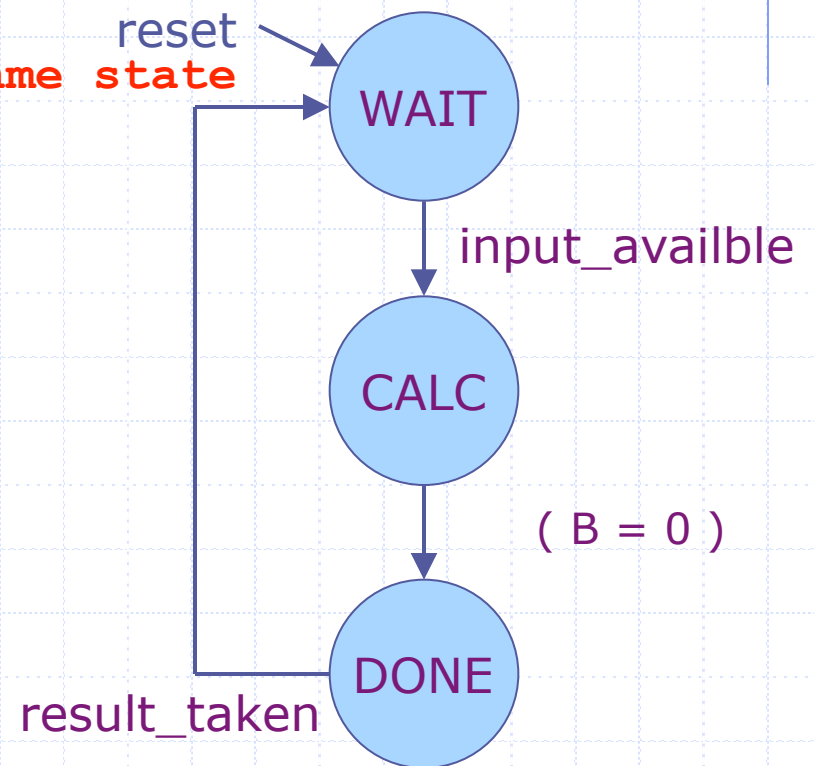
# FSM state transitions

```
always @(*)
begin
    // Default is to stay in the same state
    state_next = state;

    case ( state )
        WAIT :
            if ( input_available )
                state_next = CALC;
        CALC :
            if ( B_zero )
                state_next = DONE;
        DONE :
            if ( result_taken )
                state_next = WAIT;
    endcase
end
```



# RTL test harness requires proper handling of the ready/valid signals

