

# CSE 140, Lecture 2

## Combinational Logic

CK Cheng

CSE Dept.

UC San Diego

# Combinational Logic Outlines

## 1. Introduction

- Scope
- Boolean Algebra (Review)
- Switching Functions, Logic Diagram and Truth Table
- Handy Tools: **DeMorgan's Theorem, Consensus Theorem and Shannon's Expansion**

## 2. Specification


## 3. Synthesis

# 1.1 Combinational Logic: Scope

- Description
  - **Language:** e.g. C Programming, **BSV**, Verilog, VHDL
  - **Boolean algebra**
  - **Truth table: Powerful engineering tool**
- Design
  - Schematic Diagram
  - Inputs, Gates, Nets, Outputs
- Goal
  - Validity: **correctness**, turnaround time
  - Performance: power, timing, **cost**
  - Testability: yield, diagnosis, robustness
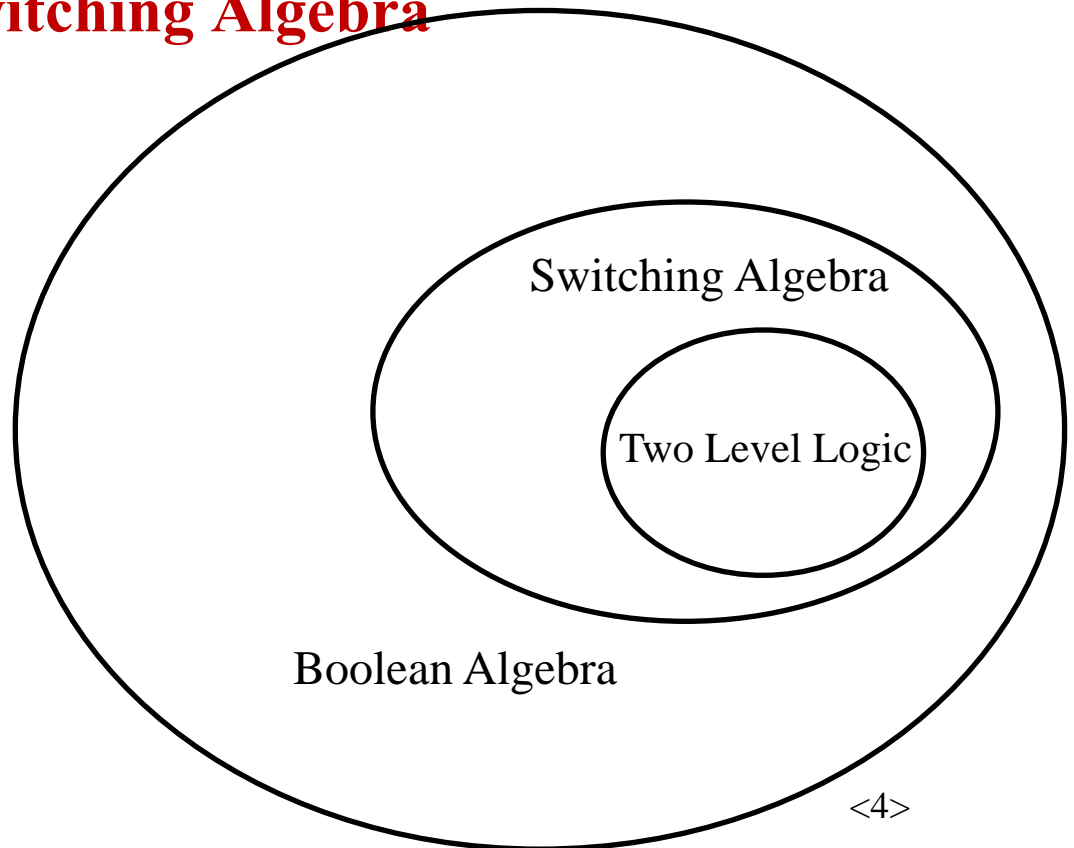
# Scope: Boolean algebra, switching algebra, logic

- Boolean Algebra: multiple-valued logic, i.e. each variable have multiple values.
- Switching Algebra: binary logic, i.e. each variable can be either 1 or 0.
- **Boolean Algebra  $\neq$  Switching Algebra**



# Scope: Switching Algebra (Binary Values)


- Typically consider only two discrete values:
  - 1's and 0's
  - 1, TRUE, HIGH
  - 0, FALSE, LOW
- 1 and 0 can be represented by specific voltage levels, rotating gears, fluid levels, etc.
- Digital circuits usually depend on specific voltage levels to represent 1 and 0
- *Bit: Binary digit*

# Scope: Levels of Logic

- Multiple Level Logic: Many layers of two level logic with some inverters, e.g.  $((((a+bc)'+ab')'+b'c+c'd)'bc+c'e)$   
(A network of two level logic)
- Two Level Logic: Sum of products, or product of sums, e.g.  $ab + a'c + a'b'$ ,  $(a'+c)(a+b')(a+b+c')$


## Features of Digital Logic Design

- Multiple Outputs
- Don't care sets

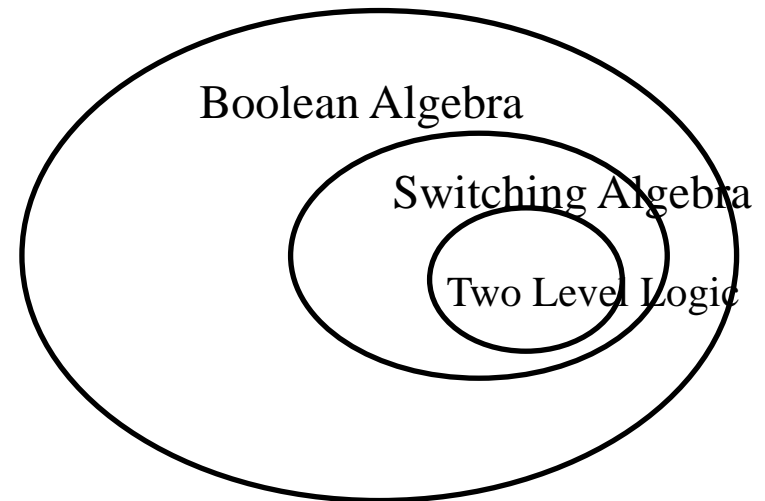
 
# 1.2 George Boole, 1815 - 1864

- Born to working class parents: Son of a shoemaker
- Taught himself mathematics and joined the faculty of Queen's College in Ireland.
- Wrote *An Investigation of the Laws of Thought* (1854): **systematize Aristotle's logic**
- Introduced binary variables
- Introduced the three fundamental logic operations: AND, OR, and NOT.



GEORGE BOOLE

Scanned at the American  
Institute of Physics

# Review of Boolean Algebra

Let  $B$  be a nonempty set with two 2-input operations, a 1-input operation  $\bar{\phantom{x}}$  (complement), and two distinct elements 0 and 1. Then  $B$  is called a Boolean algebra if the following axioms hold.

- Commutative laws:  $a+b=b+a$ ,  $a \cdot b=b \cdot a$
- Distributive laws:  $a+(b \cdot c)=(a+b) \cdot (a+c)$ ,  
 $a \cdot (b+c)=a \cdot b+a \cdot c$
- Identity laws:  $a+0=a$ ,  $a \cdot 1=a$
- Complement laws:  $a+a'=1$ ,  $a \cdot a'=0$



# Review of Boolean Algebra: Duality

Commutative laws	$a+b=b+a$	$a \cdot b=b \cdot a$
Distributive laws	$a+(b \cdot c)=(a+b) \cdot (a+c)$	$a \cdot (b+c)=a \cdot b+a \cdot c$
Identity laws	$a+0=a$	$a \cdot 1=a$
Complement laws	$a+a'=1$	$a \cdot a'=0$

Duality: We swap all operators between (+,.) and interchange all elements between (0,1). **Each pairs of laws are in duality.**

# Review of Boolean Algebra: Duality

Commutative laws	$a+b=b+a$	$a \cdot b=b \cdot a$
Distributive laws	$a+(b \cdot c)=(a+b) \cdot (a+c)$	$a \cdot (b+c)=a \cdot b+a \cdot c$
Identity laws	$a+0=a$	$a \cdot 1=a$
Complement laws	$a+a'=1$	$a \cdot a'=0$

Duality: We swap all operators between (+,.) and interchange all elements between (0,1).

**For a theorem if the statement can be proven with the laws of Boolean algebra, then the duality of the statement is also true.**

# 1.3 Switching functions: Operators and Digital Logic Gates

id	A	B	Y
0	0	0	0
1	0	1	0
2	1	0	0
3	1	1	1





**AND**  
 $Y=AB$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

**OR**  
 $Y=A+B$

A	Y
0	1
1	0

**NOT**  
 $Y=A'$

    

**Input 0 dominates Y**  
**0 blocks the output**  
**1 passes signal A**

**Input 1 dominates Y**  
**0 passes signal A**  
**1 blocks the output**

# 1.3 Switching functions: Operators and Digital Logic Gates

id	A	B	C	Y
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1	0	1	0
6	1	1	0	0
7	1	1	1	1

**AND**  
 $Y=ABC$

**0 blocks the output**  
**1 passes signal A**  
**For AND, only one row is true (minterm)**

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

**OR**  
 $Y=A+B+C$

**0 passes signal A**  
**1 blocks the output**  
**For OR, only one row is false (maxterm)**

# 1.3 Switching functions: Example on AND and OR

AND

$$Y=A'B'C$$


id	A	B	C	Y
0	0	0	0	
1	0	0	1	
2	0	1	0	
3	0	1	1	
4	1	0	0	
5	1	0	1	
6	1	1	0	
7	1	1	1	

OR

$$Y=A'+B'+C$$

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

# Switching Expression and Logic

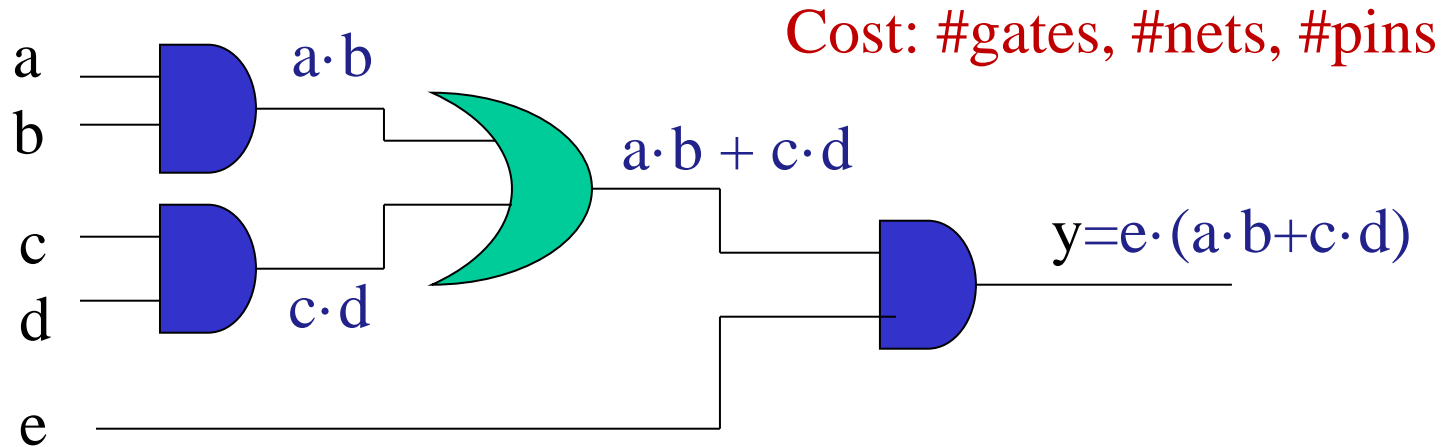

## Schematic Diagram:

5 primary inputs  
1 primary output  
4 gates (3 ANDs, 1 OR)  
9 signal nets  
12 pins

## Boolean Algebra:

5 variables  
1 expression  
4 operators (3 ANDs, 1 OR)  
5 literals

# Switching Expression and Logic


Schematic Diagram:

5 primary inputs

4 components (gates)

9 signal nets

12 pins

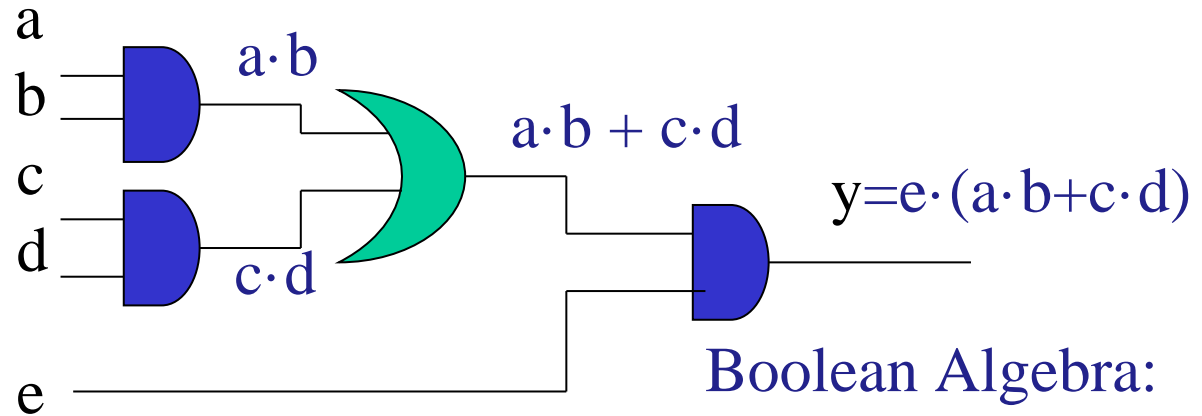

Boolean Algebra:

5 literals

4 operators

A. #inputs

B. #gates

C. #nets

D. #pins

E. None

I. #variables

II. #operators

III. #literals + #operators

IV. #literals + 2 #operators - 1

# Schematic Diagram vs. Switching Expression

- Switching Expression: #literals, #operators
- Schematic Diagram: #gates, #nets, #pins


Switching expression is related to logic implementation



# BSV Description: An example

```
function Bit#(1) fy(Bit#(1) a, Bit#(1) b, Bit#(1) c,  
  Bit#(1) d, Bit#(1) e);  
  Bit#(1) y= e &((a &b) | (c&d));  
  return y;  
endfunction
```

 “**Bit#(n)**” type declaration says that a is n bit wide.



# Laws and Logic Diagrams

## 1. Identity



$$\begin{array}{ll} A * 1 = A & A + 1 = 1 \\ A * 0 = 0 & A + 0 = A \end{array}$$

## 2. Complement



$$A + A' = 1 \quad A * A' = 0$$

## T8. Distributive Law

$$A(B+C) = AB + AC$$

  



$$A+BC = (A+B)(A+C)$$

  



# Laws and Logic Diagrams

## T7. Associativity

$$(A+B) + C = A + (B+C)$$

  

$$(AB)C = A(BC)$$

  

# 1.4 Handy Tools

## Boolean Algebra

- DeMorgan's Law: Complements


- Consensus Theorem

## Switching Logic

- Shannon's Expansion

- Truth Table


 
- Karnaugh Map (single output, two level logic)





# DeMorgan's Theorem and Digital Logic

T12. DeMorgan's Theorem  $(A+B)' = A'B'$      $(AB)' = A' + B'$

- $Y = (AB)' = A' + B'$

  

- $Y = (A + B)' = A'B'$

  

# DeMorgan's Theorem: Bubble Pushing

- Pushing bubbles backward (from the output) or forward (from the inputs) changes the body of the gate from AND to OR or vice versa.
- Pushing a bubble from the output back to the inputs puts bubbles on all gate inputs.



- Pushing bubbles on *all* gate inputs forward toward the output puts a bubble on the output and changes the gate body.



# Consensus Theorem

- $AB+AC+B'C$   
 $=AB+B'C$

- $(A+B)(A+C)(B'+C)$   
 $=(A+B)(B'+C)$



The consensus of  $AB$ ,  $B'C$  is: ?

Exercise: to prove the reduction using

- (1) Venn Diagrams,
- (2) Boolean algebra,
- (3) Logic simulation and
- (4) Shannon's expansion

# Consensus Theorem: Venn Diagrams

$$AB+AC+B'C : AB+B'C$$

  



# Consensus Theorem: Boolean Algebra

- $AB+AC+B'C$   
 $=AB+B'C$

- $(A+B)(A+C)(B'+C)$   
 $=(A+B)(B'+C)$

$$\begin{aligned} & AB+AC+B'C \\ &=AB+AC\mathbf{1}+B'C \\ &=AB+AC(\mathbf{B+B'})+B'C \\ &=AB+ABC+AB'C+B'C \\ &=AB(\mathbf{1+C})+(\mathbf{A+1})B'C \\ &=AB+B'C \end{aligned}$$

# Consensus Theorem: Logic Simulation

$$f(A,B,C) = AB + AC + B'C$$

$$g(A,B,C) = AB + B'C$$

Index	A	B	C	AB	AC	B'C	f	g
0	0	0	0	0	0	0		
1	0	0	1	0	0	1		
2	0	1	0	0	0	0		
3	0	1	1	0	0	0		
4	1	0	0	0	0	0		
5	1	0	1	0	1	1		
6	1	1	0	1	0	0		
7	1	1	1	1	1	0		





# Shannon's Expansion

- Shannon's expansion assumes a switching algebra system
- Divide a switching function into smaller functions
- Pick a variable  $x$ , partition the switching function into two cases:  $x=1$  and  $x=0$ 
  - $f(x,y,z,\dots) = xf(x=1,y,z,\dots) + x'f(x=0,y,z,\dots)$
- For example
  - $f(x) = xf(1) + x'f(0)$
  - $f(x,y) = xf(1,y) + x'f(0,y)$



# Shannon's Expansion: Example

$$f(x,y,z)=xf(?,y,z)+x'f(?' ,y,z)$$

A.  $?=0$

B.  $?=1$ .

$$f(x,y)=(x+f(?,y))(x'+f(?' ,y))$$

- A.  $?=0$
- B.  $?=1$ .

# Shannon's Expansion

- Decompose the switching function into minterms

$$f(x, y) = xf(1, y) + x'f(0, y)$$

$$= x(yf(1,1) + y'f(1,0)) + x'(yf(0,1) + y'f(0,0))$$

$$= xyf(1,1) + xy'f(1,0) + x'yf(0,1) + x'y'f(0,0).$$

id	x	y	f(x,y)
0	0	0	f(0,0)
1	0	1	f(0,1)
2	1	0	f(1,0)
3	1	1	f(1,1)

Shannon's expansion can decompose a switching function into a truth table.



# Shannon's Expansion vs Truth Table

Example:  $f(x,y) = x + x'y$

$$\begin{aligned} f(x,y) &= xf(1,y) + x'f(0,y) \\ &= x(yf(1,1) + y'f(1,0)) + x'(yf(0,1) + y'f(0,0)) \\ &= xyf(1,1) + xy'f(1,0) + x'yf(0,1) + x'y'f(0,0). \end{aligned}$$

id	x	y	f(x,y)
0	0	0	f(0,0)
1	0	1	f(0,1)
2	1	0	f(1,0)
3	1	1	f(1,1)

Shannon's expansion can decompose a switching function into a truth table.

# Shannon's Expansion

- Decompose the switching function into minterms

$$\begin{aligned}f(x, y) &= xf(1, y) + x'f(0, y) \\ &= x(yf(1,1) + y'f(1,0)) + x'(y(f(0,1) + y'f(0,0))) \\ &= xyf(1,1) + xy'f(1,0) + x'yf(0,1) + x'y'f(0,0).\end{aligned}$$

- Decompose the switching function into maxterms

$$\begin{aligned}f(x, y) &= (x' + f(1, y)) \cdot (x + f(0, y)) \\ &= (x' + (y' + f(1,1)) \cdot (y + f(1,0))) \cdot (x + (y' + f(0,1)) \cdot (y + f(0,0))) \\ &= (x' + y' + f(1,1))(x' + y + f(1,0))(x + y' + f(0,1))(x + y + f(0,0))\end{aligned}$$

# Shannon's Expansion: Example

Which variable in  $ab' + ac + bc$  can be used for expansion?

A. a

B. b

C. c

D. None of the above

# Shannon's Expansion: Example

$$F(A,B,C)=AB'+AC+BC$$

Remark: The choice of the variable for expansion is a nontrivial question.

# Review Summary: Switching Algebra and Karnaugh Map

Shannon's expansion and consensus theorem are used for logic optimization

- Shannon's expansion **divides** the problem into smaller functions
- Consensus theorem finds common terms when we **merge** small functions
- Karnaugh map mimics the above two operations in two dimensional space as a visual aid.

# Part I. Combinational Logic

## II) Specification

1. Language

2. Boolean Algebra

Canonical Expression: Sum of minterms and  
Product of maxterms

3. Truth Table: **minterms and maxterms**

4. Incompletely Specified Function

# II. Specification

## Decimal Addition

$$\begin{array}{r} 5 \\ + 7 \\ \hline 12 \end{array}$$

Carry      Sum

## Binary Addition

	1	1	1		Carry bits
		1	0	1	5
+		1	1	1	7
<hr/>					12
	1	1	0	0	
	↖		↖		
Carryout			Sums		




# Binary Addition: Hardware

- Half Adder: Two inputs (a,b) and two outputs (carry, sum).
- Full Adder: Three inputs (a,b, $c_{in}$ ) and two outputs (carry, sum).

# Half Adder

Truth Table

 

id	a	b	carry	sum
0	0	0	0	0
1	0	1	0	1
2	1	0	0	1
3	1	1	1	0

# Switching Function

Switching Expressions:

$$\text{Sum (a,b)} = a' \cdot b + a \cdot b'$$



$$\text{Carry (a, b)} = a \cdot b$$

Ex:

$$\text{Sum (0,0)} = 0' \cdot 0 + 0 \cdot 0' = 0 + 0 = 0$$

$$\text{Sum (0,1)} = 0' \cdot 1 + 0 \cdot 1' = 1 + 0 = 1$$
  
$$\text{Sum (1,1)} = 1' \cdot 1 + 1 \cdot 1' = 0 + 0 = 0$$




# BSV notes

```
function Bit#(2) ha(Bit#(1) a, Bit#(1) b);  
  Bit#(1) s = (!a & b) | (a & !b);  
  Bit#(1) c = a & b;  
  return {c, s};  
endfunction
```

- {c, s} represents bit concatenation

# Full Adder

 

Arithmetic:

$$2c_{out} + \text{sum} = a + b + c_{in}$$

id	a	b	c <sub>in</sub>	c <sub>out</sub>	sum
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

# Minterms

A product of all variables in the function.

A minterm is equal to 1 on exactly one row of the truth table.

id	a	b	c	carry	sum
0	0	0	0	0	0
1	0	0	1	0	$a'b'c$
2	0	1	0	0	$a'bc'$
3	0	1	1	$a'bc$	0
4	1	0	0	0	$ab'c'$
5	1	0	1	$ab'c$	0
6	1	1	0	$abc'$	0
7	1	1	1	$abc$	$abc$

# Maxterms

A sum of all variables in the function.

A maxterm is equal to 0 on exactly one row of the truth table.

id	a	b	c	carry	sum
0	0	0	0	$a+b+c$	$a+b+c$
1	0	0	1	$a+b+c'$	1
2	0	1	0	$a+b'+c$	1
3	0	1	1	1	$a+b'+c'$
4	1	0	0	$a'+b+c$	1
5	1	0	1	1	$a'+b+c'$
6	1	1	0	1	$a'+b'+c$
7	1	1	1	1	1

# Minterms and Maxterms

id	a	b	c	minterm	maxterm
0	0	0	0	$m_0=a'b'c'$	$M_0=a+b+c$
1	0	0	1	$m_1=a'b'c$	$M_1=a+b+c'$
2	0	1	0	$m_2=a'bc'$	$M_2=a+b'+c$
3	0	1	1	$m_3=a'bc$	$M_3=a+b'+c'$
4	1	0	0	$m_4=ab'c'$	$M_4=a'+b+c$
5	1	0	1	$m_5=ab'c$	$M_5=a'+b+c'$
6	1	1	0	$m_6=abc'$	$M_6=a'+b'+c$
7	1	1	1	$m_7=abc$	$M_7=a'+b'+c'$

Minterms cover all the outputs which are **true** (1).

Maxterms cover all the outputs which are **false** (0).



# Minterms

$$f_1(a,b,c) = a'bc + ab'c + abc' + abc$$

$$a'bc = 1 \text{ iff } (a,b,c) = (0,1,1)$$

$$ab'c = 1 \text{ iff } (a,b,c) = (1,0,1)$$

$$abc' = 1 \text{ iff } (a,b,c) = (1,1,0)$$

$$abc = 1 \text{ iff } (a,b,c) = (1,1,1)$$

$$f_1(a,b,c) = 1 \text{ iff } (a,b,c) = (0,1,1), (1,0,1), (1,1,0), \text{ or } (1,1,1)$$

Ex:  $f_1(1,0,1) = 1'01 + 10'1 + 101' + 101 = 1$

$$f_1(1,0,0) = 1'00 + 10'0 + 100' + 100 = 0$$

# Maxterms

$$f_2(a,b,c) = (a+b+c)(a+b+c')(a+b'+c)(a'+b+c)$$

$$a + b + c = 0 \text{ iff } (a,b,c) = (0,0,0)$$

$$a + b + c' = 0 \text{ iff } (a,b,c) = (0,0,1)$$

$$a + b' + c = 0 \text{ iff } (a,b,c) = (0,1,0)$$

$$a' + b + c = 0 \text{ iff } (a,b,c) = (1,0,0)$$

$$f_2(a,b,c) = 0 \text{ iff } (a,b,c) = (0,0,0), (0,0,1), (0,1,0), (1,0,0)$$

$$\text{Ex: } f_2(1,0,1) = (1+0+1)(1+0+1')(1+0'+1)(1'+0+1) = 1$$

$$f_2(0,1,0) = (0+1+0)(0+1+0')(0+1'+0)(0'+1+0) = 0$$

$$f_1(a,b,c) = a'bc + ab'c + abc' + abc$$

$$f_2(a,b,c) = (a+b+c)(a+b+c')(a+b'+c)(a'+b+c)$$

$$f_1(a, b, c) = m_3 + m_5 + m_6 + m_7 = \Sigma m(3,5,6,7)$$

$$f_2(a, b, c) = M_0M_1M_2M_4 = \Pi M(0, 1, 2, 4)$$

iClicker: Does  $f_1 = f_2$ ?

A. Yes

B. No.

The coverage of a single minterm. e.g.  $m_4 = ab'c'$

Id	a	b	$c_{in}$	carry	minterm $_4 = ab'c'$
0	0	0	0	0	0
1	0	0	1	0	0
2	0	1	0	0	0
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	0

Only one row has a 1.

The coverage of a single maxterm. E.g.  $M_4 = a' + b + c$

Id	a	b	$c_{in}$	carry	maxterm 4 = $a + b + c$
0	0	0	0	0	1
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	1
4	1	0	0	0	0
5	1	0	1	1	1
6	1	1	0	1	1
7	1	1	1	1	1

Only one row has a 0.

# Minterms and Maxterms: Summary

$$f_1(a,b,c) = a'bc + ab'c + abc' + abc$$

$$f_2(a,b,c) = (a+b+c)(a+b+c')(a+b'+c)(a'+b+c)$$

Canonical presentation of logic functions

Conversion between truth tables and switching functions

# Incompletely Specified Function

Don't care set is important because it allows us to minimize the function

Id	a	b	f (a, b)
0	0	0	1
1	0	1	0
2	1	0	1
3	1	1	-

1) The input does not happen.

2) The input happens, but the output is ignored.

Examples:

- Decimal number 0... 9 uses 4 bits. (1,1,1,1) does not happen.
- Final carry out bit (output is ignored).

# Incompletely Specified Function

id	a	b	c	g
0	0	0	0	0
1	0	0	1	1
2	0	1	0	-
3	0	1	1	1
4	1	0	0	1
5	1	0	1	-
6	1	1	0	0
7	1	1	1	1

$$\begin{aligned}g_1(a,b,c) &= a'b'c + a'bc + ab'c' + abc \\ &= m_1 + m_3 + m_4 + m_7 \\ &= \sum m(1,3,4,7)\end{aligned}$$

$$\begin{aligned}g_2(a,b,c) &= (a+b+c)(a'+b'+c) \\ &= M_0M_6 \\ &= \prod M(0,6)\end{aligned}$$



# Incompletely Specified Function

id	a	b	c	g
0	0	0	0	0
1	0	0	1	1
2	0	1	0	-
3	0	1	1	1
4	1	0	0	1
5	1	0	1	-
6	1	1	0	0
7	1	1	1	1

$$g_1(a,b,c) = \sum m(1,3,4,7)$$

$$g_2(a,b,c) = \prod M(0,6)$$

iClicker: Does  $g_1(a,b,c) = g_2(a,b,c)$ ?

A: Yes

B: No