

# Lab 2 preview

Hung-Wei Tseng


# Announcement

- Lab 1 due tomorrow
  - Mail it to h1tseng @ cs.ucsd.edu, not to the TAs
  - name your pdf as cse141L-lab1-LastName-FirstName.pdf
  - name your e-mail title as  
[CSE141LSU12] cse141L-lab1-LastName-FirstName
  - Your report will not be graded if any of the above goes wrong
  - No late reports, no group work
- Form your group from now!
  - We need 2 or 3 persons to make a processor
  - 4 or 5 are too more, we are not making burgers


# In Lab 2...

- You will be implementing the datapath elements for a single cycle processor
  - We provide ALU, data memory, instruction
  - You need to implement the rest
- Design the schematic of your processor first
  - What are the elements required for a single cycle processor
  - How to test each component
  - How to connect them together

# Lab 2: single-cycle datapath

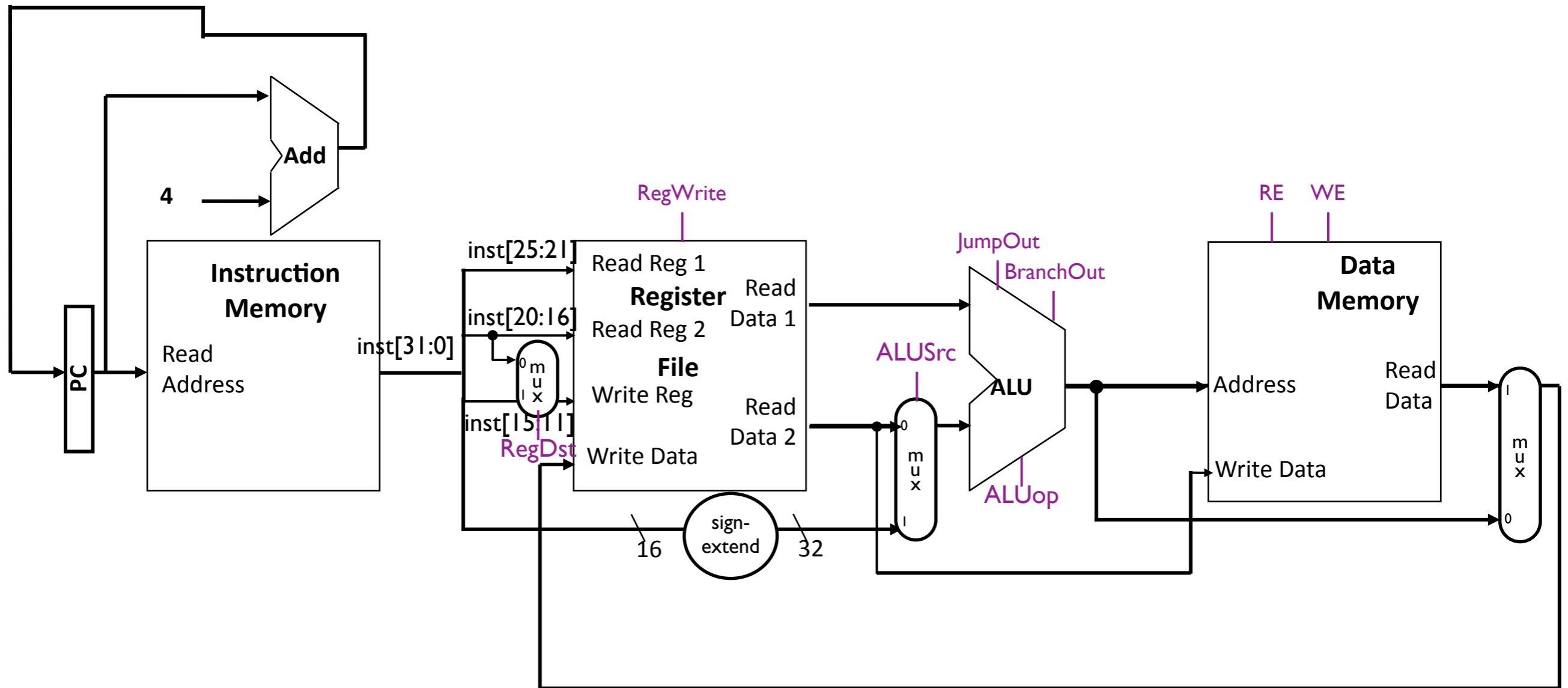


# You have to implement the processor

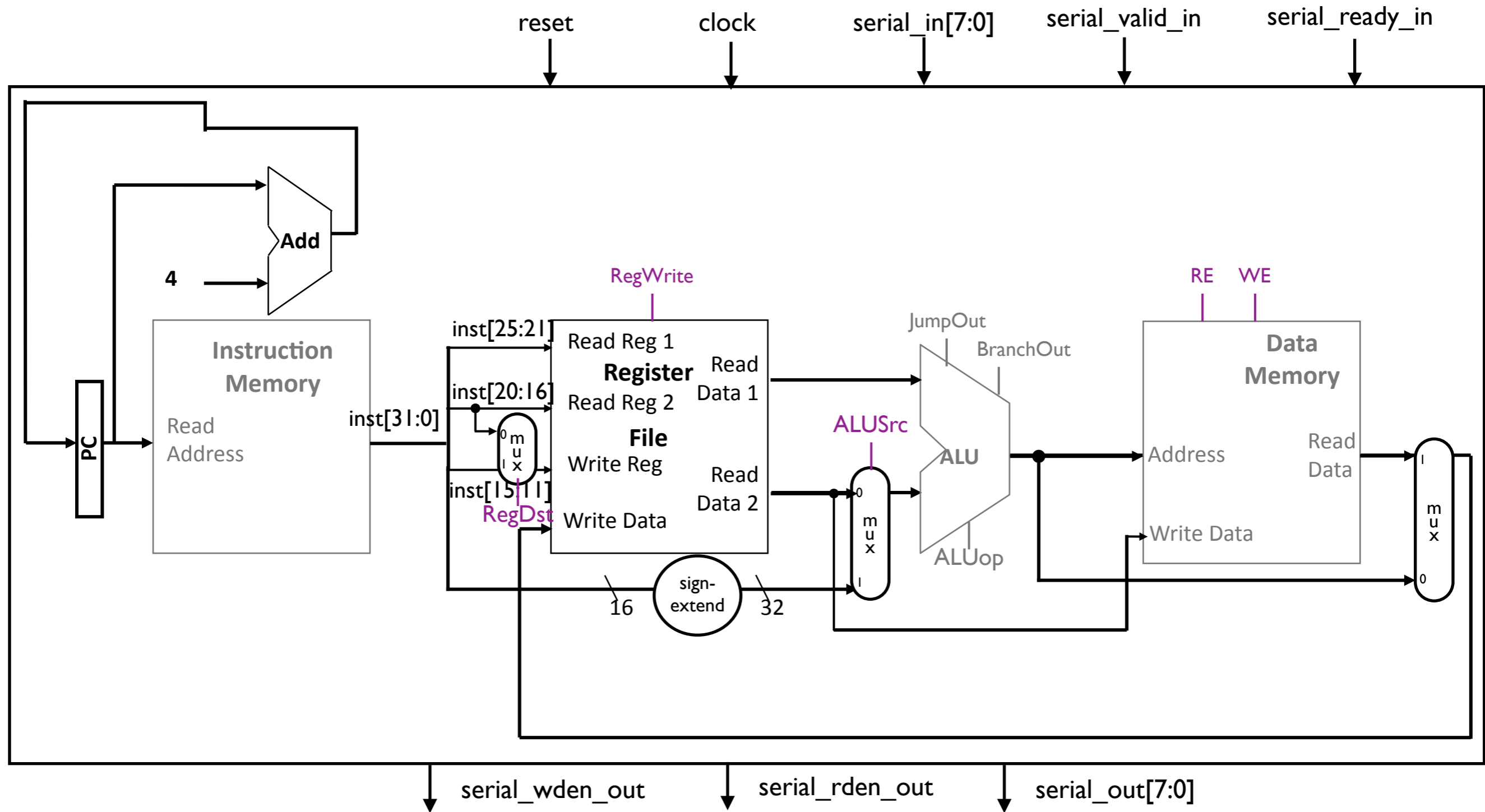


You have to implement the black parts!

# Interface of instruction memory

 


```
module inst_rom(  
    input clock,  
    input reset,  
  
    input [31:0] addr_in, //Connect to PC_next  
    output [31:0] data_out //Fetched instruction  
);  
parameter INIT_PROGRAM="c:/myfiles/blank.memh";  
endmodule
```

# Interface of ALU

 

```
module alu(  
    input [5:0] Func_in,  
    input [31:0] A_in,  
    input [31:0] B_in,  
    output [31:0] O_out,  
    output Branch_out,  
    output Jump_out  
);
```


# Interface of data memory

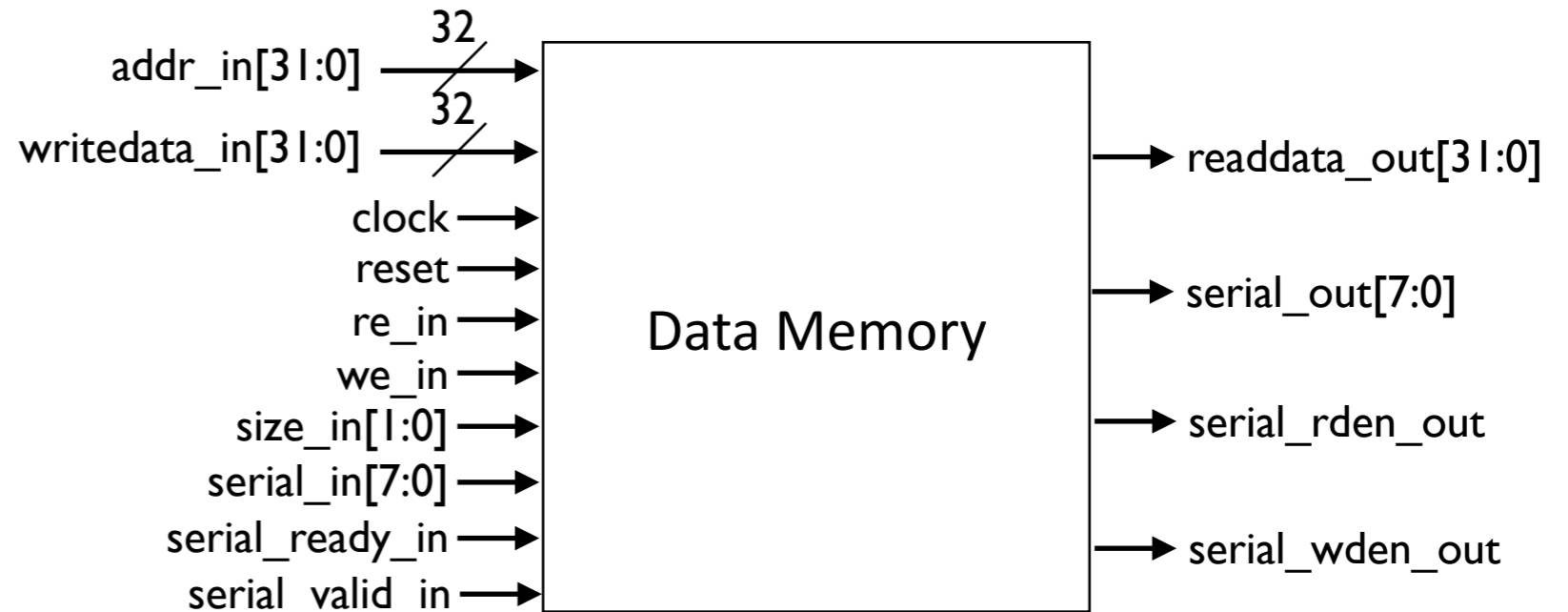

```
module data_memory(  
    input clock,  
    input reset,  
    input [31:0] addr_in, //Read/Write address  
    input [31:0] writedata_in, //Data to write to memory  
    input re_in, //Read Enable - set high when reading from memory  
    input we_in, //Write Enable - set high when writing to memory  
    output [31:0] readdata_out, //Data output for reads from memory  
    input [1:0] size_in, //Not used yet - hardwire to 2'b11  
    input [7:0] serial_in,  
    input serial_ready_in,  
    input serial_valid_in,  
    output [7:0] serial_out,  
    output serial_rden_out,  
    output serial_wren_out  
);  
parameter INIT_PROGRAM0="c:/myfiles/blank.memh";  
parameter INIT_PROGRAM1="c:/myfiles/blank.memh";  
parameter INIT_PROGRAM2="c:/myfiles/blank.memh";  
parameter INIT_PROGRAM3="c:/myfiles/blank.memh";
```




# Your register file

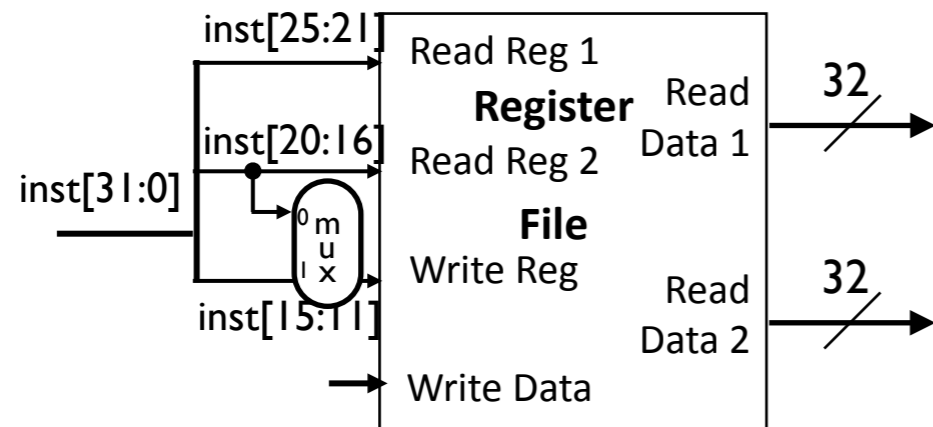

- Should contain at least the above inputs/outputs
  - Does every instruction write back data?
- Is it clocked?
- Support reset
- Deal with \$zero
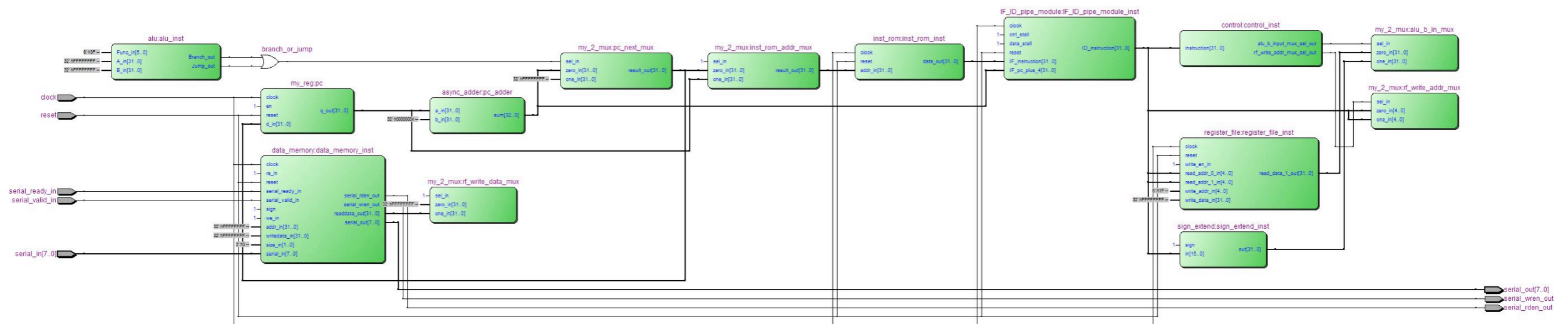
# When you interview with us

- Show us your processor.v
- Show us your register\_file.v
- Demonstrate it works: you need to design a testbench for it.
- Show us your schematic
- You may output it through the RTL viewer under analysis tool in Quartus II



**Q & A**