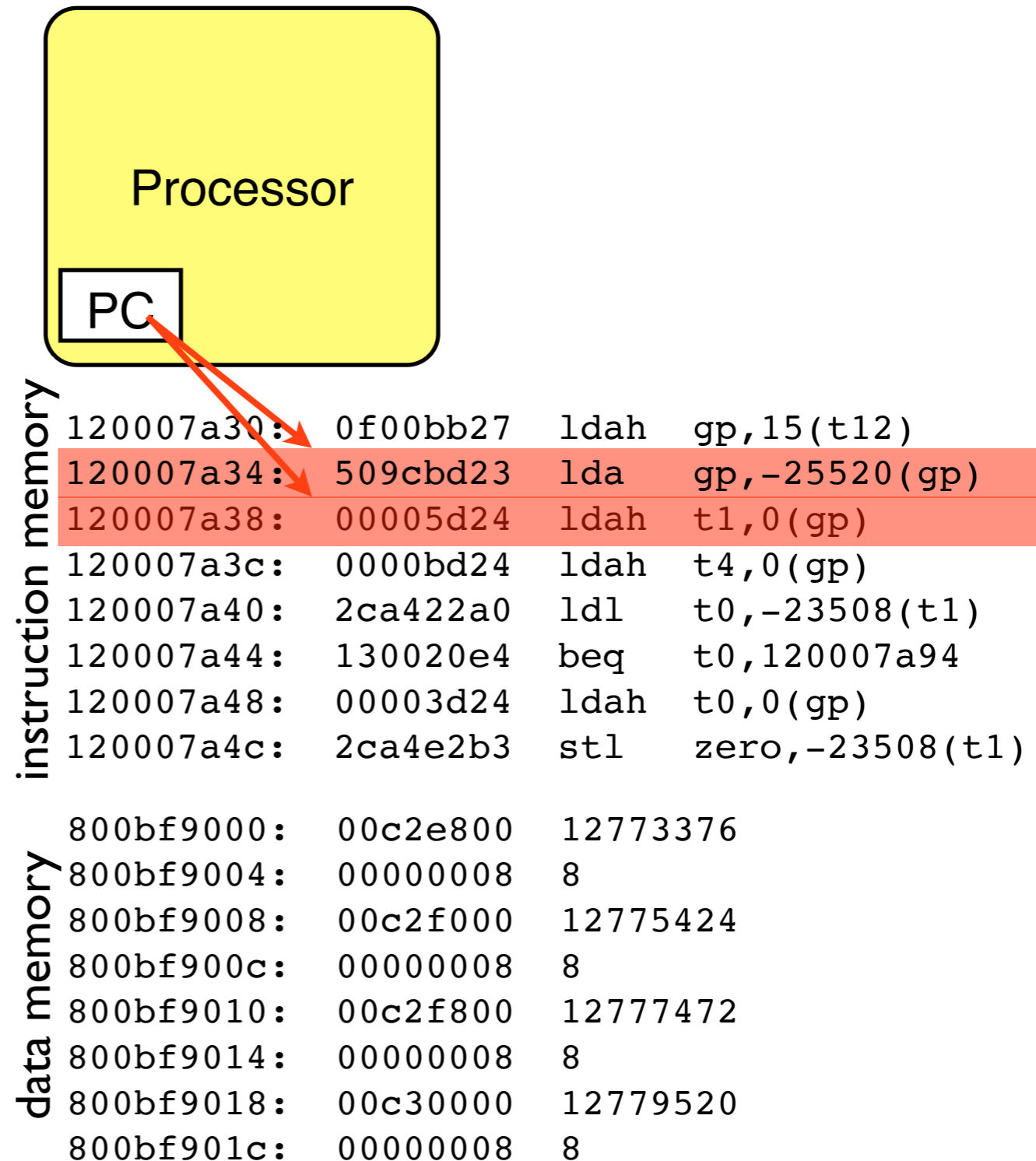


Processor Design – Single Cycle Processor

Hung-Wei Tseng


Recap: the stored-program computer

- Store instructions in memory
- The program counter (PC) controls the execution




Recap: Clock

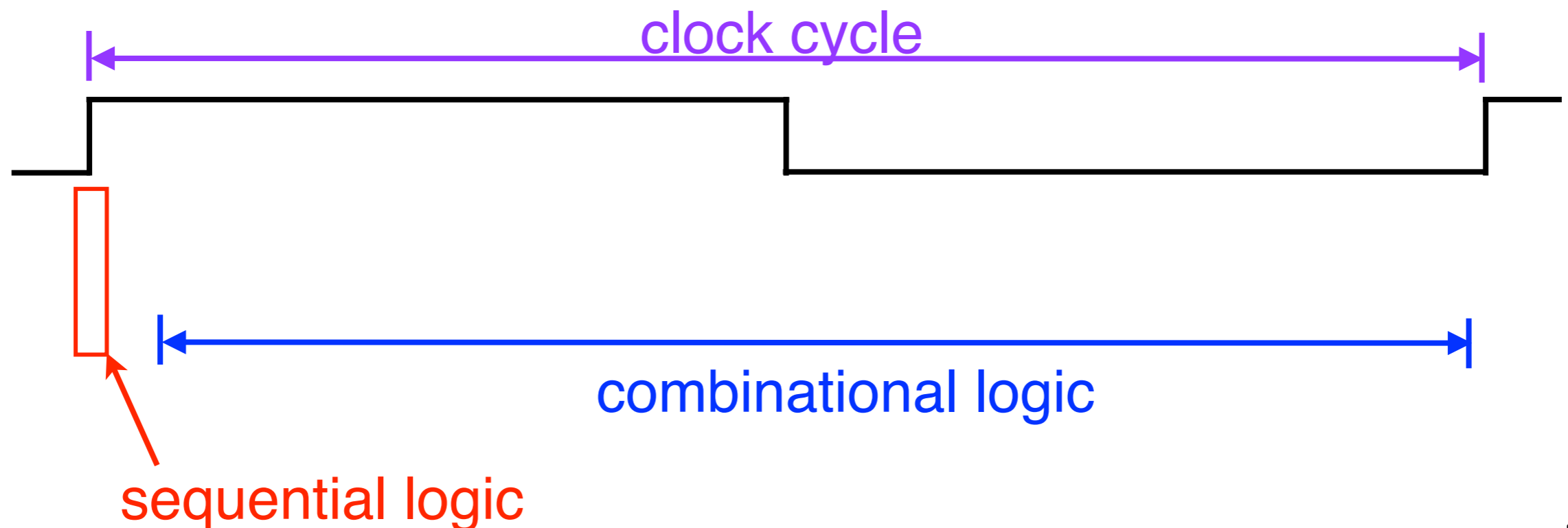- A hardware signal defines when data is valid and stable
 - Think about the clock in real life!
- We use edge-triggered clocking
 - Values stored in the sequential logic is updated only on a clock edge




Recap: MIPS ISA


- R-type: add, sub, and etc...

 

- I-type: addi, lw, sw, beq, and etc...

 

- J-type: j, jal, and etc...

 

Outline


- Implementing a Single-cycle MIPS processor

Designing a simple MIPS processor

- Support MIPS ISA in hardware
 - Design the datapath: add and connect all the required elements in the right order
 - Design the control path: control each datapath element to function correctly.
- Starts from designing a single cycle processor
 - Each instruction takes exactly one cycle to execute

Basic steps of execution

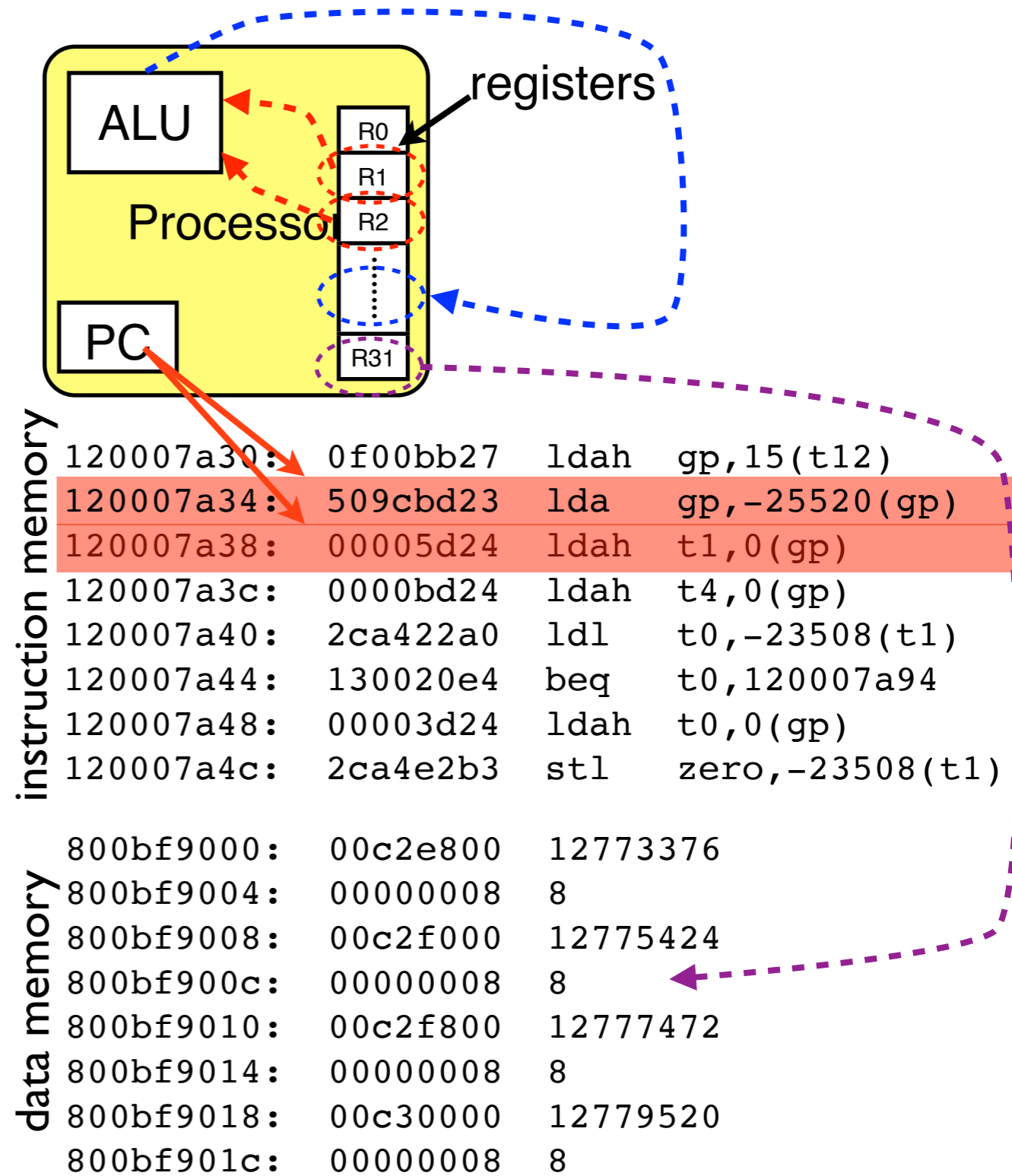- Instruction fetch: where?
instruction memory
- Decode:
 - What's the instruction?
 - Where are the operands?
registers
- Execute **ALUs**
- Memory access
 - Where is my data?
data memory
- Write back
 - Where to put the result
registers
- Determine the next PC




Recap: MIPS ISA


- R-type: add, sub, and etc...



- I-type: addi, lw, sw, beq, and etc...

 


- J-type: j, jal, and etc...

 


Implementing an R-type instruction



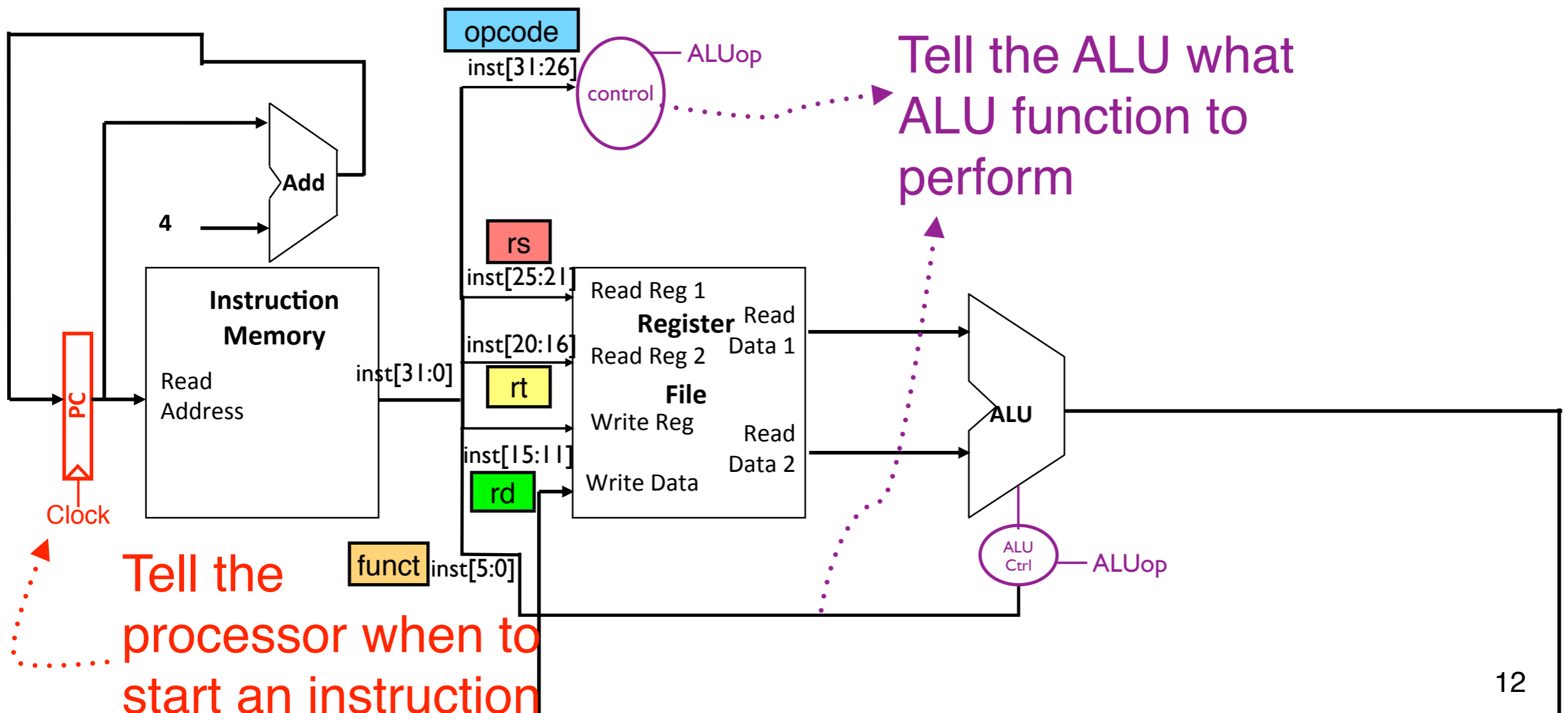instruction = MEM[PC]
 REG[rd] = REG[rs] op REG[rt]
 PC = PC + 4



Implementing a load instruction

 


instruction = MEM[PC]
 REG[rt] = MEM[signext(immediate) + REG[rs]]
 PC = PC + 4

Set different control signals for different types of instructions

Set to 1 if it's a load

Set to 1 if it's a load

Set to 0 if it's a load

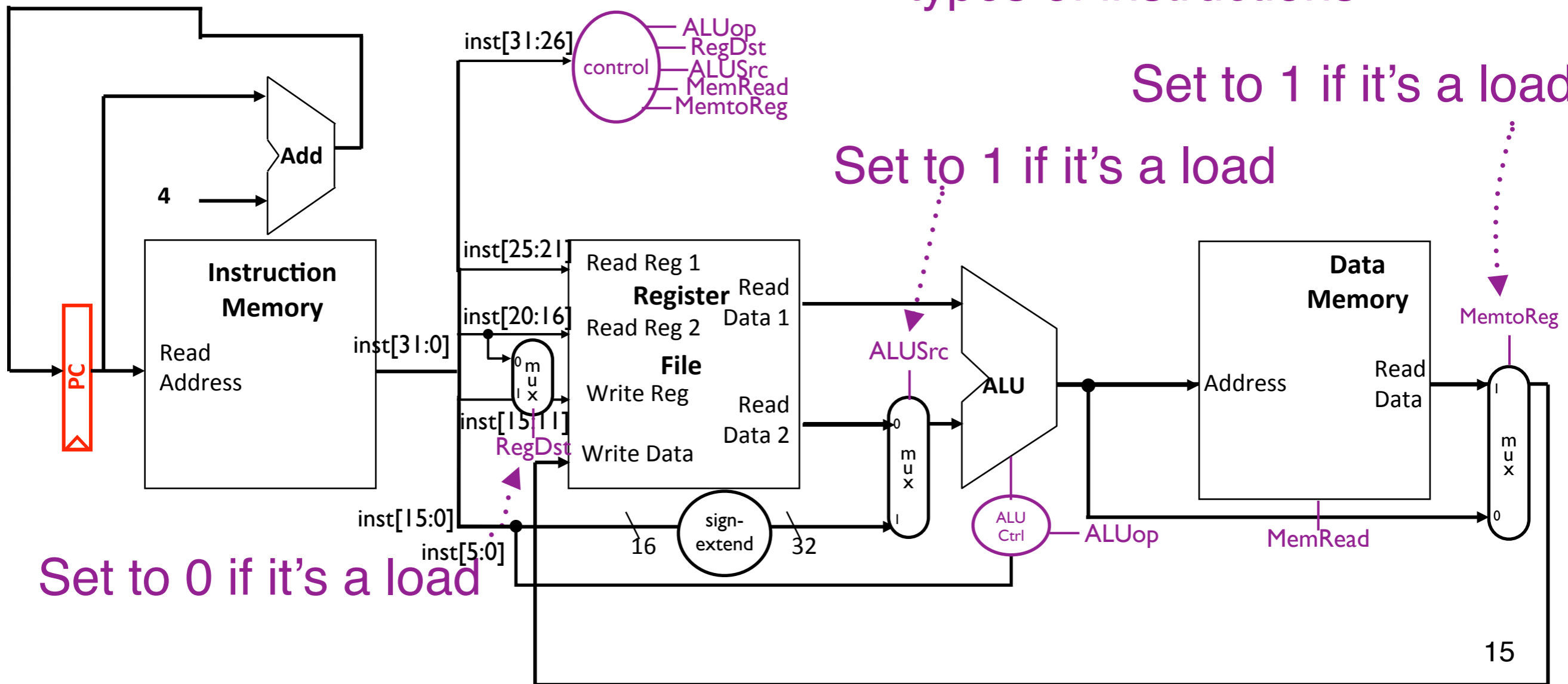

Implementing a store instruction

6 bits

5 bits

5 bits

16 bits

opcode

rs


rt

immediate / offset


instruction = MEM[PC]

MEM[signext(immediate) + REG[rs]] = REG[rt]

PC = PC + 4

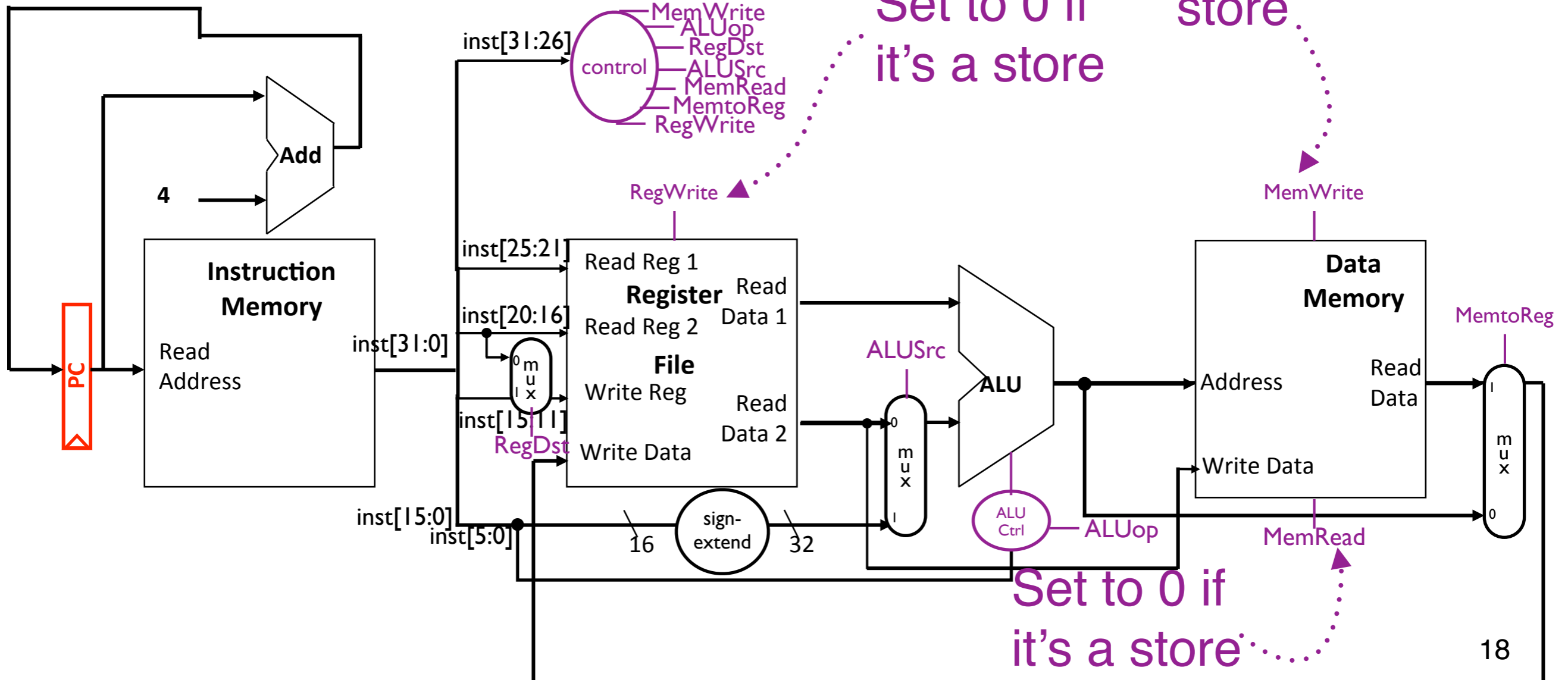

Implementing a branch instruction

 


instruction = MEM[PC]


PC = (REG[rs] == REG[rt]) ? PC + 4 + SignExtImmediate * 4 : PC + 4

PCSrc = Branch & Zero

Calculate the target address

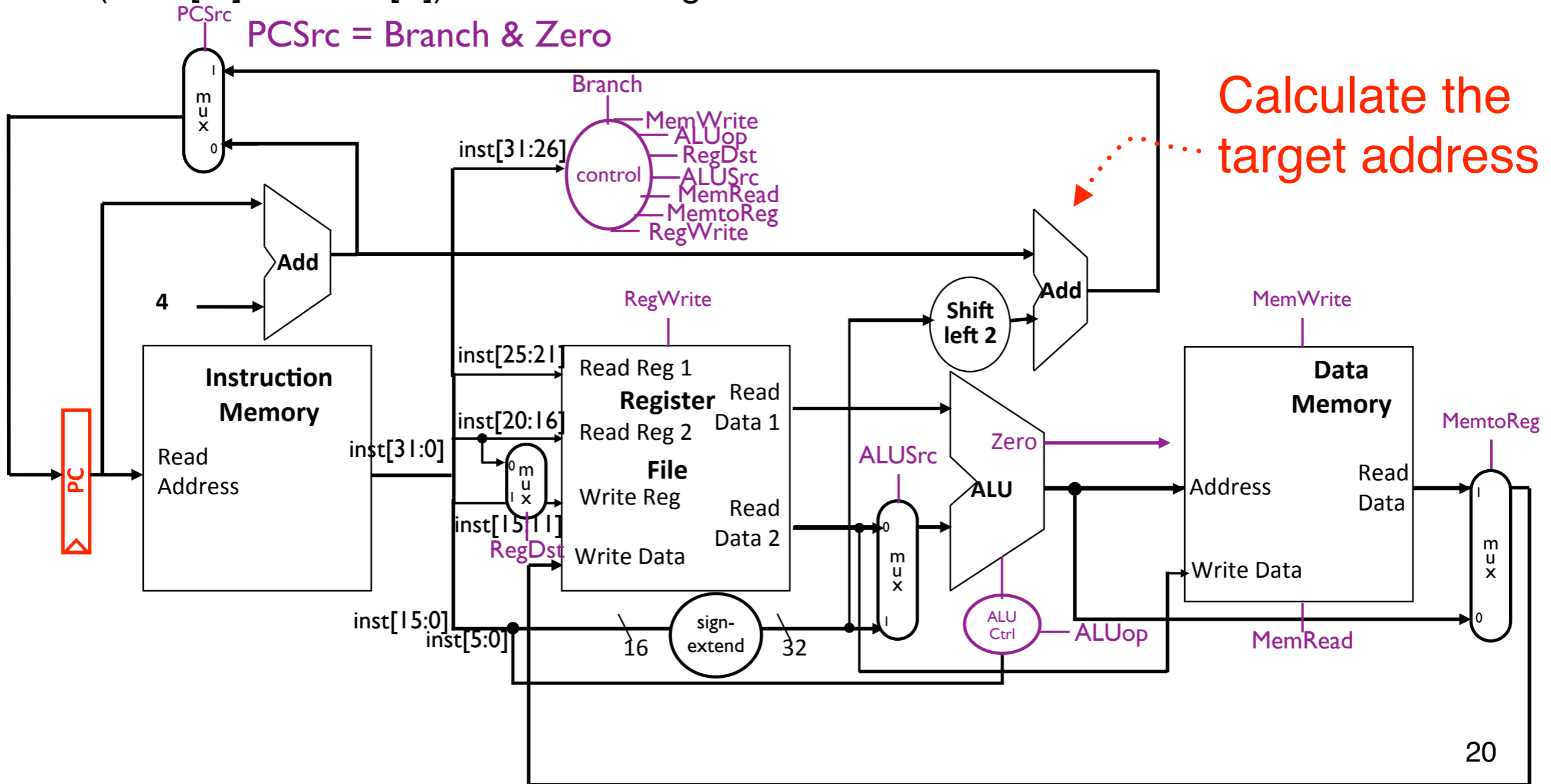

ISA and cycle time

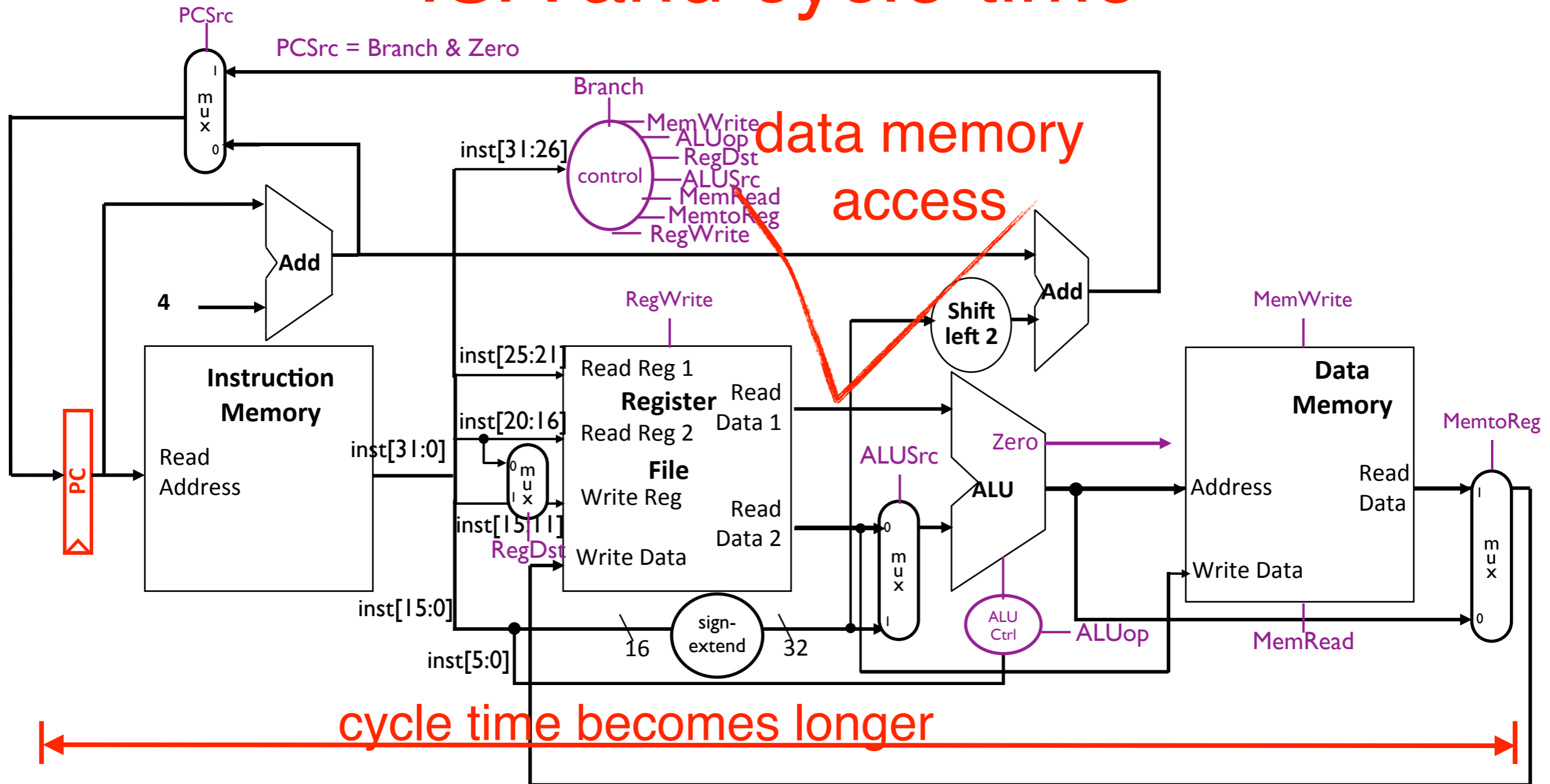

x86 supports add instruction with memory content as a source operand.
e.g. `add %eax, (%r12)` means $\%eax = \%eax + \text{memory}[\%r12]$
If MIPS wants to support this instruction, what modification is necessary? What's the performance impact?

Q & A