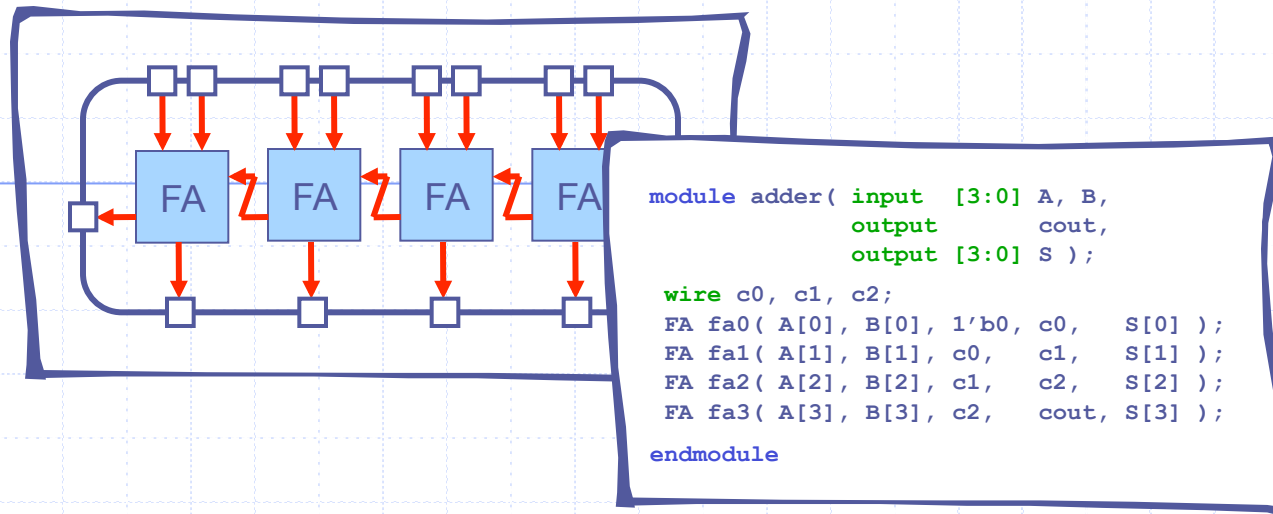


Verilog 1 - Fundamentals



6.375 Complex Digital Systems
Arvind

Courtesy of Arvind <http://csg.csail.mit.edu/6.375/>


What is Verilog?

- ◆ Verilog is a hardware description language
 - There is more to it than that, but this is what we will use it for.
- ◆ In this class, Verilog is an implementation language, not a design language
 - When you sit down to write verilog you should know *exactly* what you are implementing.
 - Draw your schematic and state machines and *transcribe* it into Verilog.
- ◆ We are constraining you to a subset of the language for two reasons
 - Reduce complexity for the course
 - These are parts that people use to design real processors

Courtesy of Arvind
Courtesy of Arvind [http://
csg.csail.mit.edu/6.375/](http://csg.csail.mit.edu/6.375/)

Verilog Fundamentals

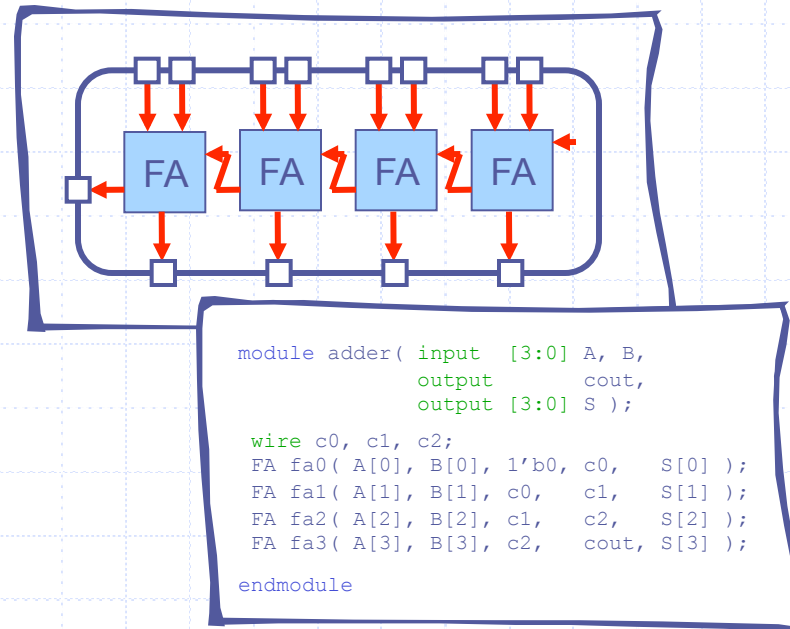- ◆ History of hardware design languages
- ◆ **Data types**
- ◆ Structural Verilog
- ◆ Simple behaviors



Courtesy of Arvind <http://csg.csail.mit.edu/6.375/>

Bit-vector is the only data type in Verilog

A bit can take on one of four values

Value	Meaning
0	Logic zero
1	Logic one
X	Unknown logic value
Z	High impedance, floating



In the simulation waveform viewer, Unknown signals are **RED**. There should be no red after reset

An X bit might be a 0, 1, Z, or in transition. We can set bits to be X in situations where we don't care what the value is. This can help catch bugs and improve synthesis quality.

“wire” is used to denote a hardware net

```
wire [15:0] instruction;  
wire [15:0] memory_req;  
wire [ 7:0] small_net;
```

  
Absolutely no type safety when connecting nets!



Courtesy of Arvind <http://csg.csail.mit.edu/6.375/>

Verilog Fundamentals

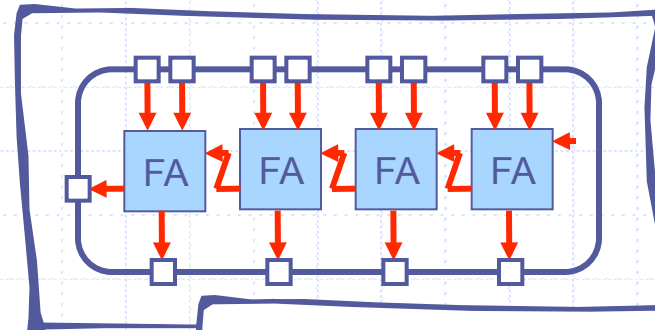- ◆ History of hardware design languages
- ◆ Data types
- ◆ **Structural Verilog**
- ◆ Simple behaviors



```
module adder( input  [3:0] A, B,
              output  cout,
              output  [3:0] S );


  wire c0, c1, c2;
  FA fa0( A[0], B[0], 1'b0, c0, S[0] );
  FA fa1( A[1], B[1], c0, c1, S[1] );
  FA fa2( A[2], B[2], c1, c2, S[2] );
  FA fa3( A[3], B[3], c2, cout, S[3] );

endmodule
```

Our Verilog Subset

- ◆ Verilog is a big language with many features not concerned with synthesizing hardware.
- ◆ The code you write for your processor should only contain the languages structures discussed in these slides.
- ◆ Anything else is not synthesizable, although it will simulate fine.
- ◆ You *MUST* follow the course coding standard

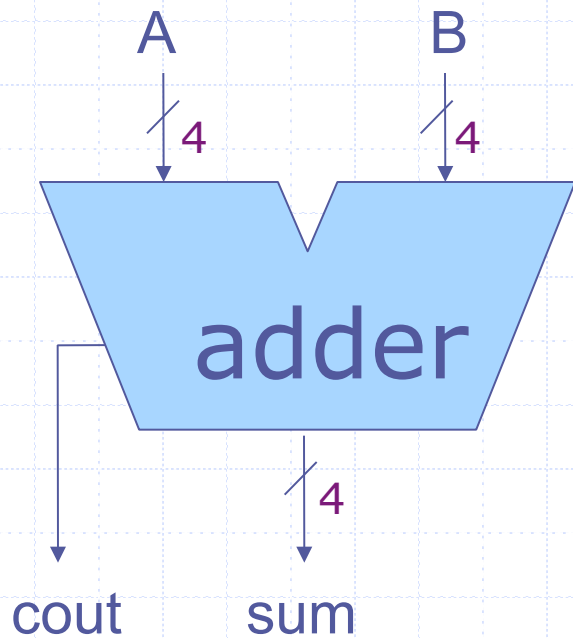A Verilog module has a name and a port list






```
module adder( input [3:0] A,  
              input [3:0] B,  
              output cout,  
              output [3:0] sum );  
  
    // HDL modeling of  
    // adder functionality  
  
endmodule
```

Ports must have a direction (or be bidirectional) and a bitwidth

Note the semicolon at the end of the port list!


A module can instantiate other modules

   

```
module adder( input  [3:0] A, B,
              output  cout,
              output  [3:0] S );
```

```
    wire c0, c1, c2;
    FA fa0( ... );
    FA fa1( ... );
    FA fa2( ... );
    FA fa3( ... );
```

```
endmodule
```

 


```
module FA( input  a, b, cin
           output cout, sum );
    // HDL modeling of 1 bit
    // full adder functionality
```

```
endmodule
```

Courtesy of Arvind <http://csg.csail.mit.edu/6.375/>

Connecting modules

 

```
module adder( input  [3:0] A, B,
              output          cout,
              output  [3:0] S );
```

```
    wire c0, c1, c2;
```

```
    FA fa0( A[0], B[0], 1'b0, c0, S[0] );
```

```
    FA fa1( A[1], B[1], c0, c1, S[1] );
```

```
    FA fa2( A[2], B[2], c1, c2, S[2] );
```

```
    FA fa3( A[3], B[3], c2, cout, S[3] );
```

```
endmodule
```

Courtesy of Arvind <http://csg.csail.mit.edu/6.375/>

Carry Chain

Alternative syntax

Connecting ports by ordered list

```
FA fa0( A[0], B[0], 1'b0, c0, S[0] );
```

Connecting ports by name (compact)

```
FA fa0( .a(A[0]), .b(B[0]),  
        .cin(1'b0), .cout(c0), .sum(S[0]) );
```

Argument order does not matter when ports are connected by name


```
FA fa0  
( .a    (A[0]),  
  .cin  (1'b0),  
  .b    (B[0]),  
  .cout (c0),  
  .sum  (S[0]) );
```

Connecting ports by name
yields clearer and less
buggy code.

Courtesy of Arvind [http://
csg.csail.mit.edu/6.375/](http://csg.csail.mit.edu/6.375/)

Verilog Fundamentals

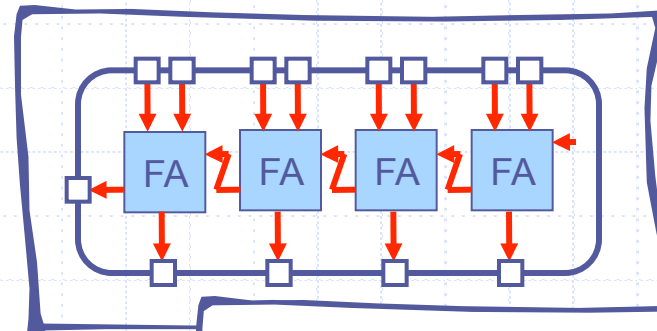- ◆ History of hardware design languages
- ◆ Data types
- ◆ Structural Verilog
- ◆ **Simple behaviors**



```
module adder( input  [3:0] A, B,
              output   cout,
              output  [3:0] S );

  wire c0, c1, c2;
  FA fa0( A[0], B[0], 1'b0, c0, S[0] );
  FA fa1( A[1], B[1], c0, c1, S[1] );
  FA fa2( A[2], B[2], c1, c2, S[2] );
  FA fa3( A[3], B[3], c2, cout, S[3] );

endmodule
```

A module's behavior can be described in many different ways but it should not matter from outside

Example: mux4


mux4: Using continuous assignments

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );

    wire out, t0, t1;
    assign out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
    assign t1 = ~( (sel[1] & d) | (~sel[1] & b) );
    assign t0 = ~( (sel[1] & c) | (~sel[1] & a) );

endmodule
```

Language defined operators

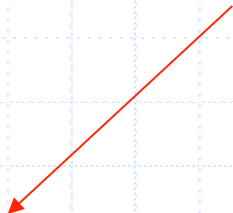

The order of these continuous assignment statements does not matter.
They essentially happen in parallel!

mux4: Behavioral style

```
// Four input multiplexer
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );

    assign out = ( sel == 0 ) ? a :
                 ( sel == 1 ) ? b :
                 ( sel == 2 ) ? c :
                 ( sel == 3 ) ? d : 1'bx;

endmodule
```

If input is undefined
we want to propagate
that information.

mux4: Using "always block"

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );

    reg out, t0, t1;

    always @( * )
    begin
        t0 = ~( (sel[1] & c) | (~sel[1] & a) );
        t1 = ~( (sel[1] & d) | (~sel[1] & b) );
        out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
    end

endmodule
```

The order of these procedural assignment statements DOES matter. They essentially happen sequentially!

“Always blocks” permit more advanced sequential idioms

```
module mux4( input  a,b,c,d
             input [1:0]
             sel,
             output out );

    reg out;
    always @( * )
    begin
        if ( sel == 2'd0 )
            out = a;
        else if ( sel == 2'd1 )
            out = b;
        else if ( sel == 2'd2 )
            out = c;
        else if ( sel == 2'd3 )
            out = d;
        else
            out = 1'bx;
    end
endmodule
```

```
module mux4( input  a,b,c,d
             input [1:0]
             sel,
             output out );

    reg out;
    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
            2'd3 : out = d;
            default : out = 1'bx;
        endcase
    end
endmodule
```

Typically we will use always blocks only to describe sequential circuits

What happens if the case statement is not complete?

```
module mux3( input  a, b, c
             input [1:0] sel,
             output out );

    reg out;

    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
        endcase
    end

endmodule
```

If sel = 3, mux will output the previous value!

What have we created?

What happens if the case statement is not complete?

```
module mux3( input  a, b, c
             input [1:0] sel,
             output out );

    reg out;

    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
            default : out = 1'bx;
        endcase
    end

endmodule
```

We CAN prevent creating state with a default statement

Parameterized mux4

```
module mux4 #( parameter WIDTH = 1 )
    ( input [WIDTH-1:0] a, b, c, d
      input [1:0] sel,
      output [WIDTH-1:0] out );
```

default value

```
    wire [WIDTH-1:0] out, t0, t1;
```

```
    assign t0 = (sel[1]? c : a);
```

```
    assign t1 = (sel[1]? d : b);
```

```
    assign out = (sel[0]? t0 : t1);
```

```
endmodule
```

Parameterization is a good practice for reusable modules

Writing a mux n is challenging

Instantiation Syntax



```
mux4#(32) alu_mux
    (.a (op1),
     .b (op2),
     .c (op3),
     .d (op4),
     .sel (alu_mux_sel),
     .out (alu_mux_out) );
```

Verilog Registers “reg”



- ◆ Wires are line names – they do not represent storage and can be assigned only once
- ◆ Regs are imperative variables (as in C):
 - “nonblocking” assignment $r \leq v$
 - can be assigned multiple times and holds values between assignments

flip-flops
  
```
module FF0 (input clk, input d,  
           output reg q);  
always @(posedge clk )  
begin  
    q <= d;  
end  
endmodule
```



  
```
module FF (input clk, input d,  
          input en, output reg q);  
always @(posedge clk )  
begin  
    if ( en )  
        q <= d;  
end  
endmodule
```



flip-flops with reset
 
```
always @(posedge clk)
begin
  if (~resetN)
    Q <= 0;
  else if (enable)
    Q <= D;
end
synchronous reset
```



Register

```
module register#(parameter WIDTH = 1)
(
    input  clk,
    input  [WIDTH-1:0] d,
    input  en,
    output [WIDTH-1:0] q
);

    always @( posedge clk )
    begin
        if (en)
            q <= d;
    end

endmodule
```

Register in terms of Flipflops

```
module register2
( input  clk,
  input  [1:0] d,
  input  en,
  output [1:0] q );

  always @(posedge clk)
  begin
    if (en)
      q <= d;
  end

endmodule
```

```
module register2
( input  clk,
  input  [1:0] d,
  input  en,
  output [1:0] q
);
  FF ff0 (.clk(clk), .d(d[0]),
          .en(en), .q(q[0]));

  FF ff1 (.clk(clk), .d(d[1]),
          .en(en), .q(q[1]));

endmodule
```

Do they behave the same?

yes