

2013 Fall CSE140L

*Digital Systems Laboratory*


Lecture #7

by

Dr. Choon Kim  
CSE Department, UCSD
 
# LAB#3: Vending Machine Controller Design

- It has many states – Init, zero cents, 5 cents, 10 cents, ....
- How to move from one state to other state?
- How to detect & handle dispensing?
- How to detect & handle One-dollar bill, credit-card and coin input?
- How to handle Reset?
- ....



# Hint: LAB3 works to be implemented

## ❑ VM(Vending Machine) operation:

- **two** always blocks (one for state transition, the other for output & next state determination)
- special cases handling

## ❑ Transition between initial state and VM-enabled modes:

- initial ->VM-enabled
- VM-enabled -> initial

## ❑ Reading inputs(sw0,1,2,5,9, etc.):


- always(\*).... or, assign....

# Mealy vs. Moore FSM


Mealy Machine:  $y(t) = f(x(t), s(t))$

Moore Machine:  $y(t) = f(s(t))$

$$s(t+1) = g(x(t), s(t))$$

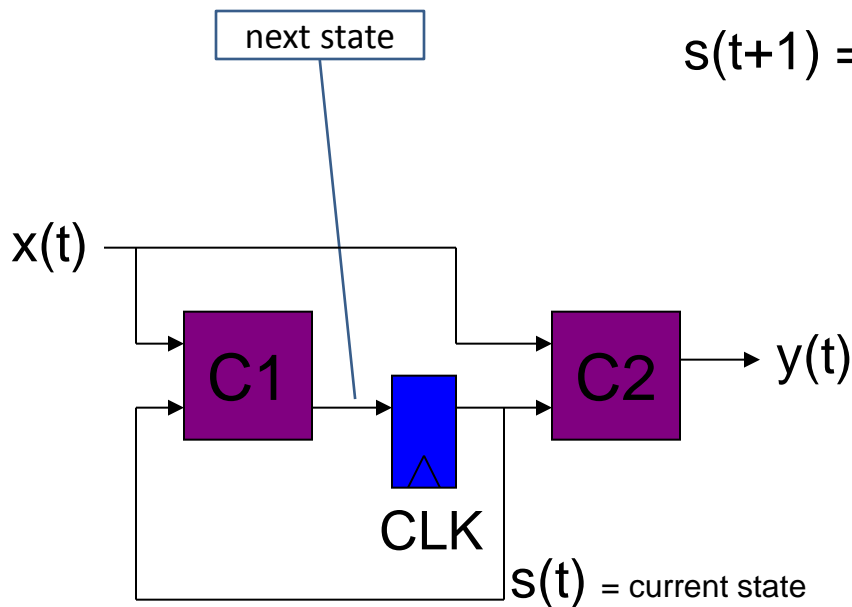

Mealy Machine

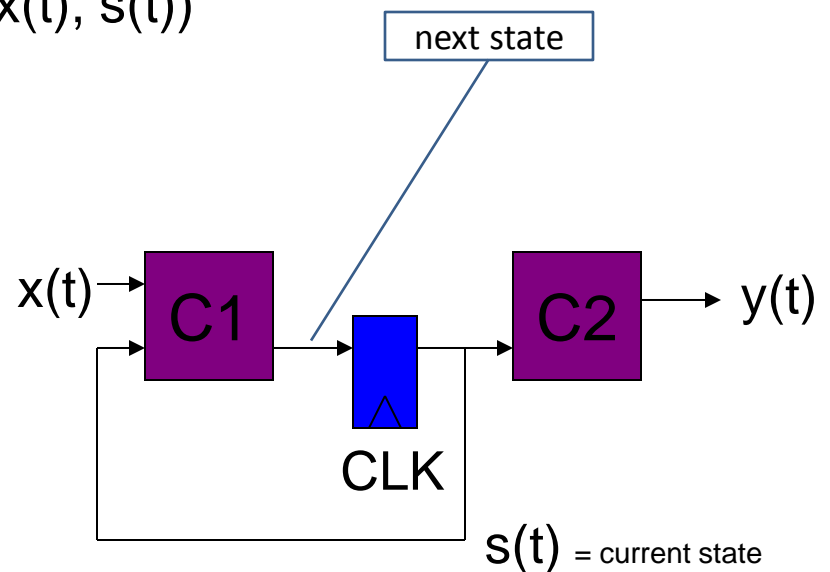

Moore Machine



# FSM design example – Moore vs. Mealy

A circuit which removes one **1** (i.e., the first 1) from every string of 1s on the input stream:

input		output
..... 00000.....	=>	..... 00000.....
..... 0 <b>1</b> 0 <b>1</b> 0.....	=>	..... 00000.....
..... 001 <b>1</b> 0.....	=>	..... 00100.....
..... 011 <b>1</b> 0.....	=>	..... 01100.....
..... 1 <b>1</b> 01 <b>1</b> .....	=>	..... 10010.....
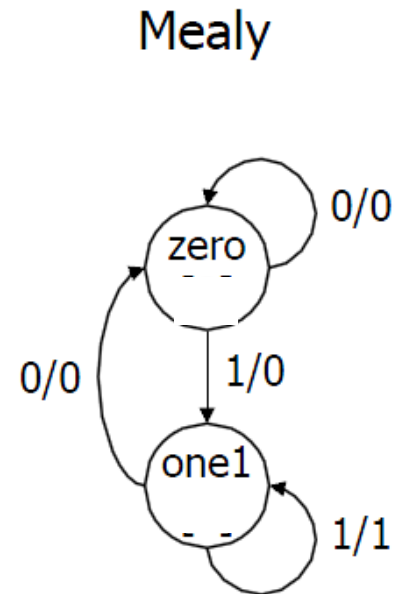 
# FSM design example – Moore vs. Mealy

- Remove one 1 from every string of 1s on the input




## Moore FSM Verilog model:(Not necessary working solution)

```
module reduce (input  clk, in,  
              output reg out);
```

```
parameter zero = 2'b00, one1 = 2'b01, two1s = 2'b10;  
reg[2:1] state, next_state;
```

```
always @(posedge clk) begin  
    state = next_state;  
end
```

```
always @(in, state) begin  
    case (state)  
        zero: begin  
            out = 0;  
            if (in) next_state= one1;  
            else  next_state= zero;  
        end  
        one1: begin  
            out = 0;  
            if (in) next_state= two1s;  
            else  next_state= zero;  
        end  
        two1s: begin  
            out = 1;  
            if (in) next_state= two1s;  
            else  next_state= zero;  
        end  
    endcase  
end  
end  
end module
```

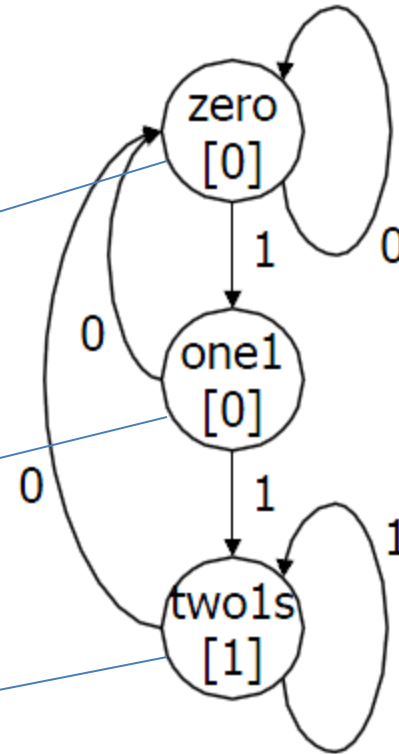

add default: statement here...


## Mealy FSM Verilog model: (Not necessary working solution)

```
module reduce (input  clk, in,  
              output reg out);
```

```
parameter zero = 1'b0, one = 1'b1;  
reg state, next_state;
```

```
always @(posedge clk) begin  
    state = next_state;  
end
```

```
always @(in, state) begin  
    case (state)  
        zero: begin  
            out = 0;  
            if (in) next_state= one;  
            else  next_state= zero;  
        end  
        one: begin  
            out = 0; ←  
            if (in) begin  
                out = 1;  
                next_state= one;  
            end  
            else begin  
                out = 0;  
                next_state= zero;  
            end  
        end  
    endcase ←  
end  
end  
end module
```

 

add default: statement here...