

2.16 Convert each of the following equations directly to gate-level circuits:

a. $F = ab' + bc + c'$

b. $F = ab + b'c'd'$

c. $F = ((a + b') * (c' + d)) + (c + d + e')$

