

6.16 Reduce the number of states for the FSM in Figure 6.90 by eliminating redundant states.

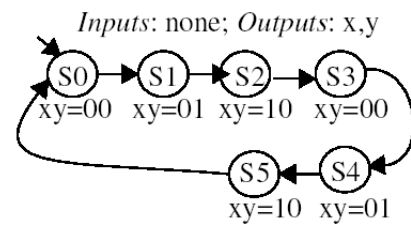


Figure 6.90: FSM example.

*Inputs: none; Outputs: x,y*

