



CSE140: Components and Design Techniques for Digital Systems

Boolean algebra & logic circuits

Tajana Simunic Rosing


Boolean algebra

- **Boolean Algebra**

- $B = \{0, 1\}$
- Variables represent 0 or 1 only
- Operators return 0 or 1 only
- Basic operators
 - \cdot is logical AND: $a \text{ AND } b$ returns 1 only when both $a=1$ and $b=1$
 - $+$ is logical OR: $a \text{ OR } b$ returns 1 if either (or both) $a=1$ or $b=1$
 - $'$ is logical NOT: $\text{NOT } a$ returns the opposite of a (1 if $a=0$, 0 if $a=1$)
- All algebraic axioms hold

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

OR

 


a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

AND



a	NOT
0	1
1	0

NOT

 

Axioms and theorems of Boolean algebra

- identity
 1. $X + 0 = X$
 - 1D. $X \cdot 1 = X$
- null
 2. $X + 1 = 1$
 - 2D. $X \cdot 0 = 0$
- idempotency:
 3. $X + X = X$
 - 3D. $X \cdot X = X$
- involution:
 4. $(X')' = X$
- complementarity:
 5. $X + X' = 1$
 - 5D. $X \cdot X' = 0$
- commutativity:
 6. $X + Y = Y + X$
 - 6D. $X \cdot Y = Y \cdot X$
- associativity:
 7. $(X + Y) + Z = X + (Y + Z)$
 - 7D. $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$

Axioms and theorems of Boolean algebra (cont'd)

- distributivity:

$$8. X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z) \quad 8D. X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$$

- uniting:

$$9. X \cdot Y + X \cdot Y' = X$$

$$9D. (X + Y) \cdot (X + Y') = X$$

- absorption:

$$10. X + X \cdot Y = X$$

$$10D. X \cdot (X + Y) = X$$

$$11. (X + Y') \cdot Y = X \cdot Y$$

$$11D. (X \cdot Y') + Y = X + Y$$

- factoring:

$$12. (X + Y) \cdot (X' + Z) = X \cdot Z + X' \cdot Y$$

$$12D. X \cdot Y + X' \cdot Z = (X + Z) \cdot (X' + Y)$$

- consensus:

$$13. (X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = X \cdot Y + X' \cdot Z$$

$$13D. (X + Y) \cdot (Y + Z) \cdot (X' + Z) = (X + Y) \cdot (X' + Z)$$

Axioms and theorems of Boolean algebra (cont'd)



- de Morgan's:
14. $(X + Y + \dots)' = X' \cdot Y' \cdot \dots$ 14D. $(X \cdot Y \cdot \dots)' = X' + Y' + \dots$
- generalized de Morgan's:
15. $f'(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) = f(X_1', X_2', \dots, X_n', 1, 0, \cdot, +)$
- establishes relationship between \cdot and $+$

Axioms and theorems of Boolean algebra (cont'd)

- Duality

- a dual of a Boolean expression is derived by replacing
 - by +, + by •, 0 by 1, and 1 by 0, and leaving variables unchanged
- any theorem that can be proven is thus also proven for its dual!
- a meta-theorem (a theorem about theorems)

- duality:

$$16. X + Y + \dots \Leftrightarrow X \cdot Y \cdot \dots$$

- generalized duality:

$$17. f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) \Leftrightarrow f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +)$$

- Different than deMorgan's Law

- this is a statement about theorems
- this is not a way to manipulate (re-write) expressions

Proving theorems

- Using the axioms of Boolean algebra:

– e.g., prove the theorem: $X \cdot Y + X \cdot Y' = X$

distributivity (8)	$X \cdot Y + X \cdot Y'$	=	$X \cdot (Y + Y')$
complementarity (5)	$X \cdot (Y + Y')$	=	$X \cdot (1)$
identity (1D)	$X \cdot (1)$	=	$X \checkmark$

– e.g., prove the theorem: $X + X \cdot Y = X$

identity (1D)	$X + X \cdot Y$	=	$X \cdot 1 + X \cdot Y$
distributivity (8)	$X \cdot 1 + X \cdot Y$	=	$X \cdot (1 + Y)$
identity (2)	$X \cdot (1 + Y)$	=	$X \cdot (1)$
identity (1D)	$X \cdot (1)$	=	$X \checkmark$

Proving theorems example

- Prove the following using the laws of Boolean algebra:
 - $(X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = X \cdot Y + X' \cdot Z$

$$(X \cdot Y) + (Y \cdot Z) + (X' \cdot Z)$$

identity

$$(X \cdot Y) + (1) \cdot (Y \cdot Z) + (X' \cdot Z)$$

complementarity

$$(X \cdot Y) + (X' + X) \cdot (Y \cdot Z) + (X' \cdot Z)$$

distributivity

$$(X \cdot Y) + (X' \cdot Y \cdot Z) + (X \cdot Y \cdot Z) + (X' \cdot Z)$$

commutativity

$$(X \cdot Y) + (X \cdot Y \cdot Z) + (X' \cdot Y \cdot Z) + (X' \cdot Z)$$

factoring

$$(X \cdot Y) \cdot (1 + Z) + (X' \cdot Z) \cdot (1 + Y)$$

null

$$(X \cdot Y) \cdot (1) + (X' \cdot Z) \cdot (1)$$

identity

$$(X \cdot Y) + (X' \cdot Z) \checkmark$$

Proving theorems (perfect induction)

- Using perfect induction (complete truth table):
 - e.g., de Morgan's:

$(X + Y)' = X' \cdot Y'$
NOR is equivalent to AND
with inputs complemented


X	Y	X'	Y'	(X + Y)'	X' · Y'
0	0	1	1		
0	1	1	0		
1	0	0	1		
1	1	0	0		

$(X \cdot Y)' = X' + Y'$
NAND is equivalent to OR
with inputs complemented

X	Y	X'	Y'	(X · Y)'	X' + Y'
0	0	1	1		
0	1	1	0		
1	0	0	1		
1	1	0	0		

Example that Applies Boolean Algebra Properties

- Want automatic door opener circuit (e.g., for grocery store)
 - Output: $f=1$ opens door
 - Inputs:
 - $p=1$: person detected
 - $h=1$: switch forcing hold open
 - $c=1$: key forcing closed
 - Want open door when
 - $h=1$ and $c=0$, or
 - $h=0$ and $p=1$ and $c=0$
- Found inexpensive chip that computes:
 - $f = c'hp + c'hp' + c'h'p$
 - Can we use it?



CSE140: Components and Design Techniques for Digital Systems


Combinational circuit building blocks:
Building gates from transistors

Tajana Simunic Rosing




Inverter delay



 
- Delay: estimate using R_n & C_g ; $R_p=2R_n$





x	F
0	1
1	0

   



Basic CMOS gates

 


x	F
0	1
1	0

  

x	y	F
0	0	1
0	1	0
1	0	0
1	1	0

  

x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

 


- Implement logic operators using transistors
 - Call those implementations **logic gates**




AND/OR gates


 
- OR/AND are harder to make than NOR/NAND



x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

 



x	y	F
0	0	0
0	1	0
1	0	0
1	1	1

  

Completeness of NAND

- Any logic function can be implemented *using just NAND gates*. Likewise for *NOR*. Why?
 - Need AND, OR and NOT


XOR/XNOR Gates

  


x	y	F
0	0	0
0	1	1
1	0	1
1	1	0

x	y	F
0	0	1
0	1	0
1	0	0
1	1	1

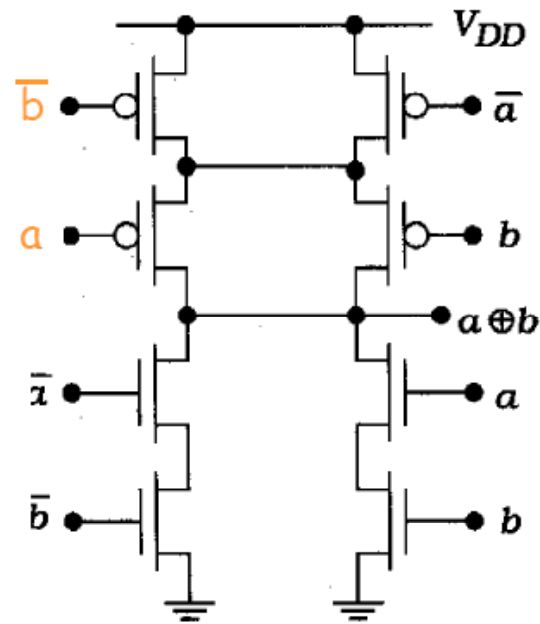- $XOR = x'y + xy' = (xy + x'y)'$ (Exclusive OR)
- $XNOR = (x'y + xy) = xy + x'y'$ (Exclusive OR)



(a) Exclusive-OR

 

(b) Exclusive-NOR

Number of Possible Boolean Functions

- # of possible functions of 2 variables:
 - 2^2 rows in truth table, 2 choices for each
 - $2^{(2^2)} = 2^4 = 16$ possible functions

a	b	F
0	0	0 or 1 2 choices
0	1	0 or 1 2 choices
1	0	0 or 1 2 choices
1	1	0 or 1 2 choices

- N variables
 - 2^N rows
 - $2^{(2^N)}$ possible functions

$2^4 = 16$
possible functions

- Cost

a	b	f0	f1	f2	f3	f4	f5	f6	f7	f8	f9	f10	f11	f12	f13	f14	f15
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
		0	a AND b		a		b	a XOR b	a OR b	a NOR b	a XNOR b	b'		a'		a NAND b	1

- a' (F12) and b' (F10): require 2 transistors for an inverter (not gate)
- a nor b (F4) and a nand b (F14): require 4 transistors
- a or b (F7) and a and b (F1): require 6 transistors
- a = b (F9) and $a \oplus b$ (F6): require 12 transistors

Circuits for binary addition

- Half adder (add 2 1-bit numbers)

– Sum =

– Cout =


Ai	Bi	Sum	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

- Full adder (carry-in to cascade for multi-bit adders)

– Sum =




– Cout =

Ai	Bi	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


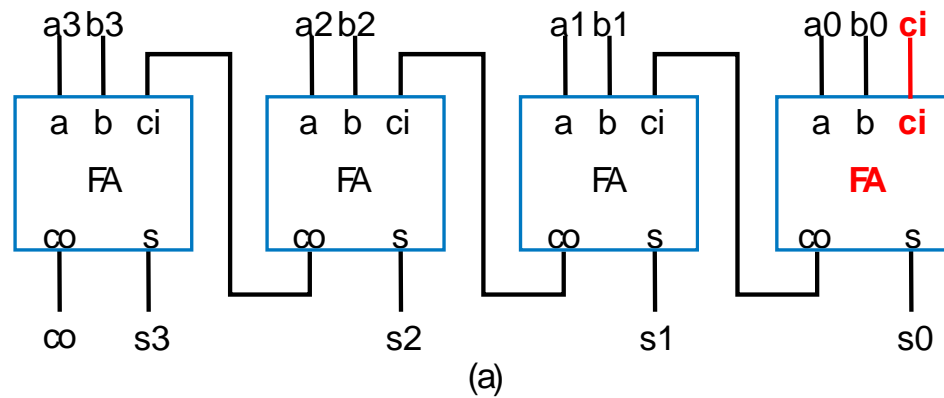  Example: 4-bit binary adder

- Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out



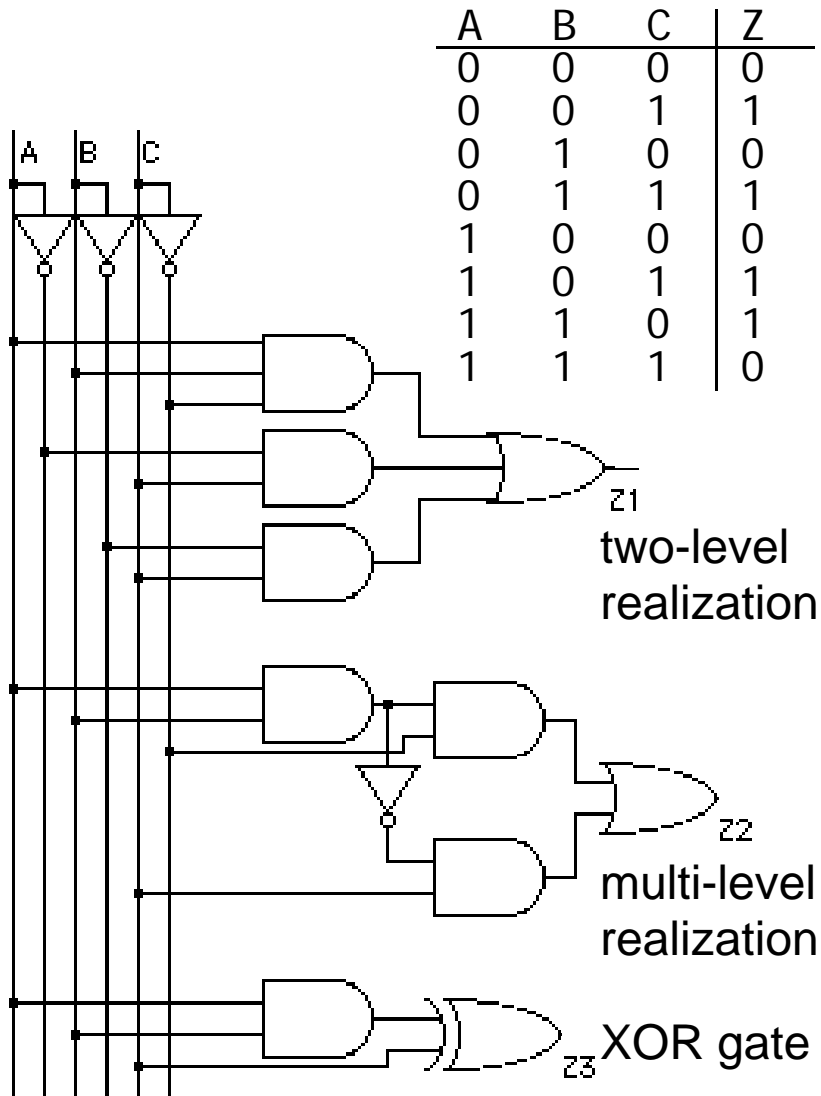Choosing different realizations of a function



Which is the best realization and why?

- Reduce number of levels of gates
 - fewer level of gates implies reduced signal propagation delays
 - minimum delay configuration typically requires more gates
- Reduce number of inputs
 - fewer inputs implies smaller and thus faster gates; fan-in can be limited
- Reduce number of gates
 - fewer gates means smaller circuits - directly influences manufacturing costs
- Exploring tradeoffs between increased circuit delay and size
 - tools to generate different solutions
 - logic minimization: reduce number of gates and complexity
 - logic optimization: reduction while trading off against delay


DeMorgan and CMOS

- Use it to figure out P & NMOS parts of gates

- DeMorgan Relations


- NAND-OR rule $\overline{a \cdot b} = \overline{a} + \overline{b}$

- bubble pushing illustration

 


- bubbles = inversions

 - NOR-AND rule $\overline{a + b} = \overline{a} \cdot \overline{b}$




- pMOS and bubble pushing

- Parallel-connected pMOS

 

- assert-low OR
- creates NAND function

- Series-connected pMOS

 

Rules for making gates

The Mathematical Method

- Given a logic function

$$F = f(a, b, c)$$

- Reduce (using DeMorgan) to eliminate inverted operations
 - inverted variables are OK, but not operations (NAND, NOR)
- Form pMOS network by complementing the **inputs**

$$F_p = f(\overline{a}, \overline{b}, \overline{c})$$

- Form the nMOS network by complementing the **output**

$$F_n = \overline{f(a, b, c)} = \overline{F}$$

- Construct F_n and F_p using AND/OR series/parallel MOSFET structures



- series = AND, parallel = OR

EXAMPLE:

$$F = \overline{ab} \Rightarrow$$

$$F_p = \overline{\overline{a} \overline{b}} = a+b; \quad \text{OR/parallel}$$
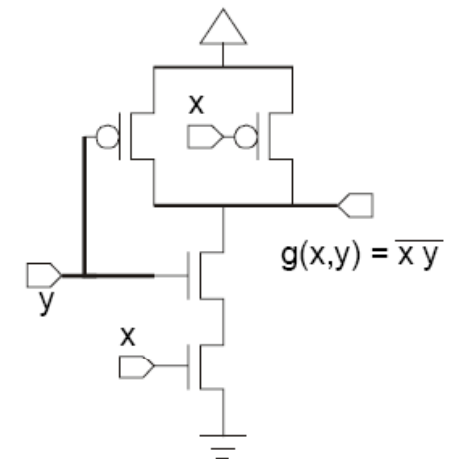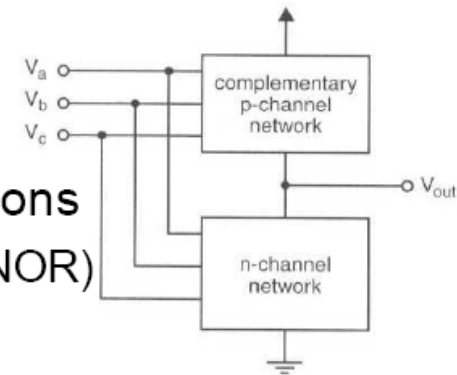
$$F_n = \overline{\overline{ab}} = ab; \quad \text{AND/series}$$



Another way of making CMOS gates

- Reducing Logic Functions

- fewest operations \Rightarrow fewest txs

- minimized function to eliminate txs

- Example: $x y + x z + x v = x (y + z + v)$

5 operations:

3 AND, 2 OR

txs =

3 operations:

1 AND, 2 OR

txs =

- Suggested approach to implement a CMOS logic function

- create nMOS network

- invert output

- reduce function, use DeMorgan to eliminate NANDs and NORs

- implement using **series** for AND and **parallel** for OR

- create pMOS network

- complement each operation in nMOS network

CMOS Example

- Construct the function below in CMOS


$$F = \overline{a + b \cdot (c + d)}; \text{ remember AND operations occur before OR}$$

- Step 1, invert output and find nMOS

- nMOS; implement $a + b \cdot (c + d)$
- Group 1: c & d in parallel
- Group 2: b in series with G1
- Group 3: a parallel to G2

- Step 2, complement operations

 
- pMOS
- Group 1: c & d in series
- Group 2: b parallel to G1
- Group 3: a in series with G2



Another example

- Construct a CMOS logic gate which implements the function:

$$F = \overline{a \cdot (b + c)}$$

 

14 transistors

pMOS

- Apply DeMorgan expansions


$$F = \overline{a + (b + c)}$$

$$F = \overline{a} + (\overline{b} \cdot \overline{c})$$

- Invert inputs for pMOS

$$F_p = a + (b \cdot c)$$

- Resulting Schematic

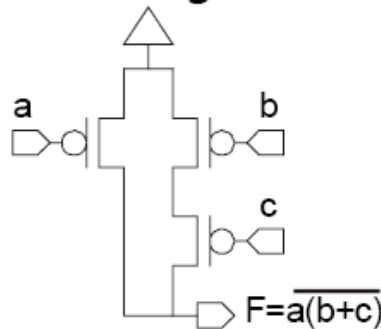


nMOS


- Invert output for nMOS

$$F_n = a \cdot (b + c)$$

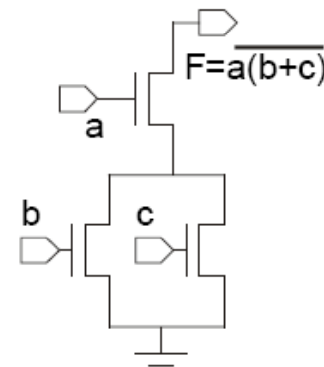- Apply DeMorgan none needed
- Resulting Schematic



6 transistors

 

One more example

- Implement the function below by constructing the nMOS network and complementing operations for the pMOS:

$$F = \overline{\overline{a} \cdot b} \cdot (a + c)$$

- nMOS**

- Invert Output

- $F_n = \overline{\overline{a} \cdot b} \cdot (a + c) = \overline{\overline{a} \cdot b} + \overline{(a + c)}$

- Eliminate NANDs and NORs

- $F_n = \overline{a} \cdot b + (\overline{a} \cdot c)$


- Reduce Function

- $F_n = \overline{a} \cdot (b + \overline{c})$

- Resulting Schematic ?

- Complement operations for pMOS**

- $F_p = a + (b \cdot c)$

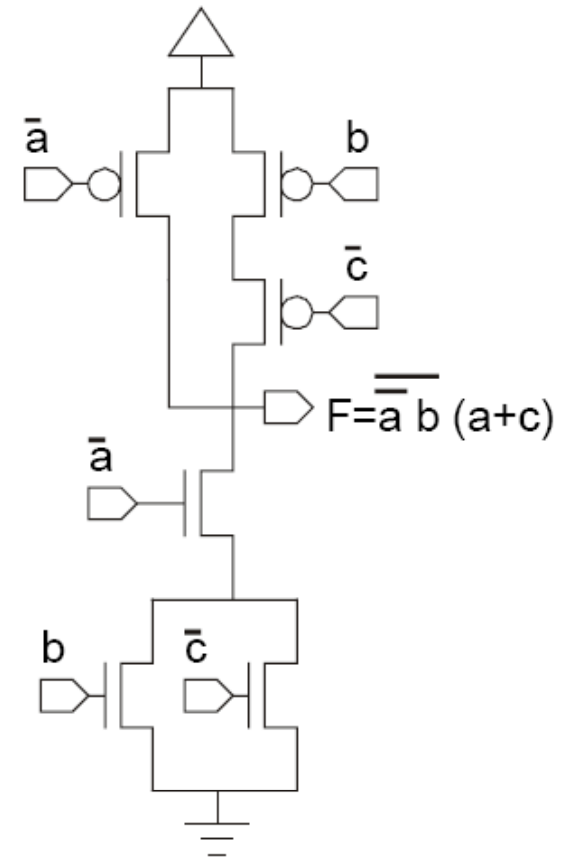

CMOS Example

- The rules:
 - NMOS connects to GND, PMOS to power supply Vdd
 - Duality of NMOS and PMOS
 - $R_p \sim 2 R_n \Rightarrow$ PMOS in series is much slower than NMOS in series
- Implement Z using CMOS: $Z = (A + BC)'$

Another CMOS Example

- Implement F using CMOS: $F=A*(B+C)$

Summary



- What we covered thus far:
 - Number representations
 - Switches, MOS transistors, Logic gates
 - Boolean algebra
 - Supplement: NMOS and PMOS transistor characteristics
- What is next:
 - Combinational logic:
 - Representations
 - Minimization
 - Implementations