

CSE 140: Components and Design Techniques for
Digital Systems

Lecture 8:
Sequential Networks and Finite State
Machines


CK Cheng

Dept. of Computer Science and Engineering
University of California, San Diego

Outlines


- Specification: Finite State Machine
 - State Table, State Diagram, Behavior
- Implementation
 - Excitation Table
 - Mealy and Moore Machines
 - Examples

Sequential Networks

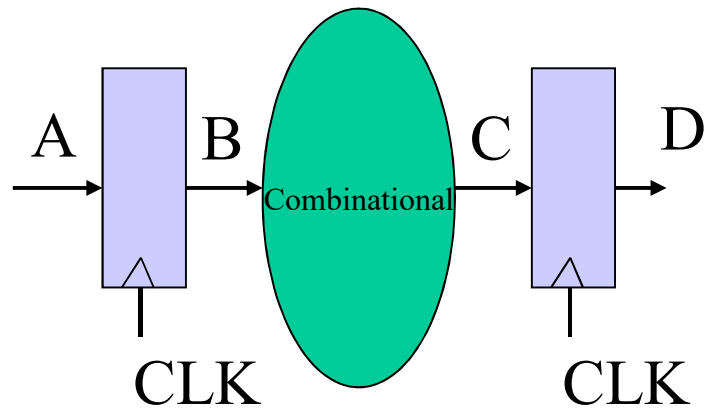

RTL: Register-Transfer Level
Description

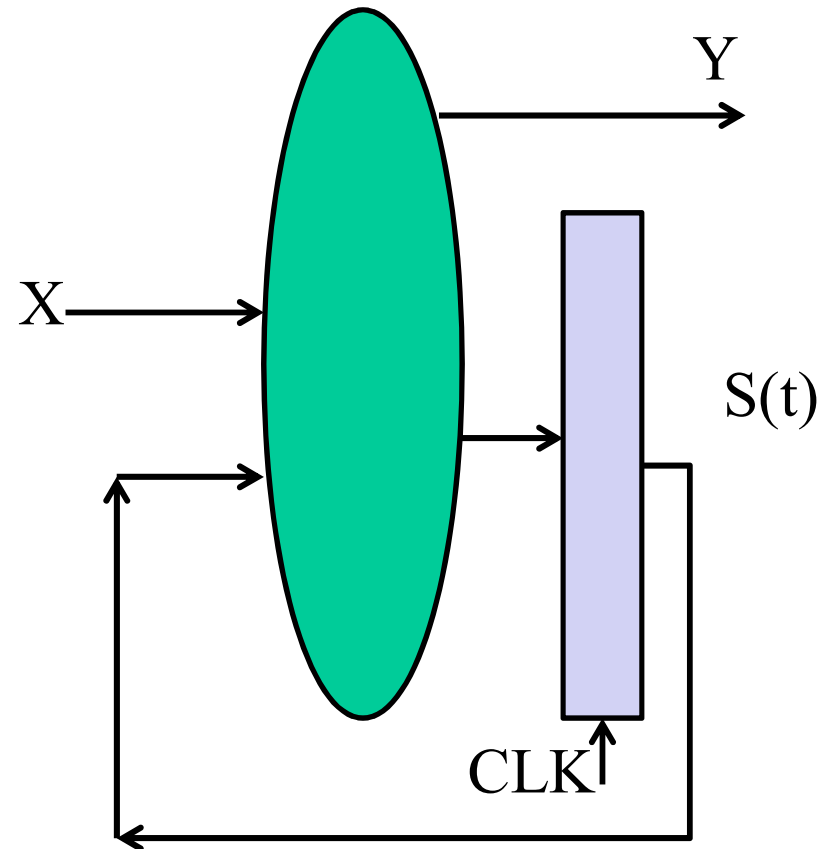1. Components F-Fs
2. Specification
3. Implementation: Excitation Table



Conceptually, we can align all registers into one single column

Specification

- Combinational Logic
 - Truth Table
 - Boolean Expression
 - Logic Diagram (No feedback loops)
- Sequential Networks:
 - State Diagram, State Assignment, State Table
 - Excitation Table and Characteristic Expression
 - Logic Diagram (FFs and feedback loops)

NOT ALL SEQUENCES ARE CREATED EQUAL

A coin has two faces. A toss of the coin lands either Head or Tail with equal probability. A series of tossing creates a sequence. Given two patterns, say HHH and HTT, the pattern appears first wins.


- A. The two patterns have an equal chance to win
- B. HHH wins more times
- C. HTT wins more times
- D. None of the above

Ⓜ Ⓜ Ⓜ Ⓜ Ⓜ Ⓜ




NOT ALL SEQUENCES ARE CREATED EQUAL

State Diagram of HHH

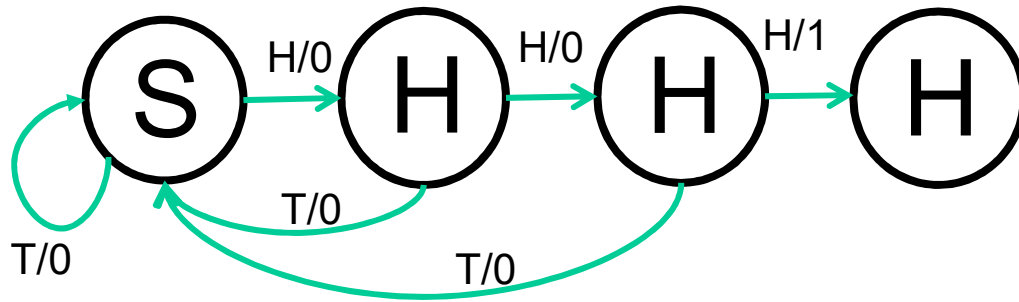

State Diagram of HTT

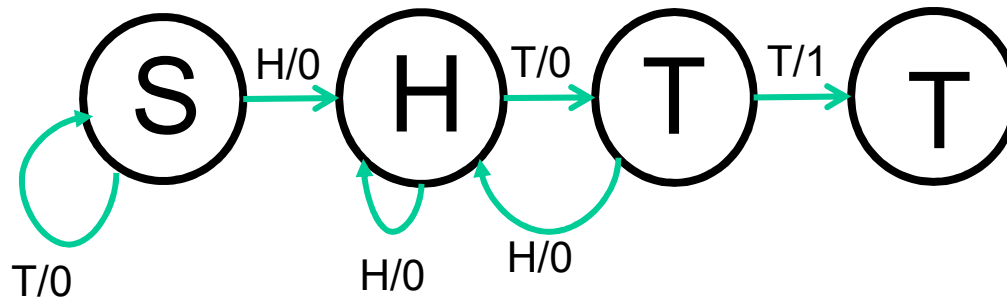

Different diagrams
yield different
expectations

Implementation: Design Flow

- Input Output Relation
- State Diagram (Transition of states)
 - State minimization (Reduction)
 - Finite state machine partitioning
- State Assignment (Map states into binary code)
 - Binary code, Gray encoding, One hot encoding, Coding optimization
- State Table (Truth table of states)
- Excitation Table (Truth table of FF inputs)
 - K Map, Minimal Expression
 - Logic Diagram

Implementation: Examples


- Example 1: a circuit with D Flip Flops
- Example 2: analysis of a sequential machine

State: What is it? Why do we need it?

Symbol/ Circuit



Behavior over time

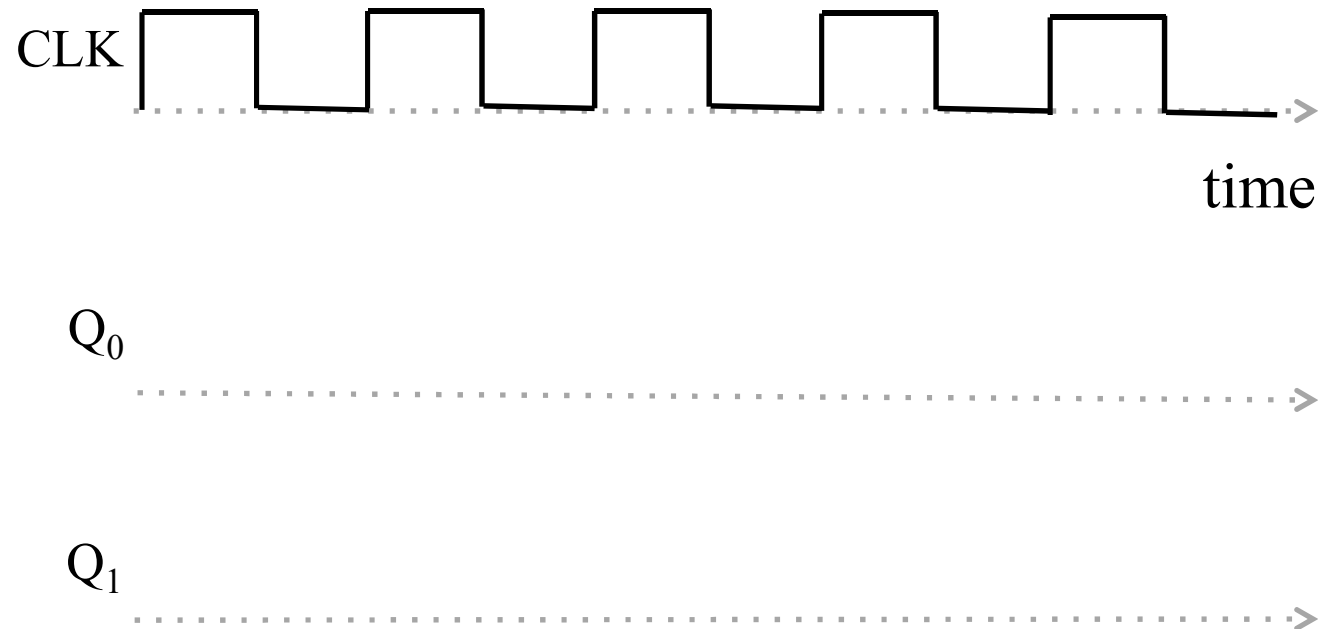

What is the expected output of the counter over time?

Finite State Machines: Describing circuit behavior over time

Symbol/ Circuit



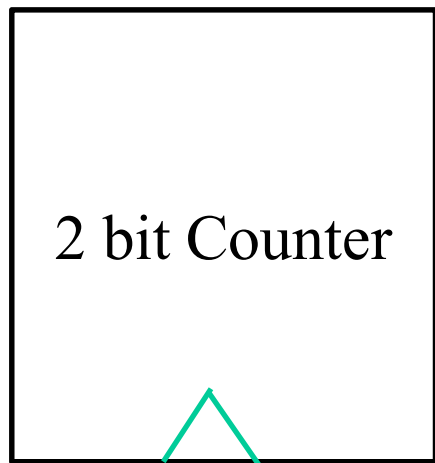


Diagram that depicts behavior over time

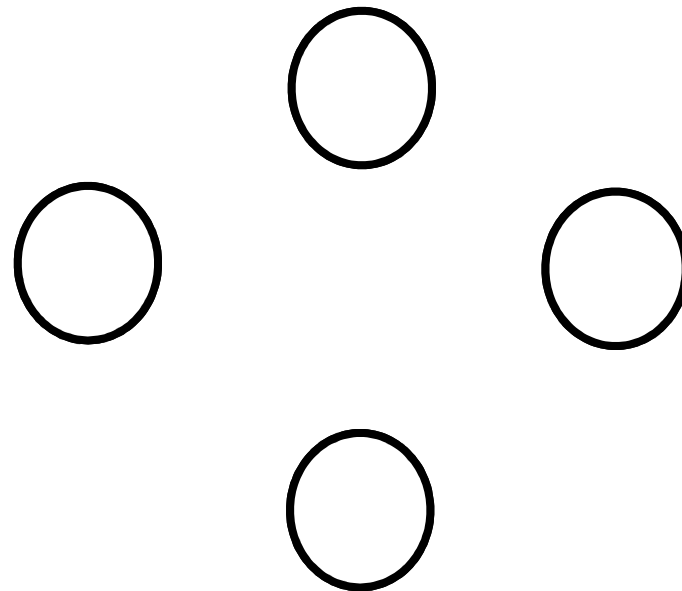

Implementing the 2 bit counter

State Diagram

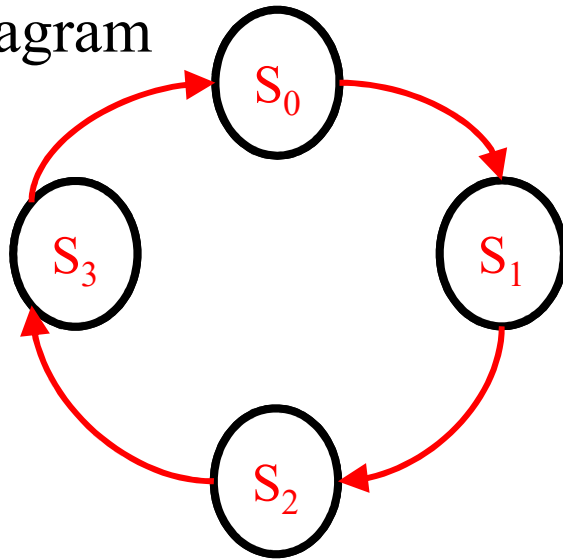

State Table: Symbol

| Current state | Next State |
|---------------|------------|
| S_0 | S_1 |
| S_1 | S_2 |
| S_2 | S_3 |
| S_3 | S_0 |

State


Assignment

| State | Q_1 | Q_0 |
|-------|-------|-------|
| S_0 | 0 | 0 |
| S_1 | 0 | 1 |
| S_2 | 1 | 0 |
| S_3 | 1 | 1 |

| $Q_1(t)$ | $Q_0(t)$ | $Q_1(t+1)$ | $Q_0(t+1)$ |
|----------|----------|------------|------------|
| | | | |
| | | | |
| | | | |
| | | | |

State Table: Binary

Implementing the 2 bit counter

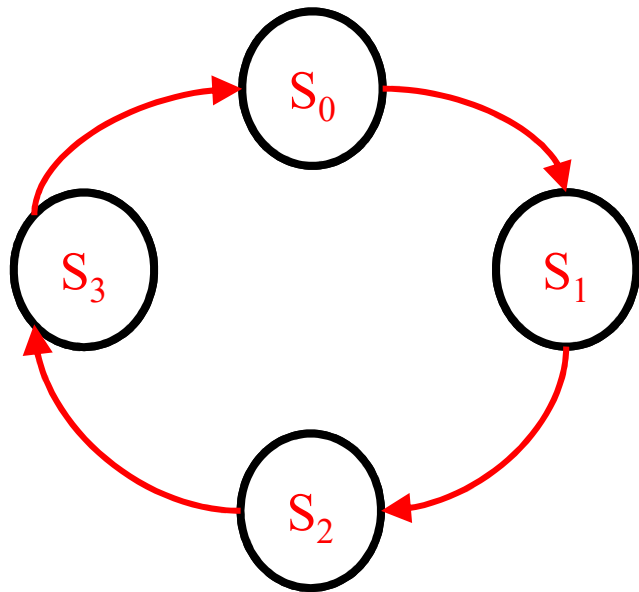

State Diagram

| Current state | Next State |
|---------------|------------|
| S_0 | S_1 |
| S_1 | S_2 |
| S_2 | S_3 |
| S_3 | S_0 |

| $Q_1(t)$ | $Q_0(t)$ | $Q_1(t+1)$ | $Q_0(t+1)$ |
|----------|----------|------------|------------|
| 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |


State Table

State Table

| $Q_1(t)$ | $Q_0(t)$ | $Q_1(t+1)$ | $Q_0(t+1)$ |
|----------|----------|------------|------------|
| 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |

$$D_0(t) = Q_0(t)'$$
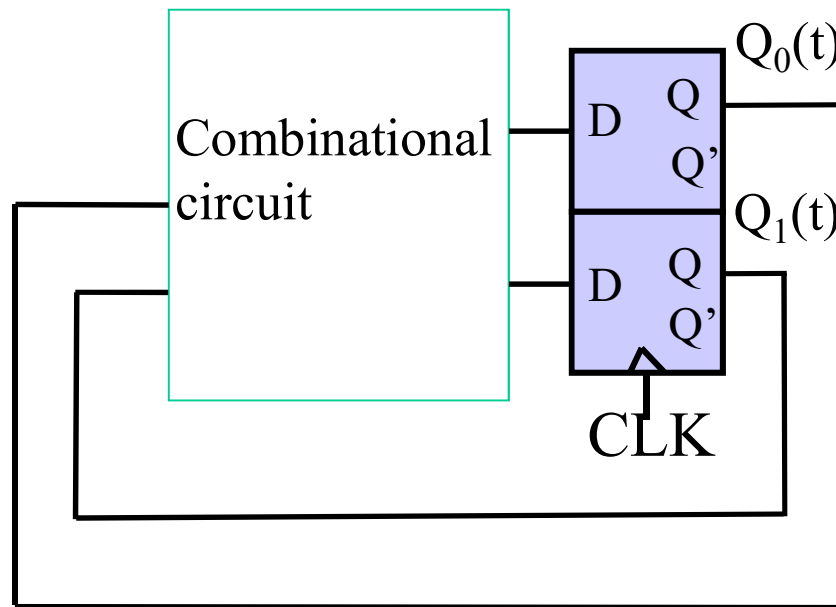
$$D_1(t) = Q_0(t) Q_1(t)' + Q_0(t)' Q_1(t)$$



Circuit with 2 flip flops


| $Q_1(t)$ | $Q_0(t)$ | $Q_1(t+1)$ | $Q_0(t+1)$ |
|----------|----------|------------|------------|
| 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |

State Table

Truth table → K map → Switching function

$$Q_0(t+1) = Q_0(t)'$$
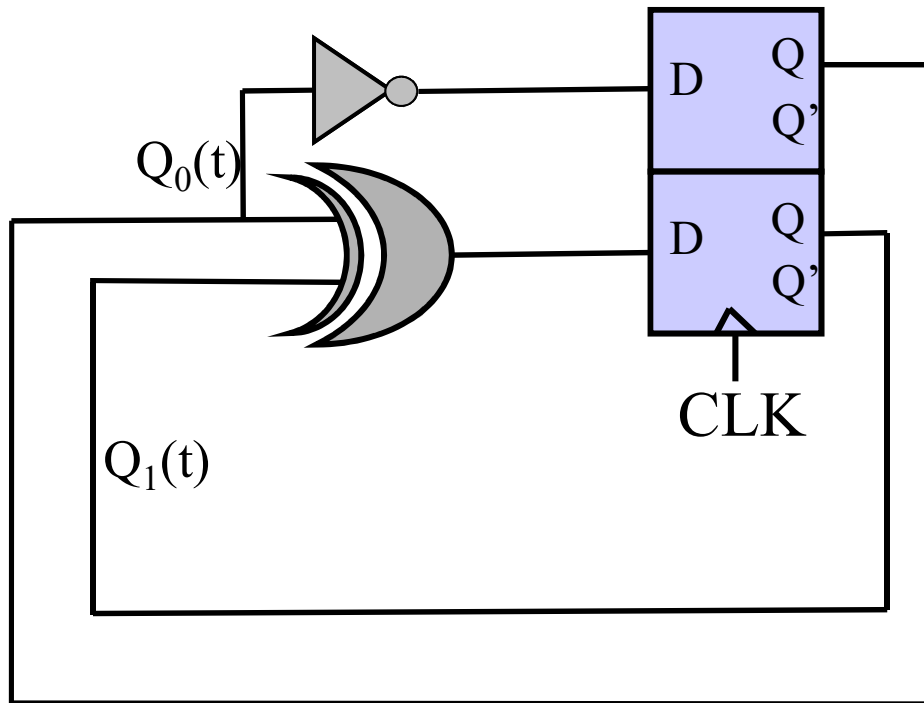
$$Q_1(t+1) = Q_0(t) Q_1(t)' + Q_0(t)' Q_1(t)$$




Implementation of 2-bit counter

We store the current state using D-flip flops so that:


- Inputs to the combinational circuit don't change while the next output is being computed
- The transition to the next state only occurs at the rising edge of the clock

Generalized Model of Sequential Circuits

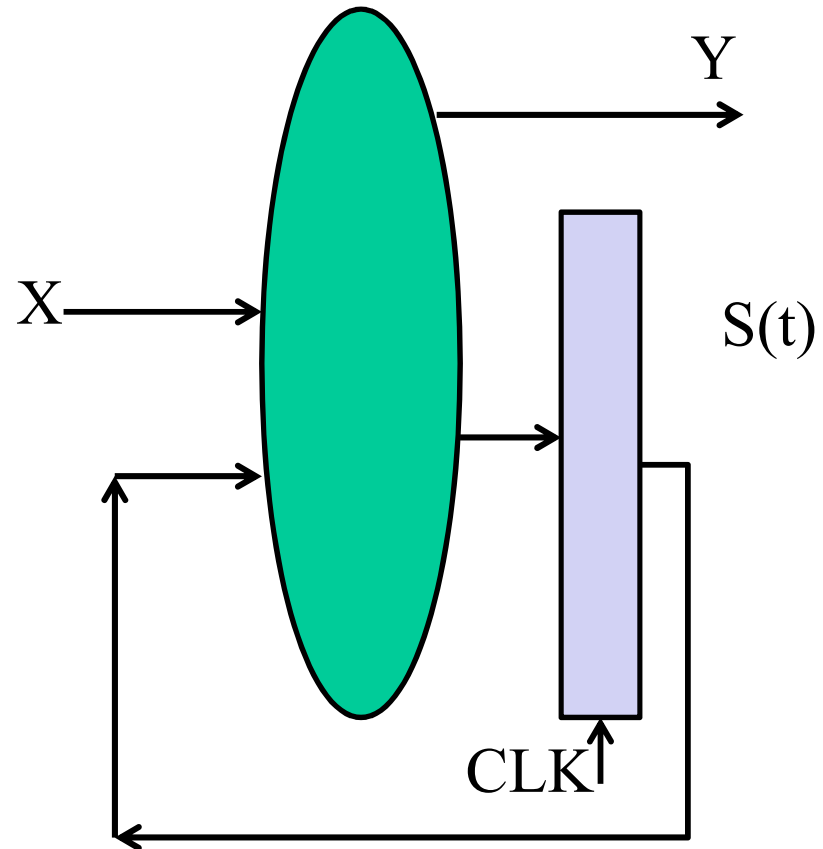

Netlist \Leftrightarrow State Table \Leftrightarrow State Diagram \Leftrightarrow Input Output Relation

| PS\Input | X=0 | X=1 |
|----------|------|------|
| S0 | S0,0 | S2,0 |
| S1 | S3,0 | S3,0 |
| S2 | S2,0 | S1,0 |
| S3 | S1,1 | S0,1 |

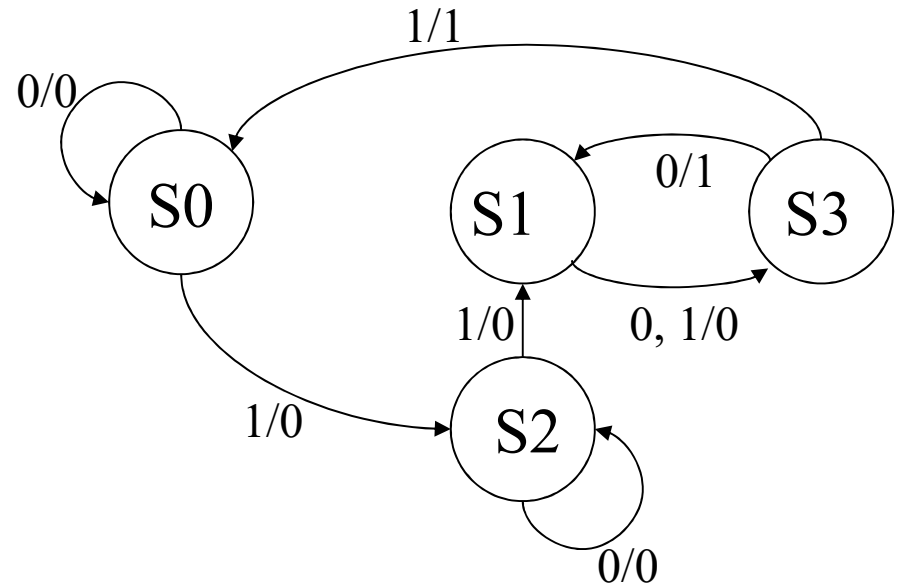


Example: Output sequence

| | | | | | | |
|--------|----|---|---|---|---|---|
| Time | 0 | 1 | 2 | 3 | 4 | 5 |
| Input | 0 | 1 | 1 | 0 | 1 | - |
| State | S0 | | | | | |
| Output | | | | | | |

Netlist \Leftrightarrow State Table \Leftrightarrow State Diagram \Leftrightarrow Input Output Relation

| PS\Input | X=0 | X=1 |
|----------|------|------|
| S0 | S0,0 | S2,0 |
| S1 | S3,0 | S3,0 |
| S2 | S2,0 | S1,0 |
| S3 | S1,1 | S0,1 |

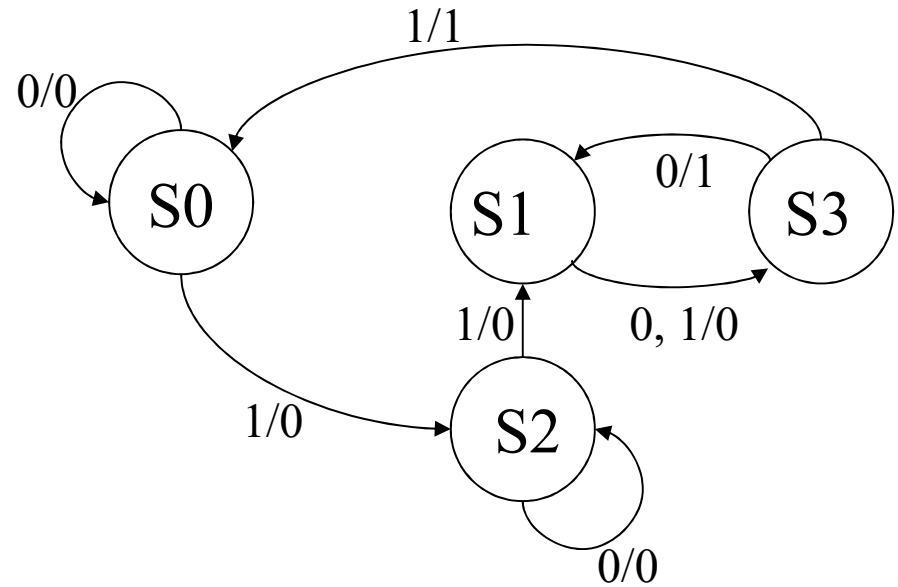

Example: Output sequence




| | | | | | | |
|--------|----|----|----|----|----|----|
| Time | 0 | 1 | 2 | 3 | 4 | 5 |
| Input | 0 | 1 | 1 | 0 | 1 | - |
| State | S0 | S0 | S2 | S1 | S3 | S0 |
| Output | 0 | 0 | 0 | 0 | 1 | 0 |

Implementation

State Diagram \Rightarrow State Table \Rightarrow Logic Diagram

- Canonical Form: Mealy and Moore Machines
 - Mealy machines: General
 - Moore machines: Output is independent of current input.
- Excitation Table
 - Truth Table of the F-F Inputs
 - Boolean algebra, K-maps for combinational logic
- Examples
- Timing

Canonical Form: Mealy and Moore Machines

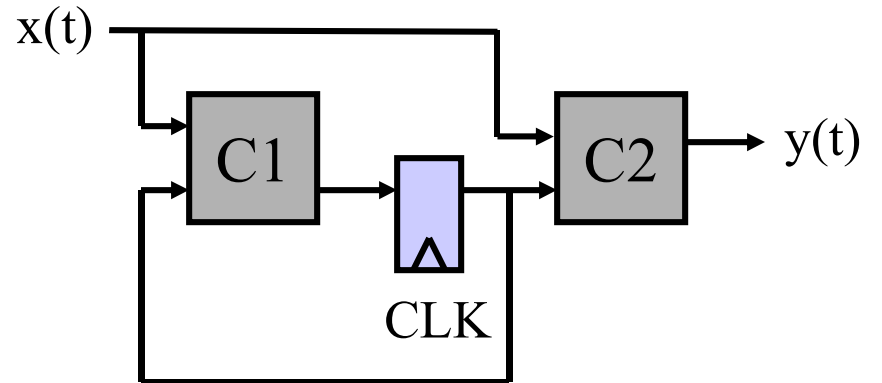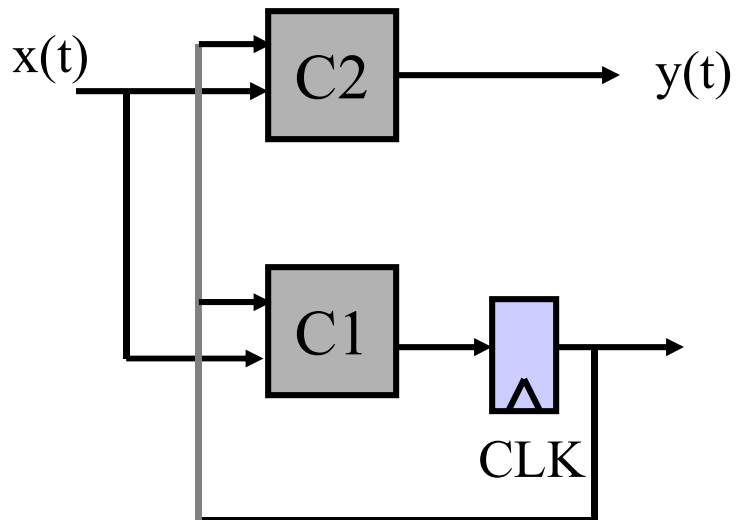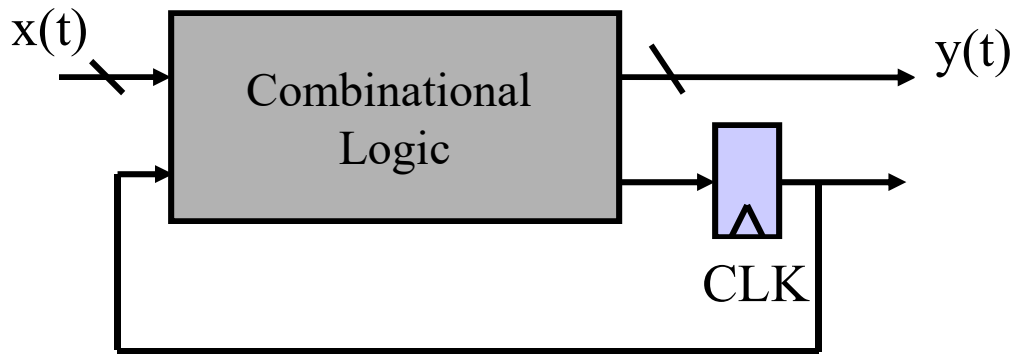


Canonical Form: Mealy and Moore Machines


Mealy Machine: $y_i(t) = f_i(X(t), S(t))$

Moore Machine: $y_i(t) = f_i(S(t))$

$$s_i(t+1) = g_i(X(t), S(t))$$

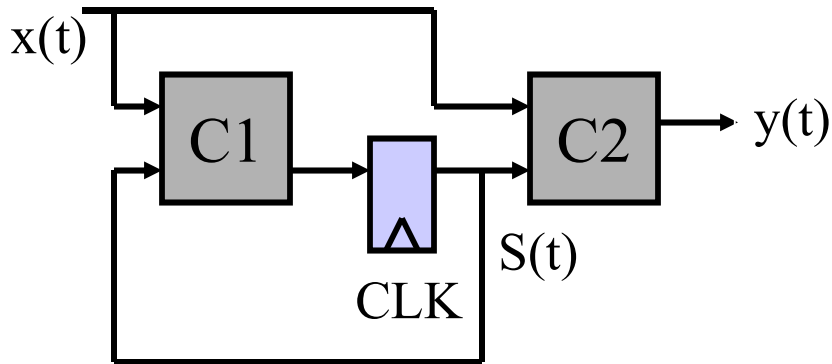

Mealy Machine

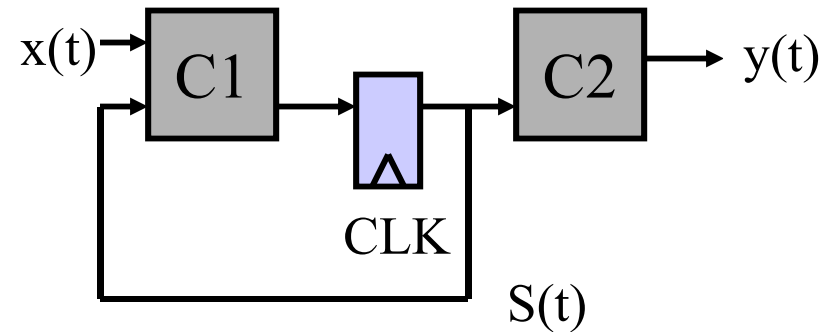

Moore Machine


Canonical Form: Mealy and Moore Machines

Mealy Machine: $y_i(t) = f_i(X(t), S(t))$


Moore Machine: $y_i(t) = f_i(S(t))$

$s_i(t+1) = g_i(X(t), S(t))$


Mealy Machine

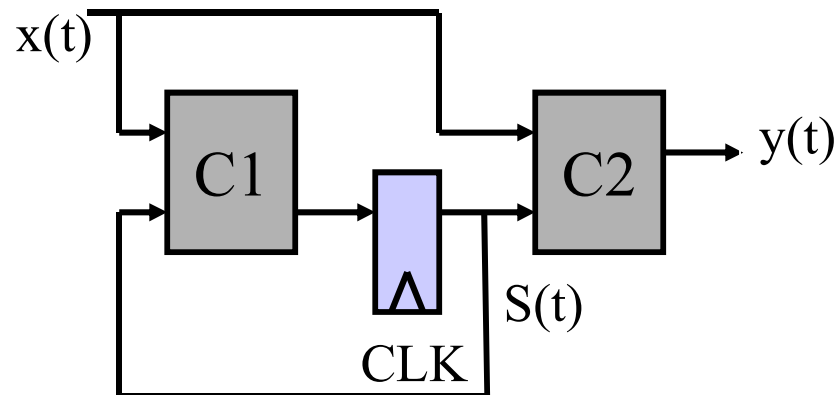


| | |
|----|------------|
| | Input |
| PS | NS, output |

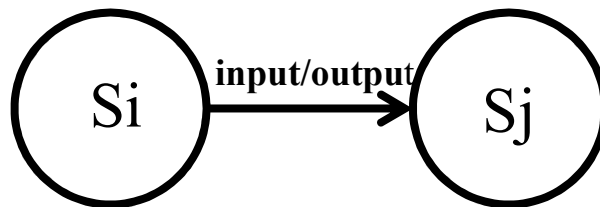

Moore Machine

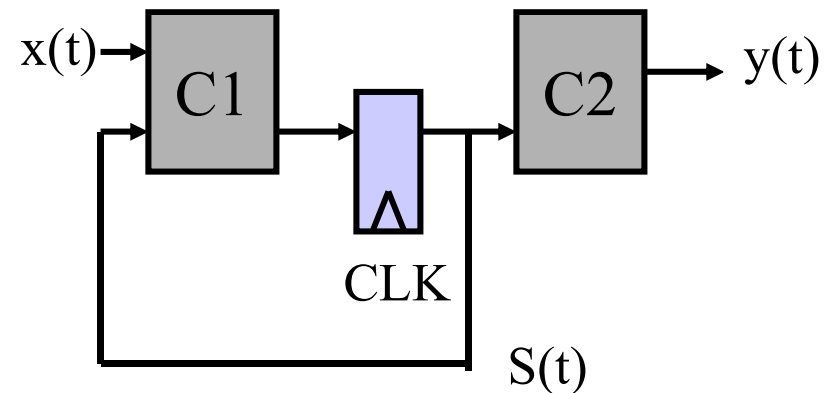

| | | |
|----|-------|--------|
| | Input | |
| PS | NS | Output |

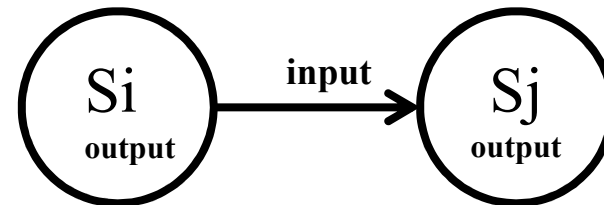

Life on Mars?



Mars rover has a binary input x . When it receives the input sequence $x(t-2, t) = 001$ from its life detection sensors, it means that it has detected life on Mars 😊 and the output $y(t) = 1$, otherwise $y(t) = 0$ (no life on Mars ☹).

Implement the Life-on-Mars
Pattern Recognizer!



Mars Life Recognizer FSM

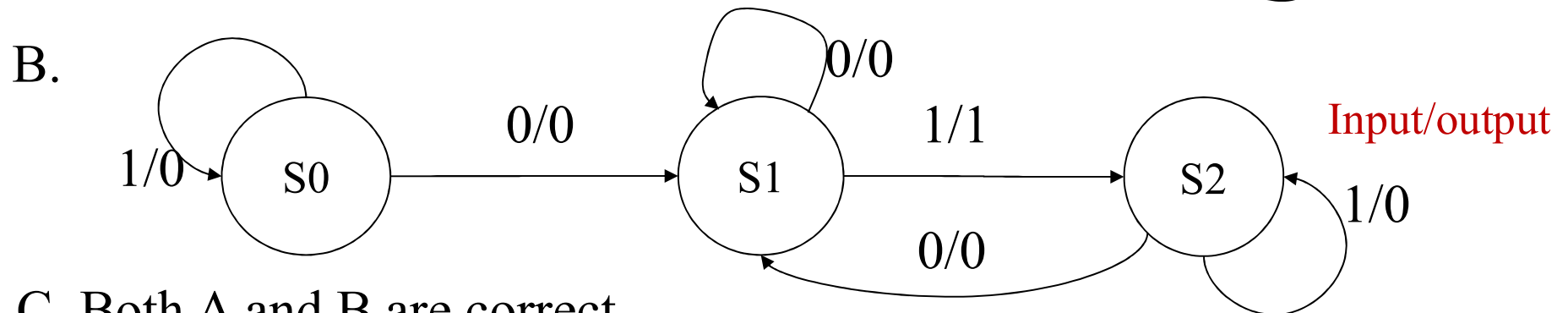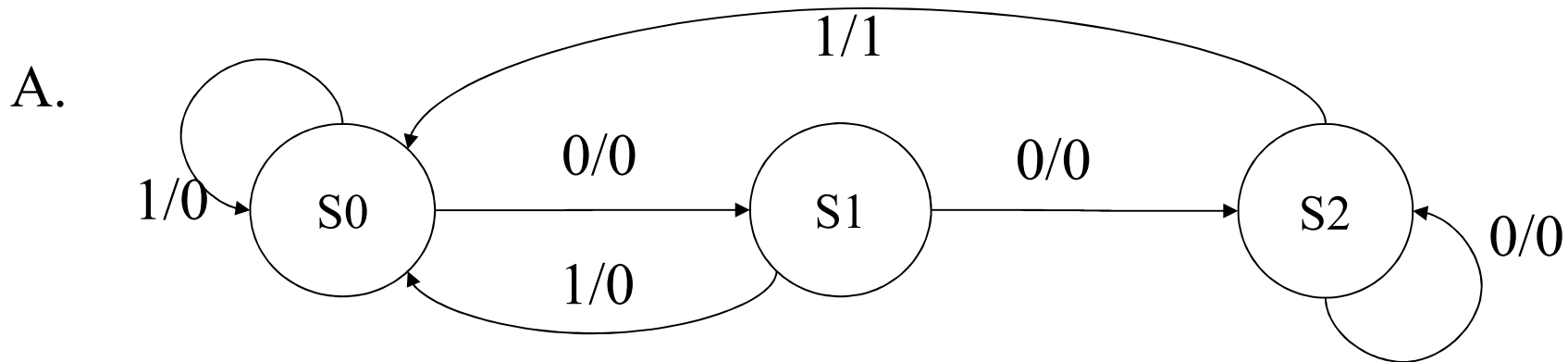Which of the following diagrams is a correct Mealy solution for the 001 pattern recognizer on the Mars rover?




C. Both A and B are correct


D. None of the above

Mars Life Recognizer FFs

Pattern Recognizer '001'

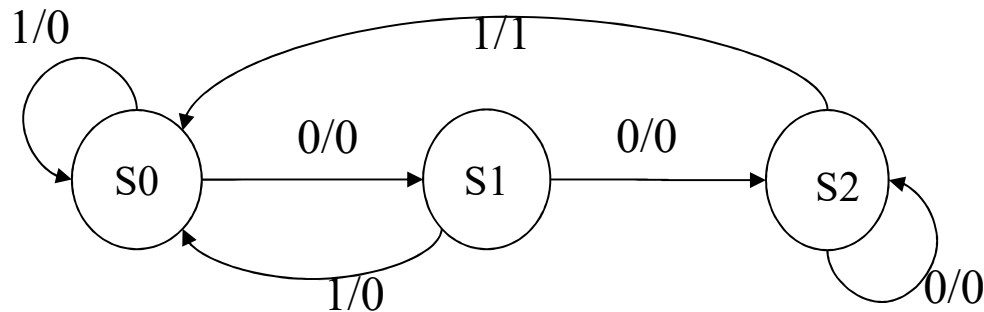



Mealy Machine

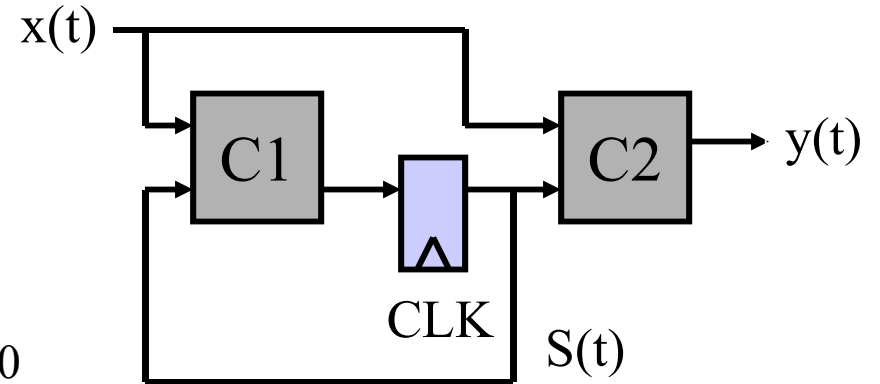

What does state table need to show to design controls of C1?

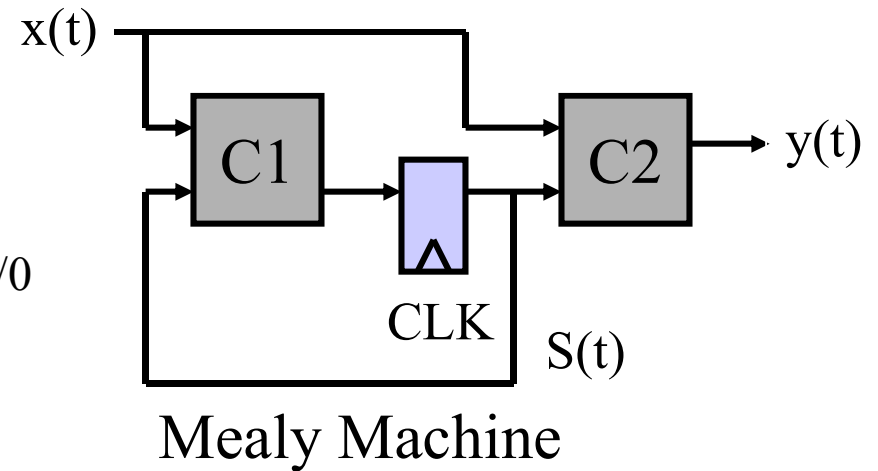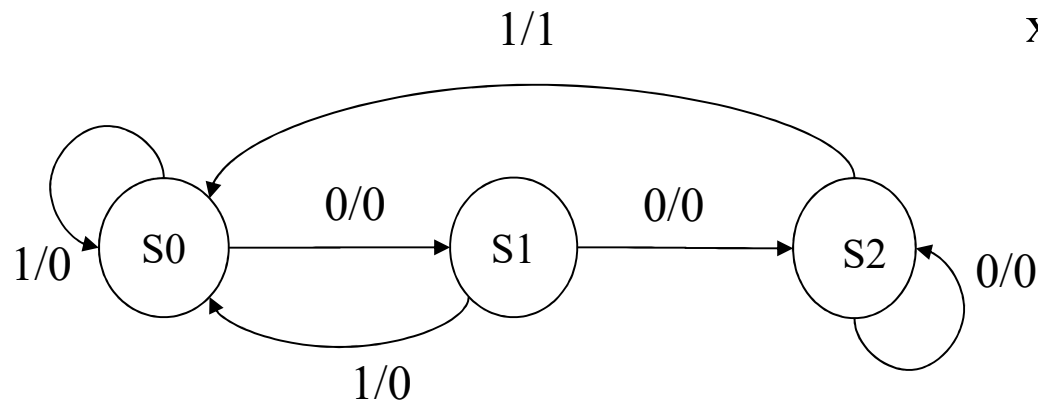- A. next state $S(t+1)$ vs. input $x(t)$, and present state $S(t)$
- B. output $y(t)$ vs. input $x(t)$, and present state $S(t)$
- C. output $y(t)$ vs. present state $S(t)$
- D. None of the above

State Diagram => State Table with State Assignment



| S(t)\x | 0 | 1 |
|--------|------|------|
| S0 | S1,0 | S0,0 |
| S1 | S2,0 | S0,0 |
| S2 | S2,0 | S0,1 |

State Assignment

S0: 00

S1: 01

S2: 10


| S(t)\x | 0 | 1 |
|--------|------|------|
| 00 | 01,0 | 00,0 |
| 01 | 10,0 | 00,0 |
| 10 | 10,0 | 00,1 |

$Q_1(t+1)Q_0(t+1), y$

State Diagram => State Table => Excitation Table => Circuit

| $Q_1(t) Q_0(t) \backslash x$ | 0 | 1 |
|------------------------------|------|------|
| 00 | 01,0 | 00,0 |
| 01 | 10,0 | 00,0 |
| 10 | 10,0 | 00,1 |


| id | $Q_1 Q_0 x$ | D_1 | D_0 | y |
|----|-------------|-------|-------|---|
| 0 | 000 | 0 | 1 | 0 |
| 1 | 001 | 0 | 0 | 0 |
| 2 | 010 | 1 | 0 | 0 |
| 3 | 011 | 0 | 0 | 0 |
| 4 | 100 | 1 | 0 | 0 |
| 5 | 101 | 0 | 0 | 1 |
| 6 | 110 | | | |
| 7 | 111 | | | |

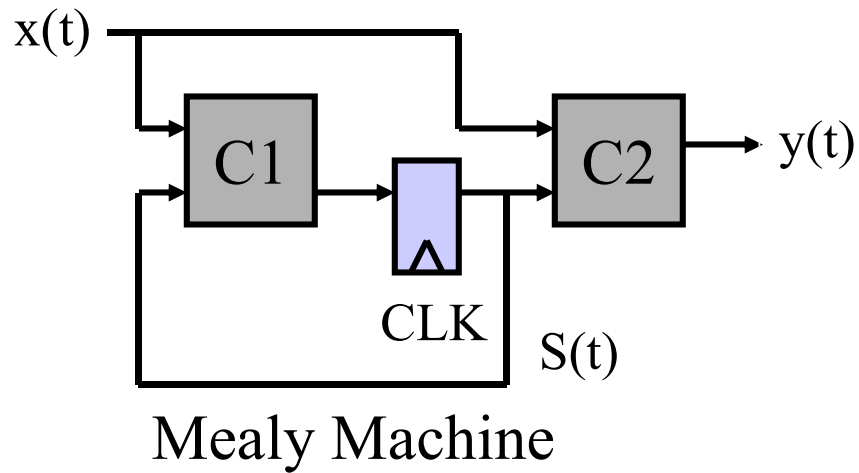

State Diagram => State Table => Excitation Table =>

Circuit

| $Q_1(t) Q_0(t) \backslash x$ | 0 | 1 |
|------------------------------|------|------|
| 00 | 01,0 | 00,0 |
| 01 | 10,0 | 00,0 |
| 10 | 10,0 | 00,1 |

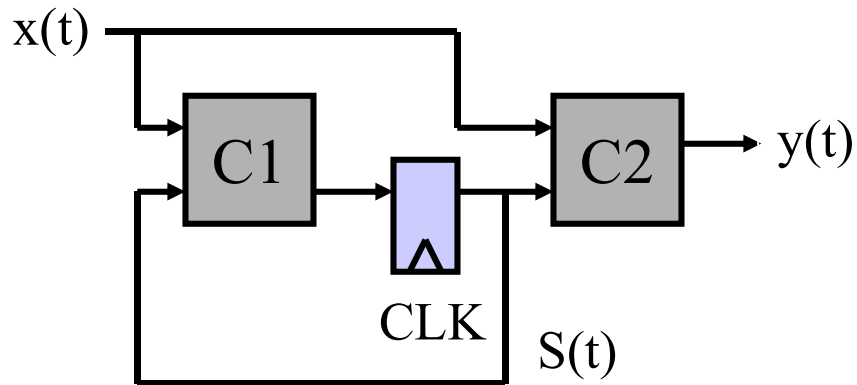

Mealy Machine

| id | $Q_1 Q_0 x$ | D_1 | D_0 | y |
|----|-------------|-------|-------|-----|
| 0 | 000 | 0 | 1 | 0 |
| 1 | 001 | 0 | 0 | 0 |
| 2 | 010 | 1 | 0 | 0 |
| 3 | 011 | 0 | 0 | 0 |
| 4 | 100 | 1 | 0 | 0 |
| 5 | 101 | 0 | 0 | 1 |
| 6 | 110 | | | |
| 7 | 111 | | | |

iClicker: What to fill in rows 6 and 7 of excitation table?

- A. All 0s
- B. All 1s
- C. All Don't Cares

State Diagram => State Table => Excitation Table => **Circuit**

| id | Q_1Q_0x | D_1 | D_0 | y |
|----|-----------|-------|-------|-----|
| 0 | 000 | 0 | 1 | 0 |
| 1 | 001 | 0 | 0 | 0 |
| 2 | 010 | 1 | 0 | 0 |
| 3 | 011 | 0 | 0 | 0 |
| 4 | 100 | 1 | 0 | 0 |
| 5 | 101 | 0 | 0 | 1 |
| 6 | 110 | X | X | X |
| 7 | 111 | X | X | X |

$D_1(t)$:


| | | Q_0 | | | |
|--------|---|-------|---|---|---|
| | | 0 | 1 | X | 1 |
| $x(t)$ | 0 | 0 | 1 | X | 1 |
| | 1 | 0 | 0 | X | 0 |
| | | Q_1 | | | |

$$D_1(t) = x'Q_0 + x'Q_1$$

$$D_0(t) = Q_1'Q_0'x'$$

$$y = Q_1x$$

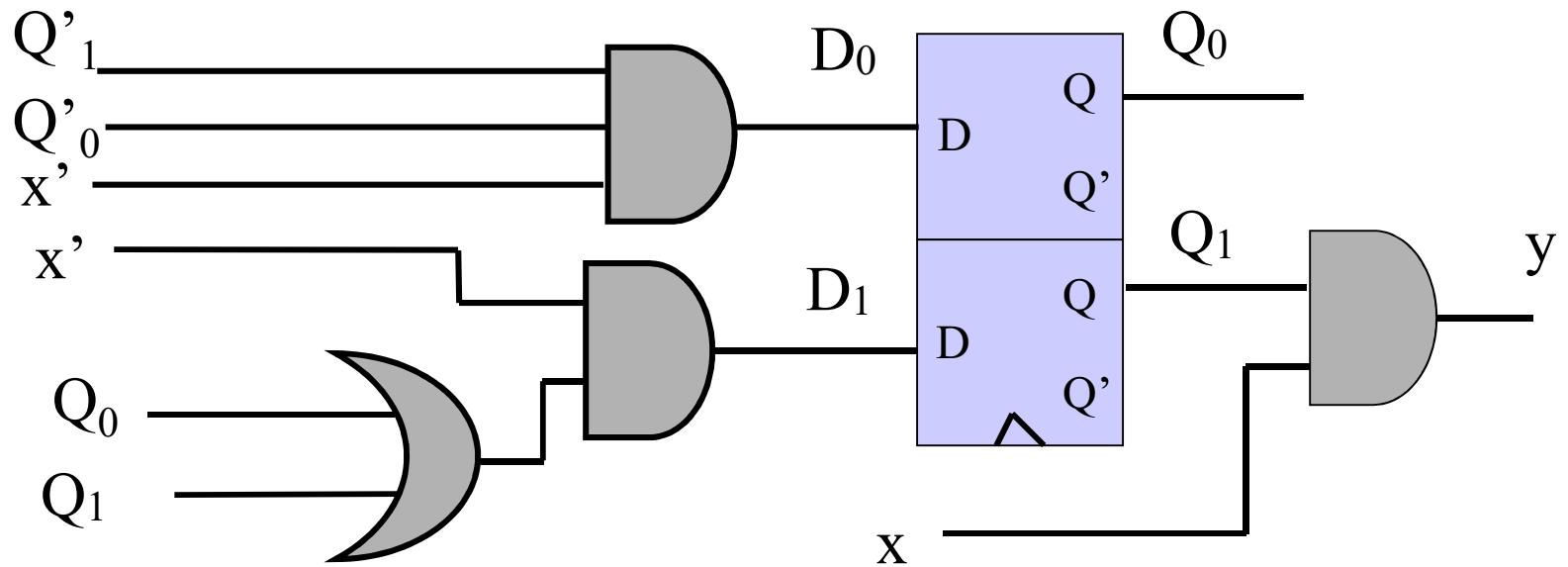
State Diagram => State Table => Excitation Table => **Circuit**



$$D_1(t) = x'Q_0 + x'Q_1$$

$$D_0(t) = Q'_1Q'_0x'$$


$$y = Q_1x$$

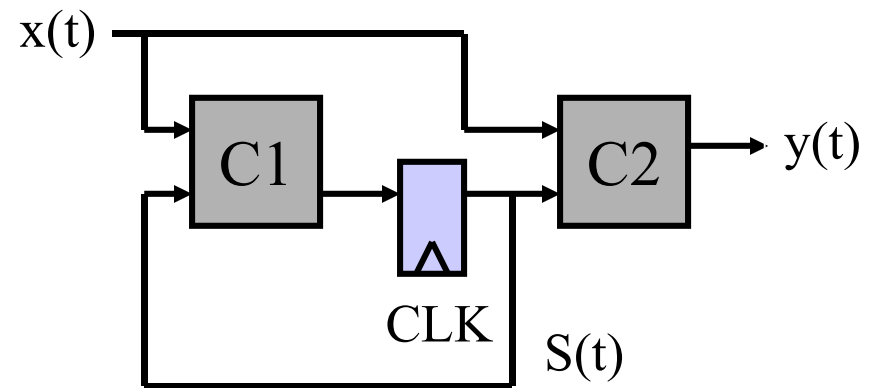

Mealy Machine

Moore FSM for the Mars Life Recognizer

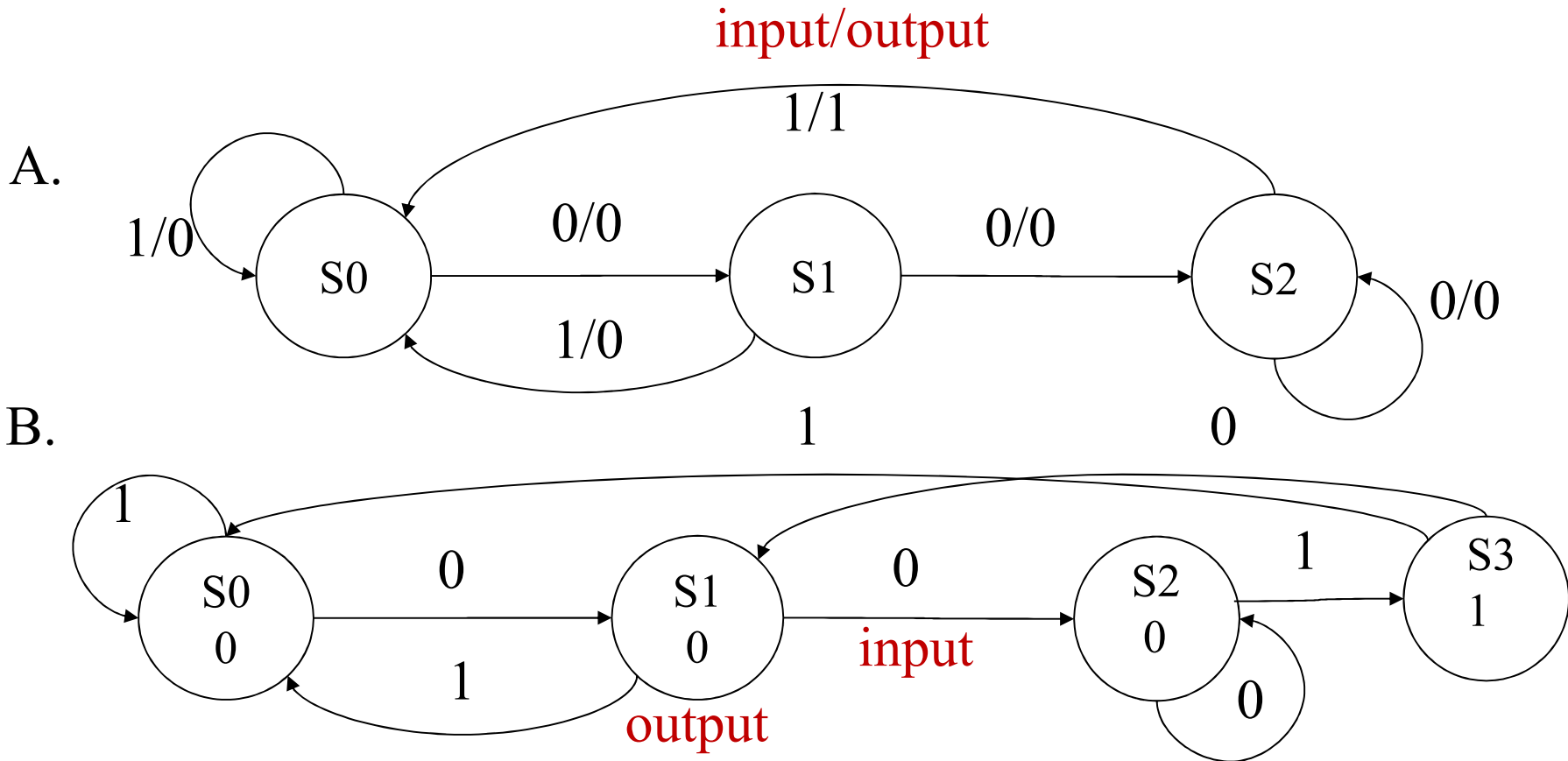Which of the following diagrams is a correct Moore solution to the '001' pattern recognizer?





C. Both A and B are correct

D. None of the above


Moore Mars Life Recognizer: FF Input Specs

Pattern Recognizer '001'

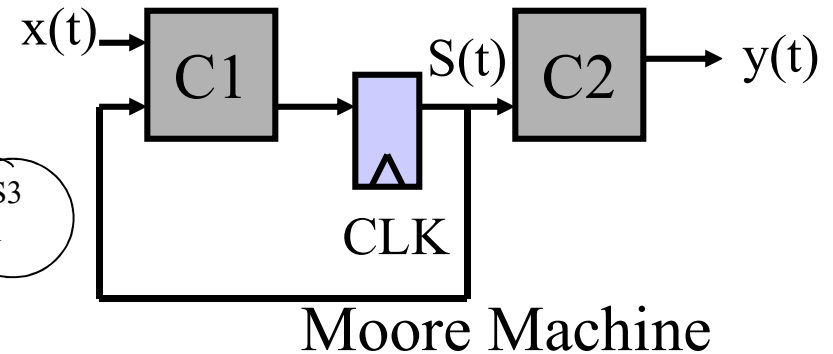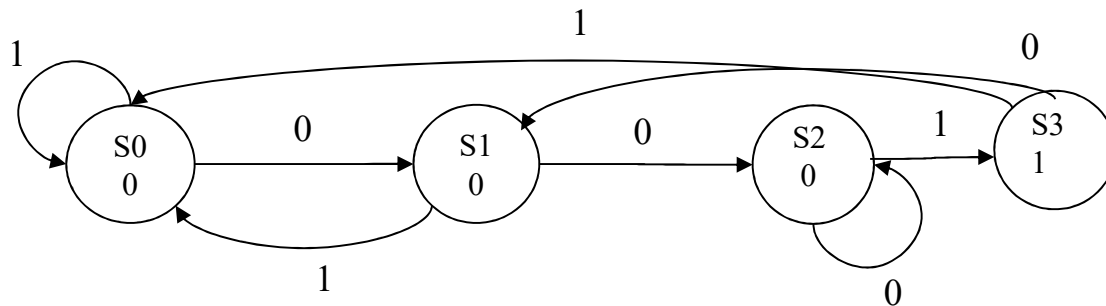

- What does state table need to show to design controls of C2?
- A.(current input $x(t)$, current state $S(t)$ vs. next state, $S(t+1)$)
 - B.(current input, current state vs. current output $y(t)$)
 - C.(current state vs. current output $y(t)$ and next state)
 - D.(current state vs. current output $y(t)$)
 - E. None of the above

Moore Mars Life Recognizer: State Table

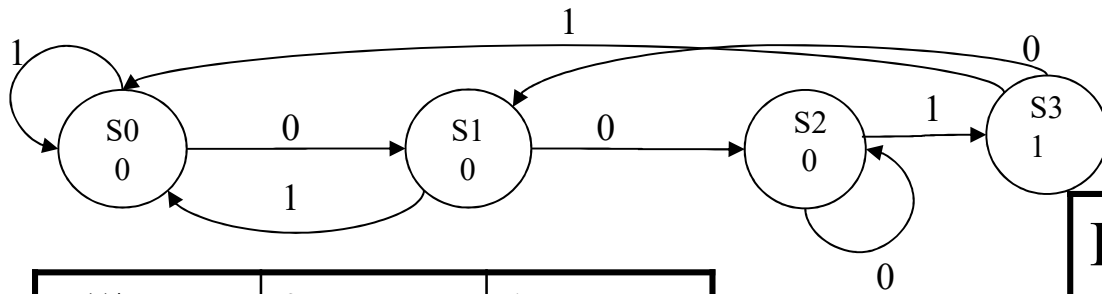

| S(t)\x | 0 | 1 |
|--------|------|------|
| S0 | S1,0 | S0,0 |
| S1 | S2,0 | S0,0 |
| S2 | S2,0 | S3,0 |
| S3 | S1,1 | S0,1 |

| Q ₁ Q ₀ \x | 0 | 1 |
|----------------------------------|------|------|
| 00 | 01,0 | 00,0 |
| 01 | 10,0 | 00,0 |
| 10 | 10,0 | 11,0 |
| 11 | 01,1 | 00,1 |

| ID | Q ₁ Q ₀ x | D ₁ | D ₀ | y |
|----|---------------------------------|----------------|----------------|---|
| 0 | 000 | 0 | 1 | 0 |
| 1 | 001 | 0 | 0 | 0 |
| 2 | 010 | 1 | 0 | 0 |
| 3 | 011 | 0 | 0 | 0 |
| 4 | 100 | 1 | 0 | 0 |
| 5 | 101 | 1 | 1 | 0 |
| 6 | 110 | 0 | 1 | 1 |
| 7 | 111 | 0 | 0 | 1 |

Q₁(t+1)Q₀(t+1), y

Mars Life Recognizer: Circuit Design

| id | Q_1Q_0x | D_1 | D_0 | y |
|----|-----------|-------|-------|-----|
| 0 | 000 | 0 | 1 | 0 |
| 1 | 001 | 0 | 0 | 0 |
| 2 | 010 | 1 | 0 | 0 |
| 3 | 011 | 0 | 0 | 0 |
| 4 | 100 | 1 | 0 | 0 |
| 5 | 101 | 1 | 1 | 0 |
| 6 | 110 | 0 | 1 | 1 |
| 7 | 111 | 0 | 0 | 1 |

$D_1(t)$:

| | | Q_0 | | | |
|--------|--|-------|---|---|---|
| $x(t)$ | | 0 | 1 | 0 | 1 |
| | | 0 | 0 | 0 | 1 |
| | | Q_1 | | | |

$D_0(t)$:


| | | Q_0 | | | |
|--------|--|-------|---|---|---|
| $x(t)$ | | 1 | 0 | 1 | 0 |
| | | 0 | 0 | 0 | 1 |
| | | Q_1 | | | |

$y(t)$:

| | | Q_0 | | | |
|--------|--|-------|---|---|---|
| $x(t)$ | | 0 | 0 | 1 | 0 |
| | | 0 | 0 | 1 | 0 |
| | | Q_1 | | | |

Mars Life Recognizer Circuit Implementation

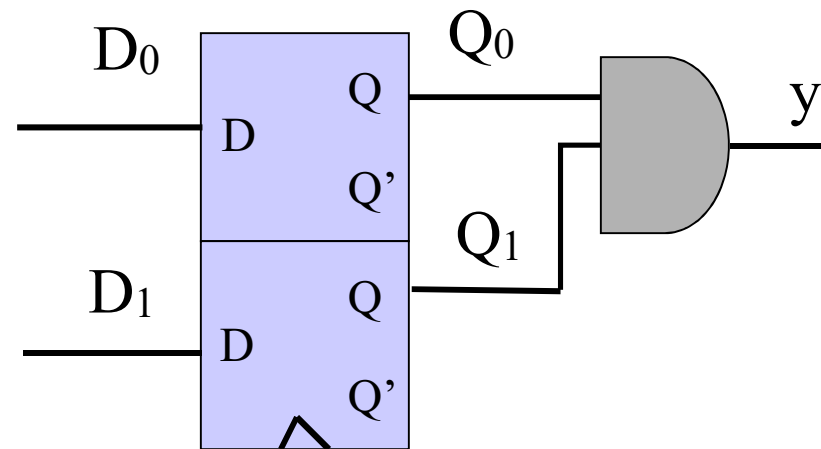
State Diagram => State Table => Excitation Table => **Circuit**



$$D_1(t) = Q_1(t)Q_0(t)' + Q_1(t)'Q_0(t)x(t)$$


$$D_0(t) = Q_1(t)'Q_0(t)'x(t)' + Q_1(t)Q_0(t)x(t)' + Q_1(t)Q_0(t)'x(t)$$

$$y(t) = Q_1(t)Q_0(t)$$

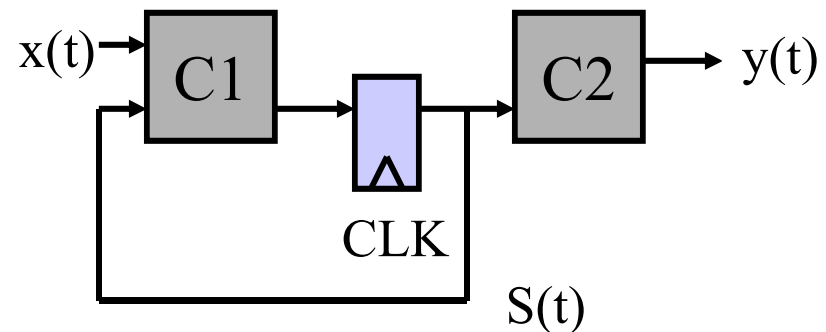


Moore Machine

Conversion from Mealy to Moore Machine

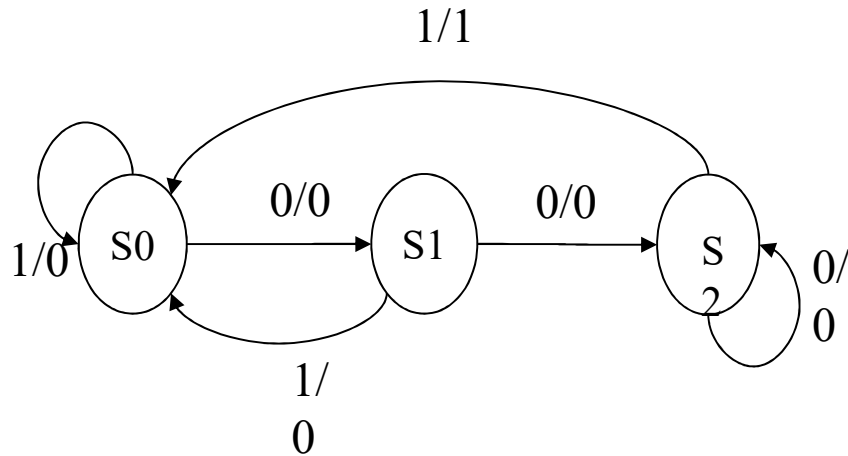

| S(t)\x | 0 | 1 |
|--------|------|------|
| S0 | S1,0 | S0,0 |
| S1 | S2,0 | S0,0 |
| S2 | S2,0 | S0,1 |

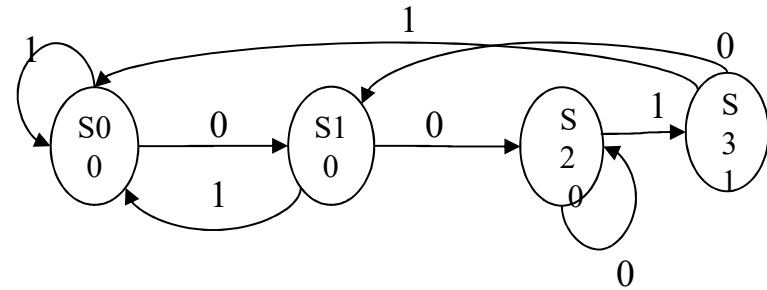

| S(t)\x | 0 | 1 |
|--------|------|------|
| S0 | S1,0 | S0,0 |
| S1 | S2,0 | S0,0 |
| S2 | S2,0 | S3,0 |
| S3 | S1,1 | S0,1 |

Conversion from Mealy to Moore Machine

| S(t)\x | 0 | 1 |
|--------|------|-------------|
| S0 | S1,0 | S0,0 |
| S1 | S2,0 | S0,0 |
| S2 | S2,0 | S0,1 |

| S(t)\x | 0 | 1 | y |
|-----------|----|-----------|---|
| S0 | S1 | S0 | 0 |
| S1 | S2 | S0 | 0 |
| S2 | S2 | S3 | 0 |
| S3 | | | |

Algorithm

1. Identify distinct (NS, y) pair
2. Replace each distinct (NS, y) pair with distinct new states
3. Insert rows of present state = new states

Conversion from Mealy to Moore Machine

Mealy

| S(t)\x | 0 | 1 |
|--------|------|-------------|
| S0 | S1,0 | S0,0 |
| S1 | S2,0 | S0,0 |
| S2 | S2,0 | S0,1 |

| S(t)\x | 0 | 1 | y |
|-----------|----|-----------|---|
| S0 | S1 | S0 | 0 |
| S1 | S2 | S0 | 0 |
| S2 | S2 | S3 | 0 |
| S3 | | | |

Moore


1. Find distinct NS, y
2. Add new states to represent distinct NS, y

iClicker


For the above Moore machine, what are the next states with respect to present state S3?

- A. S2, S3, 1
- B. S2, S0, 1
- C. S1, S0, 1
- D. S1, S0, 0
- E. None of the above.

Conversion from Mealy to Moore Machine

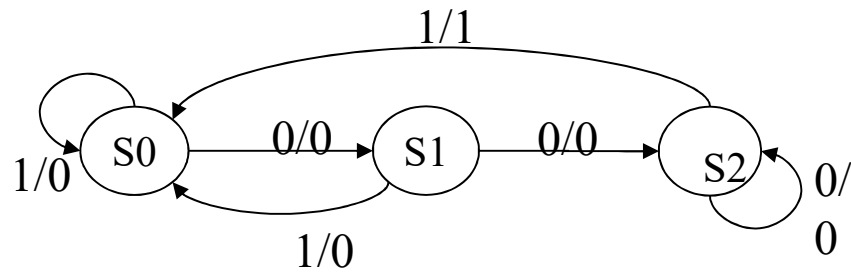

| S(t)\x | 0 | 1 |
|--------|------|------|
| S0 | S1,0 | S0,0 |
| S1 | S2,0 | S0,0 |
| S2 | S2,0 | S0,1 |

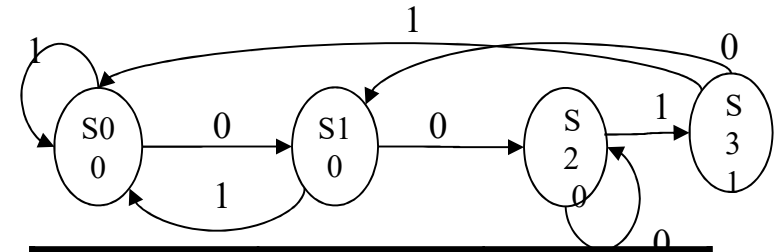


| S(t)\x | 0 | 1 |
|--------|------|------|
| S0 | S1,0 | S0,0 |
| S1 | S2,0 | S0,0 |
| S2 | S2,0 | S3,0 |
| S3 | S1,1 | S0,1 |

| Time | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 |
|--------------------|----|----|----|----|----|----|----|----|----|
| x | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| S _{mealy} | S0 | S1 | S0 | S1 | S2 | S0 | S0 | S1 | S2 |
| y _{mealy} | | | | | | | | | |
| S _{moore} | S0 | | | | | | | | |
| y _{moore} | | | | | | | | | |


iClicker S_{moore}[0-5]

- A. S0,S1,S0,S1,S2,S3
- B. S0,S1,S0,S1,S2,S0
- C. S3,S1,S0,S1,S2,S3
- D. S3,S1,S0,S1,S2,S0
- E. None of the above

Conversion from Mealy to Moore Machine

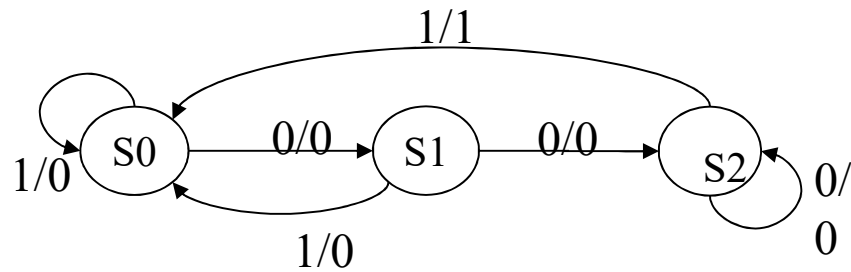

| S(t)\x | 0 | 1 |
|--------|------|------|
| S0 | S1,0 | S0,0 |
| S1 | S2,0 | S0,0 |
| S2 | S2,0 | S0,1 |

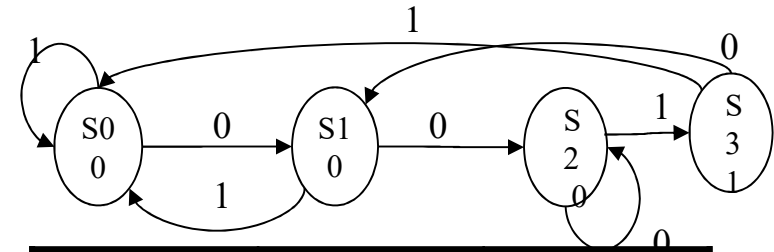

| S(t)\x | 0 | 1 |
|--------|------|------|
| S0 | S1,0 | S0,0 |
| S1 | S2,0 | S0,0 |
| S2 | S2,0 | S3,0 |
| S3 | S1,1 | S0,1 |

| Time | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 |
|--------------------|----|----|----|----|----|----|----|----|----|
| x | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| S _{mealy} | S0 | S1 | S0 | S1 | S2 | S0 | S0 | S1 | S2 |
| y _{mealy} | | | | | | | | | |
| S _{moore} | S0 | | | | | | | | |
| y _{moore} | | | | | | | | | |

iClicker y_{moore}[0-5]

A. 0,0,0,0,1,0

B. 0,0,0,0,0,1

C. 0,1,0,0,0,0

D. 0,0,0,0,0,0,

E. None of the above


Conversion from Mealy to Moore Machine

Algorithm

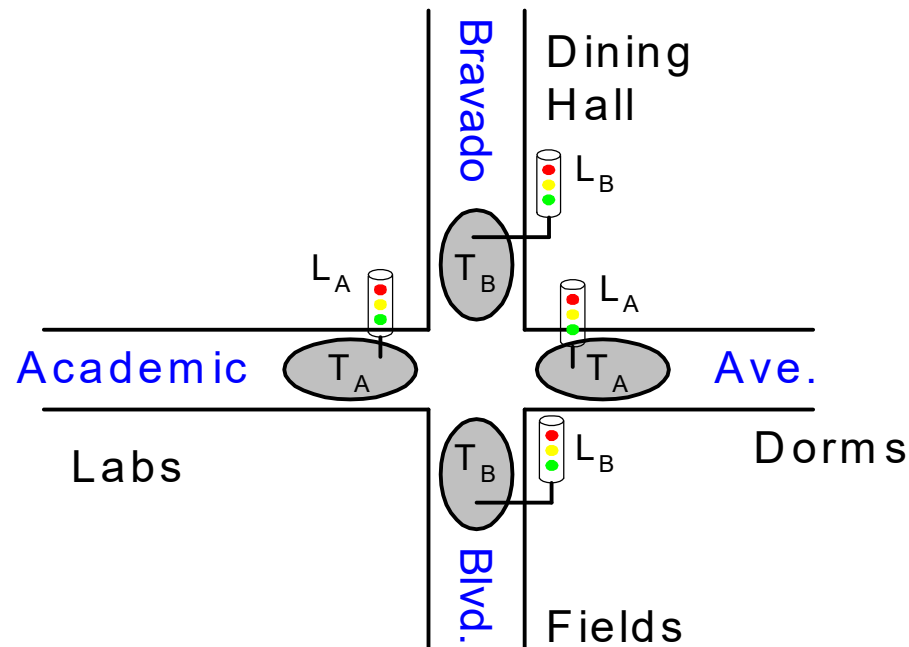1. Identify distinct (NS, y) pair
2. Replace each distinct (NS, y) pair with distinct **new states**
3. Insert rows of present state = **new states**
4. Append each present state with its output y


Finite State Machine Example

- Traffic light controller
 - Traffic sensors: T_A , T_B (TRUE when there's traffic)
 - Lights: L_A , L_B




FSM Black Box

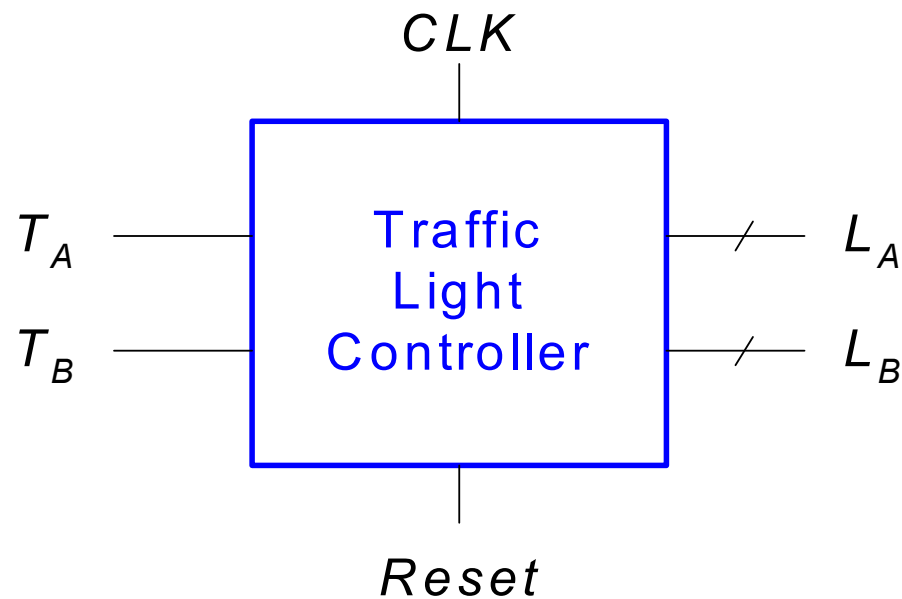- Inputs: CLK , $Reset$, T_A , T_B
- Outputs: L_A , L_B




FSM State Transition Diagram

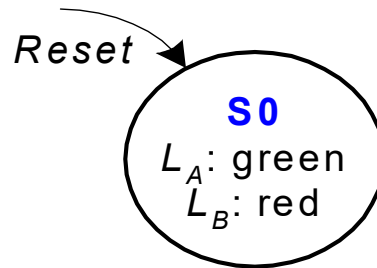- Moore FSM: outputs labeled in each state
- States: Circles
- Transitions: Arcs



FSM State Transition Diagram

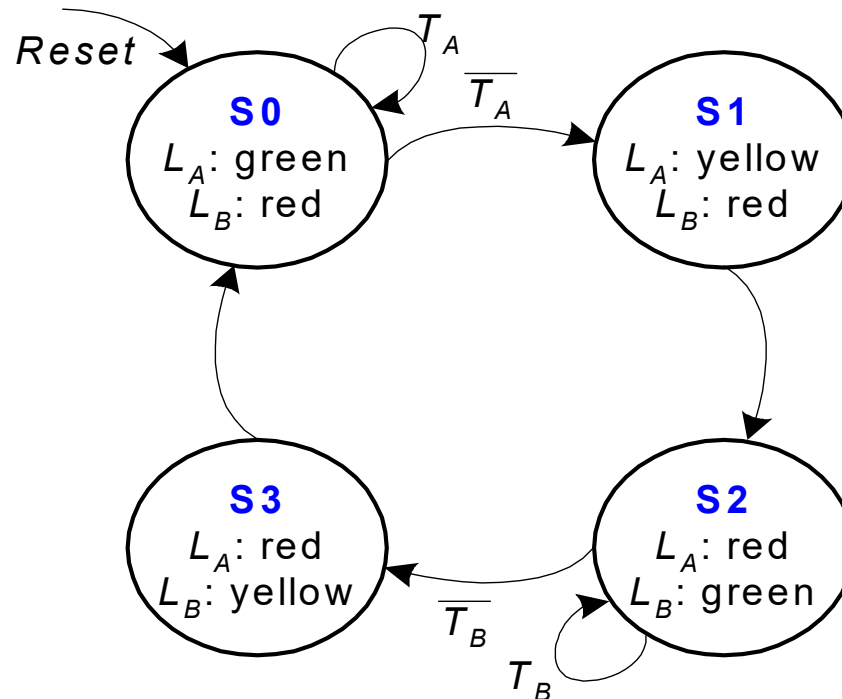- Moore FSM: outputs labeled in each state
- States: Circles
- Transitions: Arcs



FSM State Transition Table

| PS | Inputs | | NS |
|----|--------|-------|----|
| | T_A | T_B | |
| S0 | 0 | X | S1 |
| S0 | 1 | X | S0 |
| S1 | X | X | S2 |
| S2 | X | 0 | S3 |
| S2 | X | 1 | S2 |
| S3 | X | X | S0 |

State Transition Table

| PS | | Inputs | | NS | |
|----------|----------|--------|-------|------------|------------|
| $Q_1(t)$ | $Q_0(t)$ | T_A | T_B | $Q_1(t+1)$ | $Q_0(t+1)$ |
| 0 | 0 | 0 | X | 0 | 1 |
| 0 | 0 | 1 | X | 0 | 0 |
| 0 | 1 | X | X | 1 | 0 |
| 1 | 0 | X | 0 | 1 | 1 |
| 1 | 0 | X | 1 | 1 | 0 |
| 1 | 1 | X | X | 0 | 0 |

| State | Encoding |
|-------|----------|
| S0 | 00 |
| S1 | 01 |
| S2 | 10 |
| S3 | 11 |

$$Q_1(t+1) = Q_1(t) \oplus Q_0(t)$$

$$Q_0(t+1) = Q_1'(t)Q_0'(t)T_A + Q_1(t)Q_0'(t)T_B$$

FSM Output Table

| PS | | Outputs | | | |
|-------|-------|----------|----------|----------|----------|
| Q_1 | Q_0 | L_{A1} | L_{A0} | L_{B1} | L_{B0} |
| 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 1 |

| Output | Encoding |
|--------|----------|
| green | 00 |
| yellow | 01 |
| red | 10 |


$$L_{A1} = Q_1$$

$$L_{A0} = Q_1' Q_0$$


$$L_{B1} = Q_1'$$

$$L_{B0} = Q_1 Q_0$$


FSM Schematic: State Register

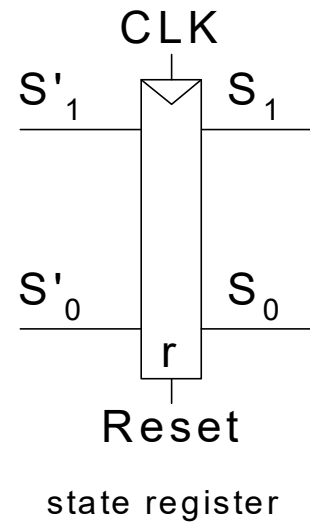

Logic Diagram

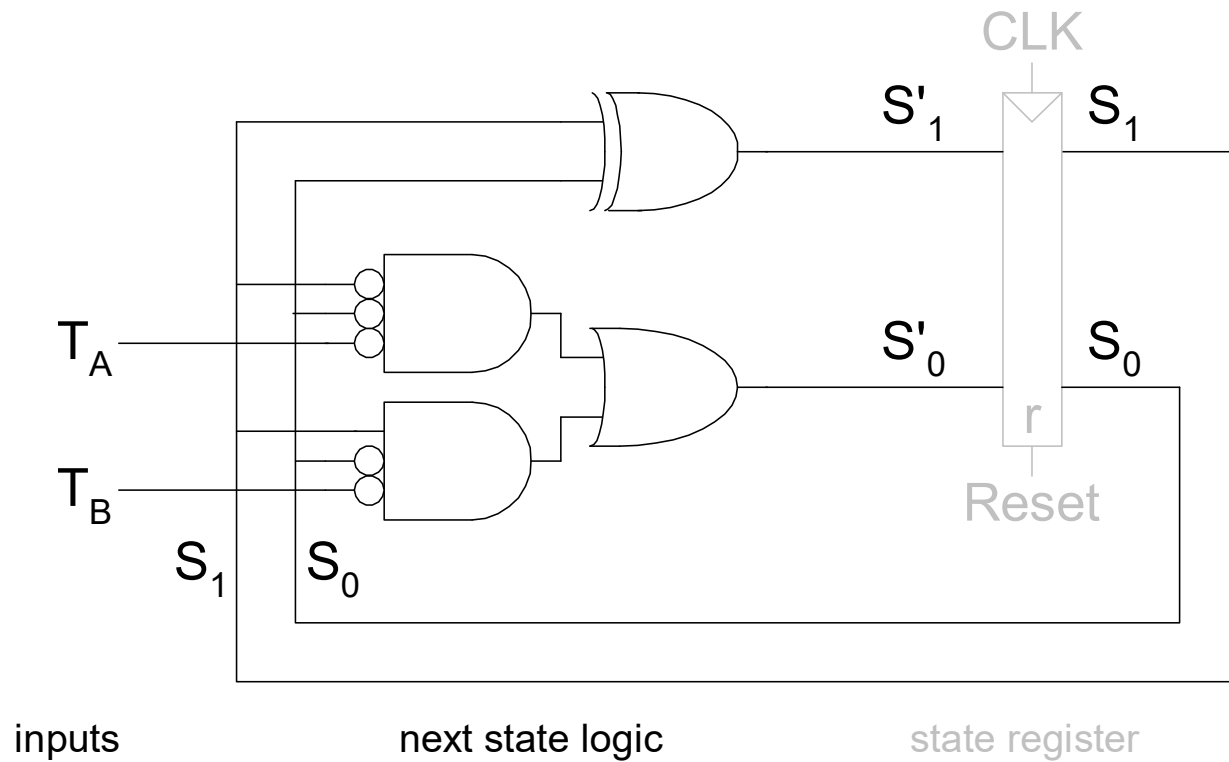

FSM Schematic: Output Logic

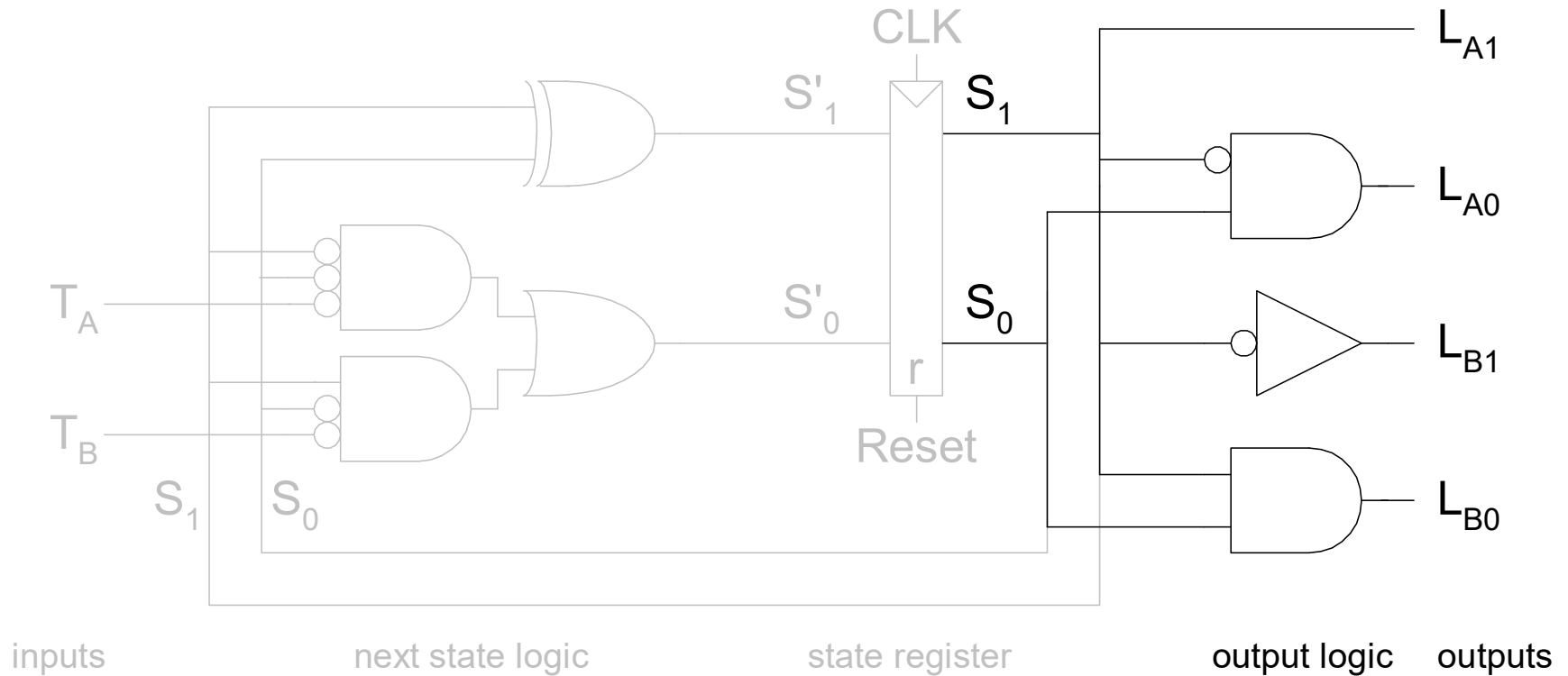

Summary: Implementation

- Set up canonical form
 - Mealy or Moore machine
- Identify the next states
 - state diagram \Leftrightarrow state table
 - **state assignment**
- Derive excitation table
 - Inputs of flip flops
- Design the combinational logic
 - **don't care set utilization**