

CSE 140: Components and Design Techniques for Digital Systems

Lecture 6: Universal Gates

CK Cheng

Dept. of Computer Science and Engineering
University of California, San Diego

Combinational Logic: Various Types of Gates

- Universal Set of Gates
 - Motivation
 - Definition
 - Examples
- Other Types of Gates
 - XOR
 - NAND / NOR
 - Block Diagram Transfers

Universal Set of Gates: Motivation

- AND, OR, NOT: Logic gates related to reasoning from Aristotle (384-322BCE).
- NAND, NOR: Inverted AND, Inverted OR gates. For VLSI technologies, all gates are inverted (AND,OR operation with a bubble at output).
- XOR: Exclusive OR gates. Parity check.
- Multiplexer + input table: Table based logic for programmability. FPGA technology.
- Neuron and Synapse: Neural network.
- Reversible Gates: Quantum computing.

In the future, we may have new sets of gates due to new technologies.
Given a set of gates, are we able to construct all possible switching functions using the gates in the set?

Universal Set

Universal set is a powerful concept to identify the coverage of a set of gates afforded by a given technology.

Criterion: If the set of gates can implement AND, OR, and NOT gates, then the set is universal.

Universal Set Definition

Universal Set: A set of gates such that every switching function can be implemented with the gates in this set.

Examples

{AND, OR, NOT}

{AND, NOT}

{OR, NOT}

Universal Set: Examples

Universal Set: A set of gates such that every switching function can be implemented with the gates in this set.

Examples

{AND, OR, NOT}

{AND, NOT} OR can be implemented with AND &

NOT gates: $a + b = (a'b')'$

{OR, NOT} AND can be implemented with OR &

NOT gates: $ab = (a' + b')'$

{XOR} is not universal

{XOR, AND} is universal

Example

Is the set {AND, OR} (but no NOT gate) universal?

A. Yes

B. No

Note that the set was used in a once popular design style as **domino logic** for high performance computing.

Example


Is the set $\{f(x, y) = xy'\}$ universal?

A. Yes


B. No

Universal Set: Examples

{NAND, NOR}

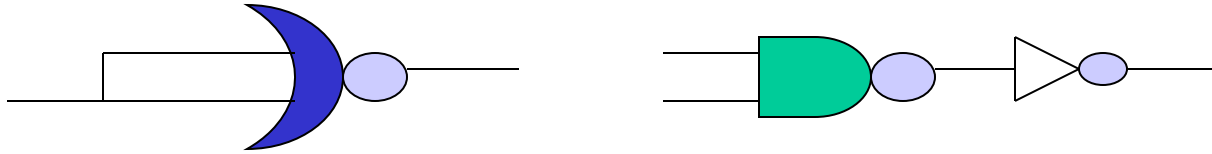

{XOR}

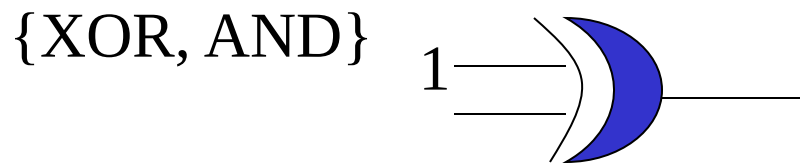

$$x \oplus 1 = x1' + x'1 = x' \text{ if constant "1" is available.}$$


Other Types of Gates: Properties and Usage

1. XOR $x \oplus y = xy' + x'y$
2. NAND, NOR
3. Block Diagram Transfers

Other Types of Gates: XOR

$$x \oplus y = xy' + x'y$$

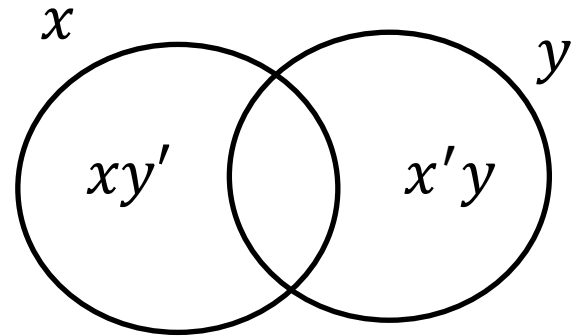It is a parity function (examples)
useful for testing because the
flipping of a single input changes the
output.




id	x	y	$x \oplus y$
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	0

	x=0	x=1
y=0	0	1
y=1	1	0

Other Types of Gates: XOR

1) XOR $x \oplus y = xy' + x'y$

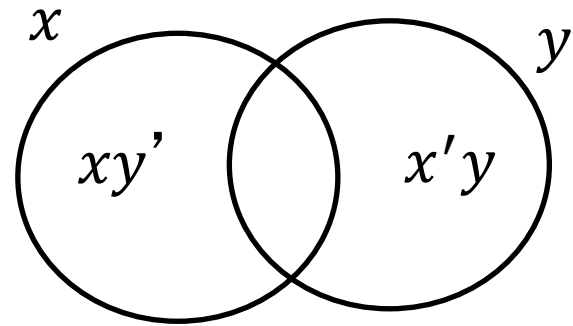


(a) Commutative $x \oplus y = y \oplus x$

(b) Associative $(x \oplus y) \oplus z = x \oplus (y \oplus z)$

Other Types of Gates: XOR

1) XOR $x \oplus y = xy' + x'y$

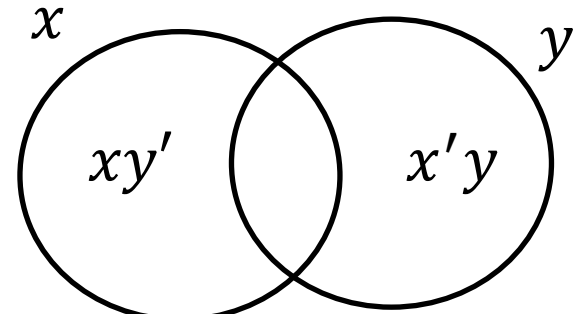

a) Commutative $x \oplus y = y \oplus x$

b) Associative $(x \oplus y) \oplus z = x \oplus (y \oplus z)$

c) $1 \oplus x = x', 0 \oplus x = x$

d) $x \oplus x = 0, x \oplus x' = 1$

Other Types of Gates: XOR

e) If $ab = 0$, then $a \oplus b = a + b$

Proof: If $ab = 0$, then

$$a = a(b + b') = ab + ab' = ab'$$

$$b = b(a + a') = ba + ba' = a'b$$

$$\text{Therefore, } a + b = ab' + a'b = a \oplus b$$

Note that in full adder, we have

$$c_{\text{out}} = ab + bc + ac = ab + c(a + b)$$

From property e), we can also write $c_{\text{out}} = ab + c(a \oplus b)$

Other Types of Gates: XOR

f) $f(x, y) = x \oplus xy' \oplus x'y \oplus (x + y) \oplus x = ?$

(Priority of operations: AND, $\oplus$, OR)

Hint: We apply Shannon's Expansion.

Other Types of Gates: XOR

Shannon's Expansion: Recap for switching functions

Formula: $f(x, y) = xf(1, y) + x'f(0, y)$

Proof by enumeration:

If $x = 1$, $f(x, y) = f(1, y)$:

$$xf(1, y) + x'f(0, y) = 1f(1, y) + 1'f(0, y) = f(1, y)$$

If $x = 0$, $f(x, y) = f(0, y)$:

$$xf(1, y) + x'f(0, y) = 0f(x, y) + 0'f(0, y) = f(0, y)$$

Other types of gates: XOR

Simplify the function (Priority of operations: AND, $\oplus$, OR)

$$f(X, Y) = X \oplus XY' \oplus X'Y \oplus (X + Y) \oplus X$$

$$\text{Case } X = 1: f(1, Y) = 1 \oplus Y' \oplus 0 \oplus 1 \oplus 1 = Y$$

$$\text{Case } X = 0: f(0, Y) = 0 \oplus 0 \oplus Y \oplus Y \oplus 0 = 0$$

Thus, using Shannon's expansion, we have

$$f(X, Y) = Xf(1, Y) + X'f(0, Y) = XY$$

XOR gates

Example: Is the equation

$$a + (b \oplus c) = (a + b) \oplus (a + c)$$

true?

A. Yes

B. No

Other Types of Gates: NAND, NOR

2) NAND, NOR gates

NAND (NOR) gates are not associative

Let $a \mid b = (ab)'$


$$(a \mid b) \mid c \neq a \mid (b \mid c)$$

Other Types of Gates: NAND, NOR

Block Diagram Transform

3) Block Diagram Transformation


a) Reduce # of inputs.

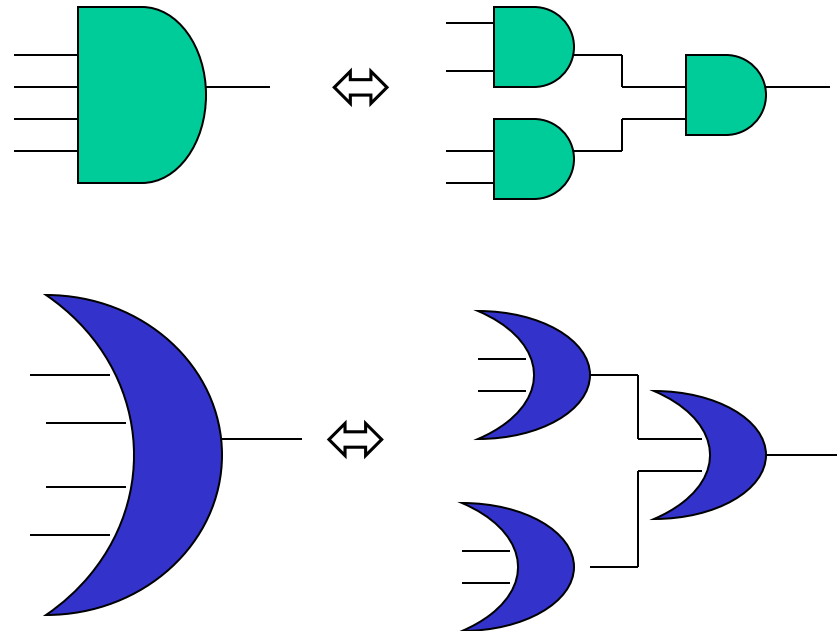


Other Types of Gates: NAND, NOR

Block Diagram Transform

b. DeMorgan's Law

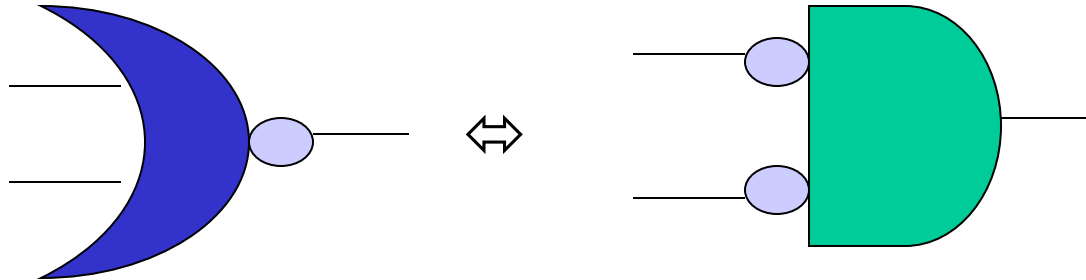

$$(a+b)' = a' b'$$

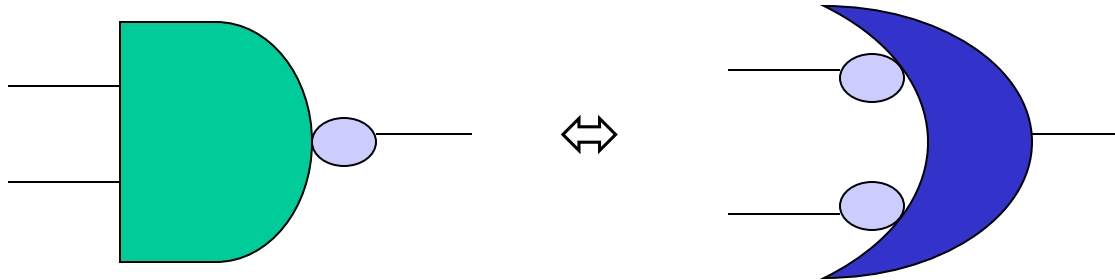


$$(ab)' = a' + b'$$


Other Types of Gates: NAND, NOR

Block Diagram Transform

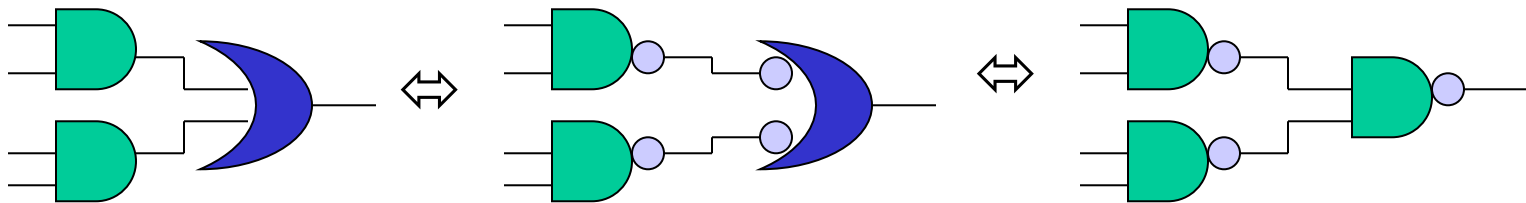c. Sum of Products (Using only NAND gates)



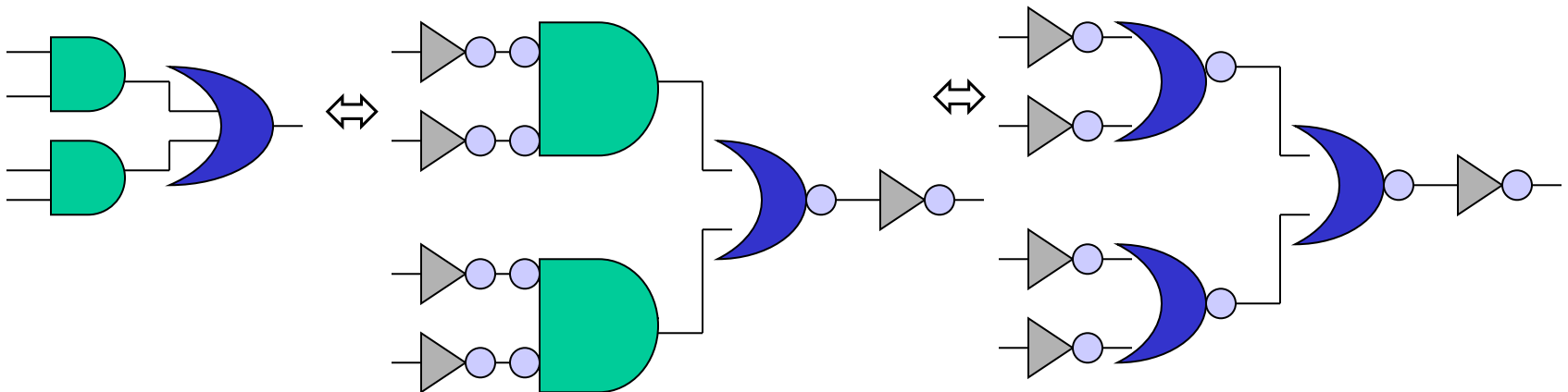
Sum of Products (We create many bubbles with NOR gates)



Other Types of Gates: NAND, NOR

Block Diagram Transform

d. Product of Sums (NOR gates only)

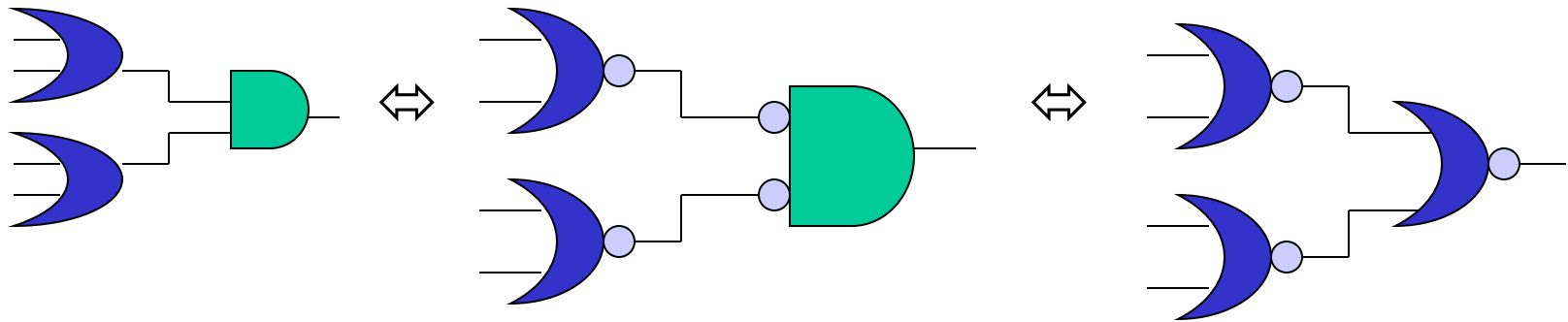

We will create many bubbles with NAND gates.

Other Types of Gates: NAND, NOR


Block Diagram Transform

Remark:

Two level NAND gates: Sum of Products

Two level NOR gates: Product of Sums

Part II. Sequential Networks

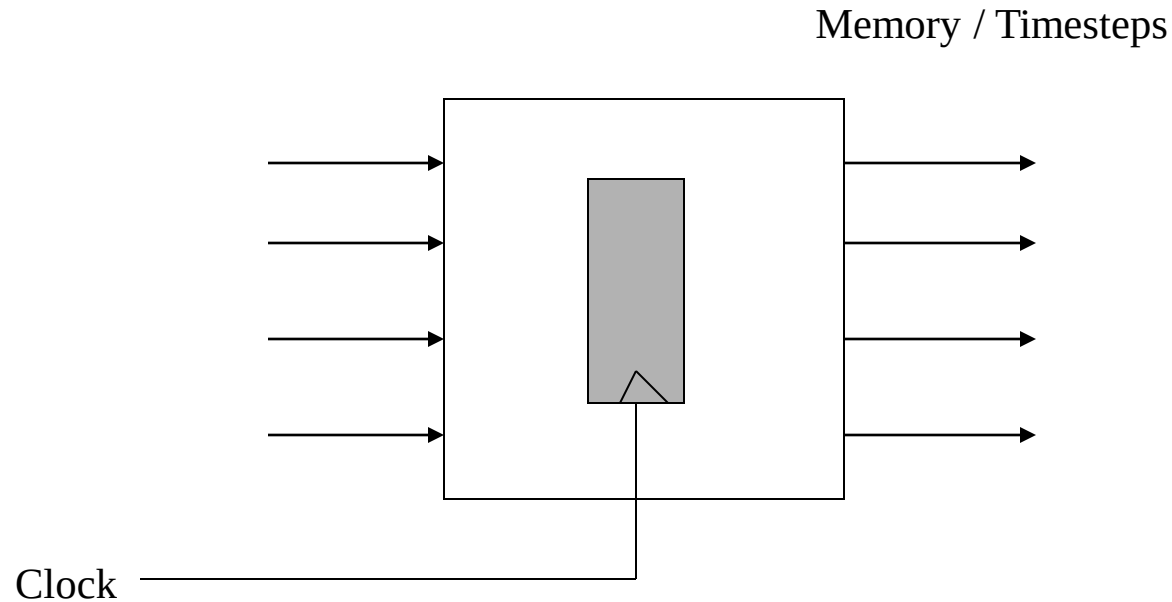

Flip flops
Specification
Implementation