

- Assignment #2
- Simple Verilog Examples
 - Combinational logic
 - Sequential logic (registers, clk)
- Verilog CPU simulation
- Verilog Blocking vs. Non-blocking
- Xilinx project CPU1

Please put your cellphone on vibrate



Assignment 2

1. Implement your CPU in Verilog in Xilinx.
2. Demo your Verilog CPU simulation & synthesis result to TA.
3. Due next Friday 6pm (8/21)
4. Grading:
 - a. Verilog Completion (no-syntax error) 40%
 - b. Simulation 40%
 - c. Synthesis 20%

- Verilog is case sensitive
- All keywords are in lower case
- Module is the basic design unit
- Module contains ports (input/output) and logical assignments


Ex1: Mux2to1

```
module mux2to1(s, a, b, y);  
    input s;  
    input a;  
    input b;  
    output y;  
  
    // This is a comment  
    assign y = (b & s) | (a & ~s);  
  
endmodule
```

  


Ex2: Mux2to1

```
module mux2to1(s, a, b, y);  
    input s;  
    input a;  
    input b;  
    output y;  
  
    wire na, nb;  
  
    assign nb = b & s;  
    assign na = a & ~s;  
    assign y = na | nb;  
  
endmodule
```

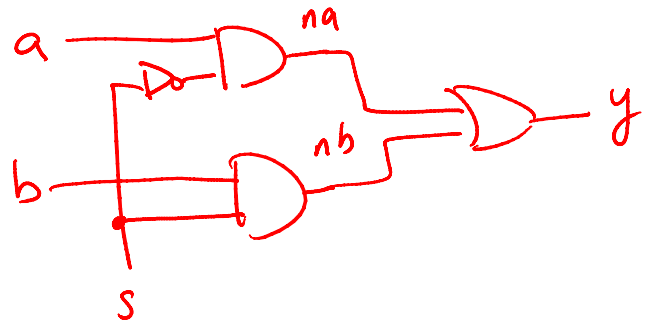

Ex3: Mux2to1


```
module mux2to1(s, a, b, y);  
    input s;  
    input a;  
    input b;  
    output y;  
  
    // conditional statement  
    assign y = s ? b : a;  
  
endmodule
```

 

Ex4: Illegal assign

```
wire na;
```
 
```
// wire is shorted together  
assign na = b & s;  
assign na = a & ~s;
```



Always block 1

```
module mux2to1(s, a, b, y);  
    input s;  
    input a;  
    input b;  
    output y;  
  
    reg y;  
  
    always @(a or b or s)  
    begin  
        if (s)  
            y = b;  
        else  
            y = a;  
    end  
  
endmodule
```

declare reg to be used in the always block

Right hand side

These are executed in sequence

Always block 2

```
module mux2to1(s, a, b, y);  
    input s;  
    input a;  
    input b;  
    output y;  
  
    reg y;  
  
    always @(a or b or s)  
    begin  
        y = (b & s) | (a & ~s);  
    end  
endmodule
```

Right Hand side

Combinational
logic

Always block 3

```
module mux2to1(s, a, b, y);  
    input s;  
    input a;  
    input b;  
    output y;
```

```
    reg y, na, nb;
```

```
    always @*
```

```
    begin
```

```
        nb = b & s;
```

```
        na = a & ~s;
```

```
        y = na | nb;
```

```
    end
```

```
endmodule
```

wild card indicates
All variables on
the Right hand side

Sequential block 1

```
always (ld or clr or d or q_old)
begin
    q = q_old;
    if (ld)
        q = d;
    if (clr)
        q = 0;
end
```

- No Else statement
- clr takes precedence

ld	clr	q
0	0	q-old
0	<u>1</u>	0
1	0	d
1	<u>1</u>	0

Sequential block 2


```
always (ld or clr or d or q_old)
begin
    q = q_old;
    if (clr)
        q = d;
    if (ld)
        q = 0;
end
```

ld	clr	q
0	0	q-old
0	1	d
<u>1</u>	0	0
<u>1</u>	1	0


- No else statement
- ld will take precedence

Common mistake
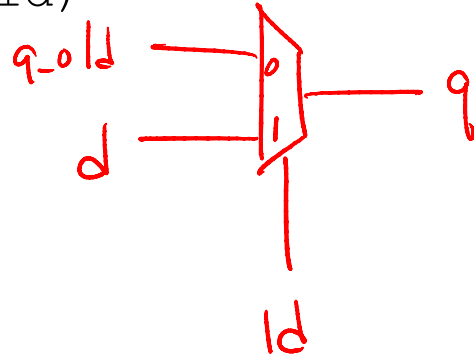
```
// correct
always (ld or d or q_old)
begin
    q = q_old;
    if (ld)
        q = d;
end
```



 
```
// mistake
always (ld or d)
begin
    if (ld)
        q = d;
end
```



- no assignment made to
q when ld = 0

Build blocks
 
```
module mux2to1(s, a, b, y);  
    input s;  
    input a;  
    input b;  
    output y;  
  
    // conditional statement  
    assign y = s ? b : a;  
  
endmodule
```



```
module mux2to1_4bit(s, a, b, y);  
    input s;  
    input [3:0] a, b;  
    output [3:0] y;  
  
    mux2to1 u3 (.a(a[3]), .b(b[3]), .s(s), .y(y[3]));  
    mux2to1 u2 (.a(a[2]), .b(b[2]), .s(s), .y(y[2]));  
    mux2to1 u1 (.a(a[1]), .b(b[1]), .s(s), .y(y[1]));  
    mux2to1 u0 (.a(a[0]), .b(b[0]), .s(s), .y(y[0]));  
  
endmodule
```

4-bit 2:1 Mux

```
module mux2to1_4bit(s, a, b, y);  
    input s;  
    input [3:0] a, b;  
    output [3:0] y;  
  
    assign y = (b & s) | (a & ~s);  
  
endmodule
```

*Combinational logic
for buses*

4-bit 4:1 Mux - if/else

```
module mux4to1_4bit(s, a, b, c, d, y);  
    input [1:0] s;  
    input [3:0] a, b, c, d;  
    output[3:0] y;  
  
    reg [3:0] y;  
  
    always @*  
    begin  
        if (s == 2'b00)  
            y = a;  
        else if (s == 2'b01)  
            y = b;  
        else if (s == 2'b10)  
            y = c;  
        else  
            y = d;  
    end  
  
endmodule
```

4-bit 4:1 Mux - case

```
module mux4to1_4bit(s, a, b, c, d, y);  
    input [1:0] s;  
    input [3:0] a, b, c, d;  
    output[3:0] y;  
  
    reg [3:0] y;  
  
    always @*  
    begin  
        case (s)  
            2'b00 : y = a;  
            2'b01 : y = b;  
            2'b10 : y = c;  
            default: y = d;  
        endcase  
    end  
  
endmodule
```

4-bit adder

```
module add4bit(a, b, s);  
    input [3:0] a, b;  
    output [3:0] s;  
  
    assign s = a + b;  
  
endmodule
```

NO carry in

NO carry out


4-bit adder w/ carry

```
module add4bit(ci, a, b, s, co);  
    input ci;  
    input [3:0] a, b;  
    output [3:0] s;  
    output co;  
  
    wire [4:0] y; ← not used in always block  
  
    assign y = {1'b0, a} + {1'b0, b} + {4'b0, ci};  
    assign s = y[3:0];  
    assign co = y[4];  
  
endmodule
```

$$\begin{array}{r} a_3 a_2 a_1 a_0 \quad \leftarrow ci \\ + \quad b_3 b_2 b_1 b_0 \\ \hline c_0 \quad s_3 s_2 s_1 s_0 \end{array}$$


D Flip flop
 
```
module latch(d, clk, q);  
  input d, clk;  
  output q;  
  
  always @(posedge clk)  
  begin  
    q <= d;  
  end  
  
endmodule
```



DFF Chain

 
```
reg qa, qb, qc;  
always @(posedge clk)  
begin  
    qa <= a;  
    qb <= qa;  
    qc <= qb;  
end
```



```
reg qa, qb, qc;  
always @(posedge clk)  
begin  
    qa <= a;  
end  
always @(posedge clk)  
begin  
    qb <= qa;  
end  
always @(posedge clk)  
begin  
    qc <= qb;  
end
```


8 bit register
 
```
module reg8bit (clk, r, d, ld, q);  
  
    input clk, r, ld;  
    input [7:0] d;  
    output [7:0] q;  
  
    always @(posedge clk)  
    begin  
        if (!r)  
            q <= 8'b0;  
        else  
            begin  
                if (ld)  
                    q <= d;  
            end  
        end  
    end  
  
endmodule
```



Finite State Machine 1
 
```
module UpDownCounter (control, clk, counter);  
  
    input control, clk;  
    output [1:0] counter;  
  
    always @(posedge clk)  
    begin  
        if (control)  
            counter <= counter + 1;  
        else  
            counter <= counter - 1;  
        end  
    end  
endmodule
```



Finite State Machine 2

```

module MooreFSM(A, clk, Z);

    input A, clk;
    output Z;
    reg Z;


    parameter s0=0, s1=1, s2=2, s3=3;
    reg [0:1] MooreState;

    always @(posedge clk)
    begin
        case (MooreState)
            s0: MooreState <= (!A) ? s0: s2;
            s1: MooreState <= (!A) ? s0: s2;
            s2: MooreState <= (!A) ? s2: s3;
            s3: MooreState <= (!A) ? s1: s3;
        endcase
    end

    always @(MooreState)
    begin
        case (MooreState)
            s0: Z = 1;
            s1: Z = 0;
            s2: Z = 0;
            s3: Z = 1;
        endcase
    end

endmodule


```

 

****Blocking vs. non-blocking**


```
// blocking assignments
always @(posedge clk)
begin
    q1 = d;
    q2 = q1;
end
```

creates DFF
then q2 sets q1

 

```
// *non-blocking assignments
always @(posedge clk)
begin
    q1 <= d;
    q2 <= q1;
end
```

Execute at the same clk cycle

 

***Non-blocking area only assigned to the LHS targets AFTER the always block completes.**

Coding guideline

1. Use blocking assignments ("=") in always blocks that are meant to represent combinational logic.
2. Use non-blocking assignments ("<=") in always blocks that are meant to represent sequential logic.
3. Do not mix blocking & non-blocking assignments in the same always block.
4. In a block with complex if/else statements, ensure all outputs are assigned default values at the beginning.
5. Do not make assignments to the same output from multiple always blocks.

Warning messages

1. "Input X1 is unused"
2. "Output X1 is stuck at VDD or GND"
3. "Output X1 and X2 shared the same net"
4. "Output X1 has no driver" (empty circuit)

Xilinx project

- Go through Xilinx project
 - Create new project
 - Write Verilog code for full-adder
 - Write Verilog code for 4-bit adder
 - Write test code
 - Run simulation
 - Synthesize the circuit

```
module fullAdder(A, B, C, SUM, COUT);
    input A;
    input B;
    input C;
    output SUM;
    output COUT;

    assign SUM = A ^ B ^ C;
    assign COUT = (A & B) | (B & C) | (A & C);

endmodule
```

```
module FourBitAdder(A, B, SUM, COUT);
    input [3:0] A;
    input [3:0] B;
    output [3:0] SUM;
    output COUT;

    fullAdder a0 (A[0], B[0], 1'b0, SUM[0], w1);
    fullAdder a1 (A[1], B[1], w1, SUM[1], w2);
    fullAdder a2 (A[2], B[2], w2, SUM[2], w3);
    fullAdder a3 (A[3], B[3], w3, SUM[3], COUT);

endmodule
```

```
module fullAdderTest_v;

    // Inputs
    reg A;
    reg B;
    reg C;

    // Outputs
    wire SUM;
    wire COUT;

    // Instantiate the Unit Under Test (UUT)
    fullAdder uut (
        .A(A),
        .B(B),
        .C(C),
        .SUM(SUM),
        .COUT(COUT)
    );

    initial begin
        // Initialize Inputs
        A = 0;
        B = 0;
        C = 0;

        // Wait 100 ns for global reset to finish
        #100;
    end
```

```
module FourBitAdderTest_v;

    // Inputs
    reg [3:0] A;
    reg [3:0] B;

    // Outputs
    wire [3:0] SUM;
    wire COUT;

    // Instantiate the Unit Under Test (UUT)
    FourBitAdder uut (
        .A(A),
        .B(B),
        .SUM(SUM),
        .COUT(COUT)
    );

    integer i, j;
    initial begin
        for (i=0; i<16; i=i+1)
            for (j=0; j<16; j=j+1)
                begin
                    A = i;
                    B = j;
                    #10 ;
                end
    end
```

```

// Add stimulus here
A = 0;
B = 0;
C = 1;
#100;

A = 0;
B = 1;
C = 0;
#100;

A = 0;
B = 1;
C = 1;
#100;

A = 1;
B = 0;
C = 0;
#100;

A = 1;
B = 0;
C = 1;
#100;

A = 1;
B = 1;
C = 0;
#100;

A = 1;
B = 1;
C = 1;
#100;

end

endmodule

```

Xilinx CPU1

- Show CPU1 in Xilinx
 - Verilog Code (Behavioral)
 - Simulation Result (timing chart)
 - Synthesis (Hardware)

Reminder

You may now turn on your cellphone ringer