

Lecture 2: Combinational Logic

CSE 140: Components and Design Techniques for Digital
Systems

Diba Mirza


Dept. of Computer Science and Engineering
University of California, San Diego

Outline

- What is a combinational circuit?
- Combinational Logic
 1. Scope
 2. Specification : Boolean algebra, truth tables
 3. Synthesis: circuits

Specifying Logic Problems: Truth tables

Example: Half Adder

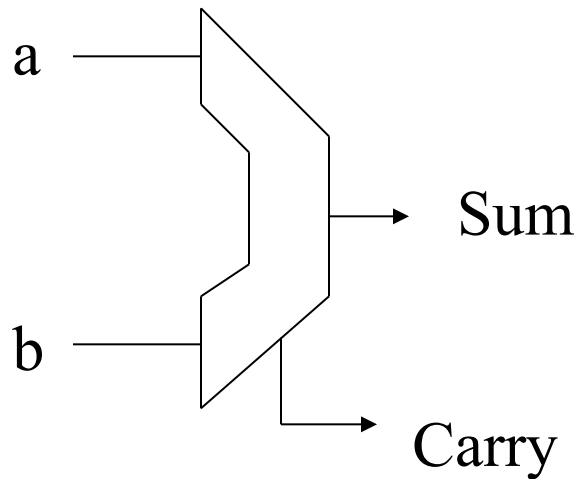

Truth Table


a	b	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

The process of designing the circuit

Truth Table

a	b	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

How?

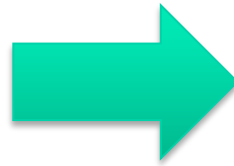

Switching Expressions or
Boolean Equation:

$$\text{Sum (a, b)} = a' b + ab'$$
$$\text{Carry (a, b)} = ab$$

Switching Function

How do we get a Boolean Equation from the truth table?

(Recall Disjunctive Normal Form in CSE 20)

Truth Table

a	b	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

SOP

Draw the circuit

Towards a compact representation of the disjunctive normal form

Min term

A B

0 0

0 1

1 0

1 1

Sum of Product Canonical Form

Minterm	A	B	Carry	Sum
A'B'	0	0	0	0
A'B	0	1	0	1
AB'	1	0	0	1
AB	1	1	1	0

I. $\text{sum}(A,B) =$

II. $\text{carry}(A,B) =$

Sum of Product Canonical Form

A	B	Y
0	0	0
1	0	0
0	1	1
1	1	1

Q: Does the following SOP canonical expression correctly express the above truth table:

$$Y(A,B) = \sum m(2,3)$$

A. Yes

B. No

Product of Sum Canonical Form

Max term	A	B	Carry	Sum
	0	0	0	0
	0	1	0	1
	1	0	0	1
	1	1	1	0

For the SOP expression we considered the combinations for which the output is 1

For the POS expression we will consider the combinations for which the output is 0

$\text{carry}(A,B)=$

Product of Sum Canonical Form is equivalent to which of the following?

- A. Conjunctive normal form
- B. Disjunctive normal form

Product of Sum Canonical Form

Max term	A	B	Carry	Sum
	0	0	0	0
	0	1	0	1
	1	0	0	1
	1	1	1	0

The POS expression for sum(A,B)

A. $(A' + B).(A + B')$

B. $A' B + AB'$

C. $(A + B').(A' + B)$

D. Either A or C

E. None of the above

Re-deriving the truth table

Truth Table

A	B	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Switching Expressions:

$$\text{Sum (A,B)} = A'B + AB'$$

$$\text{Carry (A, B)} = AB$$



Ex:

$$\text{Sum (0,0)} = 0' \cdot 0 + 0 \cdot 0' = 0 + 0 = 0$$

$$\text{Sum (0,1)} = 0' \cdot 1 + 0 \cdot 1' = 1 + 0 = 1$$

$$\text{Sum (1,1)} = 1' \cdot 1 + 1 \cdot 1' = 0 + 0 = 0$$

Logic circuit for half adder:

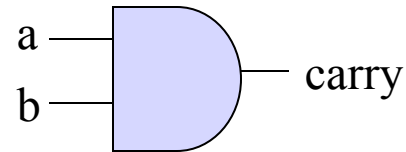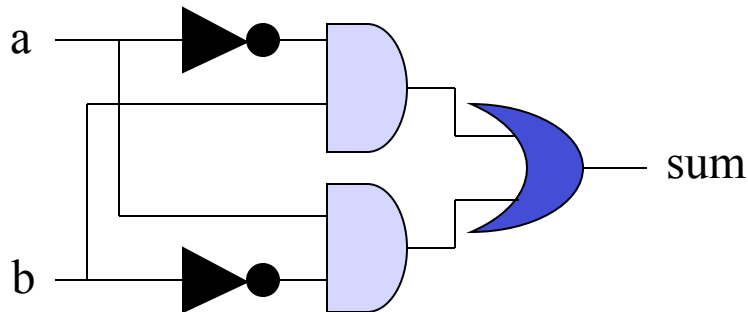

The SOP and POS forms don't usually give the optimal circuit or the simplest Boolean expression of the switching function

To optimize the circuit, we need to simplify the Boolean expression using:

1. Boolean Algebra axioms and theorems
2. Karnaugh Maps (K-Maps) (next lecture)

Axioms of Boolean Algebra


1. $B = 0$, if B not equal to 1
2. $0' = 1$
3. $1.1 = 1$
4. $0.1 = 0$
5. $a+0=a$, $a.1=a$ Identity law
6. $a+a'=1$, $a.a'=0$ Complement law

Theorems of Boolean Algebra


I. Commutative Law: $A + B = B + A$
 $AB = BA$

II. Distributive Law

$$A(B+C) = AB + AC$$


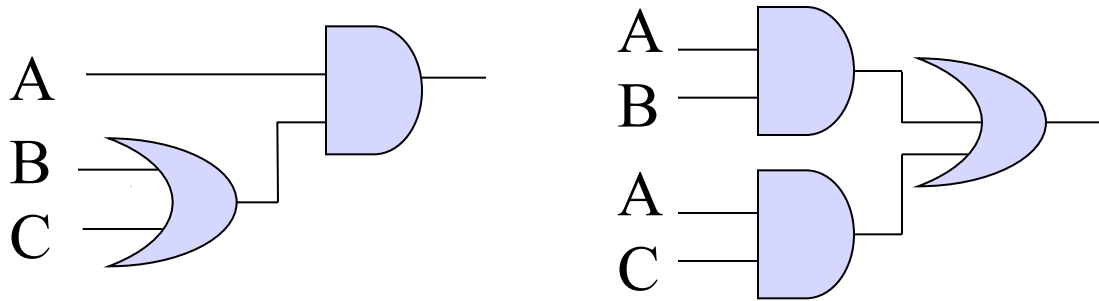


$$A+BC = (A+B)(A+C)$$


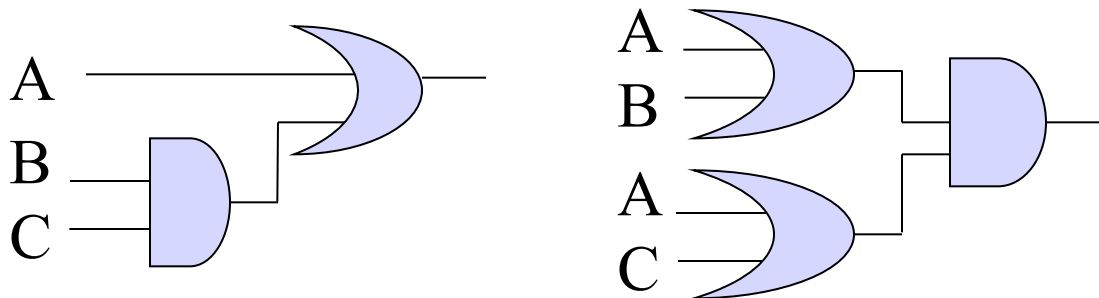


III Associativity

$$(A+B) + C = A + (B+C)$$

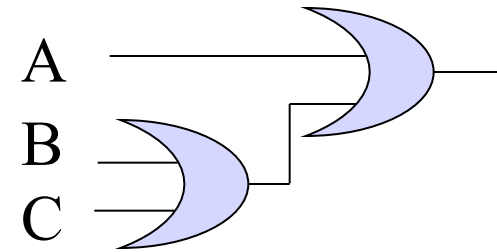
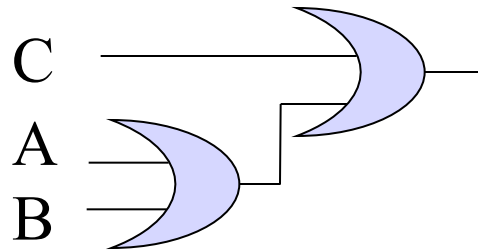


$$(AB)C = A(BC)$$

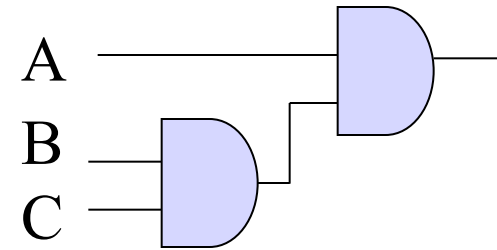
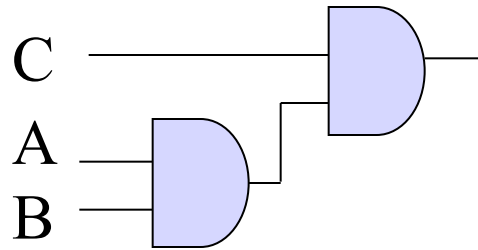


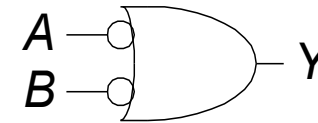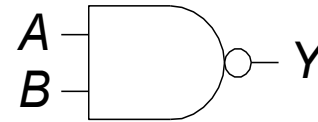V. DeMorgan's Theorem

- $Y = \overline{AB} = \overline{A} + \overline{B}$




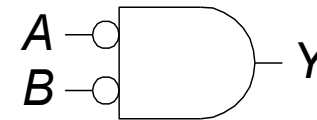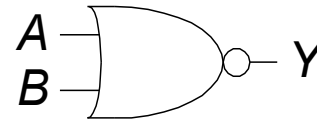- $Y = \overline{\overline{A} + \overline{B}} = \overline{A} \cdot \overline{B}$



Circuit Transformation: Bubble Pushing

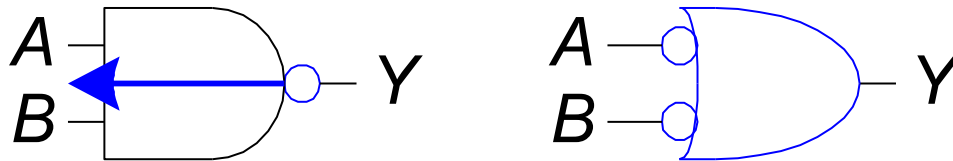
- Pushing bubbles backward (from the output) or forward (from the inputs) changes the body of the gate from AND to OR or vice versa.
- Pushing a bubble from the output back to the inputs puts bubbles on all gate inputs.



- Pushing bubbles on *all* gate inputs forward toward the output puts a bubble on the output and changes the gate body.





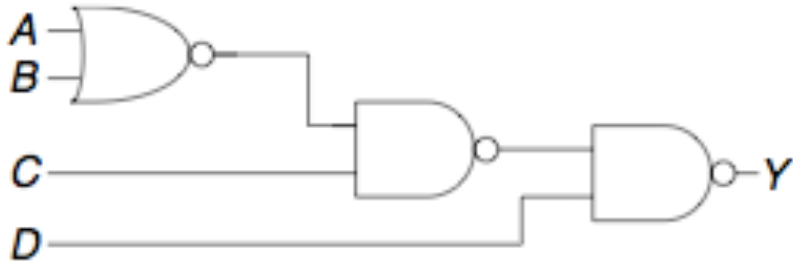Example of transforming circuits using bubble pushing



IV: Consensus Theorem:

$$AB + B' C + AC = AB + B' C$$

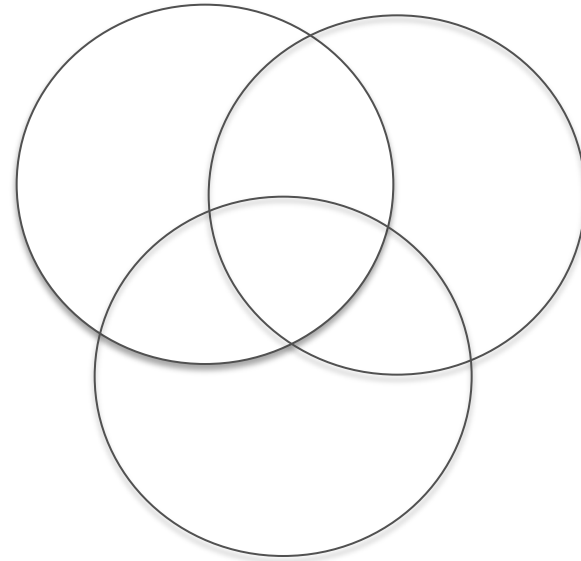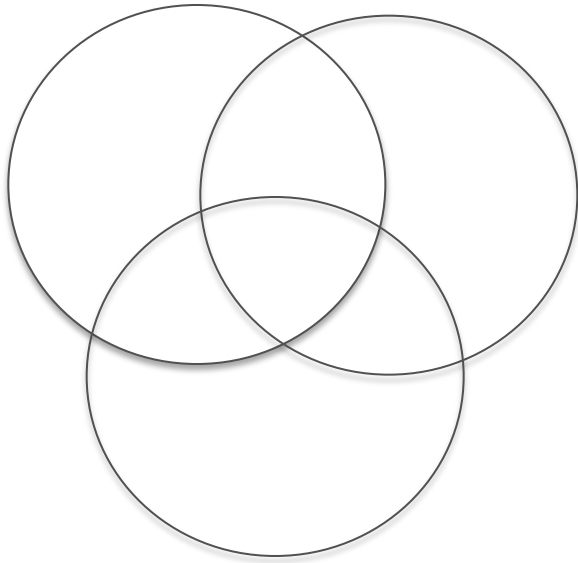

Venn Diagrams

PI Q: Which of the following is $AC' + BC + BA$ equal to?

A. $AB + C'A$

B. $AC' + CB$

C. $BC + AB$

D. None of the above

Proof of consensus Theorem using Boolean Algebra

$$AB+B'C+AC = AB+B' C$$

We are in a position to build a circuit to do n-bit Binary Addition

$$\begin{array}{r}
 5 \\
 + 7 \\
 \hline
 12
 \end{array}$$

An arrow points from the red '1' to the label "Carry".
 An arrow points from the '2' to the label "Sum".


	1	1	1	←	Carry bits
		1	0	1	5
+		1	1	1	7
	1	1	0	0	12
	↖		↖		
	Carryout		Sums		

Binary Addition: Hardware

- Half Adder: Two inputs (a,b) and two outputs (carry, sum).
- Full Adder: Three inputs (a,b,c) and two outputs (carry, sum).

Full Adder


Truth Table

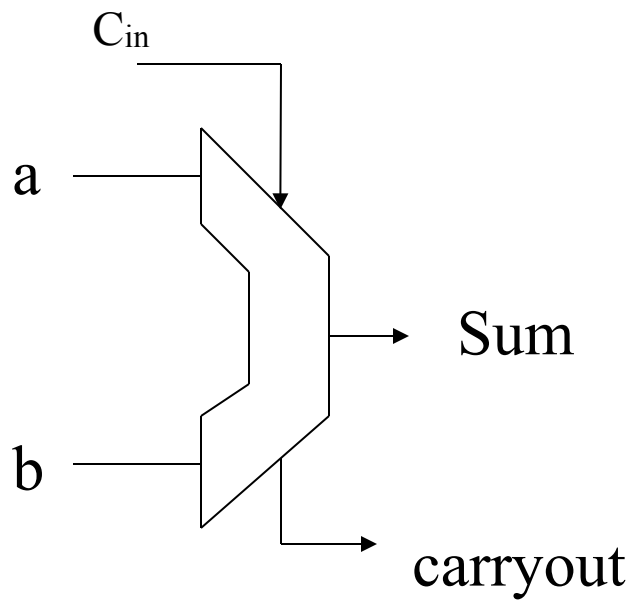


Id	a	b	c_{in}	carryout	sum
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

Minterm and Maxterm

Id	a	b	c _{in}	carryout	
0	0	0	0	0	$a+b+c$
1	0	0	1	0	$a+b+c'$
2	0	1	0	0	$a+b'+c$
3	0	1	1	1	$a' b c$
4	1	0	0	0	$a'+b+c$
5	1	0	1	1	$a b' c$
6	1	1	0	1	$a b c'$
7	1	1	1	1	$a b c$

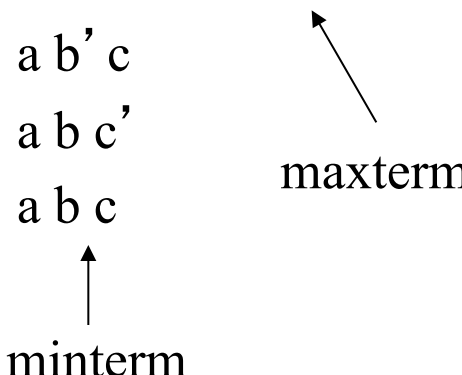

 ↑
 minterm

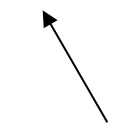

 ↑
 maxterm

Minterm and Maxterm

Id	a	b	c _{in}	carryout		
0	0	0	0	0		a+b+c
1	0	0	1	0		a+b+c'
2	0	1	0	0		a+b'+c
3	0	1	1	1	a' b c	
4	1	0	0	0		a'+b+c
5	1	0	1	1	a b' c	
6	1	1	0	1	a b c'	
7	1	1	1	1	a b c	

PI Q: Is $f_1 = f_2$?
 A. Yes
 B. No


$$\text{Carryout} = f_1(a,b,c) = a'bc + ab'c + abc' + abc$$

$$= m_3 + m_5 + m_6 + m_7 = \Sigma m(3,5,6,7)$$

$$f_2(a,b,c) = (a+b+c)(a+b+c')(a+b'+c)(a'+b+c)$$

$$= M_0M_1M_2M_4 = \Pi M(0, 1, 2, 4)$$

Full Adder

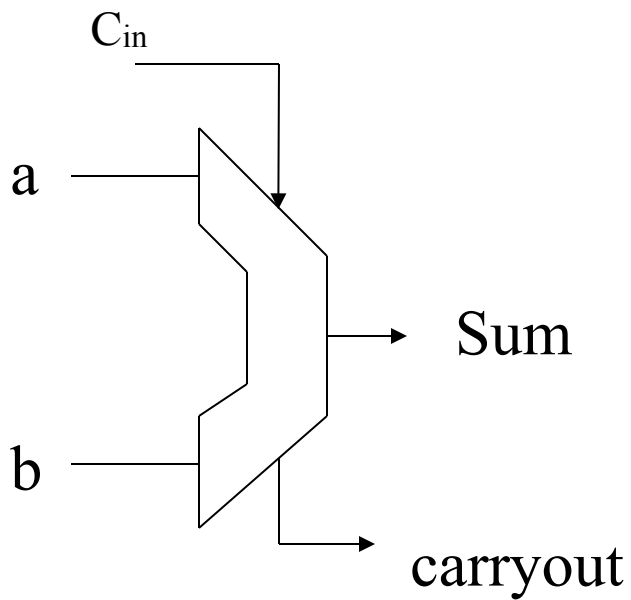

Truth Table

Id	a	b	c_{in}	carryout	sum
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

Circuit for full adder

$$\text{Carryout (a,b,c)} = a'bc + ab'c + abc' + abc$$

$$\text{Sum(a,b,c)} = \Sigma m(1,2,4,7)$$

Ultimate goal...

- Optimize the circuit to be the simplest possible
- Reduction of canonical expressions
(Next lecture)