



CSE140: Components and Design Techniques for Digital Systems

Logic minimization algorithm summary

Definition of terms for two-level simplification

- ON-set:
 - the set of all 1s in the result of a logic function (i.e. all “boxes” of a Kmap where the value is 1)
- OFF-set:
 - the set of all 0s in the result of a logic function (i.e. all “boxes” of a Kmap where the value is 0)
- SOP: Sum of Products
- Canonical SOP = minterms expansion
- Minimal SOP = resulting from 2-level minimization (i.e. Kmaps) by covering 1s
- Similar definitions for POS

Definition of terms for two-level simplification

- **Implicant**
 - single element of ON-set or DC-set or any group of these elements that can be combined to form a subcube
- **Prime implicant**
 - implicant that can't be combined with another to form a larger subcube
- **Essential prime implicant**
 - prime implicant is essential if it alone covers an element of ON-set
 - will participate in ALL possible covers of the ON-set
 - DC-set used to form prime implicants but not to make implicant essential
- **Cover:**
 - a subset of implicants that covers all 1s in the Kmap
- **Objective:**
 - grow implicant into prime implicants (minimize literals per term)
 - cover the ON-set with as few prime implicants as possible (minimize number of product terms)

Examples to illustrate terms

				A	
		0	X	1	0
		1	1	1	0
C		1	0	1	1
		0	0	1	1
				B	
				D	

				A	
		0	0	1	0
		1	1	1	0
C		0	1	1	1
		0	1	0	0
				B	
				D	

Examples to illustrate terms

		A		
	0	X	1	0
	1	1	1	0
C	1	0	1	1
	0	0	1	1
		B		D

6 prime implicants:

$A'B'D$, BC' , AC , $A'C'D$, AB , $B'CD$

essential

minimum cover: $AC + BC' + A'B'D$

5 prime implicants:

BD , ABC' , ACD , $A'BC$, $A'C'D$

essential

minimum cover: 4 essential implicants

		A		
	0	0	1	0
	1	1	1	0
C	0	1	1	1
	0	1	0	0
		B		D

Algorithm for two-level simplification

- **Algorithm:** minimum sum-of-products expression from a Karnaugh map
 - **Step 1:** choose an element of the ON-set
 - **Step 2:** find "maximal" groupings of 1s and Xs adjacent to that element
 - consider top/bottom row, left/right column, and corner adjacencies
 - this forms prime implicants (number of elements always a power of 2)
 - Repeat Steps 1 and 2 to find all **prime implicants**
 - **Step 3:** revisit the 1s in the K-map
 - if covered by single prime implicant, it is essential, and participates in final cover
 - 1s covered by essential prime implicant do not need to be revisited
 - **Step 4:** if there remain 1s not covered by essential prime implicants
 - select the smallest number of prime implicants that cover the remaining 1s

Algorithm for two-level simplification (example)

		A		
	X	1	0	1
	0	1	1	1
C	0	X	X	0
	0	1	0	1
		B		

		A		
	X	1	0	1
	0	1	1	1
C	0	X	X	0
	0	1	0	1
		B		

2 primes around $A'BC'D'$

		A		
	X	1	0	1
	0	1	1	1
C	0	X	X	0
	0	1	0	1
		B		

2 primes around $ABC'D$

		A		
	X	1	0	1
	0	1	1	1
C	0	X	X	0
	0	1	0	1
		B		

3 primes around $AB'C'D'$

		A		
	X	1	0	1
	0	1	1	1
C	0	X	X	0
	0	1	0	1
		B		

2 essential primes

		A		
	X	1	0	1
	0	1	1	1
C	0	X	X	0
	0	1	0	1
		B		

minimum cover (3 primes)

Essential primes

Which are the essential prime implicants?

- A. CD'
- B. BD
- C. $AC'D$
- D. All of the above
- E. None of the above

		A		D
C	X	0	X	0
	0	1	X	1
	0	X	X	0
	X	1	1	1
		B		


For more practice: think about essential prime implicants!



CSE140: Components and Design Techniques for Digital Systems


Muxes and demuxes

Multiplexer (Example)

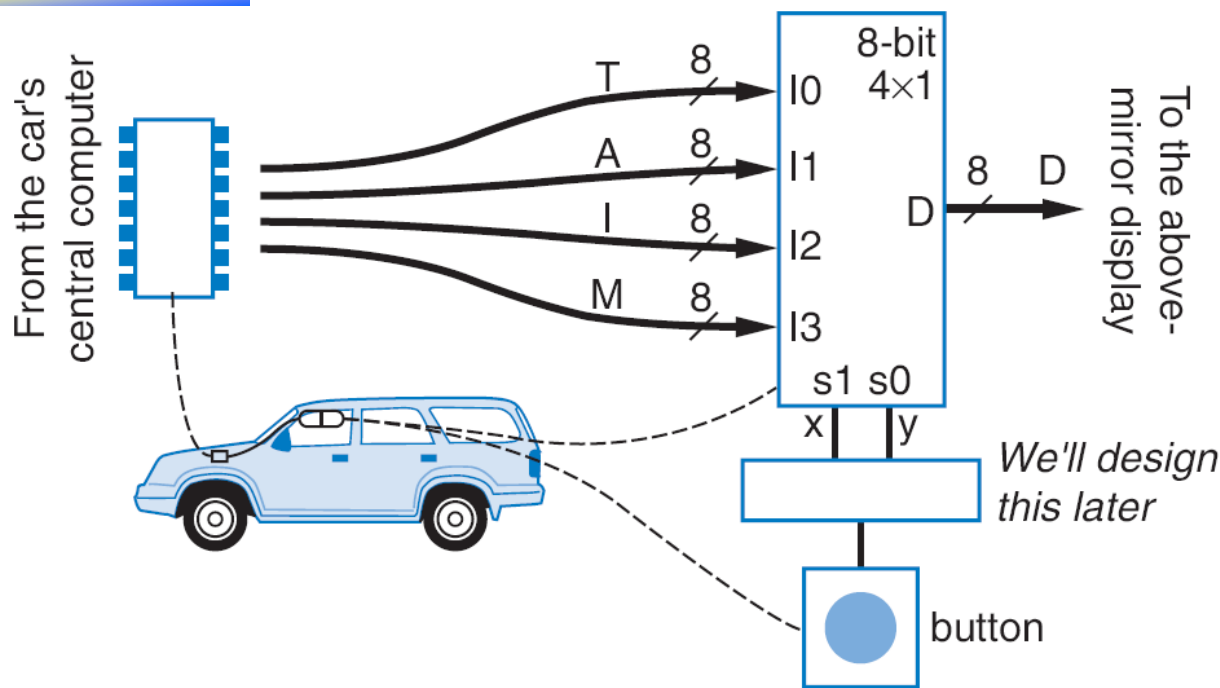

- Four possible display items
 - Temperature (T), Average miles-per-gallon (A), Instantaneous mpg (I), and Miles remaining (M) -- each is 8-bits wide
 - Choose which to display using two inputs x and y
 - Use 8-bit 4x1 mux


Multiplexer (Example)

 

- You are not sure whether an input of the MUX would have a 1 or a 0
- You should build the MUX with a component that is good at passing both 0s and 1s

Transmission Gate: Mux/Tristate building block


- nMOS are on when $gate=1$
 - good at passing 0s from source to drain
 - pass 1's poorly from source to drain
- pMOS are on when $gate=0$
 - good at passing 1s from source to drain
 - pass 0's poorly from source to drain
- Transmission gate is a better switch
 - passes both 0 and 1 well
- When $EN = 1$, the switch is ON:
 - $EN = 0$ and A is connected to B
- When $EN = 0$, the switch is OFF:
 - A is not connected to B
- *The pass transistor acts as a tristate buffer*

 

Floating: Z, Tristate Buffer and Tristate Busses

- Floating, high impedance, open, high Z
 - Disconnected
- Floating nodes are used in tristate busses
 - many different drivers, but only one is active at once


Tristate Buffer

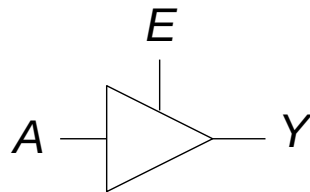

<i>E</i>	<i>A</i>	<i>Y</i>
0	0	Z
0	1	Z
1	0	0
1	1	1

Note: do not
confuse this with
the inverter symbol!

Tristate Bus

 


2:1 Multiplexer or Mux



- Selects between one of N inputs to connect to output
- $\log_2 N$ -bit select input – control input
- **Example: 2:1 Mux**

Logic gates

Pass gates

 

Tristates

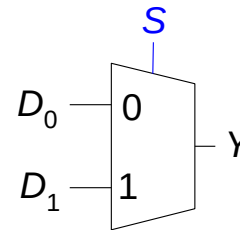 


S	D_1	D_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

S	Y
0	D_0
1	D_1


Y	$D_0 D_1$					
	S		00	01	11	10
0	0		0	0	1	1
1	1		0	1	1	0

$$Y = D_0 \bar{S} + D_1 S$$

 

Multiplexers/selectors

 
- 2:1 mux: $Z = A'I_0 + AI_1$
- 4:1 mux: $Z = A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3$
- 8:1 mux: $Z = A'B'C'I_0 + A'B'CI_1 + A'BC'I_2 + A'BCI_3 + AB'C'I_4 + AB'CI_5 + ABC'I_6 + ABCI_7$
- In general: $\sum_{k=0}^{2^n-1} m_k I_k$
 - shorthand form for a $2^n:1$ Mux



For example

Logic using Multiplexers


- Example of 2:1 mux implementation

 

You can implement a 2-variables logic function using a 2:1 multiplexer:


- Use one variable for the selection input
- Connect the MUX inputs to either
 - The second variable (in true or complemented form)
 - GND
 - VDD
- You can also use larger MUXs (see next slide)

B. No

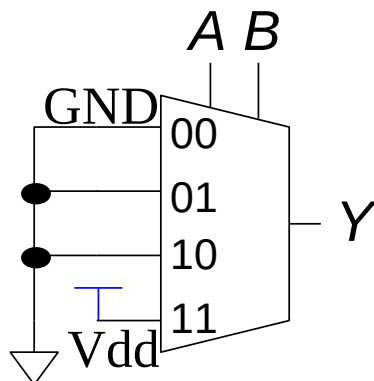
$$Y = AB$$


Mux as general-purpose logic

- Example: $Z(A,B,C) = AC + BC' + A'B'C$

 

Cascading muxes

 


Function $Z(A,B,C)$ implemented by 2:1 Muxes above is:

- A. $A'B'C' + ABC + BC'$
- B. $(A' + AC)B + B'C'$
- C. $A'B' + B'C + BC'$
- D. $A' + AC + BC'$
- E. None of the above

Mux example: Logical function unit

C0	C1	C2	Function	Comments
0	0	0	1	always 1
0	0	1	$A + B$	logical OR
0	1	0	$(A \bullet B)'$	logical NAND
0	1	1	$A \text{ xor } B$	logical xor
1	0	0	$A \text{ xnor } B$	logical xnor
1	0	1	$A \bullet B$	logical AND
1	1	0	$(A + B)'$	logical NOR
1	1	1	0	always 0

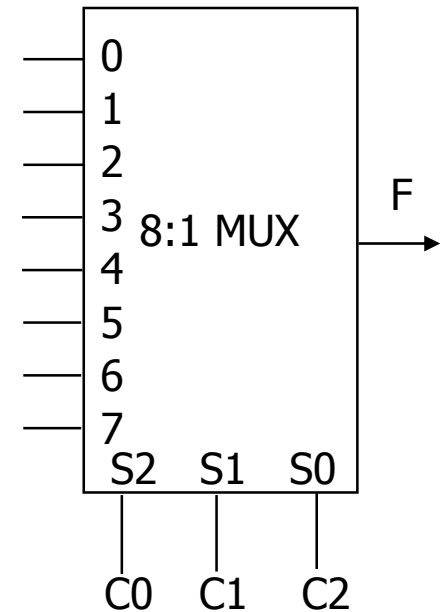




BREAK !

Demux or Decoder

 - N inputs, 2^N outputs
- One-hot outputs: only one output HIGH at a time when enable signal is 1 (EN=1)



For the moment, we call it decoder or demuxer with no distinction. We'll see the (slight) difference later

A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Decoder: logic equations & implementation

- Decoders/demultiplexers

- control inputs (called “selects” (S)) represent binary index of output to which the input is connected
- data input usually called “enable” or G in equations->

1:2 Decoder:


$$\begin{aligned} 00 &= G \bullet S' \\ 01 &= G \bullet S \end{aligned}$$

2:4 Decoder:

$$\begin{aligned} 00 &= G \bullet S1' \bullet S0' \\ 01 &= G \bullet S1' \bullet S0 \\ 02 &= G \bullet S1 \bullet S0' \\ 03 &= G \bullet S1 \bullet S0 \end{aligned}$$


 
3:8 Decoder:

$$\begin{aligned} 00 &= G \bullet S2' \bullet S1' \bullet S0' \\ 01 &= G \bullet S2' \bullet S1' \bullet S0 \\ 02 &= G \bullet S2' \bullet S1 \bullet S0' \\ 03 &= G \bullet S2' \bullet S1 \bullet S0 \\ 04 &= G \bullet S2 \bullet S1' \bullet S0' \\ 05 &= G \bullet S2 \bullet S1' \bullet S0 \\ 06 &= G \bullet S2 \bullet S1 \bullet S0' \\ 07 &= G \bullet S2 \bullet S1 \bullet S0 \end{aligned}$$



Logic Using Decoders

- OR minterms

  

Example: $F = \sum m(3,4,7)$


Example of demux as general-purpose logic

$$F1 = A'BC'D + A'B'CD + ABCD$$

$$F2 = ABC'D' + ABC$$

$$F3 = (A' + B' + C' + D')$$

 How many 4:16 demux are required to implement these three functions?




Another example

- $F(A,B,C) = \Pi M(0,2,4)$

Tree of Decoders


 
Implement a $6\text{-}2^6$ decoder with $3\text{-}2^3$ decoders.



You can use smaller decoders
to build a larger one


Demultiplexer and Decoder

  - **Demultiplexer:** has a data input and it reports it on the output line specified by the selection
- **Decoder:** takes an input address and switches to 1 the corresponding output line
- Note: the behavior of a decoder with “enable” would be the same of a demultiplexer, but we give different names to the inputs



Multi-level logic

- $x = A D F + A E F + B D F + B E F + C D F + C E F + G$
 - reduced sum-of-products form – already simplified
 - 6 x 3-input AND gates + 1 x 7-input OR gate (that may not even exist!)
 - 25 wires (19 literals plus 6 internal wires)
- $x = (A + B + C) (D + E) F + G$
 - factored form – not written as two-level S-o-P
 - 1 x 3-input OR gate, 2 x 2-input OR gates, 1 x 3-input AND gate
 - 10 wires (7 literals plus 3 internal wires)

 

Multi-level logic

- No global definition of “optimal” multilevel circuit
 - Optimality depends on user-defined goals
 - Synthesize an implementation that meets design goals
- Synthesis requires CAD-tool help
 - No simple hand methods like K-maps
 - CAD tools manipulate Boolean expressions
 - Factoring, decomposition, etc
- Advantages over 2-level logic
 - Smaller circuits
 - Reduced fan-in
 - Less wires
- Disadvantages w.r.t 2-level logic
 - More difficult design
 - Less powerful optimizing tools
 - Dynamic hazards