
Implementing and Using a Mixed-Signal Test Bus

Stephen Sunter


sunter@logicvision.com

© Stephen K. Sunter, 2004 Permission is hereby given to distribute freely,
providing there is no fee charged and this copyright notice is included.

Tutorial outline

- Introduction to Mixed-Signal Boundary Scan and Test
 - 1149.1, .4, and LF analog test buses
- Architecture and Design of 1149.4
 - Architecture, Instruction set, ABM & TBIC design
- System Test Methodologies
 - Test automation, BSDL
 - System test methods

 Introduction to Mixed-Signal Boundary Scan




Introduction to Boundary Scan

- Motivation for developing boundary scan
 - Circuit board size getting too small/expensive to probe
 - Need standard access to on-chip test capabilities
- Expected benefits
 - Lower test cost – less hardware, complexity
 - Faster time to market – more automation, reuse
- Result: JTAG, IEEE 1149.1 - 1990
 - Serial, digital access to all IC “digital” pins
 - Standard 4~5 pin Test Access Port


1149.1 digital control

(only mandatory TAP pins shown)

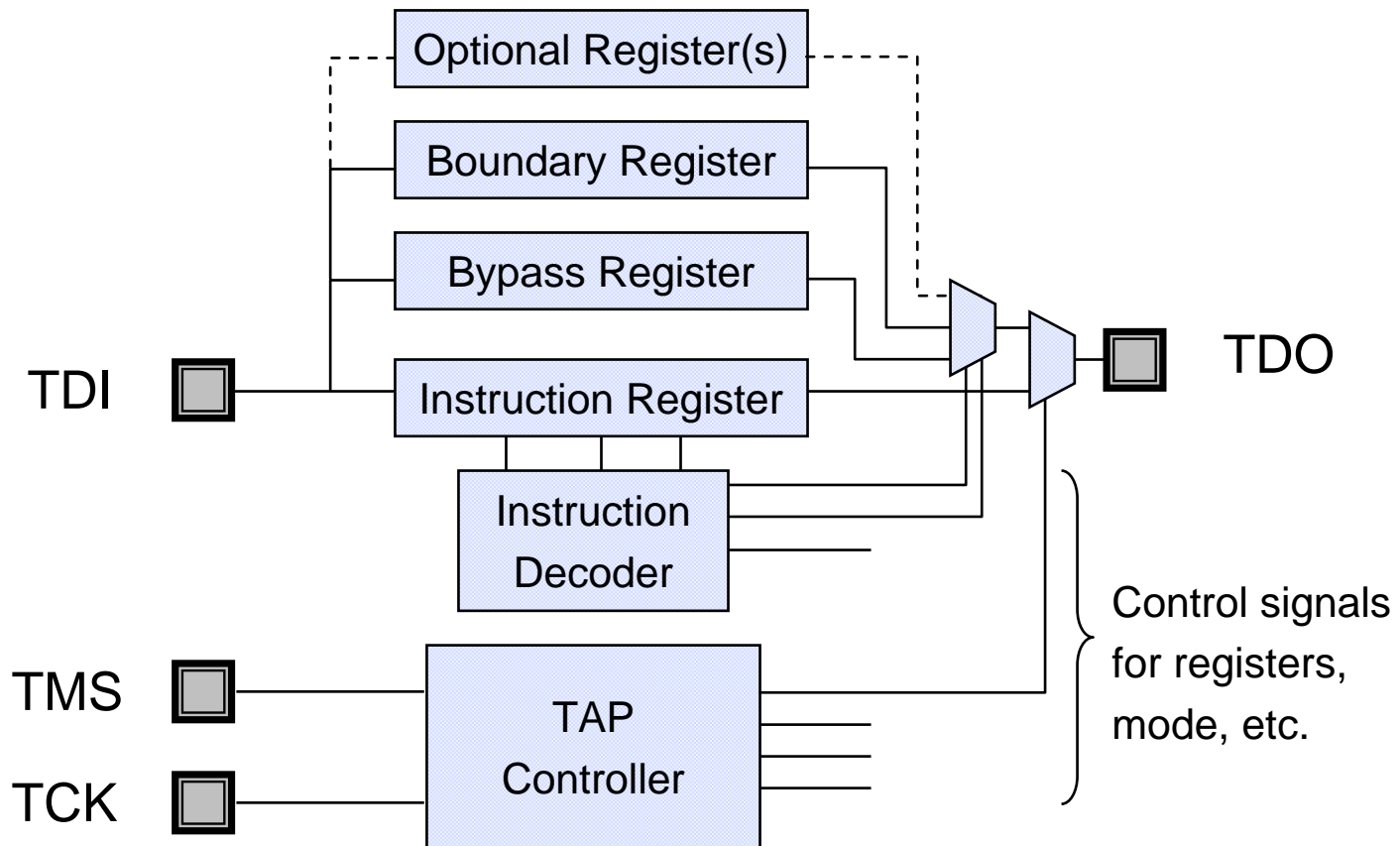
- 4 pin Test Access Port used for all control and observation



1149.1 view of digital IC

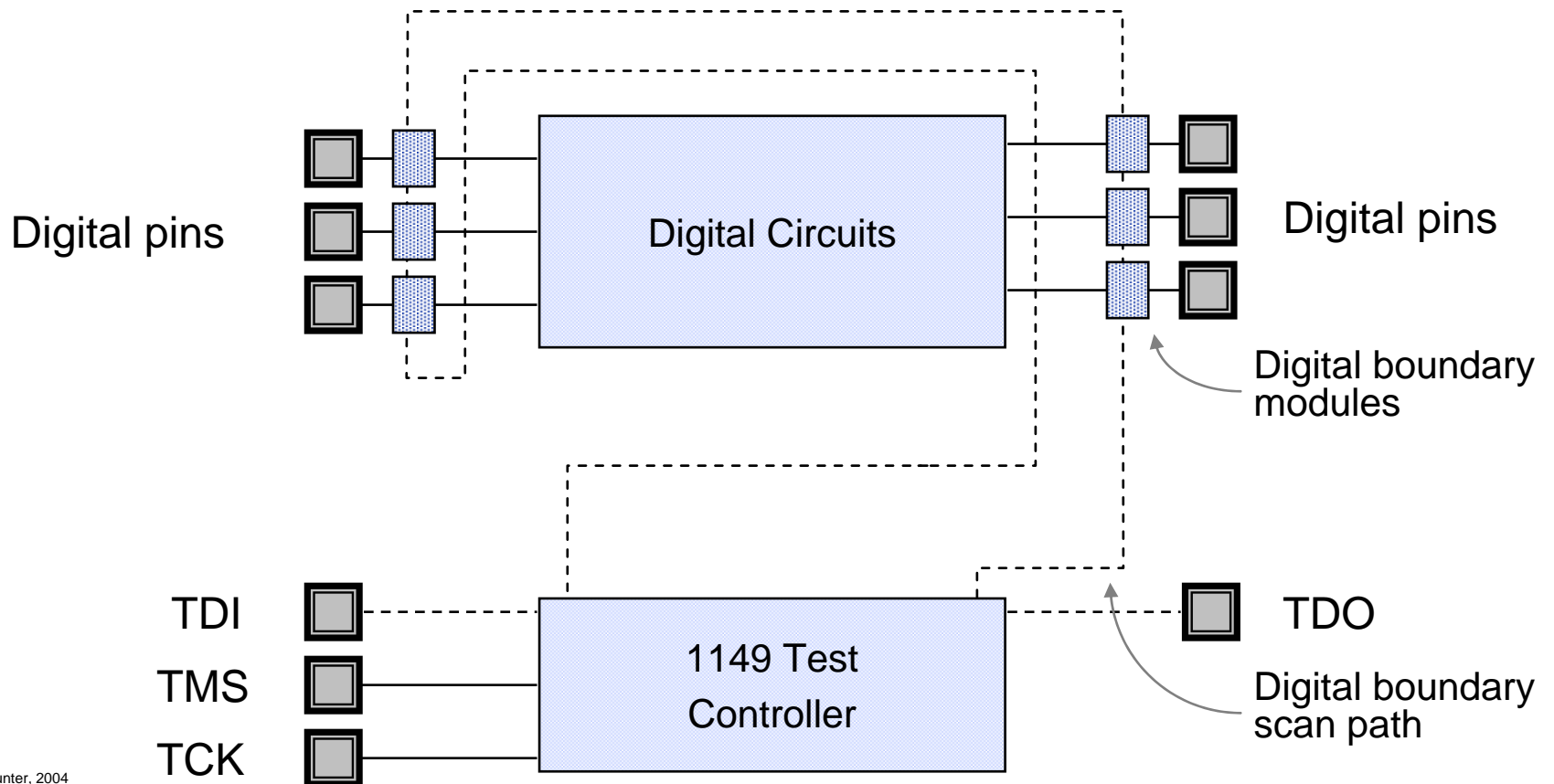

1149.1 view of mixed-signal IC

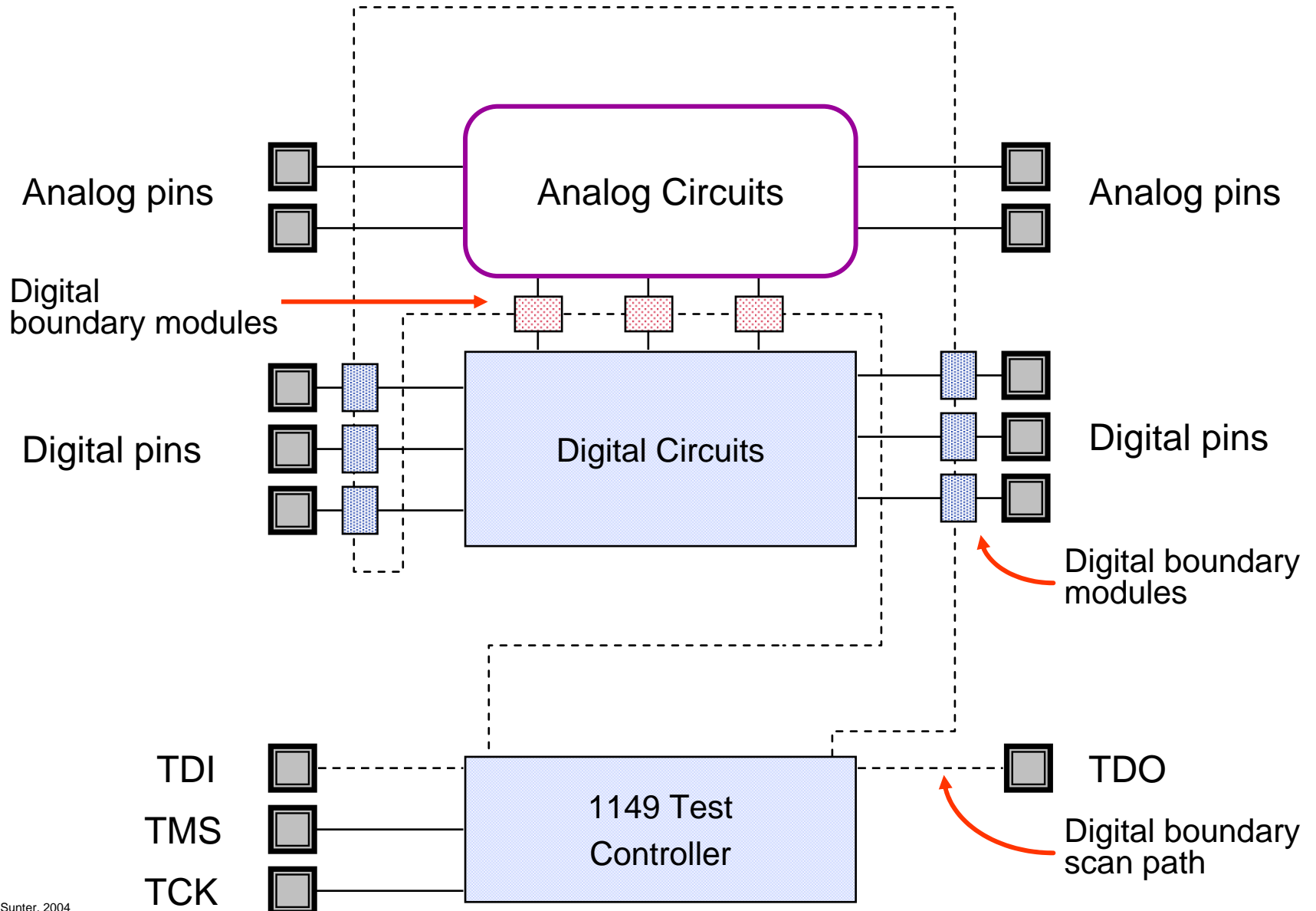


What's wrong with this picture?

- Analog pins not handled by 1149.1
 - New ICs & boards with mixed-signal is >50%
 - Number of digital pins with analog circuitry is growing
 - termination resistors, pull-ups, capacitors
- Differential pins not handled by 1149.1
 - Number of differential pins growing
 - Higher speed, lower V_{DD} , lower power, less EMI
- Digital ICs can have significant analog content
 - V_{BIAS} , V_{REF} , on-chip V_{DD}/V_{BB} generation

Introduction to 1149.4


- Motivation for developing boundary scan
 - 1149.1 success is limited by analog circuitry
 - Board passive components getting too small to probe
 - *P1149.4 Working Group started in 1992*
- Expected benefits
 - Lower test cost, time to market, ... *for all boards*
- Result: IEEE 1149.4 - 1999
 - Serial, analog access to all IC “analog” pins
 - Standard 2 pin Analog TAP (low frequency, analog bus)

1149.4 view of mixed-signal IC

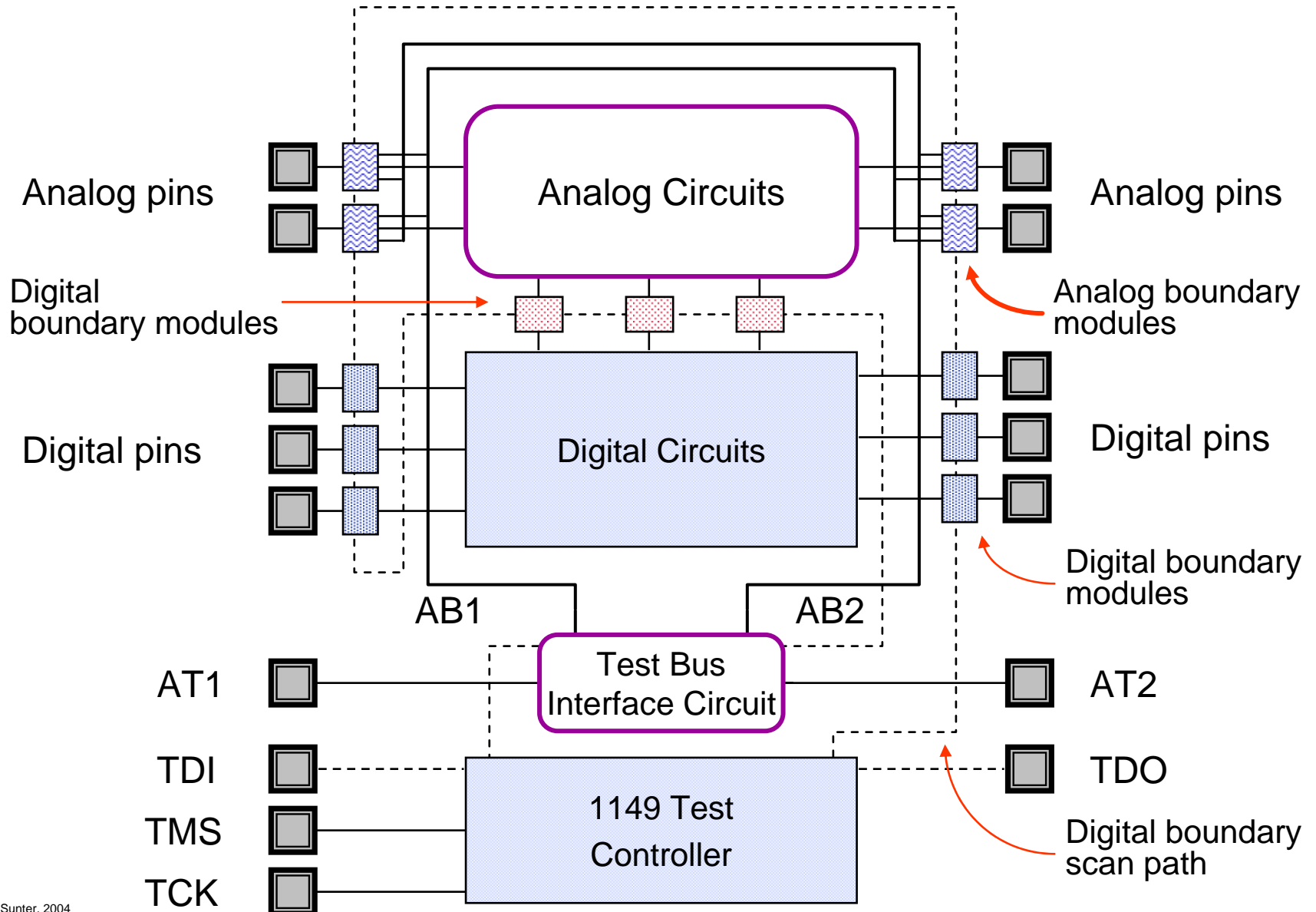


1149.1 board-level view

 - Parallel control bus
- Serial (or parallel) data bus




1149.4 board-level view

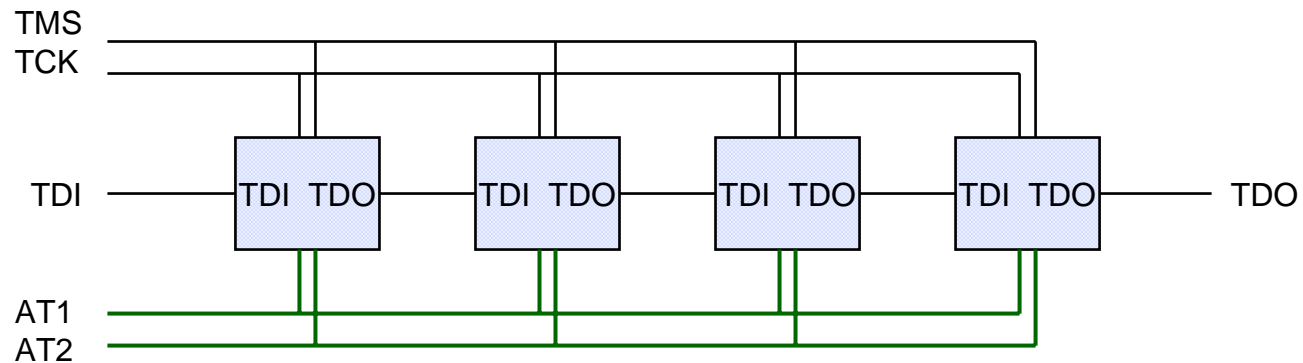- 1149.1 control and data buses
- Parallel analog bus



1149.4 board-level view

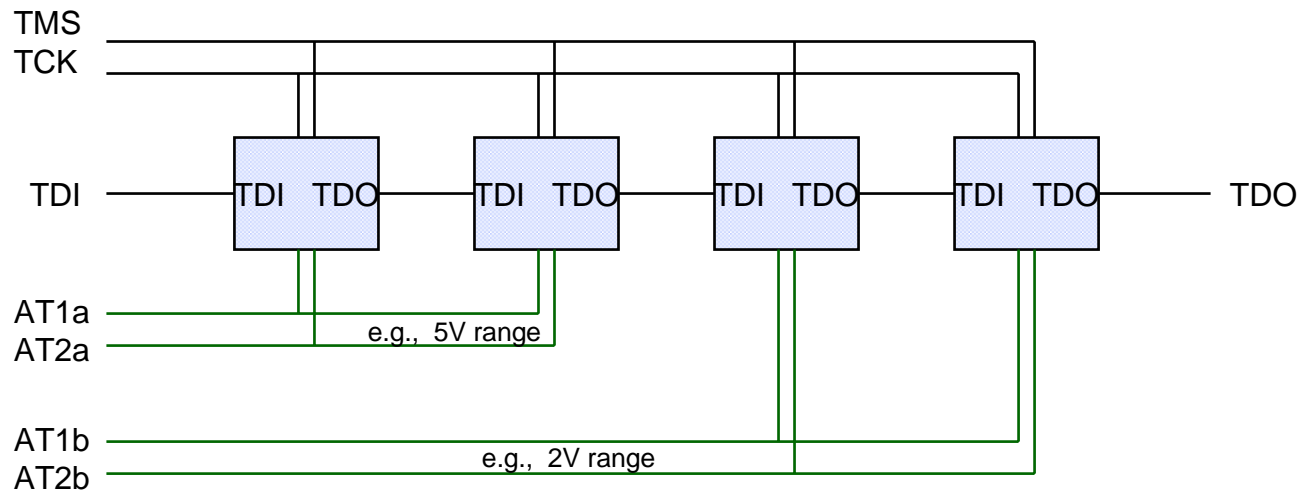- Alternative arrangement to accommodate ...
 - Multiple voltage ranges
 - Diverse frequency ranges
 - Large number of devices



Why low frequency bus?

LF: <100 kHz (allows <1ms measurements)

- Won't affect, or be affected by, other circuitry
 - Coupling via interconnect C and L is minimal at LF
 - Most interference is from digital at HF – easy to LPF
- Relatively cheap to measure accurately
 - 16~24b resolution Generators/Digitizers are LF
 - Can implement on-chip using sigma-delta
- 1149.4 requires LF, but does not preclude HF

Why analog 2-wire bus?

- Continuous time, voltage, current
 - Choose sampling rate, accuracy, precision... post-silicon
 - Many parameters inherently analog
- Lowest power, widest voltage range
 - CMOS transmission gates + logic: \approx zero DC current
 - CMOS transmission gates convey voltages outside rails
- Two wires
 - Stimulus/response, force/measure, \pm differential

Myths about LF analog bus

X Not useful for HF analog circuit test

✓ Can measure DC biases, termination impedances, and can drive/monitor AC via on-chip mod/demod

X Not useful for digital circuit test

✓ Can measure output drive (V_{OL}/I_{OL}), V_{IL} , pull-ups, V_{DD} , ... without probing the pins


X Slow – long test times

✓ Up to 50 measurements/ms, with 16-bit accuracy


X 1149.4 is a set of constraints for a LF analog bus

✓ All rules had to satisfy criteria of “necessary & sufficient”

Pin test circuitry overview

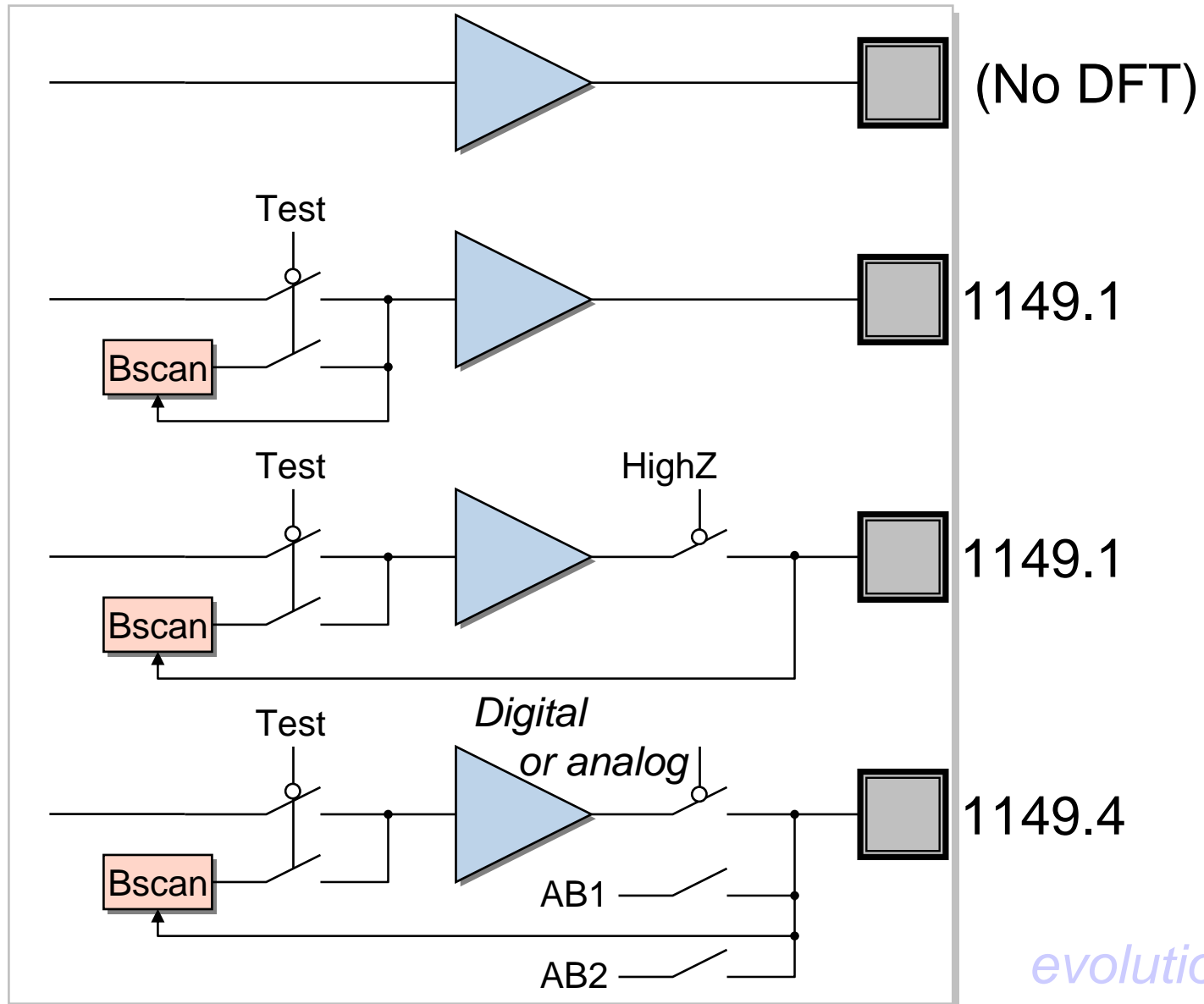

Pin test circuitry overview

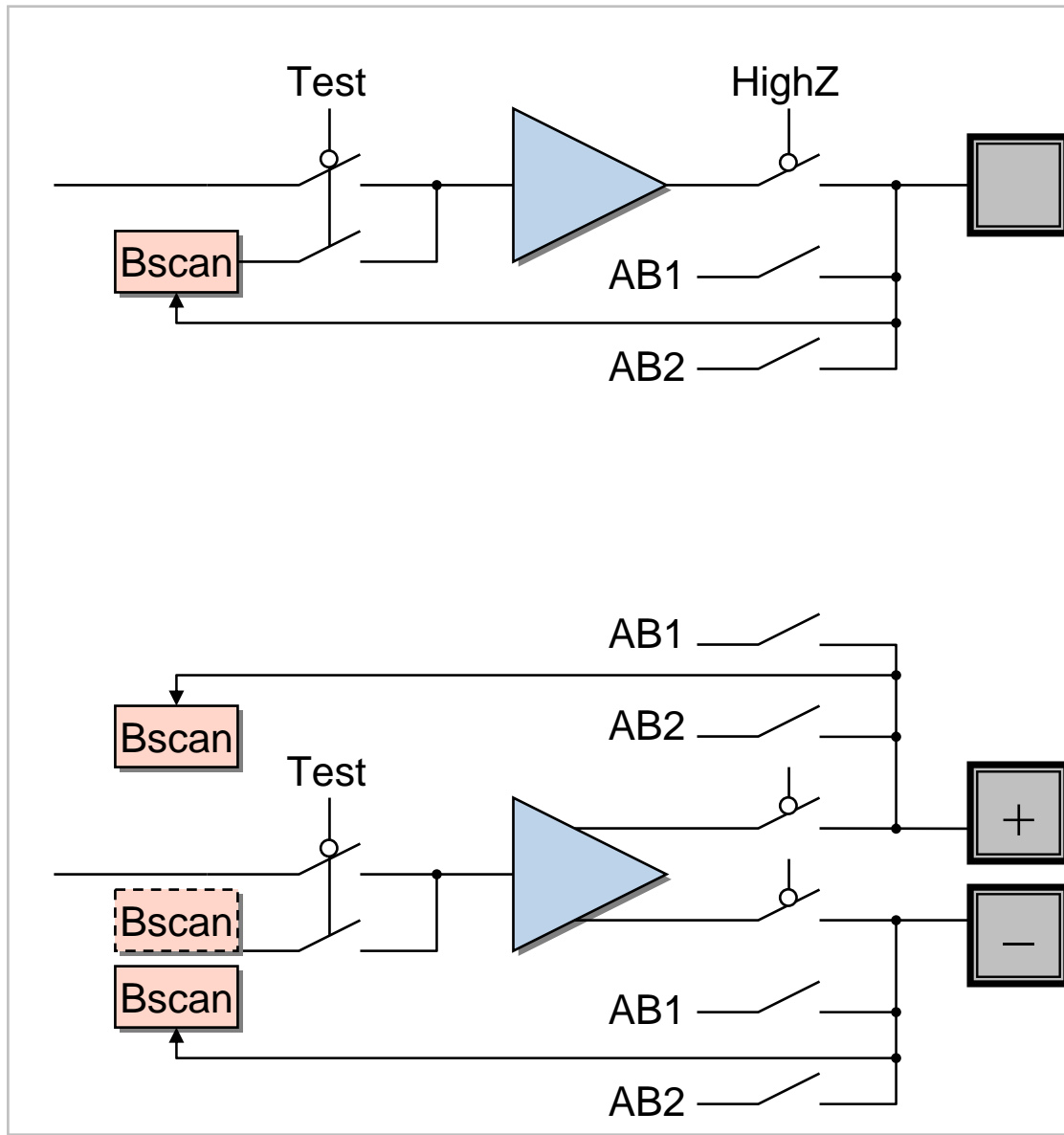

1149.4
Single-ended
Digital or analog

1149.4
Differential
Analog

Required test functions for each pin

Each “analog” pin shall be able to

Achieve isolation

- Connect to core
- Disconnect from core, i.e., from all active circuitry (“CD state”)




Perform tests equivalent to 1149.1

- Drive pin's V_{MAX} , V_{MIN} (D.C.)
- Compare V_{PIN} to pin's V_{TH} , where $V_{TH} \approx (V_{MIN}+V_{MAX})/2$


101101

Facilitate analog parametric tests

 - Deliver analog ground (V_G) via power rail
- Deliver current to pin via AT1 pin and AB1 bus
- Monitor pin's voltage via AB2 bus and AT2 pin



Required test functions

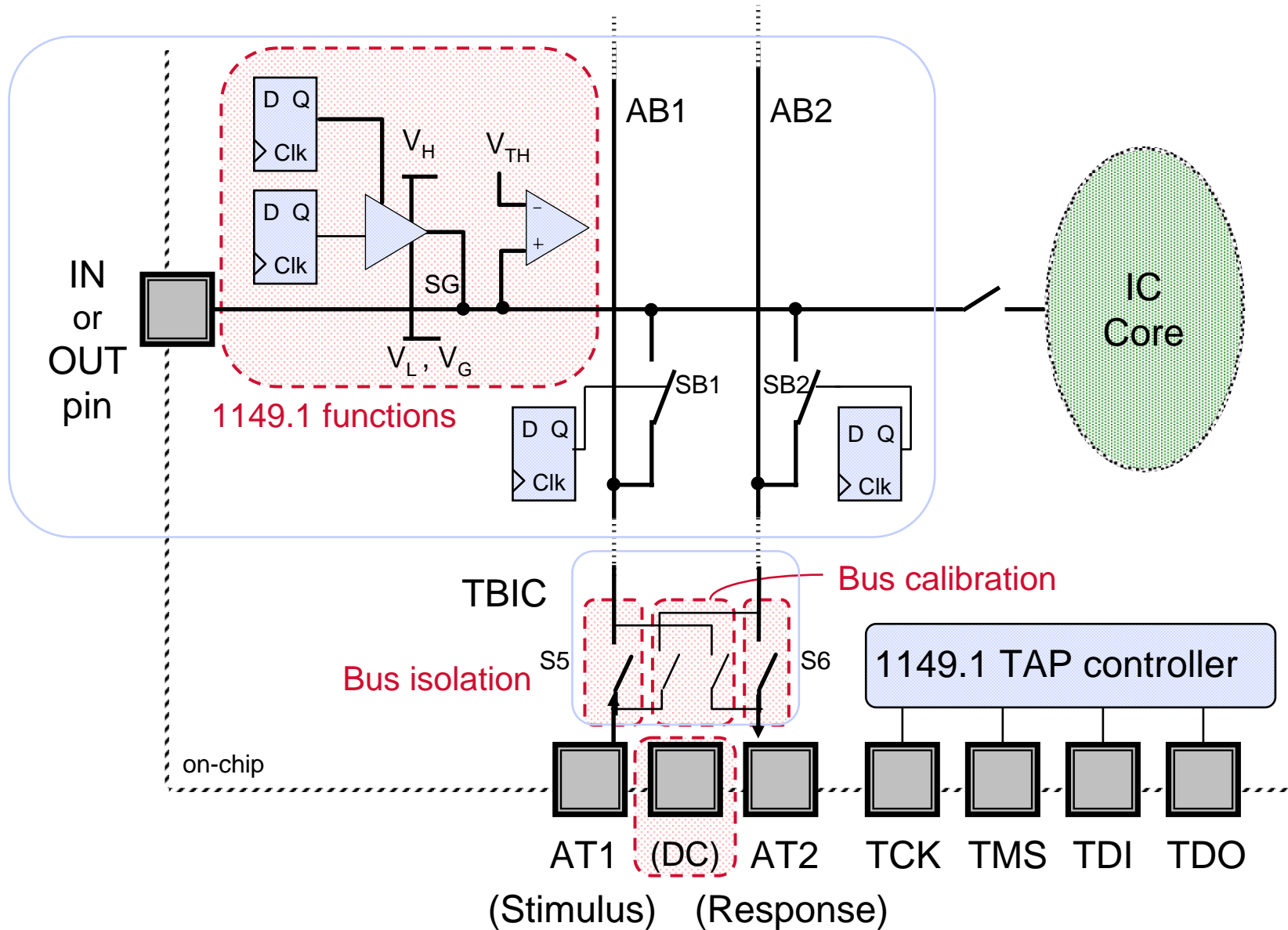

Test pins


- TCK Clock Rising edge latches TMS, TDI
Falling edge updates TDO
- TMS Mode Select Determines next state
- TDI Data In Instructions or scan data
- TDO Data Out Test results or for next chip
- TRST Reset Resets test circuitry (optional)

- AT1 Analog Test Stimulus current bus
- AT2 Analog Test Resultant voltage bus
- AT1N Analog Test Inv. stimulus current (optional)
- AT2N Analog Test Inv. resultant voltage (optional)

Analog Test Access Port (ATAP)


AT1: stimulus input

- at least capable of conveying $\pm 100 \mu\text{A}$
 - may be any combination of AC and DC
 - DC–10 kHz minimum bandwidth ($\pm 0.04 \text{ dB/} \pm 0.5\%$)
 - sufficient for state-of-the-art ATE to achieve $< 1\%$ accuracy

 


AT2: response output

 - at least capable of conveying $\pm 100 \text{ mV}$
 - range at ABM: $V_{SS} - 100 \text{ mV}$ to $V_{DD} + 100 \text{ mV}$
 - ensures that protection diodes are not activated



$V_{SS} - 100 \text{ mV} ?$

 - Why does voltage range of analog buffer need to extend 100 mV outside power rails?



< 100 μA and < 100 mV ?

- Max switch resistance permitted is 10 k Ω
 - 1 k Ω appears optimal
 - Switch resistance is non-linear
 - >100 μA may cause >1% distortion and inaccuracy
- CUT impedance for 1% accuracy is 10 Ω ~100 k Ω
 - 1k Ω is geometric mean – 100 μA causes 100 mV
 - Larger AC voltage swing around V_{SS} or V_{DD} may activate protection diodes
- But ... for some measurements, >1 mA is OK !

Core access

- Not required, and has no rules
 - Must not interfere with boundary tests
 - Permit separate analog buses for boundary, core

- Facilitates ...
 - Reusable, *ad hoc* tests for random analog circuitry
 - Within company, from IP suppliers, and from universities
 - Systematic parametric test access
 - Measure temperature, impedance, drive, switching point, ...
 - Inject corrected signals, analog faults, deviations, ...

Feature overview


Capabilities

- Continuous time voltage & current access, via 2 analog pins
- Measure R, C, L, drive, etc. with <1% accuracy
- True differential access, and other options
- 1149.1-compliant


Mixed-signal tester per pin + core access

Benefits/value

 - Parametric structural test of IC & board
- Standard access: reusable analog tests
- *In situ* diagnosis/test: virtual guided probe
- Infrastructure for self-test



Architecture and Design of 1149.4

 

Outline


- Design of ABM, TBIC, TAP
- Details
 - Switches, core disconnect
 - Differential pins
 - Design vs. accuracy, speed
 - On-chip access
- Accessing HF signals
- Example ICs

ABM switch settings in EXTEST

data	control	AB1	AB2	←switch
D	C	B1	B2	
0	0	x	x	CD (tristate)
1	0	x	x	Drive “ground” out
data	1	x	x	Drive data out (1149.1)
x	x	1	x	Connect pin to AB1
x	x	x	1	Connect pin to AB2

x = don't care

Example ABM schematic

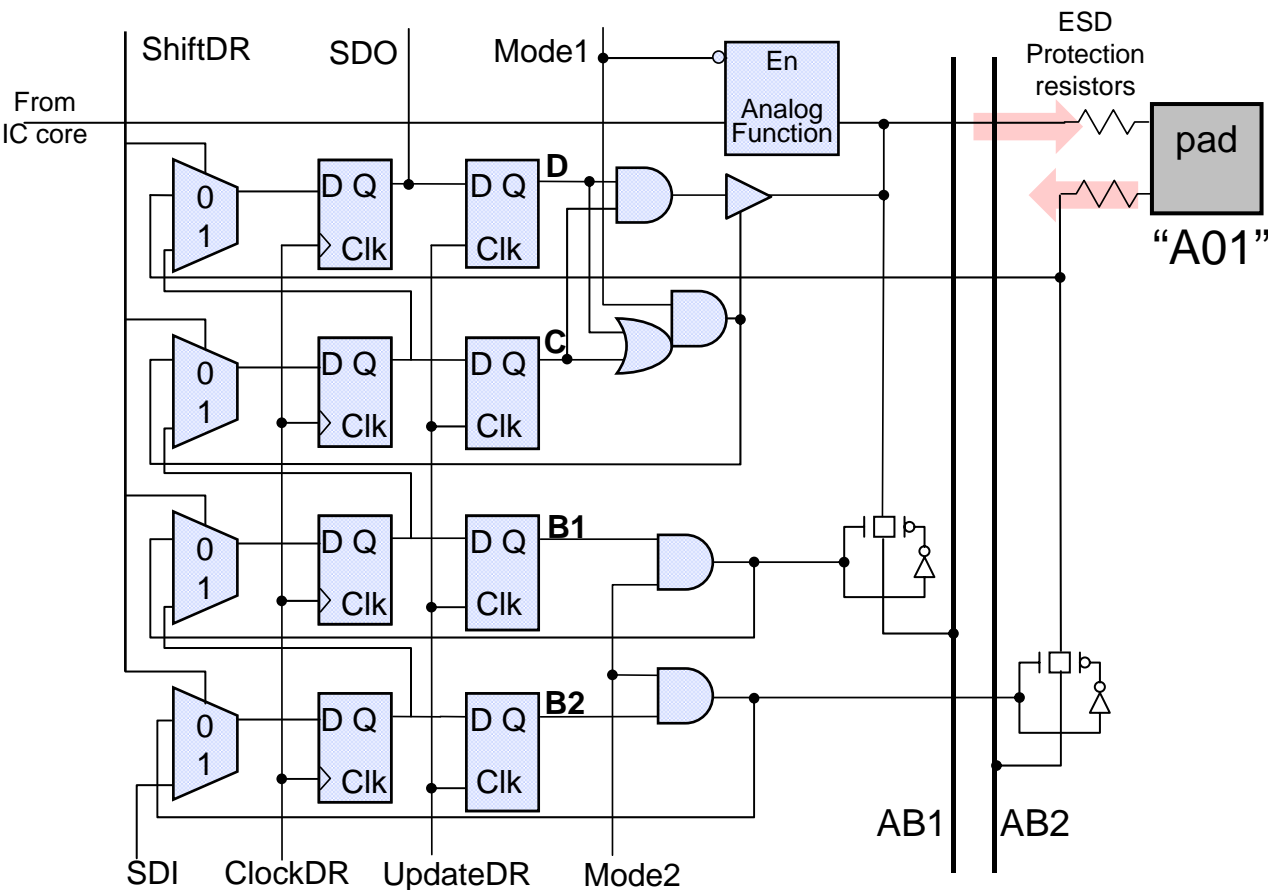

Where is the V_{TH} comparator?

What is value of V_{TH} ?

What is value of V_G ?

How would you modify this to handle a digital I/O pin?

Lines from my_bscan_cells.all

```
constant LV_B2: CELL_INFO:=
((INTERNAL, EXTEST, UPD),
(INTERNAL, SAMPLE, ZERO));
```

```
constant LV_B1: CELL_INFO:=
((INTERNAL, EXTEST, UPD),
(INTERNAL, SAMPLE, ZERO));
```

```
constant LV_D: CELL_INFO:=
((BIDIR_IN, EXTEST, PI),
(BIDIR_OUT, EXTEST, PO),
(BIDIR_IN, SAMPLE, PI),
(BIDIR_OUT, SAMPLE, PO),
```


```
constant LV_C:CELL_INFO:=
((CONTROL, EXTEST, UPD),
(CONTROL, SAMPLE, PI));
```

Lines from my_chip.bsd file


```
-- this end closest to TDO
--num cell port function safe [ccell disval rslt]
" 0 (LV_D, A01, bidir, 0, 1, 0, Z),"&
" 1 (LV_C, *, control, 0),"&
" 2 (LV_B1, *, internal, 0),"&
" 3 (LV_B2, *, internal, 0),"&
```

etc.

.1 and .4 TAP overview

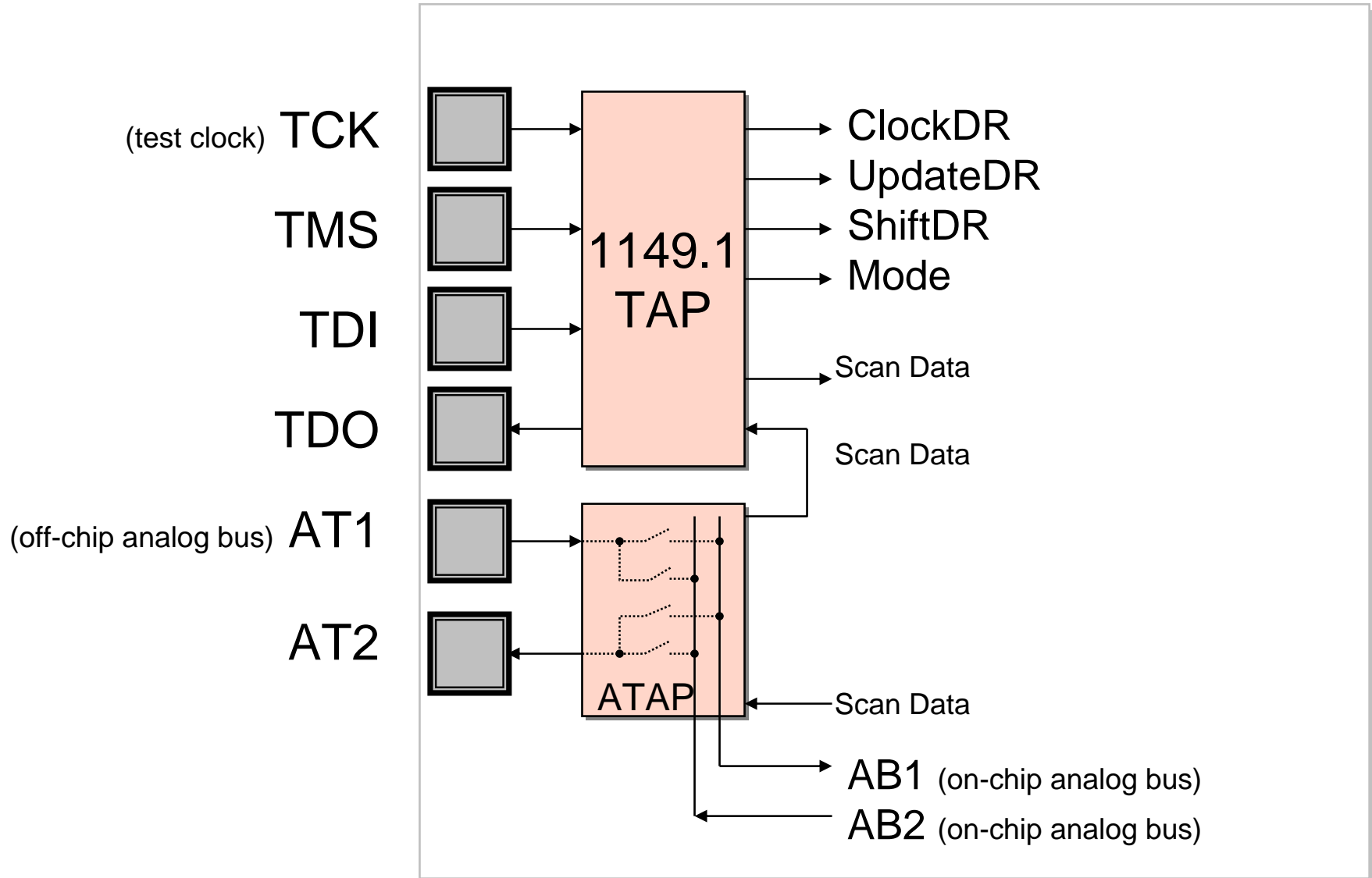

Example TBIC schematic

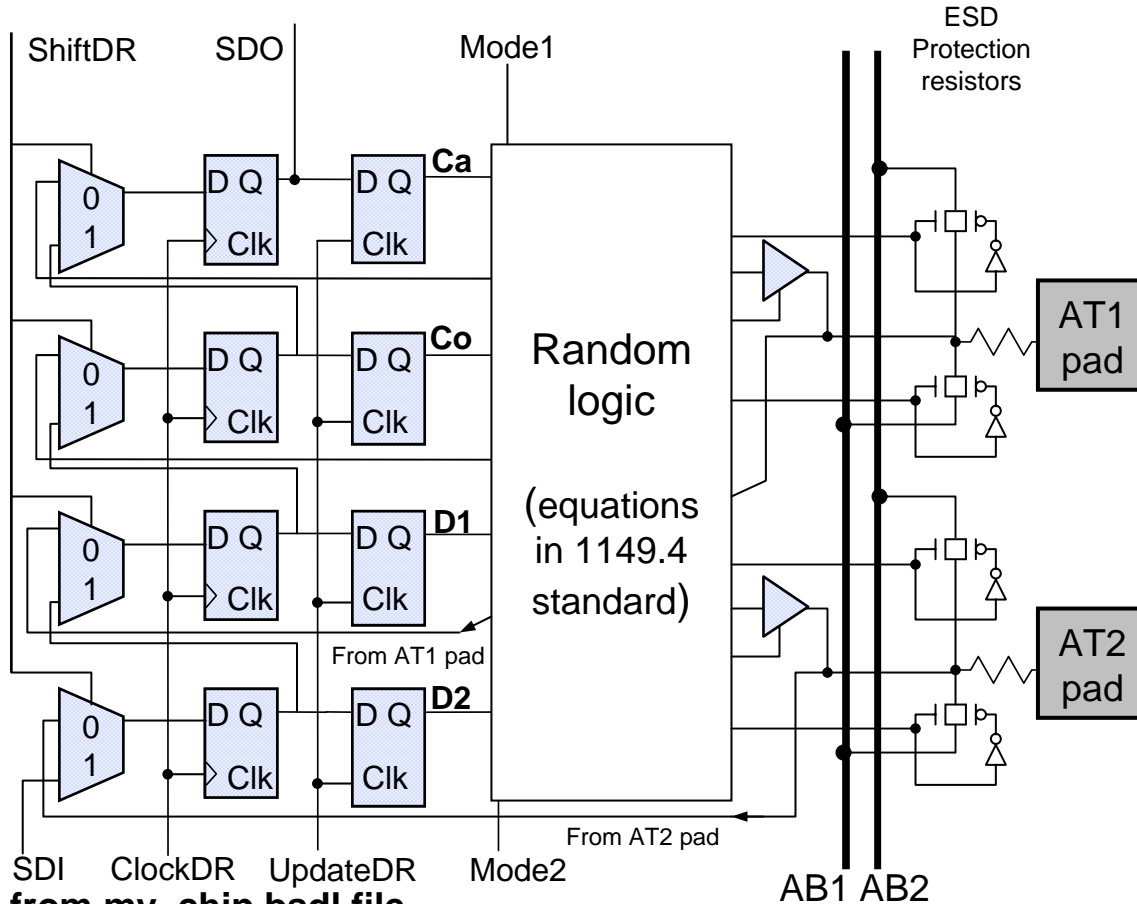

Lines from my_bscan_cells.all
 constant LV_CA: CELL_INFO :=
 ((INTERNAL, EXTEST, X),
 (INTERNAL, SAMPLE, X)),

constant LV_CO: CELL_INFO :=
 ((CONTROL, EXTEST, X),
 (CONTROL, SAMPLE, PI)),

constant LV_D: CELL_INFO:=
 ((BIDIR_IN, EXTEST, PI),
 (BIDIR_OUT, EXTEST, PO),
 (BIDIR_IN, SAMPLE, PI),
 (BIDIR_OUT, SAMPLE, PO)),


Lines from my_chip.bSDL file

-- this end closest to TDO

--num	cell	port	function	safe	[ccell	disval	rslt]
" 20	(LV_Ca,	*	internal,	0),"&			
" 21	(LV_Co,	*	control,	0),"&			
" 22	(LV_D,	AT1,	bidir,	0,	21,	0,	Z),"&
" 23	(LV_D,	AT2,	bidir,	0,	21,	0,	Z),"&

etc.

TAP state diagram (1149.1)

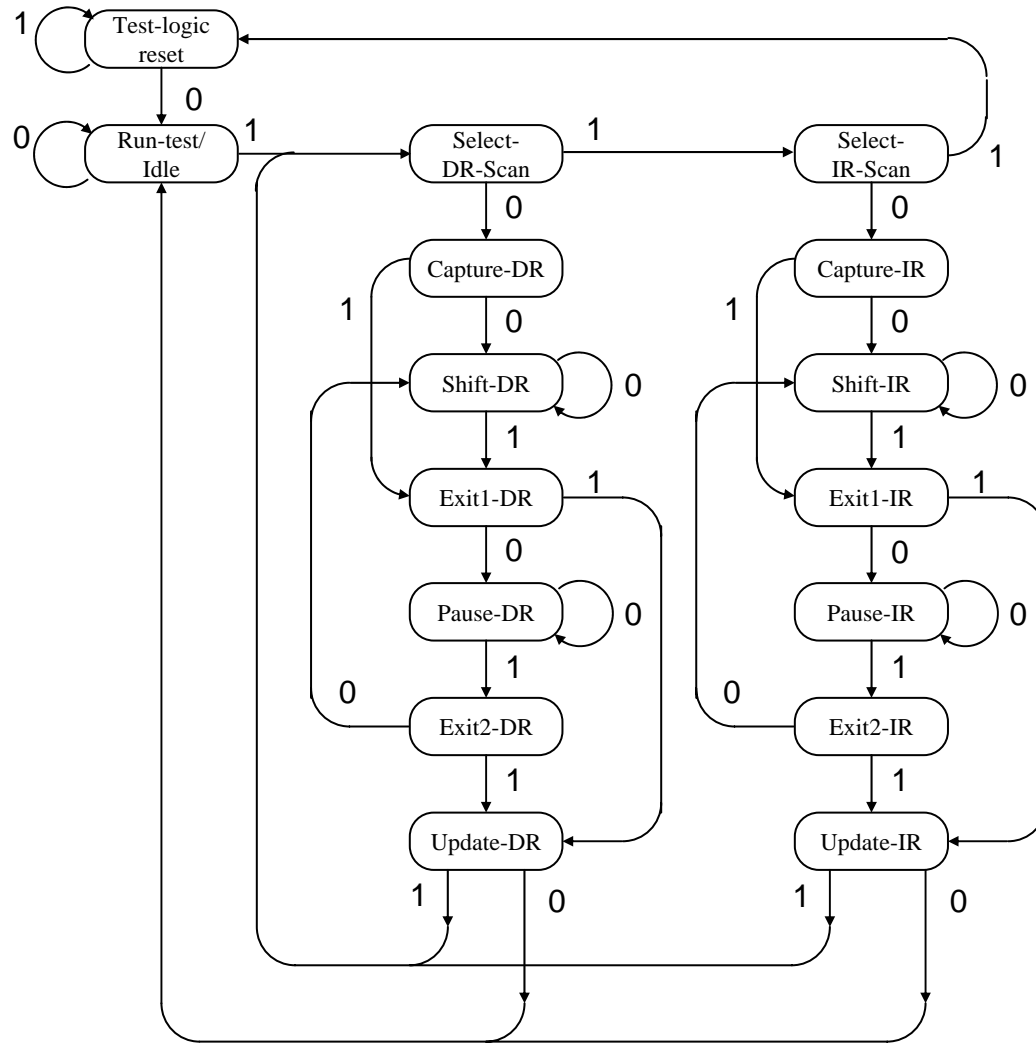

© IEEE

The state transitions are determined by the value of TMS on the rising edge of TCK.

RTL synthesis

- TAP controller typically needs one more bit in IR
 - Analog mode, or *PROBE* instruction
- ATAP and ABMs
 - All synthesizable logic, in IC core, except
 - Transmission gates
 - Connections to pad
 - Optional analog buffers
 - Optional analog comparators
 - Must ensure that analog bus is not “optimized” by synthesis

1149.4 Instructions





- *EXTEST*
 - Disable mission-mode influence of pins (“Core Disconnect”)
 - Drive any pin to VDD/VSS, sample its logic value, access via AT1/AT2
- *PROBE*
 - Mission-mode
 - Sample any pin’s logic value, access via AT1 and/or AT2
- *INTEST*
 - Analog pins: same as *PROBE*
 - Digital pins: same as 1149.1 (plus access via AT1/AT2)
- *CLAMP, HIGHZ, BYPASS* same as 1149.1

What is a 'switch' in 1149.4 ?

- Allows signals to propagate from one wire to another
- Can be disabled to isolate one signal from the other
- Does *not* need to have 'low' impedance (500Ω is OK)

    Examples

- CMOS transmission gate
 - allows bi-directional current flow
- Voltage buffer; $0 < \text{gain} < 1$
- Current buffer; $0.5 < \text{gain} < 2$




Achieving isolation: CD state

(Core Disconnect)

Ideal isolation

(disconnect, zero influence)

 
- pin completely isolated from on-chip circuitry



Practical isolation


(high Z, minimal influence)

 - outputs tri-stated
- inputs to transistor gates only, and function



Minimum isolation


(CD state, predictable influence)

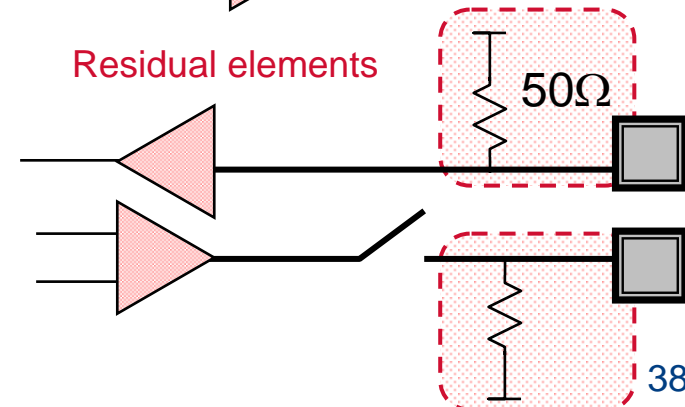

Residual Elements


- Circuitry permitted to connect to a pin in CD state:
 - can be modeled with linear passive elements (R, C, L) and *independent* DC voltage or current source
 - connects only to other analog or power pins, not digital or core
 - documented for IC user

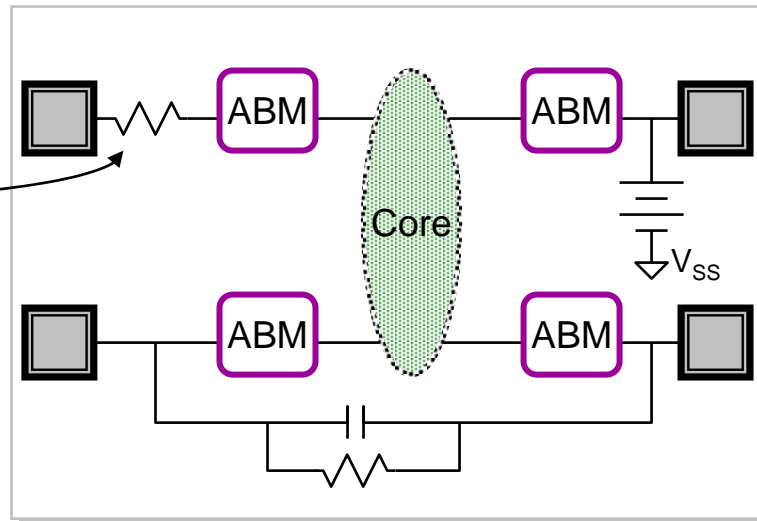Be especially careful to document any series resistance in the metalization, pad, bond wire, and lead frame



Differential function pins

 
- Each pin must have its own ABM
 - Inverting pins access AB1 and AB2, or optionally AB1N and AB2N
 - Non-inverting pins access AB1 and AB2
 - Non-inverting pin's ABM monitors comparison result
 - ABM +/- pair drives at least V_H/V_L , V_L/V_H , V_G/CD , CD/V_G , CD/CD



- Note: similar to 1149.6 + analog bus

Measuring impedance

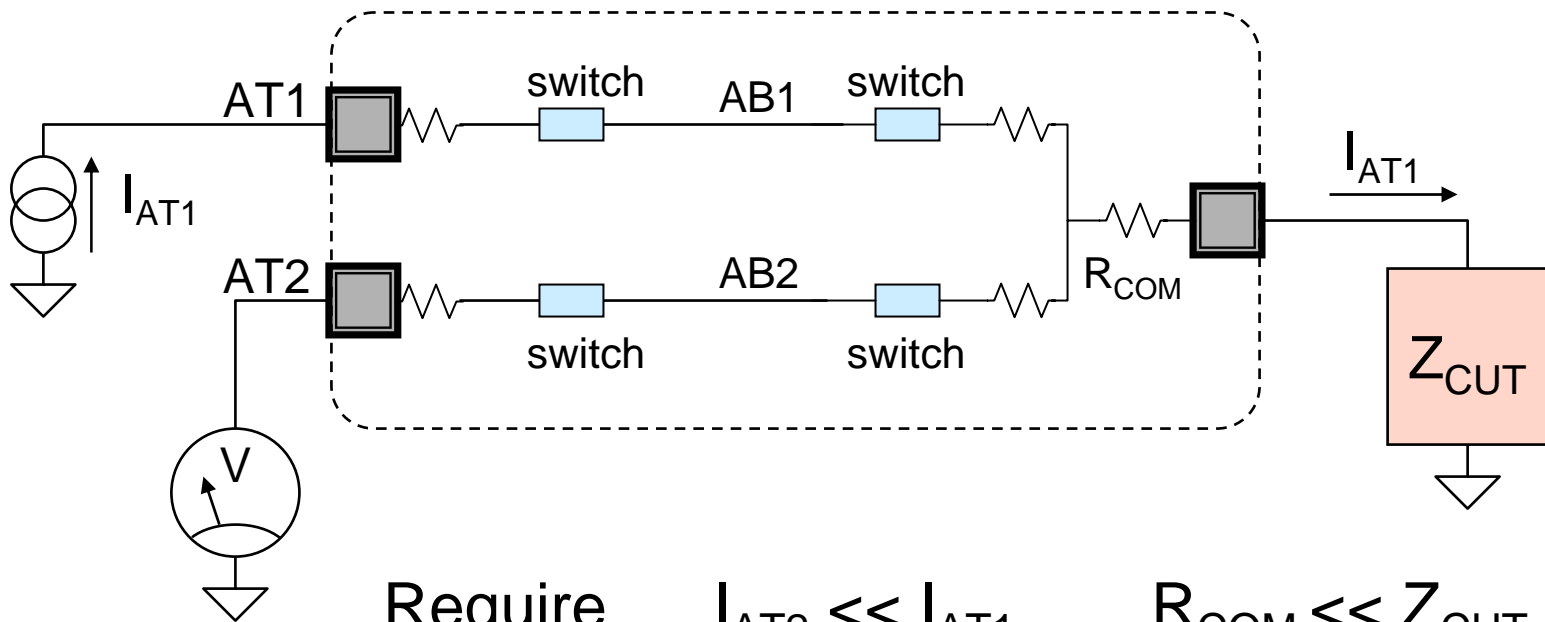- Kelvin probe (or four probe) principle
 - Apply known current via AT1/AB1 path ($<100 \mu\text{A}$)
 - Measure voltage via AT2/AB2 path



Require

$$I_{AT2} \ll I_{AT1}$$



($>10 \text{ M}\Omega$)

$$R_{COM} \ll Z_{CUT}$$

($<0.5 \Omega$)

Performing tests equivalent to 1149.1

 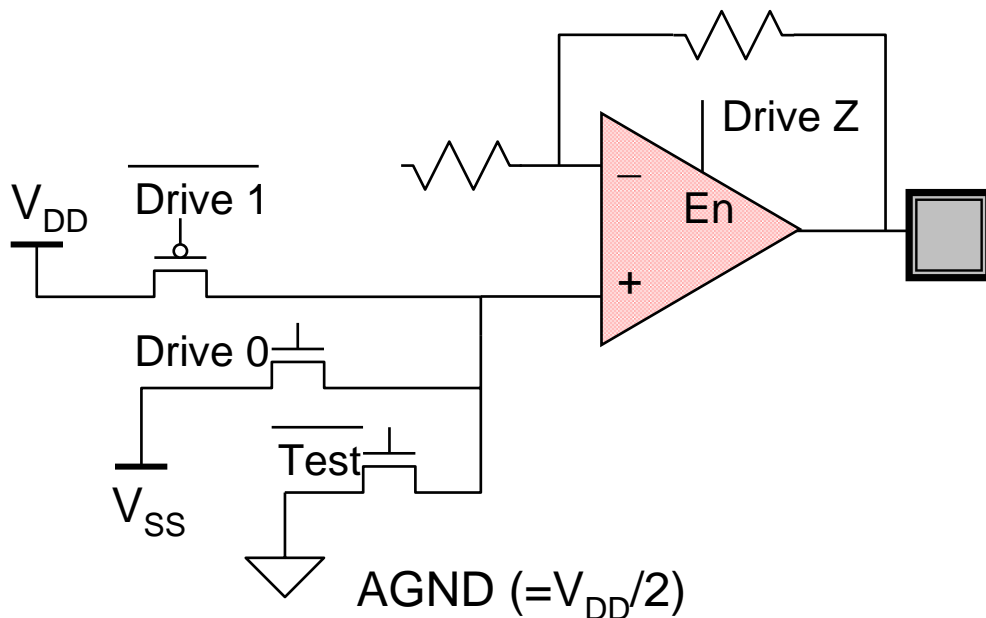
- Driving a logic 0 or logic 1
 - Force pin driver to drive its normal DC max. or min. voltage
 - Function driver best: high current, verifies driver connection to pin
 - Alternate (digital) driver may be used
 - *Objective*: largest practical voltage swing to allow fast, simple test



Performing tests equivalent to 1149.1


- Sensing a logic 0 or logic 1
 - Detect pin voltage relative to mid-rail threshold voltage, V_{TH}
 - V_{TH} is between 25% and 75% of $(V_{MAX}-V_{MIN})$
 - Value is captured as 0 or 1 in boundary scan register

Examples

 

Weak Nand (or Nor)

 - minimal size
- small current (100 μA during Test)
- 1 ns response time




Minimum size comparator

- size of 3 Nands
- minimal current (μA)
- 50 ns response time


ABM, TBIC implementation in ASICs

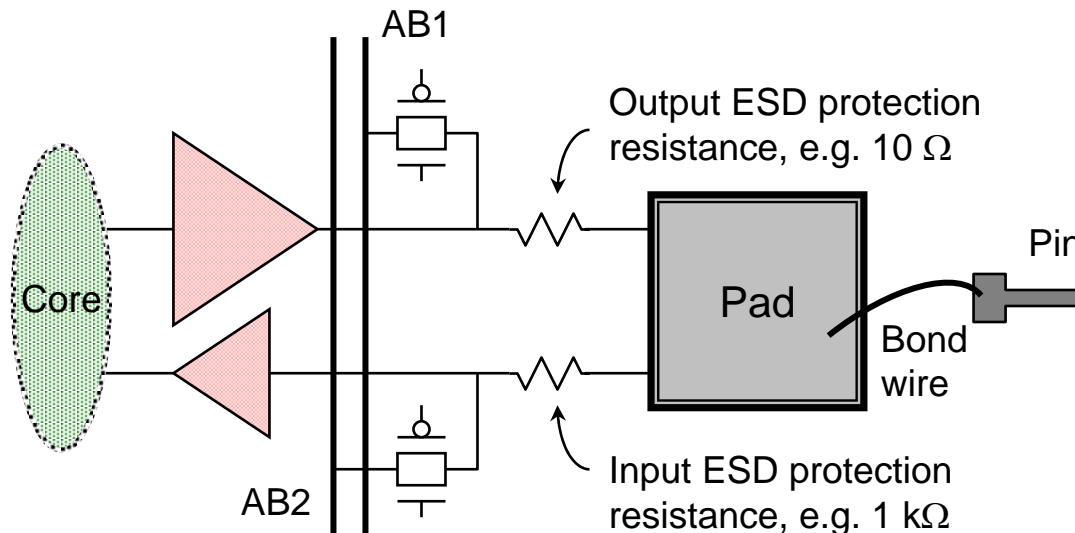- 1149.1 is implementable without help from ASIC supplier
 - All circuitry is digital, and placement not important
- Implementing 1149.4 will typically require pad cell changes
 - Two, unbuffered, ESD-protected accesses to pads
 - Transmission gates that can be connected to pads (via ESD prot.)




Accessing internal signals

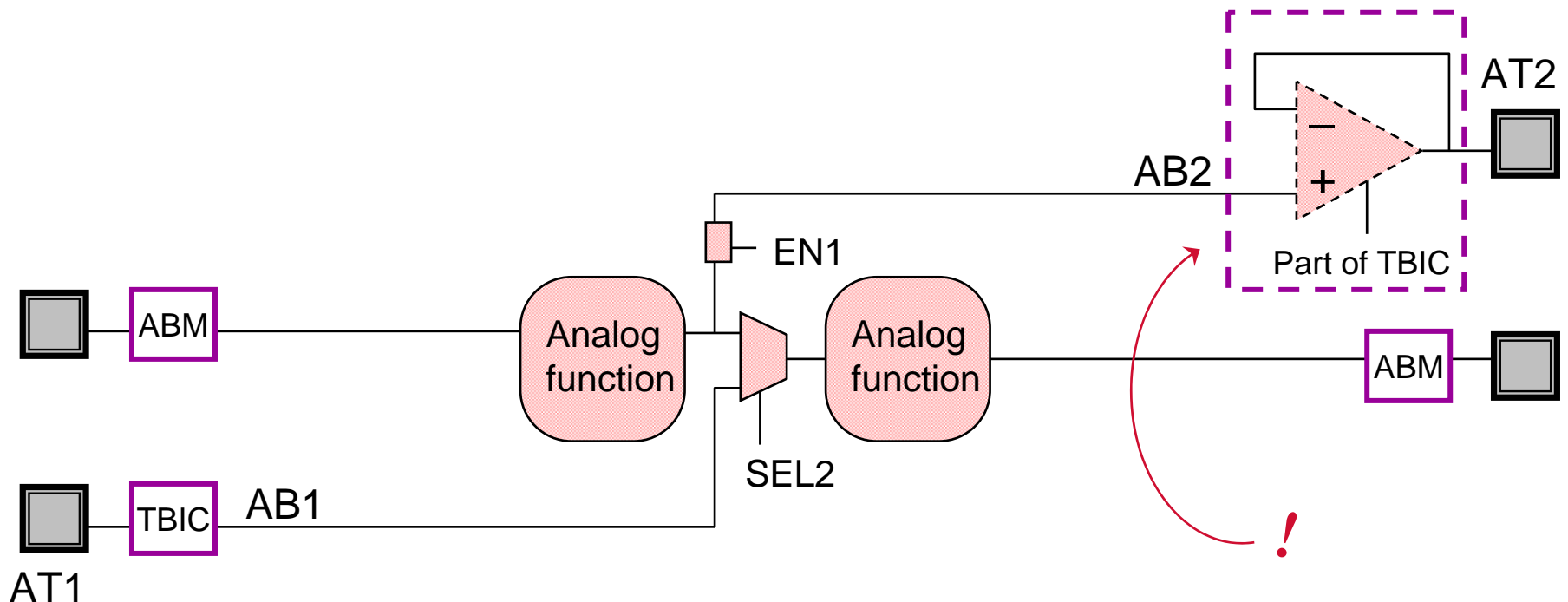- AB1 and AB2 can access core signals
- Access switches are enabled by dedicated scan bits
 - Enabled via private instruction, and not part of boundary register
 - Both AB2, AB1 would typically convey voltage, between V_{DD} / V_{SS}





Internal analog scan

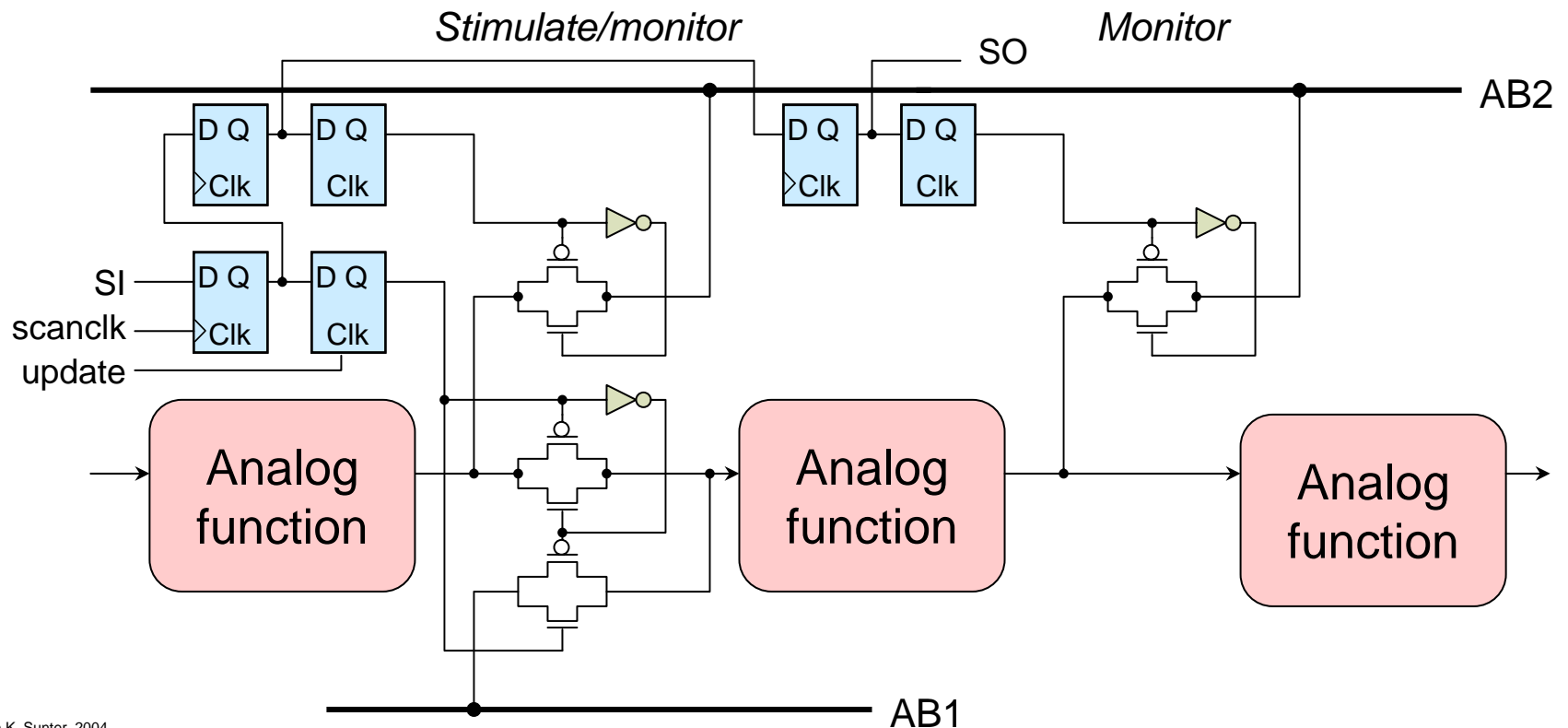- Internal analog buses is a common design practice
 - See reference article by Andlauer & Vu, of Tality
- Limitations of only providing/accessing one signal
- Use update latches to avoid creating transients during scan




Multiple analog buses

 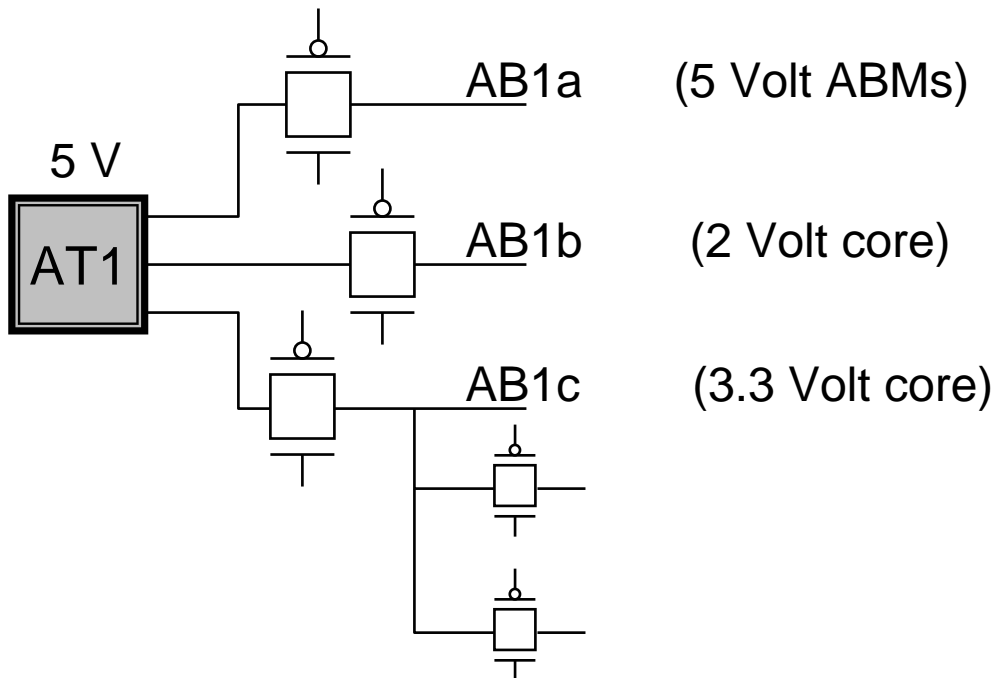- AB1 and AB2 may be partitioned into many buses
 - Allows multiple voltages, frequency ranges, etc.
 - Reduces bus capacitance 'seen' by accessed node
 - ~30 nodes per bus is practical upper limit for CMOS $<0.25\mu\text{m}$
 - may need hierarchical analog buses (more switches in series)



Testing HF analog paths

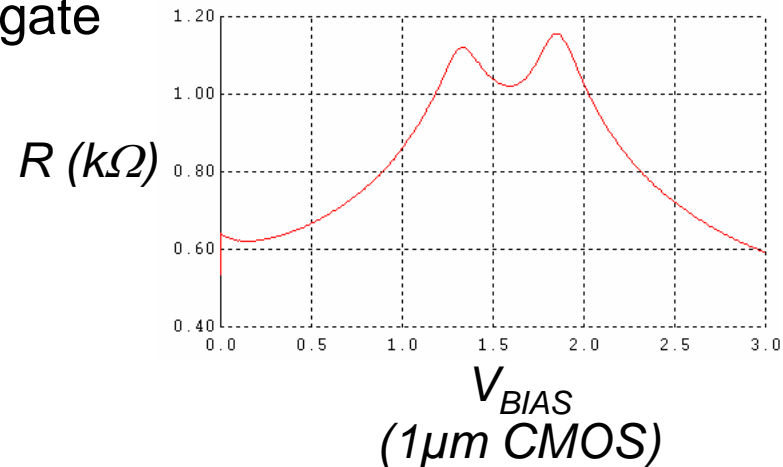- Monitor average voltage
 - Switch resistance and bus capacitance are LPF (but note that transmission gate is non-linear R)






- Under-sample
 - Example: under-sample 10 MHz signal to obtain 10 kHz signal on bus
 - See next 9 slides

Early capture

(K. Lofstrom, ITC'96)

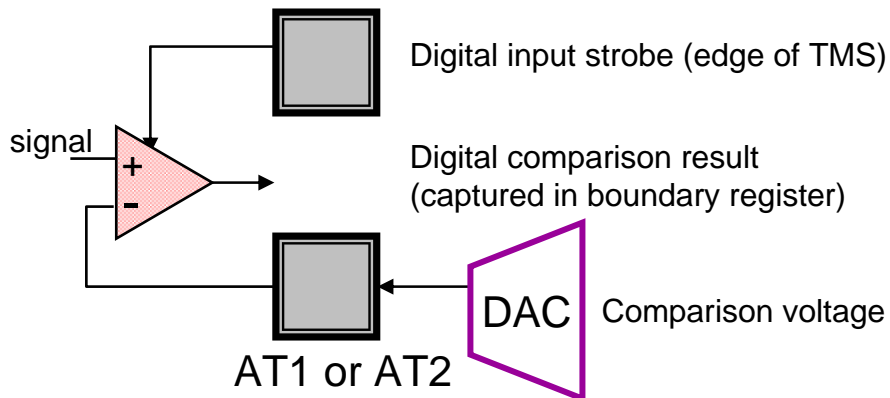 
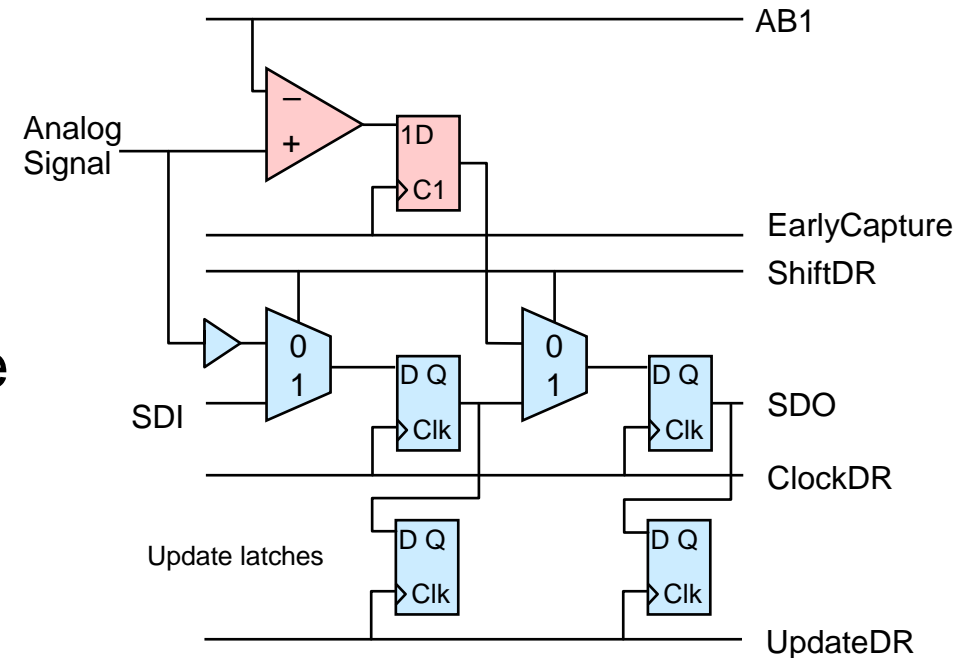
- Analog bus provides DC reference for comparator
- Modified 1149.1 TMS signal used for strobe edge
- Perform binary search to determine signal voltage



HF under-sampling

- An under-sampling technique (R.Mason, D&T Oct'99)
 - Transmission gate clocked by narrow digital pulse
 - On-chip storage capacitance and buffer
 - (Extension to this in ITC'03 paper 9.4)

  
Sampling clock **5 ns pulses @ 9.99 MHz**



HF under-sampling via 1149.4 IC

Improvements

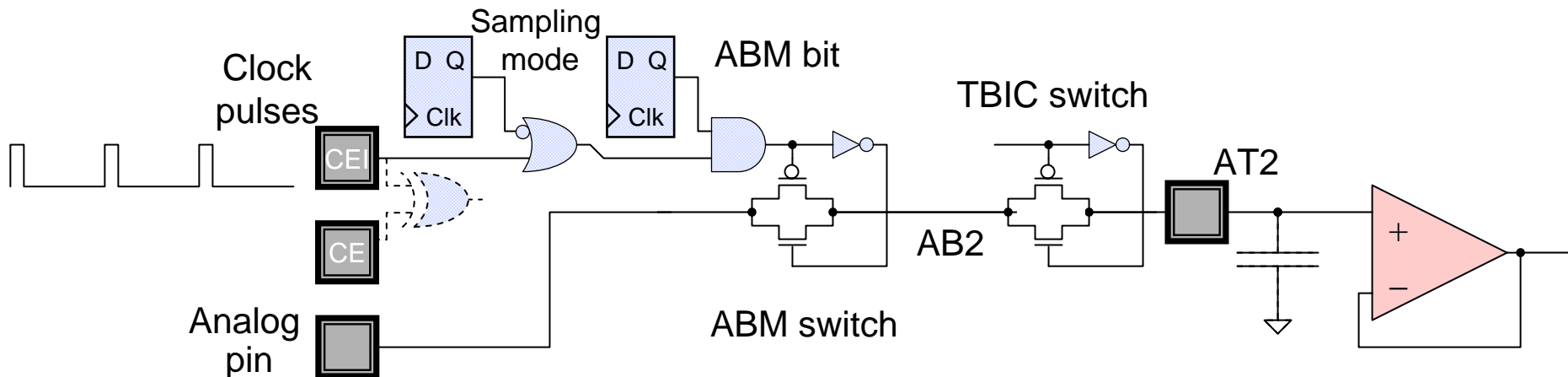- Re-use ABM transmission gate
- Exploit off-chip bus capacitance (as LPF)
- Keep bus frequency <10 kHz



$$f_{BUS} = f_{CUT} - n f_{CLK}$$

Limits to bandwidth

Example: $f_{\text{SAMPLE}} = 10 \text{ MHz}$

$\tau = 5 \text{ ns}$

$C_{\text{BUS}} = 100 \text{ pF}$

$R_{\text{SW}} = 1 \text{ k}\Omega$


1. Pulse duty cycle <100% increases apparent R_{SW} that drives bus capacitance

$$f_{\text{BUS-3dB}} = \tau f_{\text{SAMPLE}} / 2\pi R_{\text{SW}} C_{\text{BUS}}$$

$$f_{\text{BUS-3dB}} \approx 80 \text{ kHz}$$

 2. Non-zero pulse width causes $(\sin x)/x$ roll-off

Amplitude $\propto \sin(n \pi \tau / T_S) / (n \pi \tau / T_S)$



$$f_{\text{SIGNAL-3dB}} = 0.44 / \tau$$

$$f_{\text{SIGNAL-3dB}} \approx 88 \text{ MHz}$$

(Sunter, ITC'01)


Analog bus buffers

- How to provide a buffer between AB2 and AT2 ?
 - Rule: high input impedance (10 M Ω)
 - Rule: handle signals between $V_{SS}-100\text{mV}$ and $V_{DD}+100\text{mV}$
 - Rule: <1% non-linearity


Full-swing op-amp
output range: $V_{DD}-V_{SS}$
→ insufficient output range

Inverting amplifier, gain <1
input/output range: OK
→ typ. input impedance <1M Ω

 
Standard CMOS digital 3-state inv
input/output range: OK
input impedance: OK
→ non-linear, but can be calibrated



 OK for core signals, but not compliant for pin signals



\$ area


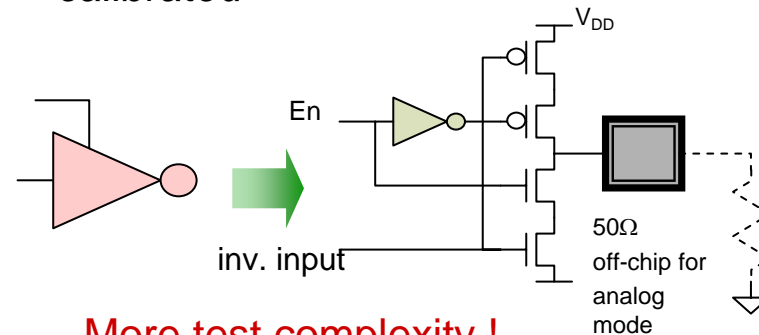


More test complexity !

Conclusion: simple CMOS transmission gates may be best

Monitoring HF signals directly

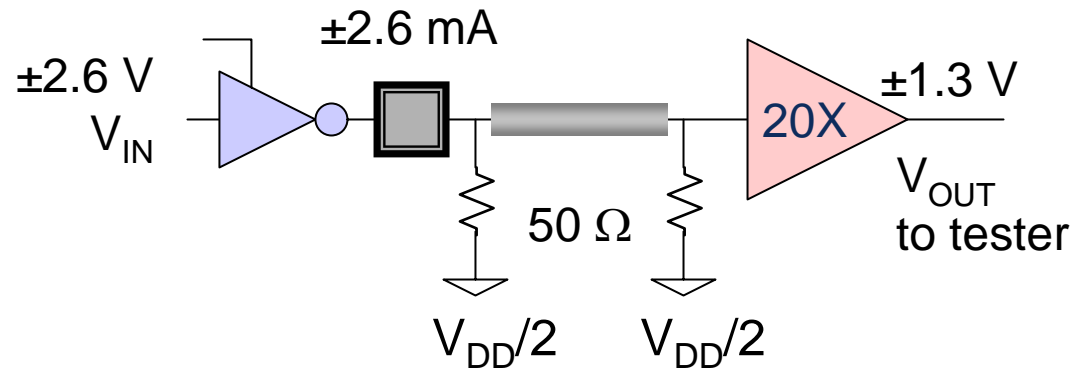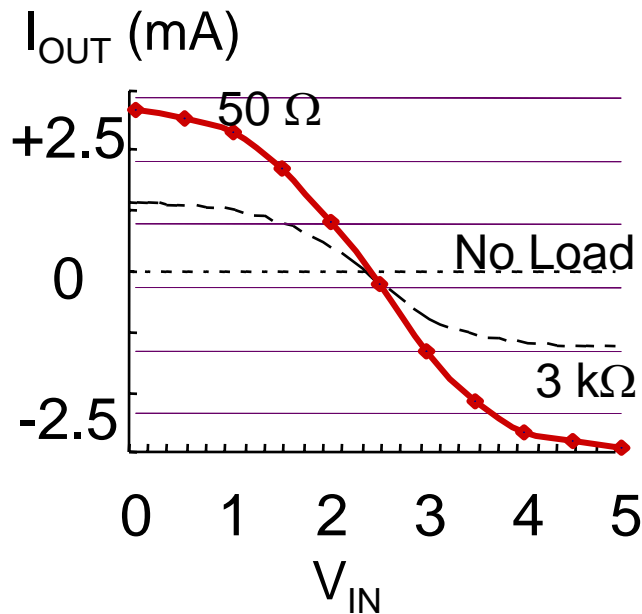- Analog buffers monitor with less impact on CUT





- Bandwidth >30 MHz
- Calibrate non-linearity via TBIC, and use for analog signals
- Or use unloaded for digital output
- Buffers enabled by bits (one for AB1, one for AB2) in second data register


Sunter, VTS'96

Under-sampling analog buffer

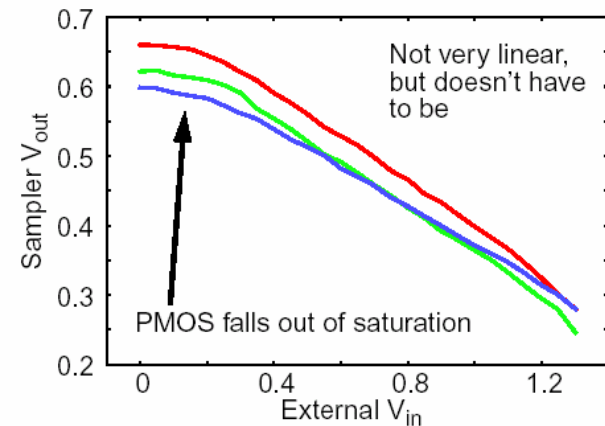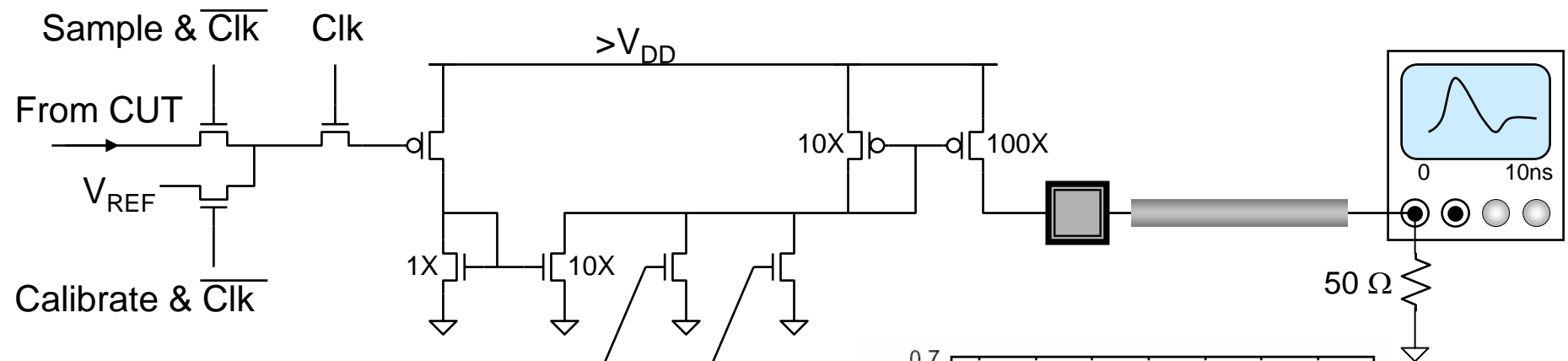
- Measured transfer function for strobed, 1 transistor monitor (near minimum size) with current mirrors for gain
- >1 GHz bandwidth



DFT for high-speed A/D and D/A ?

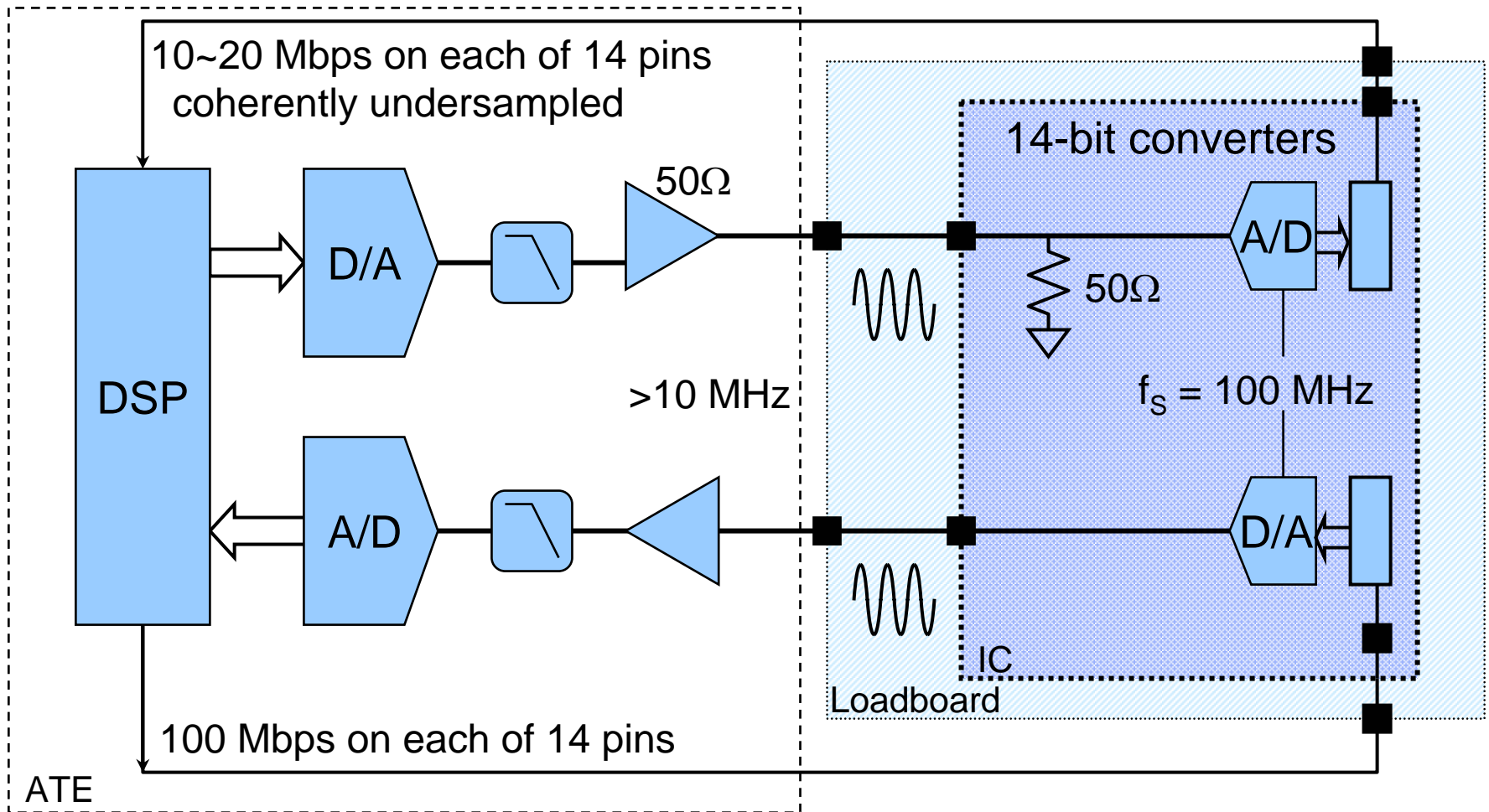

Synchronous under-sampling

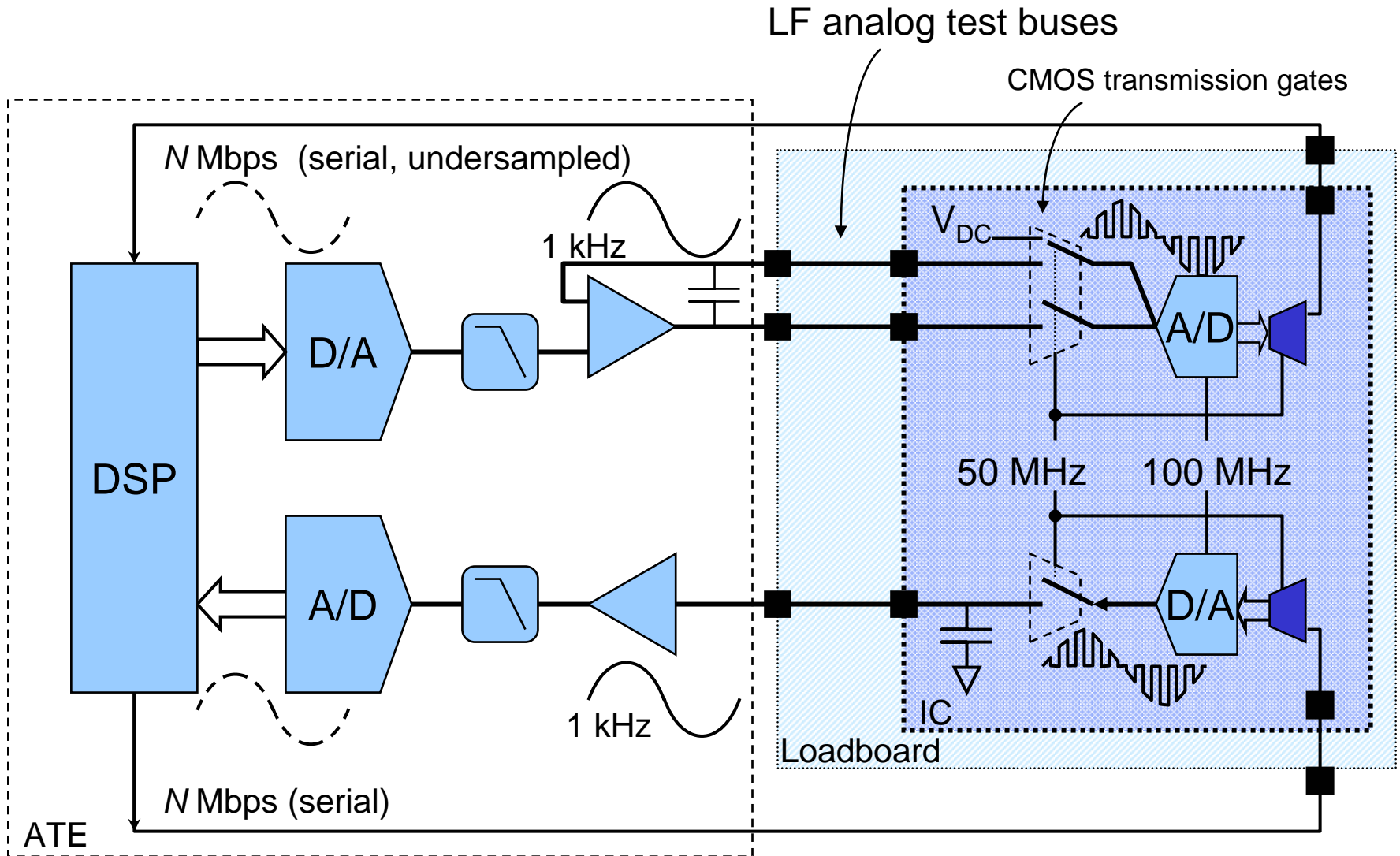


Shown single-ended. Typically, differential.

Sunter, ITC'03

1149.4 ICs and lessons learned

- K.Lofstrom/IMP, 1996
 - Basic scheme works
 - Early Capture technique for HF signals
 - Switches in series with outputs impractical
 - T-switches important
- HP/Matsushita, 1998
 - ABM gate count is small
 - Layout of AB switch connections important
 - Switch non-linearity and leakage significant
- LogicVision/NationalSemi., 2000
 - TBIC buffer design is non-trivial
 - ABMs on digital pins can meet 1149.1 rules
 - $R_{COM} < 1\Omega$ essential for accuracy
 - IC also known as D4access, and SCANSTA400

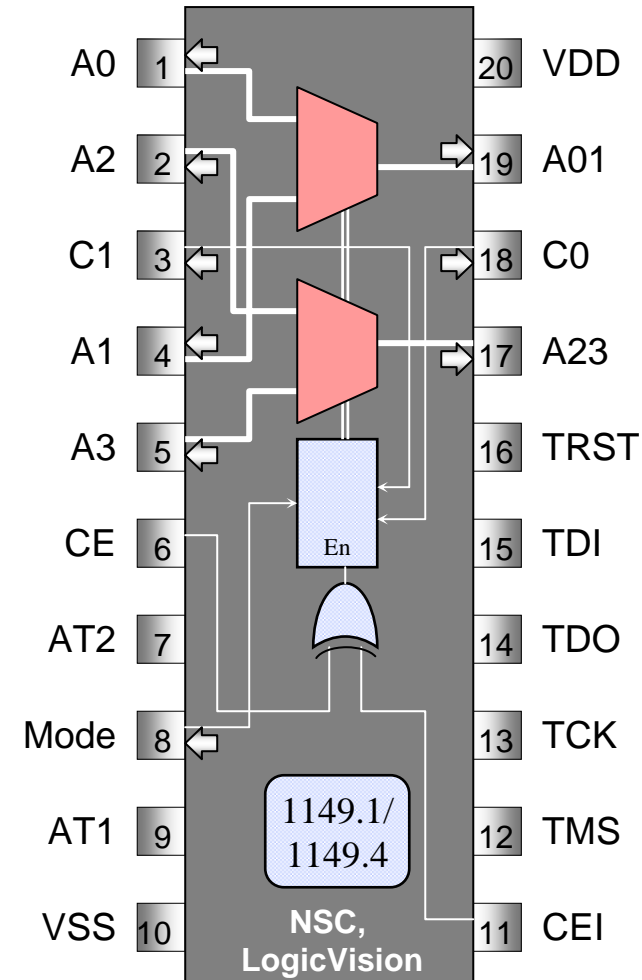


Pinout, showing internal circuit blocks and ABM-probed pins, when configured as a differential mux/demux.

Summary

- Basic architecture is robust, simple
 - Suitable for logic synthesis
 - A few details are essential for accuracy
 - Almost no rules for internal access – innovation rules!
 - Analog bus access is a common design practice
- A variety of techniques for HF access
 - Under-sampling
 - V/I \rightarrow I/V buffers, limited-swing voltage buses
- Experimental results published for 3 chips

System Test Methods


Stephen Sunter

 

Outline

- Automating Test
 - BSDL
 - Analog BSDL
- “EXTESTing”
 - Pins: digital, analog, power
 - Board-level paths: digital, differential
 - Using commercially available software
 - Tester within a laptop PC
- References
- Conclusions

Example 1149.4 IC, with 11 ABMs

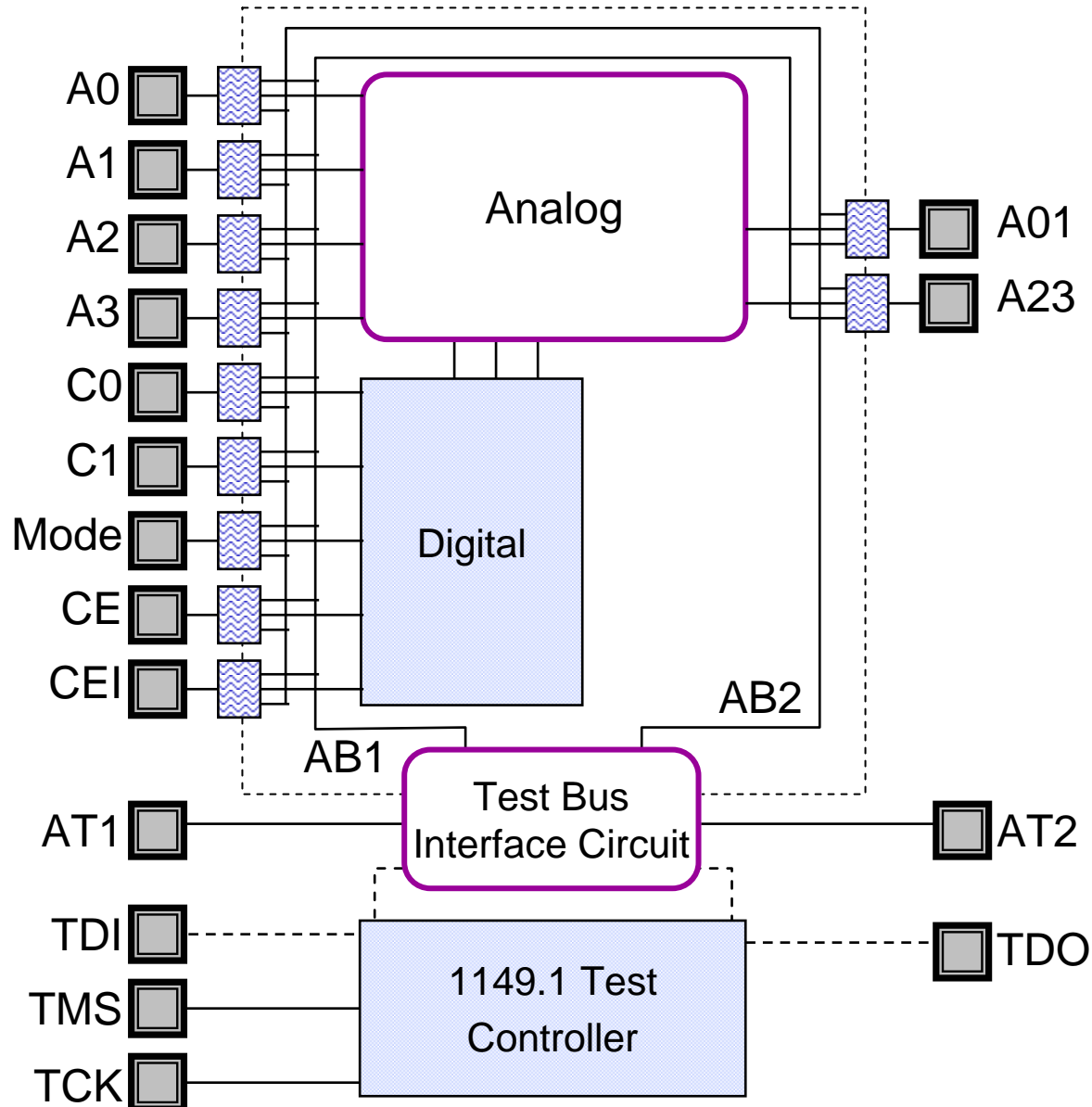

ABM/TBIC description file

```
package MY_BSCAN_CELLS is
  use STD_1149_1_1994.all;           -- comments
  constant LV_B2: CELL_INFO;        -- ABM B2 control bit
  constant LV_B1: CELL_INFO;        -- ABM B1 control bit
  constant LV_D: CELL_INFO;         -- ABM D data bit, for analog pins, or for TBIC D1,D2
  constant LV_C: CELL_INFO;        -- ABM C control bit, for analog pins
  constant LV_CA: CELL_INFO;       -- TBIC CA control bit
  constant LV_CO: CELL_INFO;       -- TBIC CO control bit
end MY_BSCAN_CELLS;
```

```
package body MY_BSCAN_CELLS is
  use STD_1149_1_1994.all;
  constant LV_B2: CELL_INFO :=
    ((INTERNAL, EXTEST, UPD), (INTERNAL, SAMPLE, ZERO));
  constant LV_B1: CELL_INFO :=
    ((INTERNAL, EXTEST, UPD), (INTERNAL, SAMPLE, ZERO));
  constant LV_D: CELL_INFO :=
    ((BIDIR_IN, EXTEST, PI), (BIDIR_OUT, EXTEST, PO),
     (BIDIR_IN, SAMPLE, PI), (BIDIR_OUT, SAMPLE, PO));
  constant LV_C: CELL_INFO :=
    ((CONTROL, EXTEST, UPD), (CONTROL, SAMPLE, PI));
  constant LV_CA: CELL_INFO :=
    ((INTERNAL, EXTEST, X), (INTERNAL, SAMPLE, ONE));
  constant LV_CO: CELL_INFO :=
    ((CONTROL, EXTEST, X), (CONTROL, SAMPLE, PI));
end MY_BSCAN_CELLS;
```

Example BSDL file (top half)

```
-- comment
entity my_chip is
  generic (PHYSICAL_PIN_MAP : string := "DEFAULT_PACKAGE_NAME");
  port (
    CE           : inout  bit;
    ...
    AT1          : inout  bit;
    AT2          : inout  bit;
    TCK          : in     bit;
    ...
    TDO          : out    bit;
    VDD          : linkage bit;
    VSS          : linkage bit);
  use STD_1149_1_1994.all;
  use MY_BSCAN_CELLS.all;
  attribute COMPONENT_CONFORMANCE of top: entity is "STD_1149_1_1993";
  attribute PIN_MAP of top: entity is PHYSICAL_PIN_MAP;
  constant DEFAULT_PACKAGE_NAME: PIN_MAP_STRING :=
    "A0      : 1      , " &
    "A2      : 2      , " &
    ...
    "VDD     : 20     " ;
  attribute TAP_SCAN_RESET of TRST      : signal is true;
  ...
  attribute TAP_SCAN_CLOCK of TCK       : signal is (2.0e+07, BOTH);
  attribute INSTRUCTION_LENGTH of top: entity is 20;
-- continued on next slide
```

All 1149.4 pins are "inout"

Example BSDL file (bottom half)

```

attribute INSTRUCTION_OPCODE of top: entity is
  "BYPASS   (11111111111111111111)," &
  "EXTEST   (00000000000000000000)," &
  "         (111111111111111101000)," &
  "SAMPLE   (011111111111111111000)," &
  "PROBE    (111111111111111111000)," & -- 1149.4 instruction
  "HIGHZ    (0111111111111111001111)," &
  "CLAMP    (111111111111111101111) " ;
--

```

Mode2 (points to 01000)
Mode1-inv (points to 01111)
Selects boundary scan register (points to 01000)
Selects bypass register (points to 01111)

```

attribute INSTRUCTION_CAPTURE of top: entity is "xxxxxxxxxxxxxxxxxxxx01";
attribute REGISTER_ACCESS of top: entity is "BOUNDARY (PROBE)";
attribute BOUNDARY_LENGTH of top: entity is 48;

```

```

attribute BOUNDARY_REGISTER of top: entity is
-- This end is closest to TDO
-- num  cell      port      function      safe      Control      Disable      Disable
--      [ccell  disval  rslt]
"  0  (LV_B1      , *      , internal    , 0      )
"  1  (LV_B2      , *      , internal    , 0      )
"  2  (LV_C       , *      , control     , 0      )
"  3  (LV_D       , A3     , bidir       , 0      , 2      , 0      , Z      ),"&
...
" 20  (LV_CA      , *      , internal    , 0      )
" 21  (LV_CO      , *      , control     , 0      )
" 22  (LV_D       , AT1    , bidir       , 0      , 21     , 0      , Z      ),"&
" 23  (LV_D       , AT2    , bidir       , 0      , 21     , 0      , Z      ),"&
...
" 47  (LV_D       , A0     , bidir       , 0      , 46     , 0      , Z      )";
end my_chip;

```

Safe value
Control cell
Disable value
Disable result

Red arrows point from the *Control cell* column to the *control* function entries in rows 2 and 21.

EXTEST switch settings

ABM

<u>D</u>	<u>C</u>	(AB1) <u>B1</u>	(AB2) <u>B2</u>	(analog access switches)
0	0	0/1	0/1	CD (tristate)
1	0	0/1	0/1	Drive "ground" out
data	1	0/1	0/1	Drive data out (1149.1)


TBIC

<u>Ca</u>	<u>Co</u>	(AT1) <u>D1</u>	(AT2) <u>D2</u>	
0	0	0/1	0/1	Connect AT1→AB1 or AB2→AT2
0	1	data	data	Drive data out (1149.1)
1	0	1	0	Calibrate: AT1→AB1→AT2
1	0	0	1	Calibrate: AT1→AB2→AT2


[all other settings are undefined]

EXTEST switch connections

ABM

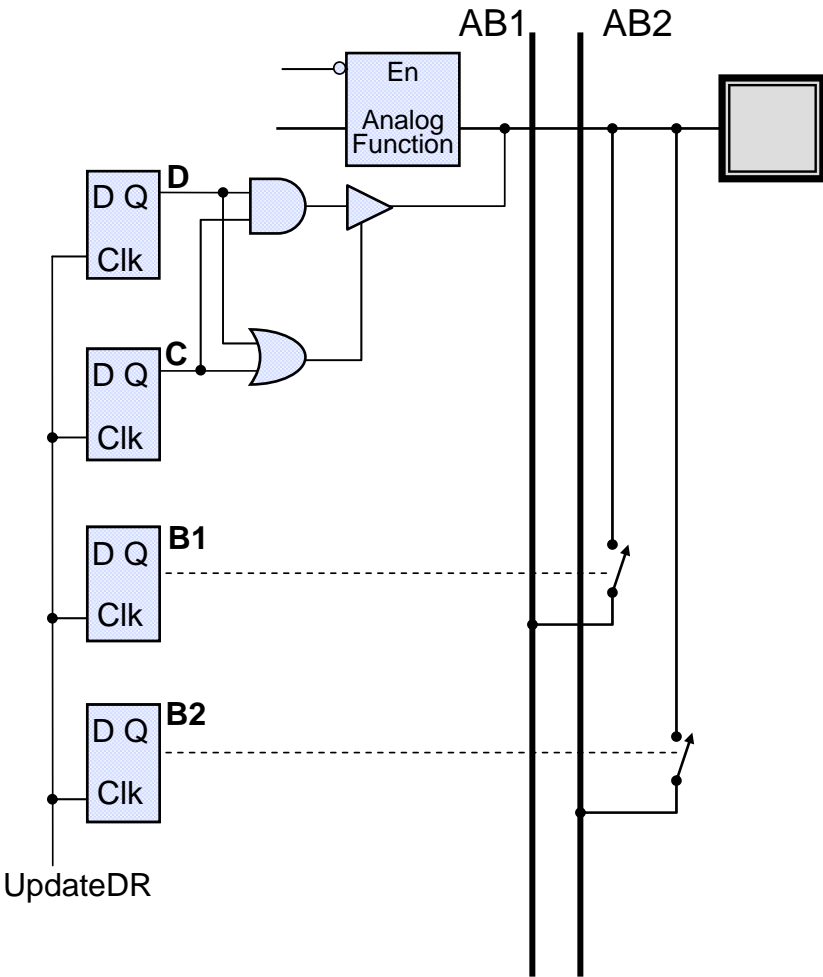

TBIC

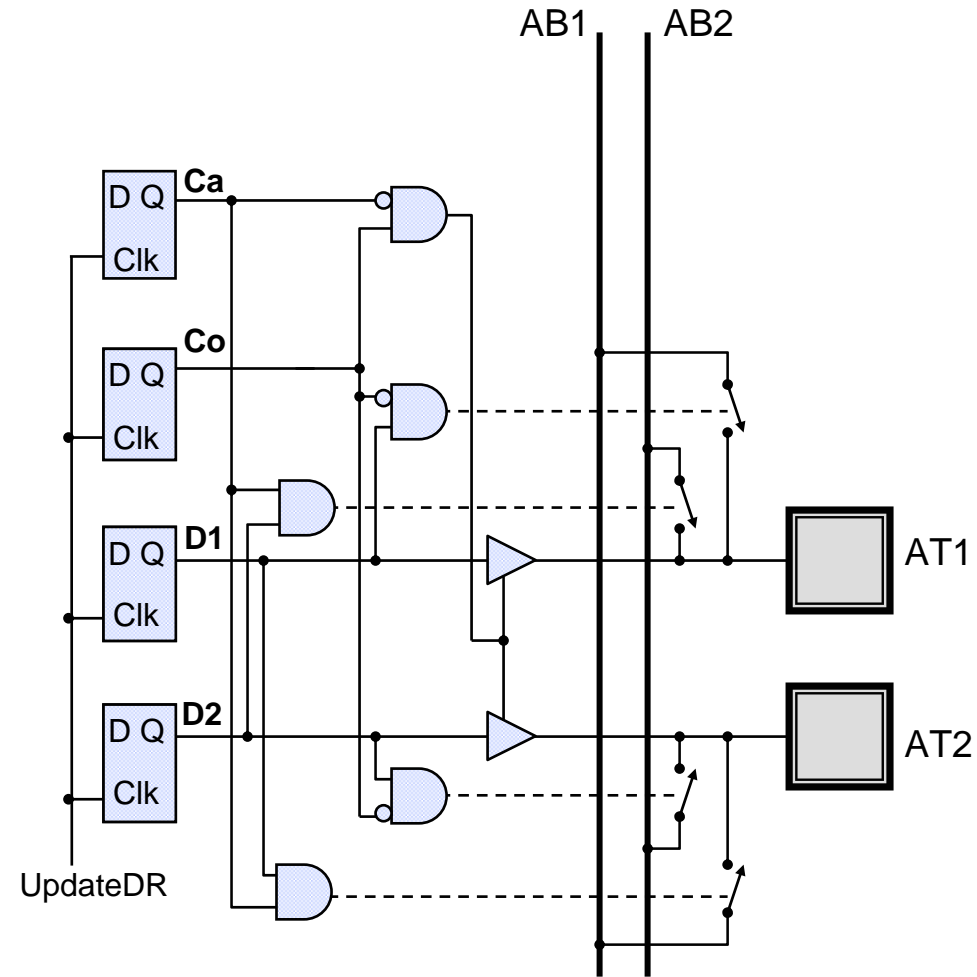


For simplicity, Mode1 and Mode2 connections are not shown.

Summary of Instructions

Instruction	Requirement	TDI – TDO path	Mode of function pins
<i>BYPASS</i>	Mandatory	Direct (bypass)	Function
<i>SAMPLE/ PRELOAD</i>	Mandatory	Bscan register	Function
<i>EXTEST</i>	Mandatory	Bscan register	Test
<i>PROBE</i>	Mandatory	Bscan register	Function
<i>INTEST</i>	Optional	Bscan register	Test – digital pins Function – analog pins, clock pins
<i>CLAMP</i>	Optional	Direct (bypass)	Test
<i>HIGHZ</i>	Optional	Direct (bypass)	High-Z – digital pins CD-state – analog pins
<i>RUNBIST</i>	Optional	Bscan register	Test – output pins Function – input pins
<i>IDCODE</i>	Optional	Ident. register	Function
<i>USERCODE</i>	Optional	Ident. register	Function


Example circuit board

TAP, ATAP signals not shown

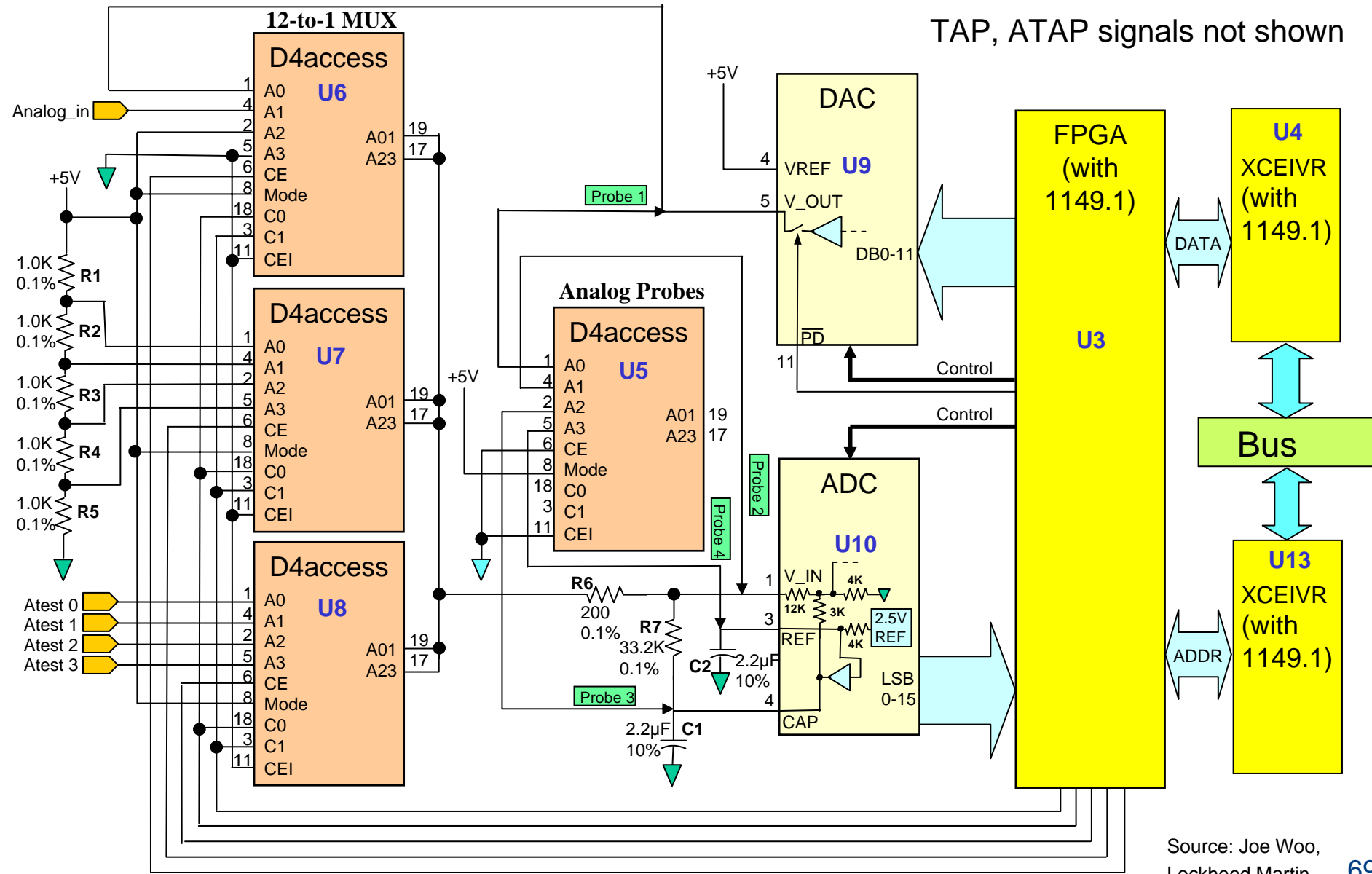

Measuring DC impedance at A3 pin

 - Load EXTEST instruction (refer to BSDL, next slide)




- Load boundary scan register

- Enable TBIC switches: AT1→AB1, AB2→AT2
- Enable A3 ABM switches: AB1→pin, pin→AB2
- Disable all other switches



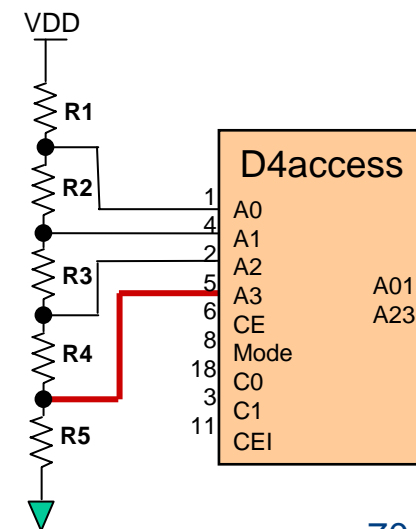- Apply 100 μ A to A3, via AT1
- Measure V_{A3} , via AT2




Example BSDL file (again)

```
attribute INSTRUCTION_OPCODE of top: entity is
  "BYPASS    (111111111111111111111111)," &
  "EXTEST    (0000000000000000000000)," &
             " 111111111111111101000)," &
  "SAMPLE    (0111111111111111111111000)," &
  "PROBE     (1111111111111111111111000)," & -- 1149.4 instruction
  "HIGHZ     (01111111111111111111001111)," &
  "CLAMP     (1111111111111111111101111) " ;
--          ^Mode2          ^Mode1-inv
attribute INSTRUCTION_CAPTURE of top: entity is "xxxxxxxxxxxxxxxxxxxx01";
attribute REGISTER_ACCESS of top: entity is "BOUNDARY (PROBE)" ;
attribute BOUNDARY_LENGTH of top: entity is 48;
attribute BOUNDARY_REGISTER of top: entity is
-- This end is closest to TDO
-- num  cell          port    function          safe    [ccell disval  rslt]
"   0  (LV_B1        , *      , internal        , 0    )                    ,"&
"   1  (LV_B2        , *      , internal        , 0    )                    ,"&
"   2  (LV_C         , *      , control         , 0    )                    ,"&
"   3  (LV_D         , A3     , bidir          , 0    ,    2    , 0    , Z    ),"&
...
"  20  (LV_CA        , *      , internal        , 0    )                    ,"&
"  21  (LV_CO        , *      , control         , 0    )                    ,"&
"  22  (LV_D         , AT1    , bidir          , 0    ,   21    , 0    , Z    ),"&
"  23  (LV_D         , AT2    , bidir          , 0    ,   21    , 0    , Z    ),"&
...
"  47  (LV_D         , A0     , bidir          , 0    ,   46    , 0    , Z    )";
end my_chip;
```

Testing digital pins

- Output drive
 - Via boundary scan, drive pin to logic 0 (or 1)
 - Apply $\geq 100 \mu\text{A}$ via AT1; measure V_{PIN} via AT2
- Pull-up impedance, or pin+wire capacitance
 - Via boundary scan, drive pin to CD (don't use *HIGHZ* instruction)
 - Apply $10 \mu\text{A}$ (AC for capacitance) via AT1; measure V_{PIN} via AT2

Why?


Testing power pins


■ Power rail voltage

- Via boundary scan, drive unloaded pin to logic 0 (V_{SS}) or 1 (V_{DD}) or monitor a pin connected to another V_{DD} access (see U6-A2 pin)
- Measure V_{PIN} via AT2
(transmission gates can monitor voltages 100 mV beyond rails)
- millivolt changes in power rail voltage may indicate faults

■ How to detect rail glitches with excess amplitude?

- Power rail quality test – next 3 slides




Power rail impedance

 

- R, L of power rail is a key source of delay faults
 - Output signal skew
 - Propagation delay
- How much impedance is too much?
 - When it causes delay faults (or changes of state)
- Power pins typically not tested
 - ICs can have 100's, boards may have 1000's
 - Proposals for testing: X-ray, measure IR_{DC} on-chip

Power rail test

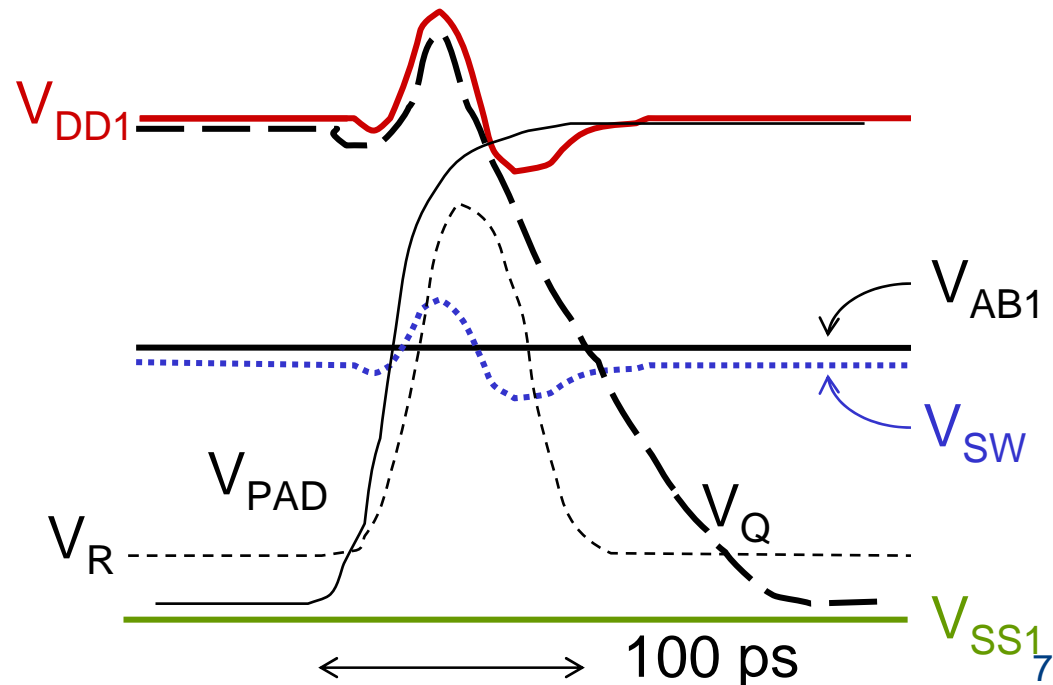  - Test whether logic gate's switching point changed
 - Via AT1, apply $V_{SW} + 100$ mV to flip-flop's reset
 - Via boundary scan, cause nearby output pin transition
 - Flip-flop changes state if power rail glitch > 200 mV




Power rail test - discussion

■ Benefits

- Programmable sensitivity via AB1 voltage
- Use active-low (or high) reset to detect positive (or negative) glitches
- Minimal IC area, and scannable

■ Limitations

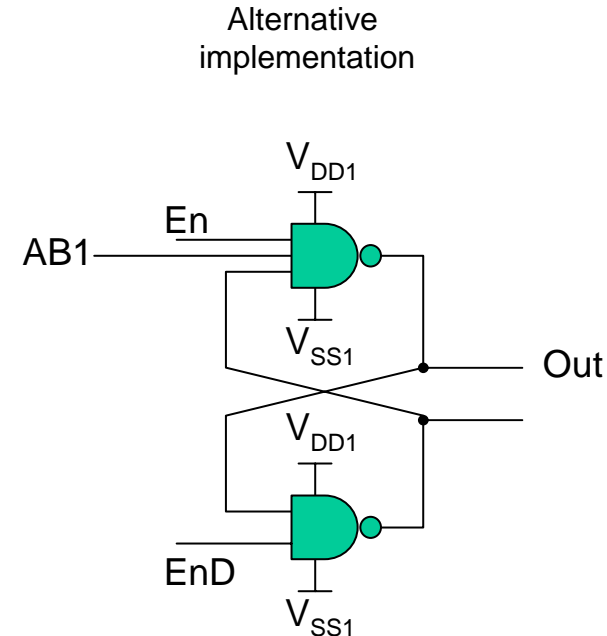- Must measure V_{SW} for each die, or flip-flop
- Analog bus noise – capacitance to quiet signals helps, so noise margin needs to be characterized



Testing analog pins

- Measuring input and output impedance
 - Similar to digital, except use *PROBE* or *INTEST* so that analog pin voltage is mid-range (and driven by function driver)


- Analog stimulus for core input
 - Limited drive via analog bus
 - Use AT1 to force stimulus voltage
 - Use AT2 to monitor stimulus voltage at input pin (and adjust stimulus as necessary) then to monitor response at output pin

Testing digital paths

 - Example: digital control signals
 - FPGA digital output has 1149.1
 - D4access digital input has 1149.4
 - Use conventional 1149.1 test software
(BSDL: B1, B2 bits declared INTERNAL, safe value = 0)

Differential interconnect testing

- (Discussed earlier)
- 8 boundary scan bits per pair




Differential interconnect tests

- A noise tolerant test for each DC-coupled pair
 - Drive logic 1 (then logic 0)
 - Measure received average pin voltages, via AT1 (–) and AT2 (+) simultaneously!
 - Capture received logic values (may ignore single-ended values)


- A noise tolerant test for each AC-coupled pair
 - Transmitter and receiver in CD state (e.g., high Z)
 - Drive sine wave at transmitter pin via AT1
 - Measure response at each receiver pin via AT2

LVDS example

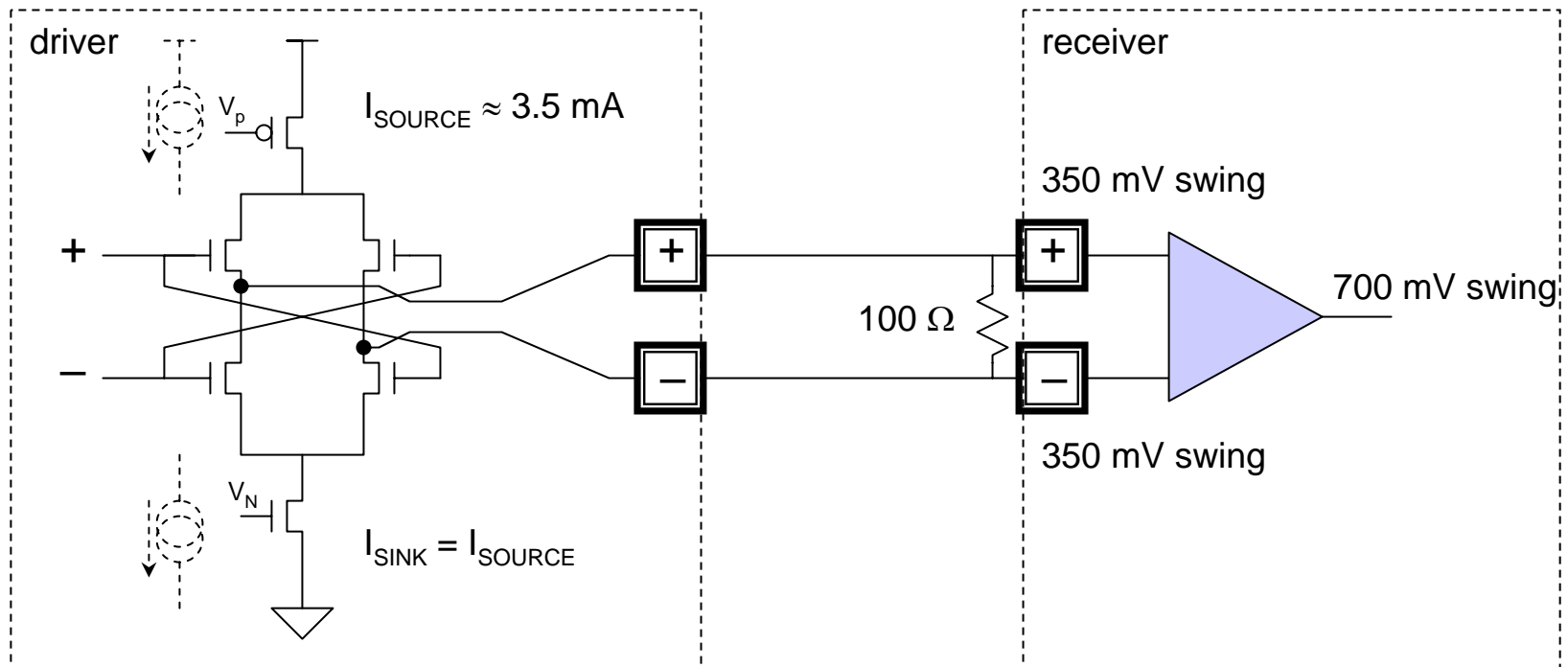- Correct termination resistance essential >100 Mb/s
- Testable by 1149.4, but not by 1149.1



Pin test circuitry overview

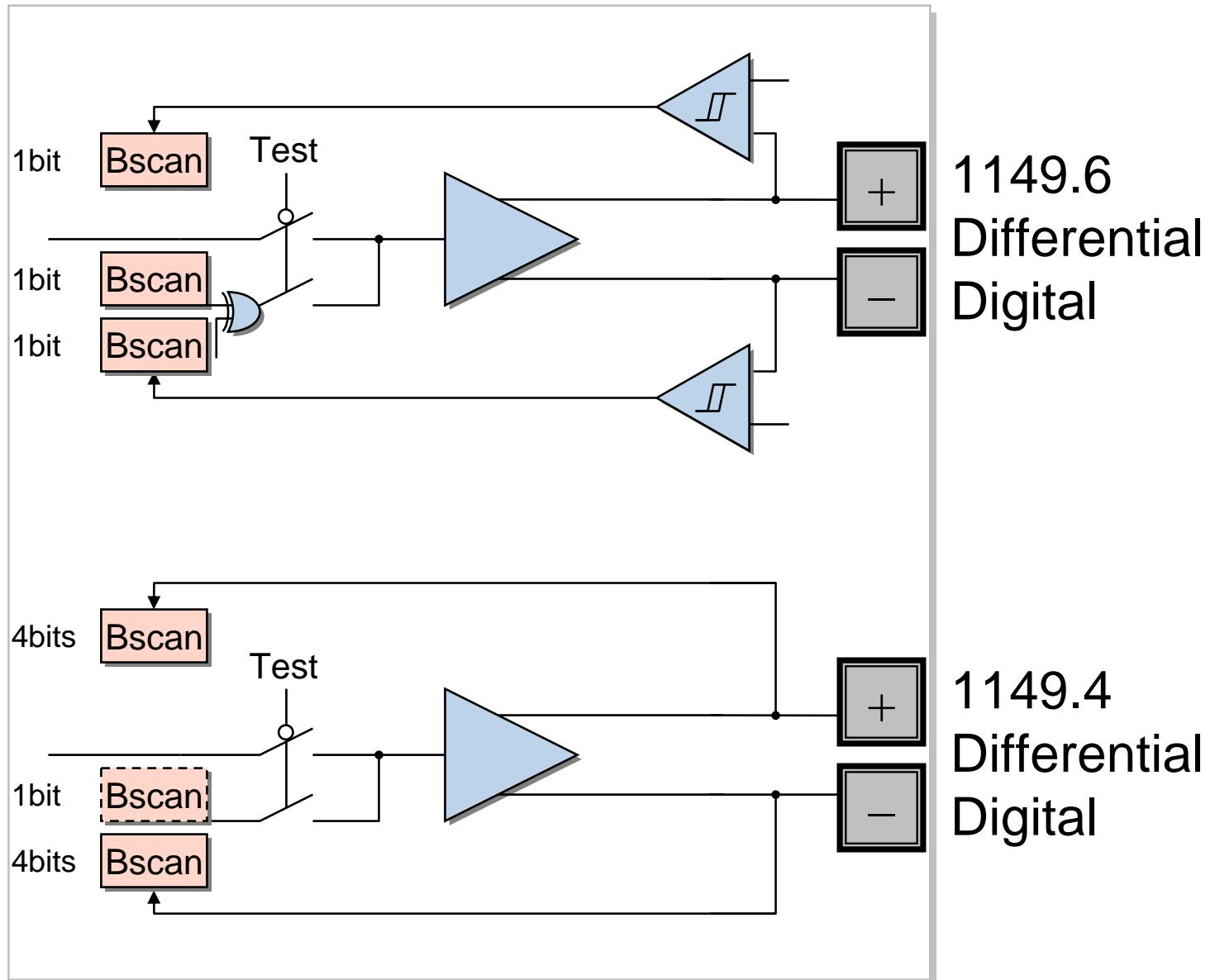

Differential interconnect testing

- 1149.4 vs. 1149.6
 - Measures R,C
 - +2 analog pins
 - Analog stimulus
 - Crummy switches
 - +2 crummy comparators/pair
 - + one instruction
 - 1~10 ms/pin
= 1~10 sec/1K pins
(but whole board test time >3 min.)
- Only pass/fail
- No extra pins
- Digital stimulus (1149.1)
- Hysteretic comparator, RC (?)
- +2~4 accurate comparators/pair
- + two instructions
- ~1 ms for all pins in parallel

Probing wires via the Internet

- 1149.1-based test via the Internet is available from many vendors (ASSET, Corellis, Intellitech, JTAG, ...)
- 1149.4 facilitates diagnosis of almost-failures or parametric failures
- Demonstrated by Lockheed Martin using representative demonstration board, off-the-shelf software, and LogicVision/NationalSemi. chip

Example of 1149.4-based board access

- Accessing a continuous signal
- Implemented using a variety of off-the-shelf software (from ASSET, Ohio Design Automation, National Instruments)
- Demonstrated with the National Semiconductor IC (SCANSTA400)

The screenshot displays a LabVIEW environment with three windows:

- sk0018970_501_skm.edf - InterComm:** A schematic diagram of a circuit component labeled U13. It shows a 12-to-1 MUX (Multiplexer) with 12 input channels (A0-A11) and 12 output channels (A01-A12). The component is connected to various pins and signals.
- sk0018972_501_layout.cad - InterComm:** A physical layout diagram of the circuit board, showing the placement of components and their interconnections.
- DFT dot4test.vi:** A test control panel with the following elements:
 - Test Select:** Four indicator lights labeled S1-A, S1-H, S1-J, and S1-K.
 - Functional Test Diagnostics:** A "Start/Stop" button and an "EXIT" button.
 - 12-to-1 MUX Channel:** A rotary selector switch with positions 1 through 12.
 - DAC Input:** A 12-bit DAC register with bits 11 down to 0. The "DAC Value" is 0.000.
 - ADC Value:** The "ADC Value" is 0.000.
 - Buttons:** "Write DAC" and "Read ADC" buttons.
 - DMM Scope:** A digital multimeter (DMM) scope showing a continuous sine wave signal. The vertical axis is labeled "Volts" (0.0 to 6.0) and the horizontal axis is labeled "msec" (0.00 to 5.00). The scope is set to 1 ms/div.


The Windows taskbar at the bottom shows the Start button, several application icons, and the system tray with the time 2:52 PM.

Example of 1149.4-based board access

■ Measuring a resistance

■ Demonstrated by Lockheed Martin across their Intranet, via Microsoft's NetMeeting

Laptop PC Mixed-Signal Tester

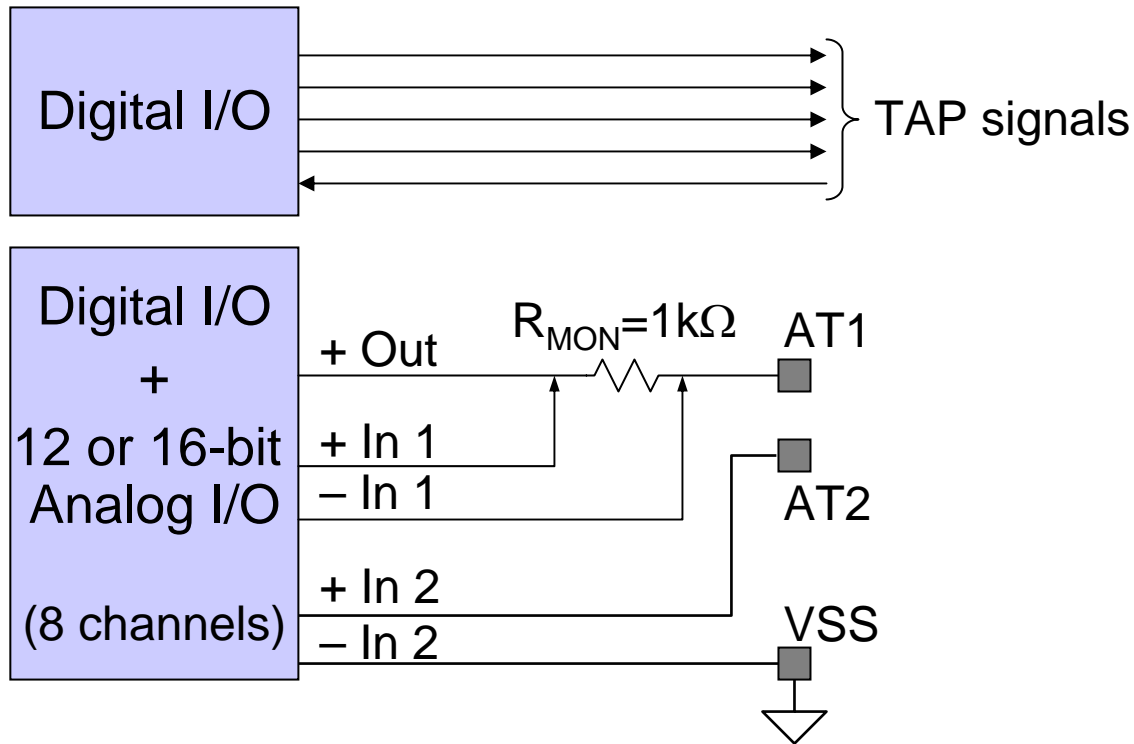

- Digital/Analog I/O cards commercially available from many suppliers (PCMCIA card or USB connection)
- Resistor + 2nd input channel can monitor delivered current

Test Automation

- When will Analog BSDL happen?
 - Only in response to market demand
 - Simple 1149.4 applications may not need ABSDL
 - Monitoring pin signal voltages
 - Measuring input/output impedances
 - Fault detection for 1 or 2 element networks
 - Automation not essential for few 1149.4 ICs/ board
 - Manual coding of documented values, bits

Summary

- 1149.4 access can test paths and pins
 - Analog, digital, differential, power rails, etc.
- Analog ATPG is key, but not yet available
 - Useful 1149.4 tests can be done with 1149.1 software
 - Analog hardware commercially available & linkable
- 1149.4 facilitates unique remote tests

Conclusions

- 1149.4: a serial access structure, not a test solution
 - Many 1149.4-based *solutions* published
 - Faster parametric digital tests
 - Higher frequency mixed-signal tests
 - Unique diagnostic capabilities
- History: difficult to get 1149.4 right first time (it's analog)
 - Help is available
- Most companies waiting for “market pull” before developing formal 1149.4 products
 - Some companies forging ahead anyway
 - ICs with 1149.4 were, and are being, designed at multiple companies

General References

- IEEE Std. 1149.4-1999: Standard for a Mixed Signal Test Bus
- 1149.4 WG web page: <http://grouper.ieee.org/groups/1149/4/index.html>
 - P1149.4 Working Group Meeting Minutes, test chip reports, etc.
- Analog and Mixed-Signal Boundary Scan – A Guide to the IEEE 1149.4 Test Standard, ed. by A.Osseiran, Kluwer Academic Publishers, 1999
 - A few chapters available at <http://www.chipcenter.com/TestandMeasurement/techarch.html>
- Proceedings of *ITC and VTS* (especially those on next slide)

Other 1149.4-related references

(in chronological order)

- B.Wilkins, “A Structure for Board-Level Mixed-Signal Testability”, ITC, Sept. 1992
- C.Thatcher, R.Tulloss, “Towards a Test Standard for Board and System Level Mixed-Signal Interconnects”, ITC, Oct. 1993
- K.Parker, J.McDermid, S.Oresjo, “Structure and Metrology for an Analog Testability Bus,” ITC, Oct 1993, pp. 309-22
- J.Matos, A.Leão, J.Ferreira, “Control and Observation of Analog Nodes in Mixed-Signal Boards,” ITC, Oct 1993, pp. 323-31
- S.Sunter, “A Low Cost 100 MHz Analog Test Bus”, VLSI Test Symposium, May, 1995
- S.Sunter, “The P1149.4 Mixed-Signal Test Bus: Costs and Benefits”, ITC, Oct. 1995
- S.Sunter, “Cost/Benefit Analysis of the P1149.4 Mixed Signal Test Bus,” IEE Proc. – Circuits, Devices and Systems, Vol. 143, No. 6, pp. 393-98, Dec 1996
- K.Lofstrom, “A Demonstration IC for the P1149.4 Mixed-Signal Test Standard,” ITC, Oct 1996, pp. 92-98
- K.Lofstrom, “Early Capture for Boundary Scan Timing Measurements,” ITC, Oct 1996, pp. 417-22
- The Boundary-Scan Handbook, Second edition, K.Parker, Kluwer Academic, USA, 1998
- R.Mason, “Mixed Signal DFT at GHz Frequencies”, VLSI Test Symposium, April, 1998
- Analog and Mixed-Signal Test, Edited by B.Vinnakota, Prentice Hall, USA, 1998
- J.McDermid, “Limited Access Testing: IEEE 1149.4 Instrumentation and Methods”, ITC, 1998, pp. 388-95
- R.Ho, B.Amrutur, K.Mai, B.Wilburn, T.Mori, M.Horowitz, “Applications of On-chip Samplers for Test and Measurement of Integrated Circuits”, IEEE Symposium on VLSI Circuits, June 1998, paper C12.1
- R. Mason, S. Ma, “Analog DFT Using an Undersampling Technique,” IEEE Design & Test of Computers, Oct-Dec 1999, pp. 84-88
- S.Sunter, K.Filliter, J.Woo, P.McHugh, “A General Purpose 1149.4 IC with HF Analog Test Capabilities”, ITC, 2001, pp. 38-45
- R.Andlauer, P.Vu, “Analog Test Bus Grows in Importance”, Electronic News, May 27, 2002, pg. 32
- S.Sunter, B.Nadeau-Dostie, “Complete, Contactless I/O Testing – Reaching the Boundary in Minimizing Digital IC Testing Cost”, ITC 2002, pp. 446-55
- I.Duzevik, “Preliminary Results of Passive Component Measurement Methods Using an IEEE 1149.4 Compliant Device”, Board Test Workshop, Oct. 2002 (www.national.com/appinfo/scan/files/duzevik_BTW02_paper.pdf)
- U.Kac, F.Novak, F.Azaïs, P.Nouet, M.Renovell, “Extending IEEE Std. 1149.4 Analog Boundary Modules to Enhance Mixed-Signal Test”, IEEE Design & Test of Computers, Mar-Apr 2003, pp. 32-39
- S.Sunter, “Testing High Frequency ADCs and DACs with a Low Frequency Analog Bus”, ITC 2003