

## Midterm 2 Solution

1

1.1

Universal set of gates is a set of gates such that every Boolean function can be implemented with gates in this set.

Alter: A Universal set of gates is one from which the three basic Boolean functions (NOT, AND and OR) can be implemented.

1.2

1.2.1 {OR, NOT}

Yes. AND can be implemented as  $ab = (a' + b)'$

1.2.2 {NAND, NOR}

Yes.

NOT can be implemented by tying one input of NAND gate to 1.

AND can be implemented by inverting the output of NAND gate i.e.  $ab = ((ab)')'$

Similarly OR can be implemented by inverting the output of a NOR gate

1.2.3  $\{f(x, y)\}$ , where  $f(x, y) = x'y$

Yes.

$f(x, 1) = x'$  i.e. NOT can be implemented

$f(x', y) = xy$  i.e. AND can be implemented

OR can be implemented using the above two because  $x + y = (x'y)'$

1.2.4  $\{f(x, y, z)\}$ , where  $f(x, y, z) = (x'y' + xy)z$

Yes.

$f(x, 0, 1) = x'$  i.e. NOT can be implemented

$f(x, 1, z) = xz$  i.e. AND can be implemented

OR can be implemented using the above two because  $x + y = (x'y)'$

Rubric:

- For each of the above parts, award 3 points if the conclusion as well as the reason is correct.
- For parts 1.2.1 and 1.2.2, deduct 1 point if the conclusion is correct but reason is not provided.
- For parts 1.2.3 and 1.2.4, deduct 2 points if the conclusion is correct but the reason is not provided.
- If the conclusion is incorrect, award 1 point for every functionality that is shown to be implemented by that set

2

If  $AB = 0$  then  $A \oplus B = A + B$ .

Proof:

$$A = A(B+B')$$

$$= AB + AB' \quad (\text{Distributivity})$$

$$= 0 + AB' \quad (AB = 0)$$

Also,

$$B = B(A+A')$$

$$= AB + A'B \quad (\text{Distributivity})$$

$$= 0 + A'B \quad (AB = 0)$$

Therefore,  $A+B=AB'+A'B$

Alter:

Let  $X = A \oplus B$  and  $Y = A + B$

$X = Y$  iff  $X + Y' = 1$  and  $XY' = 0$

$$\begin{aligned}
 X+Y' &= A \oplus B + (A + B)' \\
 &= AB' + A'B + A'B' \quad (\text{DeMorgan's}) \\
 &= AB' + A'B + A'B' + A'B' \quad (A+A=A) \\
 &= B'(A + A') + A'(B + B') \quad (\text{Distributivity}) \\
 &= B' + A' \quad (\text{Identity}) \\
 &= (AB)' \quad (\text{DeMorgan's}) \\
 &= 1 \quad (AB=0)
 \end{aligned}$$

$$\begin{aligned}
 XY' &= (A \oplus B)(A + B)' \\
 &= (AB' + A'B)(A'B') \quad (\text{DeMorgan's}) \\
 &= AB'A'B' + A'BA'B' \quad (\text{Distributivity}) \\
 &= 0 \quad (\text{Complement})
 \end{aligned}$$

Rubric:


- Deduct 1 point if the laws/properties are not listed
- For the alternative approach, award 5 points if the criterion for equality is listed, 5 points if  $X + Y' = 1$  is proved correctly and 5 points if  $XY' = 0$  is proved correctly

### 3


Rubric:

Only the outputs for the first 10 clock levels (includes both high and low levels) are considered. 1 point is deducted for every output at that level found incorrect.

#### 3.1

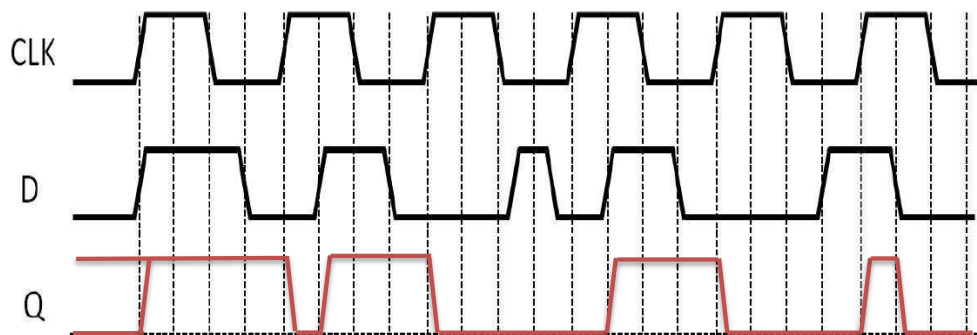

#### 3.2

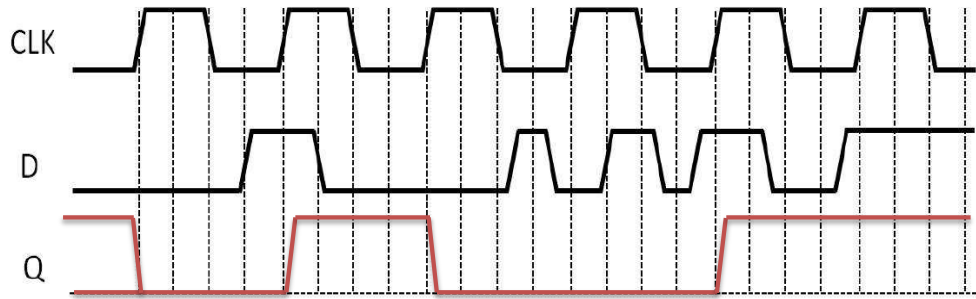

4

4.1 Boolean expressions for the next states and the output.

$$\begin{aligned}
 Q_0(t+1) &= XQ_1(t) + X'Q_0(t) \\
 Q_1(t+1) &= XQ_1(t) + XQ_0(t) \\
 M &= X'Q_1(t)Q_0(t)
 \end{aligned}$$

According to those Boolean equations, the following transition table can be derived.

present state			input	next state			output
state	$Q_1(t)$	$Q_0(t)$	$X$	state	$Q_1(t+1)$	$Q_0(t+1)$	$M$
$S_0$	0	0	0	$S_0$	0	0	0
$S_0$	0	0	1	$S_1$	0	1	0
$S_1$	0	1	0	$S_0$	0	0	0
$S_1$	0	1	1	$S_2$	1	0	0
$S_2$	1	0	0	$S_0$	0	0	0
$S_2$	1	0	1	$S_3$	1	1	0
$S_3$	1	1	0	$S_0$	0	0	1
$S_3$	1	1	1	$S_3$	1	1	0

4.2

The following state diagram can be obtained from the transition table.

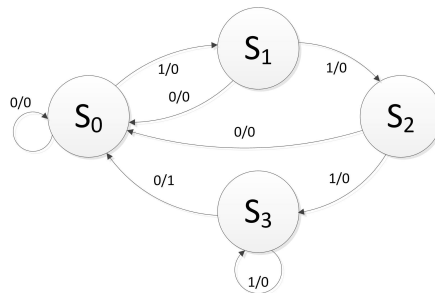


Figure 1: State diagram of Problem 4.

4.3

This FSM outputs  $M = 1$  once finds pattern  $X = 1110$ .

Rubric:

cycle	1	2	3	4	5	6	7	8	9	10
$X$	1	1	1	0	0	0	1	1	1	0
state	$S_0$	$S_1$	$S_2$	$S_3$	$S_0$	$S_0$	$S_0$	$S_1$	$S_2$	$S_3$
$M$	0	0	0	1	0	0	0	0	0	1

- Get 7 points for correct transition table.
- Get 2 points for each correct Boolean function of  $Q_0$ ,  $Q_1$  and  $M$  if the transition table is incorrect.
- Deduct 2 points for each incorrect Boolean function but correct transition table.
- Deduct 1 points for one incorrect row in the transition table.
- Deduct 1 points for one incorrect transition in the state diagram.
- Deduct 1 points for one incorrect state/ $M$  in 4.3
- Deduct 2 points for correctly describing state diagram and the table in 4.3 of the incorrect transition table in 4.1.
- Deduct 7 points for incorrect state diagram based on incorrect transition table in 4.1.
- Deduct 7 points for no state diagram.
- Deduct 5 points for incorrect table in 4.3 based on incorrect transition table in 4.1.
- Deduct 3 points for incorrect label in the state diagram, e.g., no output on transition edges.
- Get 5 points for correct description of FSM functionality.
- Get 5 points for correct table in 4.3.
- Get 5 points for correct description of FSM functionality but with 1 cycle shift of  $M$ .
- Deduct 2 points for incorrect states in the table but correct description of FSM functionality.

## V

$T$	$Q(t)$	$Q(t+1)$	$D$
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

In this table,  $T$ ,  $Q(t)$  and  $Q(t+1)$  show the expected functionality of a T flip-flop, and  $D$  shows the corresponding values required for  $Q(t+1)$ . Boolean expression for  $D$  of a D flip-flop is

$$D = Q(t)'T + Q(t)T'$$

The final logic diagram is as

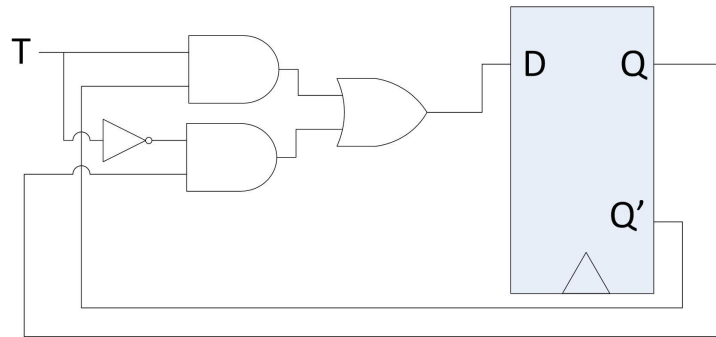


Figure 2: Logic diagram of Problem 5.

Rubric:

- Get 12 points for correct excitation table of  $T(t)$ ,  $Q(t)$ ,  $Q(t + 1)$  and  $D(t)$ .
- Get 15 points for implementing D flip-flop with T flip-flop.
- Get 2 points for correct K map from the incorrect excitation table.
- Get 6 points for incomplete Boolean expression for  $D$ .
- Get 12 points for correct Boolean expression for  $D$ .
- Deduct 2 points for minor notation incorrectness in the correct logic diagram.