 



# CSE140 - HW #4

Due Thursday February 11, 11:59PM

In this homework, we practice the analysis and synthesis of sequential networks. For the first problem, we draw the timing diagram of the latch and flip-flop. For the second problem, we translate a pattern recognizer into state diagrams and state tables. For the third problem, we analyze the behavior of a sequential circuit. For the last problem, we design the circuit from a given description.

 1. Timing Diagram of Latch and Flip-Flop: Given the input waveforms shown below, sketch the outputs.





2. A sequential network has one binary input  $x(t)$  and one binary output  $y(t)$ . The network produces  $y = 1$ , whenever input pattern  $x(t - 2, t) = 100$  or  $110$ . Otherwise, the output  $y = 0$ .

2.1 Design the system as a Mealy machine with a minimal number of states.

- (i) Draw the state diagram.
- (ii) Write the state table.

2.2 Design the system as a Moore machine with a minimal number of states.

- (i) Draw the state diagram.
- (ii) Write the state table.

3. Given the circuit as described in zyBook 3.8.2, replace the state register with two T flip-flops.

- (i) Write the state table.
- (ii) Draw the state diagram.

4. A state machine has one input  $x(t)$  and two-bit state  $(Q_1(t), Q_0(t))$ . The machine is described by the following state equations.

$$Q_1(t+1) = Q_0(t) + x'(t)Q_1'(t),$$

$$Q_0(t+1) = Q_1'(t) + x(t)Q_0(t).$$

$$y(t) = Q_1(t)Q_0(t)$$

Use two JK flip-flops and a minimal two-level NAND network to implement the machine.

- (i). Write the state excitation table and draw the state diagram.
- (ii). Show your derivation (K maps) and draw the logic diagram.