

CSE 140 Lecture 12

Combinational Standard Modules

CK Cheng

CSE Dept.

UC San Diego

Part III. Standard Modules

Interconnect Modules:


1. Decoder, 2. Encoder

3. Multiplexer, 4. Demultiplexer

Multiplexer

- Definition
- Logic Diagram
- Application

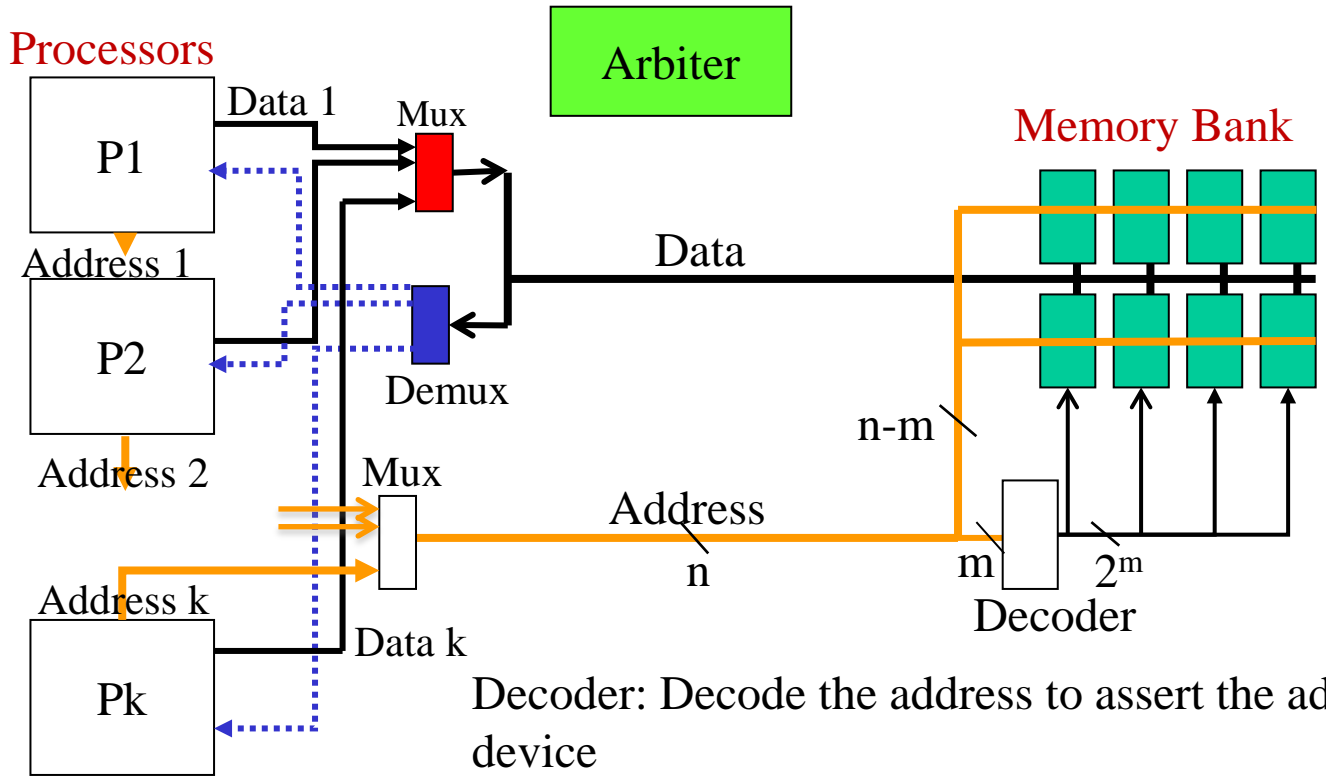Interconnect: Decoder, Encoder, Mux, DeMux




Decoder: Decode the address to assert the addressed device

Mux: Select the inputs according to the index addressed by the control signals

iClicker: Multiplexer Definition

- A. A device that interleaves two or more activities
- B. A communications device that combines several signals for transmission over a single medium
- C. A logic circuit that sends one of several inputs out over a single output channel.
- D. The circuit that uses a common communications channel for sending two or more messages or signals.
- E. All of the above

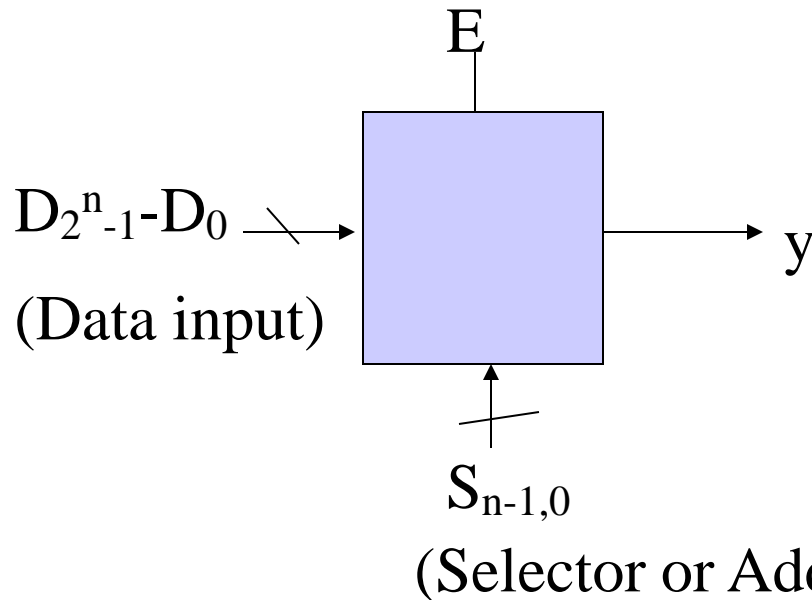3. Mux (Multiplexer) Definition: A digital module that selects one of data inputs according to the binary address of the selector.



Description

If $E = 1$


$y = D_i$ where $i = (S_{n-1}, \dots, S_0)$

Else

$y = 0$

Multiplexer (Mux): Definition

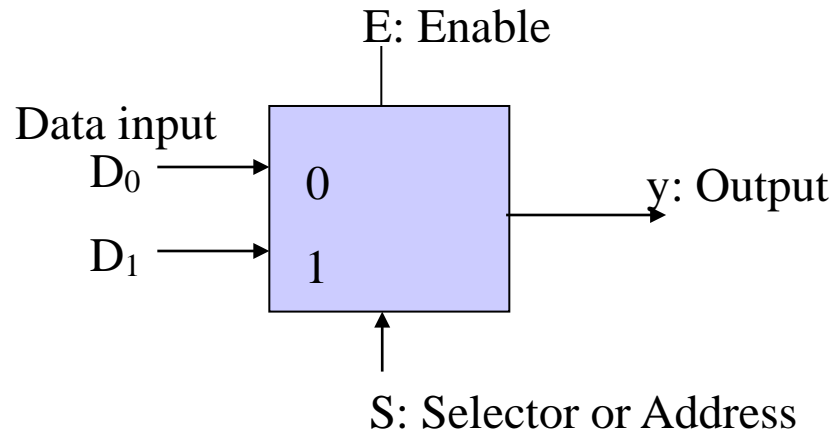- Selects between one of N inputs to connect to the output.
- $\log_2 N$ -bit select input – control input




PI Q: What is the output of the following MUX?

A.0


B.1

C.Can't say

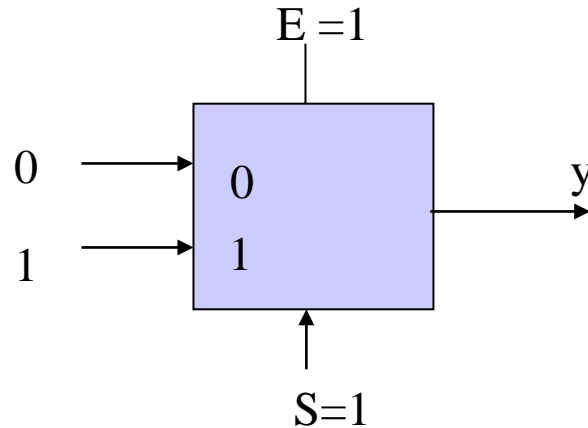


Multiplexer (Mux): Definition

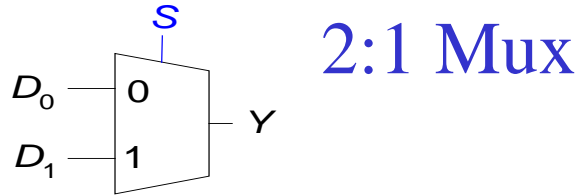- Selects between one of N inputs to connect to the output.
- $\log_2 N$ -bit select input – control input
- Example:




S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		

Multiplexer Definition: Example

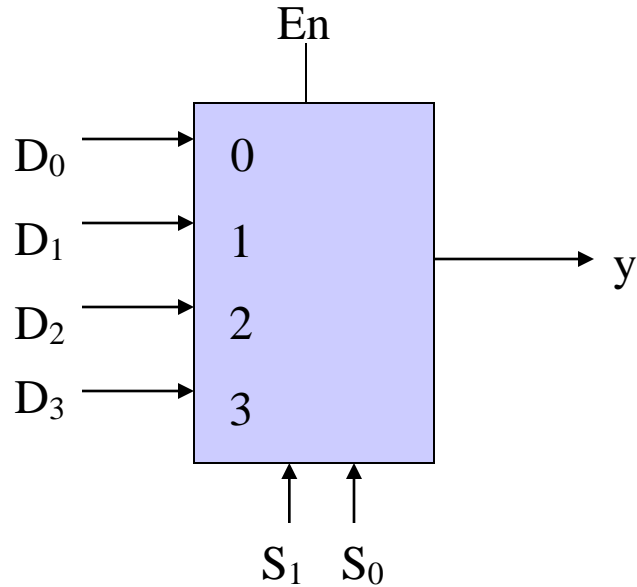

S_1	S_0	y

Multiplexer Definition: Example

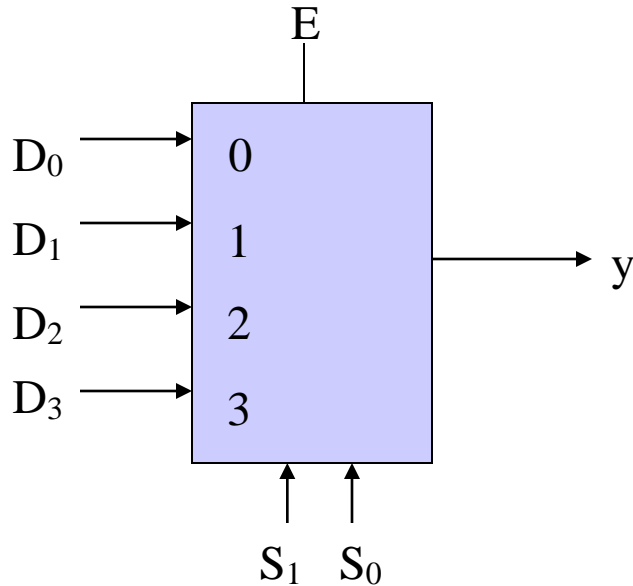

$E=1$:

If $D_0 = 0$ and $S_1S_0 = 00 \Rightarrow y = 0$


If $D_0 = 1$ and $S_1S_0 = 00 \Rightarrow y = 1$

Multiplexer: Logic Diagram


- Logic gates
 - Sum-of-products form

Y	$D_0 D_1$	00	01	11	10
S					
0		0	0	1	1
1		0	1	1	0

$$Y = D_0 \bar{S} + D_1 S$$

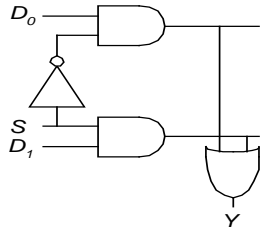

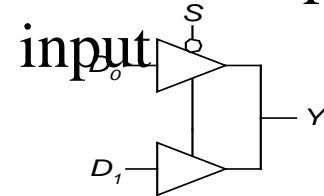- Tristates
 - For an N-input mux, use N tristates
 - Turn on exactly one to select the appropriate




Multiplexer Application

- Mux for a Boolean function with truth table as input

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = AB$$

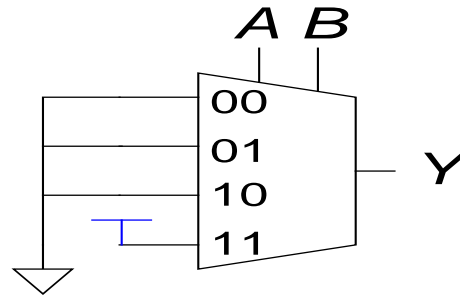


Multiplexer: Application

$$Y = AB$$

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	0
1	0	0
1	1	1

<i>A</i>	<i>Y</i>
0	0
1	<i>B</i>

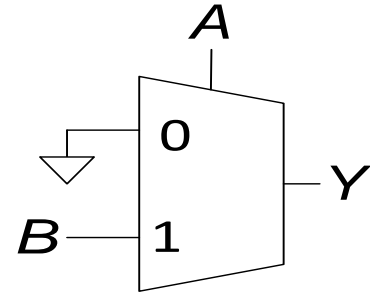

Multiplexer Application: universal set {Mux}

We use selector to decompose the function into smaller functions (less number of variables), which follows


Shannon's expansion.

We simplify the decomposed functions using **K-map**, which follows **consensus theorem.**

Multiplexer Application: universal set {Mux}


Example 1: Given $f(a,b,c) = \sum m(0,1,7) + \sum d(2)$, implement with an 8-input Mux.

Id	a	b	c	f
0	0	0	0	1
1	0	0	1	1
2	0	1	0	-
3	0	1	1	0
4	1	0	0	0
5	1	0	1	0
6	1	1	0	0
7	1	1	1	1

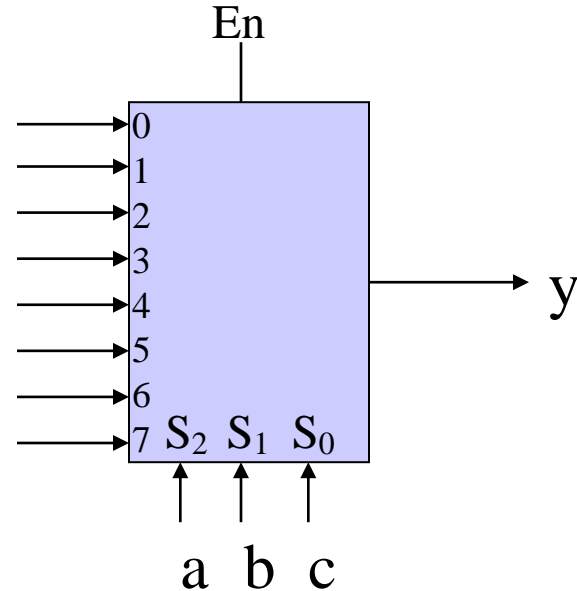


Example 2: Given $f(a,b,c) = \sum m(0,1,7) + \sum d(2)$, implement with 4-input Muxes.

a	b	c = 0	c = 1	D(c)
0	0			$D_0(c) =$
0	1			$D_1(c) =$
1	0			$D_2(c) =$
1	1			$D_3(c) =$

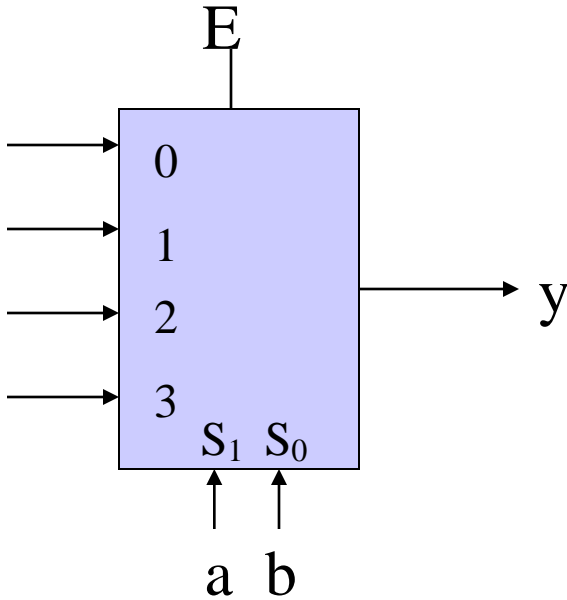

Example 3: Given $f(a,b,c) = \Sigma m(0,1,7) + \Sigma d(2)$, implement with 2-input Muxes.

a	00	01	10	11	D(b,c)
0	1	1	-	0	$D_0(b,c)$
1	0	0	0	1	$D_1(b,c)$

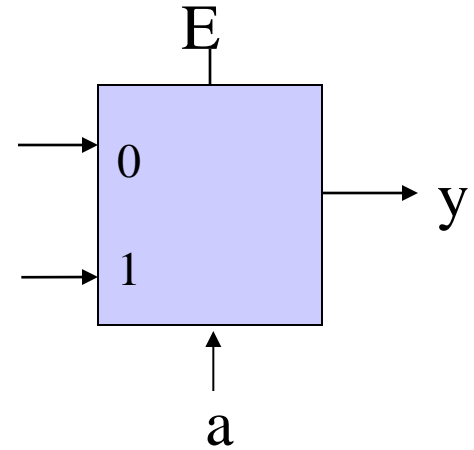

Example 3: Given $f(a,b,c) = \Sigma m(0,1,7) + \Sigma d(2)$, implement with 2-input Muxes.


a	00	01	10	11	D(b,c)
0	1	1	-	0	$D_0(b,c)$
1	0	0	0	1	$D_1(b,c)$

$$D_0(b,c) = b'$$

	1	-
c	1	0
	<u>b</u>	

$$D_1(b,c) = bc$$


	0	0
c	0	1
	<u>b</u>	

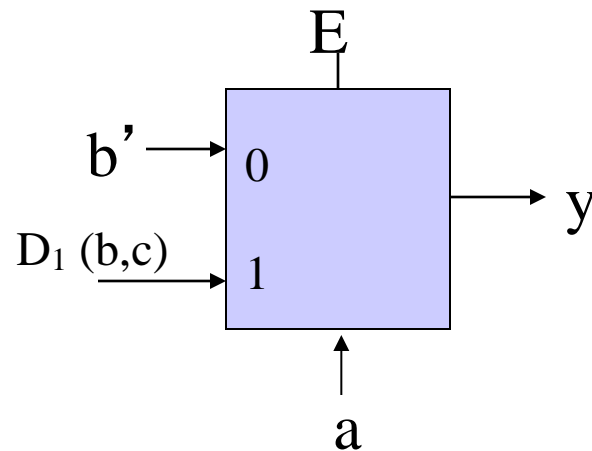

Example 3: Given $f(a,b,c) = \Sigma m(0,1,7) + \Sigma d(2)$, implement with 2-input Muxes.

$D_1(b,c)$


b	c = 0	c = 1	
0	0	0	$l_1(0) = 0$
1	0	1	$l_1(c) = c$

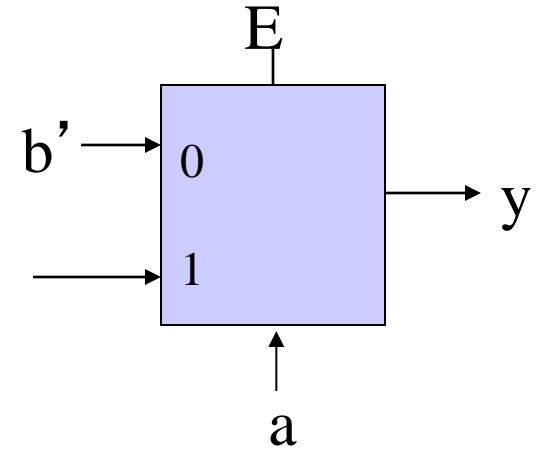

Example 3: Given $f(a,b,c) = \Sigma m(0,1,7) + \Sigma d(2)$, implement with 2-input Muxes.


$D_1(b,c)$

b	c = 0	c = 1	
0	0	0	$l_1(0) = 0$
1	0	1	$l_1(c) = c$

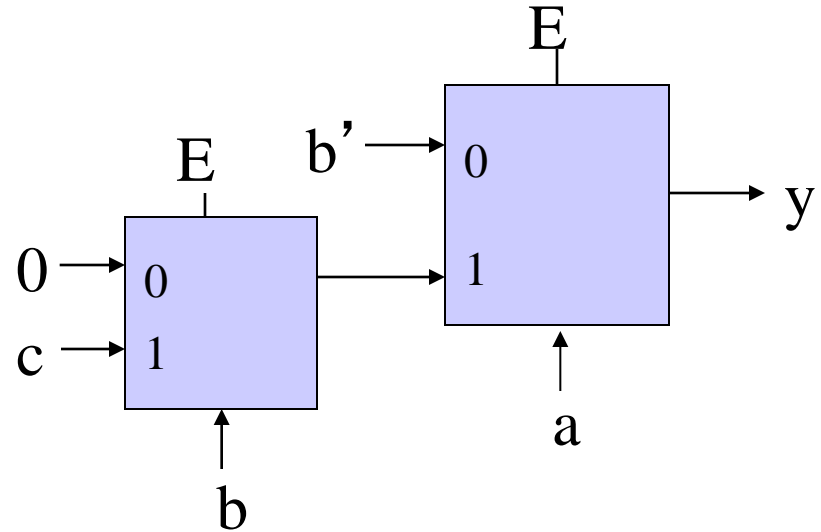


Example 4: Given $f(a,b,c) = \sum m(0,2,4,7) + \sum d(3,5)$, implement with 2-input Muxes.


f		bc				
		00	01	10	11	
a	0	1	0	1	-	$D_0(b,c)$
	1	1	-	0	1	$D_1(b,c)$

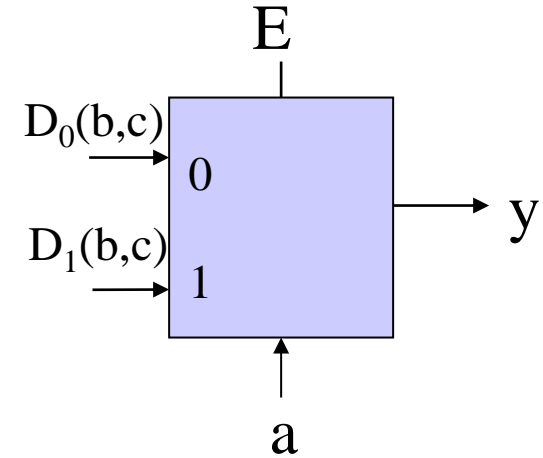

4. Demultiplexers

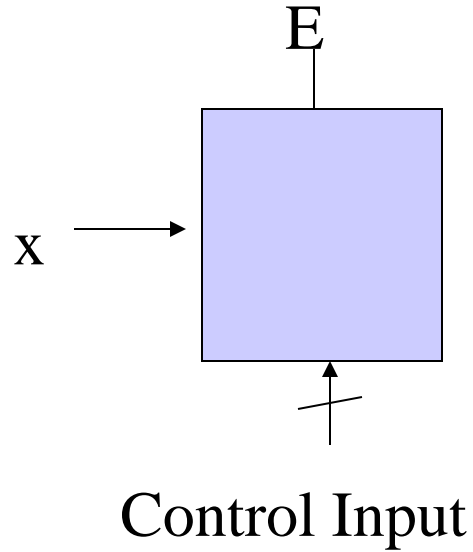


4. Demultiplexers

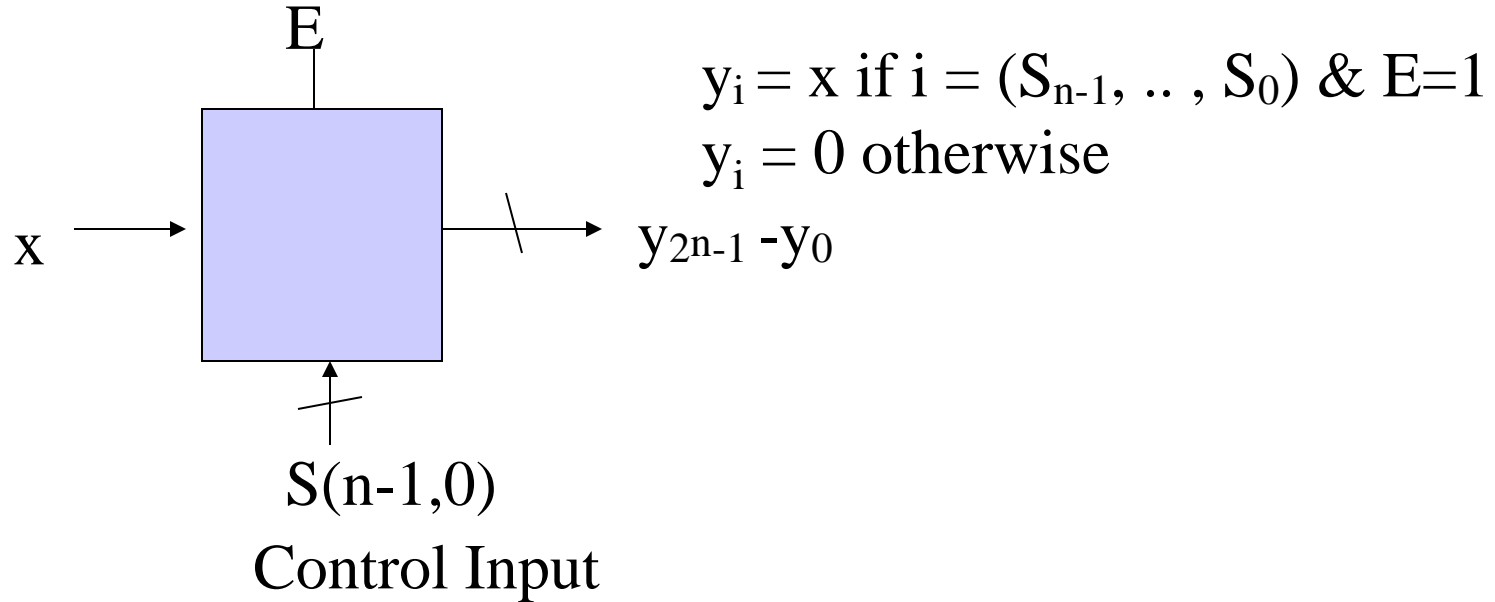

Shifters


- **Logical shifter:** shifts value to left or right and fills empty spaces with 0's
 - Ex: $11001 \gg 2 = 00110$
 - Ex: $11001 \ll 2 = 00100$
- **Arithmetic shifter:** same as logical shifter, but on right shift, fills empty spaces with the old most significant bit (msb).
 - Ex: $11001 \ggg 2 = 11110$
 - Ex: $11001 \lll 2 = 00100$
- **Rotator:** rotates bits in a circle, such that bits shifted off one end are shifted into the other end
 - Ex: $11001 \text{ ROR } 2 = 01110$
 - Ex: $11001 \text{ ROL } 2 = 00111$

Shifter


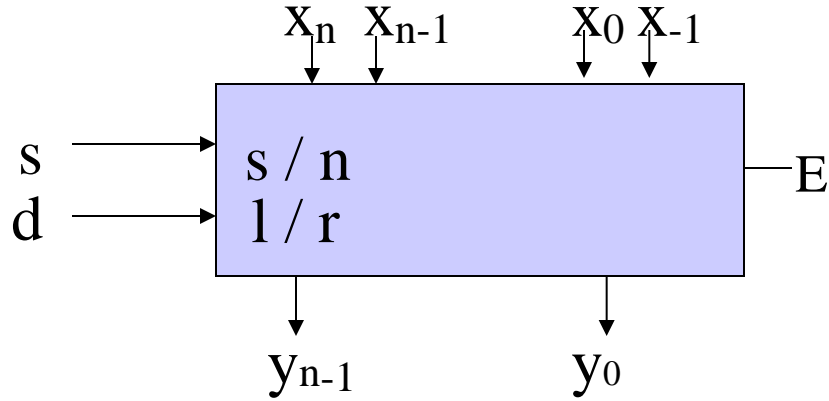


$$\begin{aligned}
 y_i &= x_{i-1} \text{ if } E = 1, s = 1, \text{ and } d = L \\
 &= x_{i+1} \text{ if } E = 1, s = 1, \text{ and } d = R \\
 &= x_i \text{ if } E = 1, s = 0 \\
 &= 0 \text{ if } E = 0
 \end{aligned}$$



Can be implemented with a mux

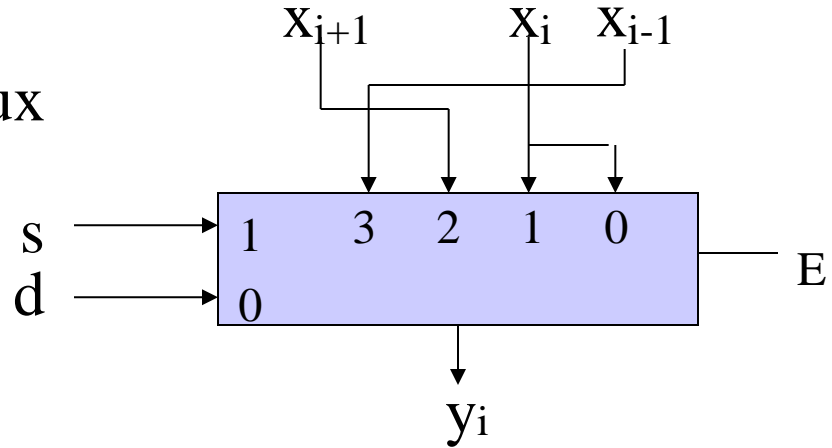

Shifter Design

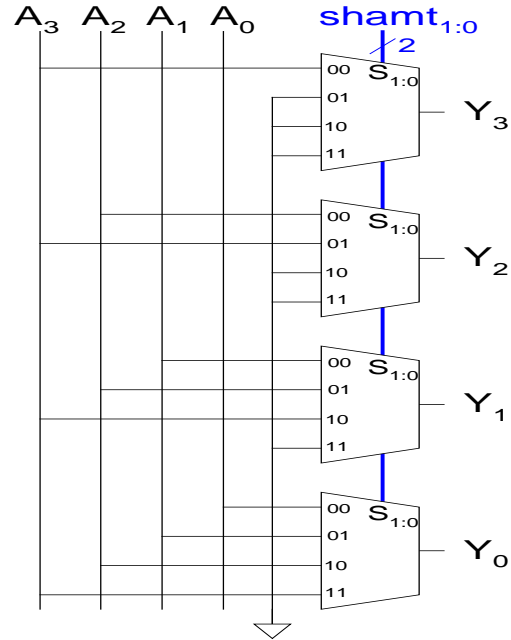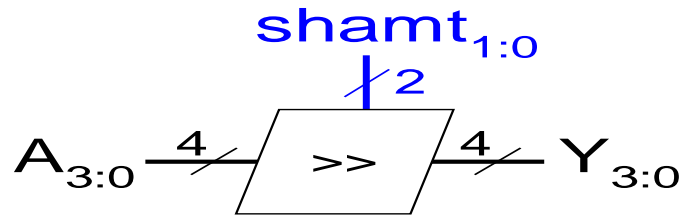

Barrel Shifter

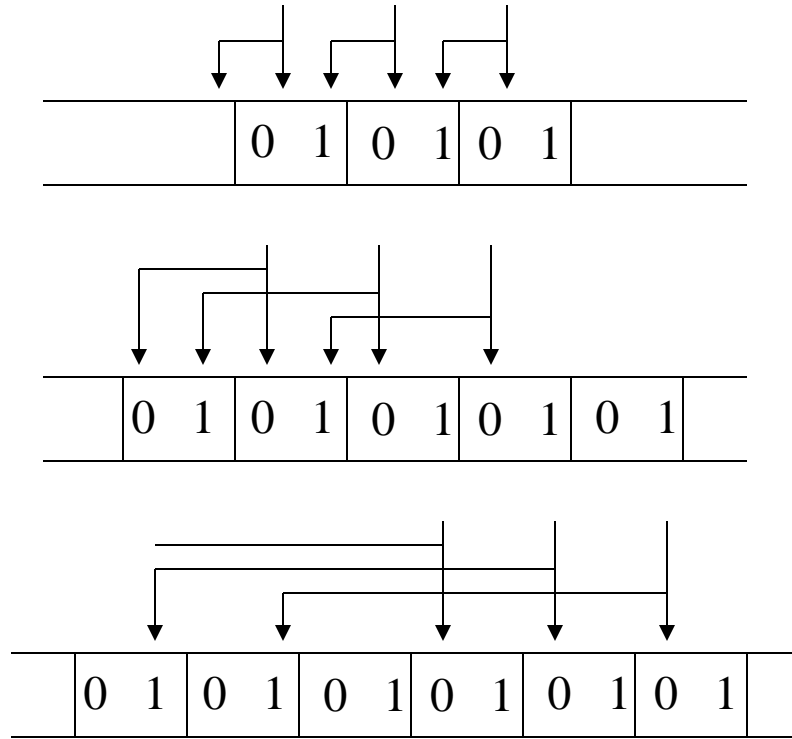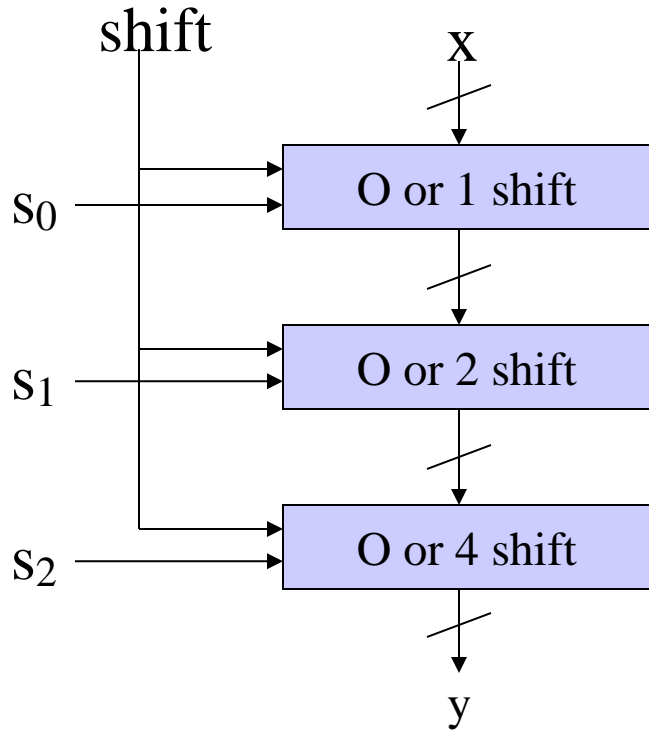

Shifters as Multipliers and Dividers

- A left shift by N bits multiplies a number by 2^N
 - Ex: $00001 \ll 2 = 00100$ ($1 \times 2^2 = 4$)
 - Ex: $11101 \ll 2 = 10100$ ($-3 \times 2^2 = -12$)
- The arithmetic right shift by N divides a number by 2^N
 - Ex: $01000 \ggg 2 = 00010$ ($8 \div 2^2 = 2$)
 - Ex: $10000 \ggg 2 = 11100$ ($-16 \div 2^2 = -4$)