

# CSE 140 Lecture 13

## Standard Combinational Modules

CK Cheng

CSE Dept.

UC San Diego

# Part III. Standard Modules

Interconnect

Operators.

Representation of numbers

Adders

1. Full Adder
2. Half Adder
3. Ripple-Carry Adder
4. Carry Look Ahead Adder
5. Prefix Adder

ALU

Comparator

Shifter

Multiplier

Division

# Design Flow

- Specification: Data Representations
- Arithmetic: Algorithms
- Logic: Synthesis
- Layout: Placement and Routing

# 1. Representation of numbers

## Negative Numbers

- 2's complement of n-bit vector  
-x:  $2^n - x$
- 1's complement of n-bit vector  
-x:  $2^n - x - 1$

# 1. Representation

- 2's Complement

$-x: 2^n - x$

e.g.  $16 - x$

- 1's Complement

$-x: 2^n - x - 1$

e.g.  $16 - x - 1$

Id	2's comp.	1's comp.
0	0	15
-1	15	14
-2	14	13
-3	13	12
-4	12	11
-5	11	10
-6	10	9
-7	9	8
-8	8	

# 1. Representation

Id	-Binary	sign mag	2's comp	1's comp
0	0000	1000	0000	1111
-1	0001	1001	1111	1110
-2	0010	1010	1110	1101
-3	0011	1011	1101	1100
-4	0100	1100	1100	1011
-5	0101	1101	1011	1010
-6	0110	1110	1010	1001
-7	0111	1111	1001	1000
-8			1000	

# Representation

## 1's Complement

For a negative number, we take the positive number and complement every bit.

## 2's Complement

For a negative number, we do 1's complement and plus one.

$$(b_{n-1}, b_{n-2}, \dots, b_0): -b_{n-1}2^{n-1} + \sum_{i < n-1} b_i 2^i$$

$b_{n-1}=1$  iff the number is negative

# Representation

## 2's Complement

- $x+y$
- $x-y: x+2^n-y=2^n+x-y$
- $-x+y: 2^n-x+y$
- $-x-y: 2^n-x+2^n-y$   
 $= 2^n+2^n-x-y$
- $-(-x)=2^n-(2^n-x)=x$

## 1's Complement

- $x+y$
- $x-y: x+2^n-y-1=2^n-1+x-y$
- $-x+y: 2^n-x-1+y=2^n-1-x+y$
- $-x-y: 2^n-x-1+2^n-y-1$   
 $= 2^n-1+2^n-x-y-1$
- $-(-x)=2^n-(2^n-x-1)-1=x_8$



# Examples

$$2 + 3 = 5$$

$$0\ 0\ 1\ 0$$

$$0\ 0\ 1\ 0$$

$$+ 0\ 0\ 1\ 1$$

---


$$0\ 1\ 0\ 1$$

$$2 - 3 = -1\ (2's)$$

$$0\ 0\ 0\ 0$$

$$0\ 0\ 1\ 0$$

$$+ 1\ 1\ 0\ 1$$

---


$$1\ 1\ 1\ 1$$

$$2 - 3 = -1\ (1's)$$

$$0\ 0\ 1\ 0$$

$$+ 1\ 1\ 0\ 0$$

---


$$1\ 1\ 1\ 0$$

Check for overflow (2's)

$$-2 - 3 = -5\ (2's)$$

$$1\ 1\ 0\ 0$$

$$1\ 1\ 1\ 0$$

$$+ 1\ 1\ 0\ 1$$

---


$$1\ 0\ 1\ 1$$

$$-2 - 3 = -5\ (1's)$$

$$1\ 1\ 0\ 0$$

$$1\ 1\ 0\ 1$$

$$+ 1\ 1\ 0\ 0$$

---


$$1\ 0\ 0\ 1$$

$$1$$

---


$$1\ 0\ 1\ 0$$

$$3 + 5 = 8$$

$$0\ 1\ 1\ 1$$

$$0\ 0\ 1\ 1$$

$$+ 0\ 1\ 0\ 1$$

---


$$1\ 0\ 0\ 0$$

$$C_4C_3$$

$$-3 + -5 = -8$$

$$1\ 1\ 1\ 1$$

$$1\ 1\ 0\ 1$$

$$+ 1\ 0\ 1\ 1$$

---


$$1\ 0\ 0\ 0$$

$$C_4C_3\ 9$$

# Addition: 2's Complement Overflow


In 2's complement:

$$\text{overflow} = c_n \oplus c_{n-1}$$

Exercise:


1. Demonstrate the overflow with more examples.
2. Prove the condition.
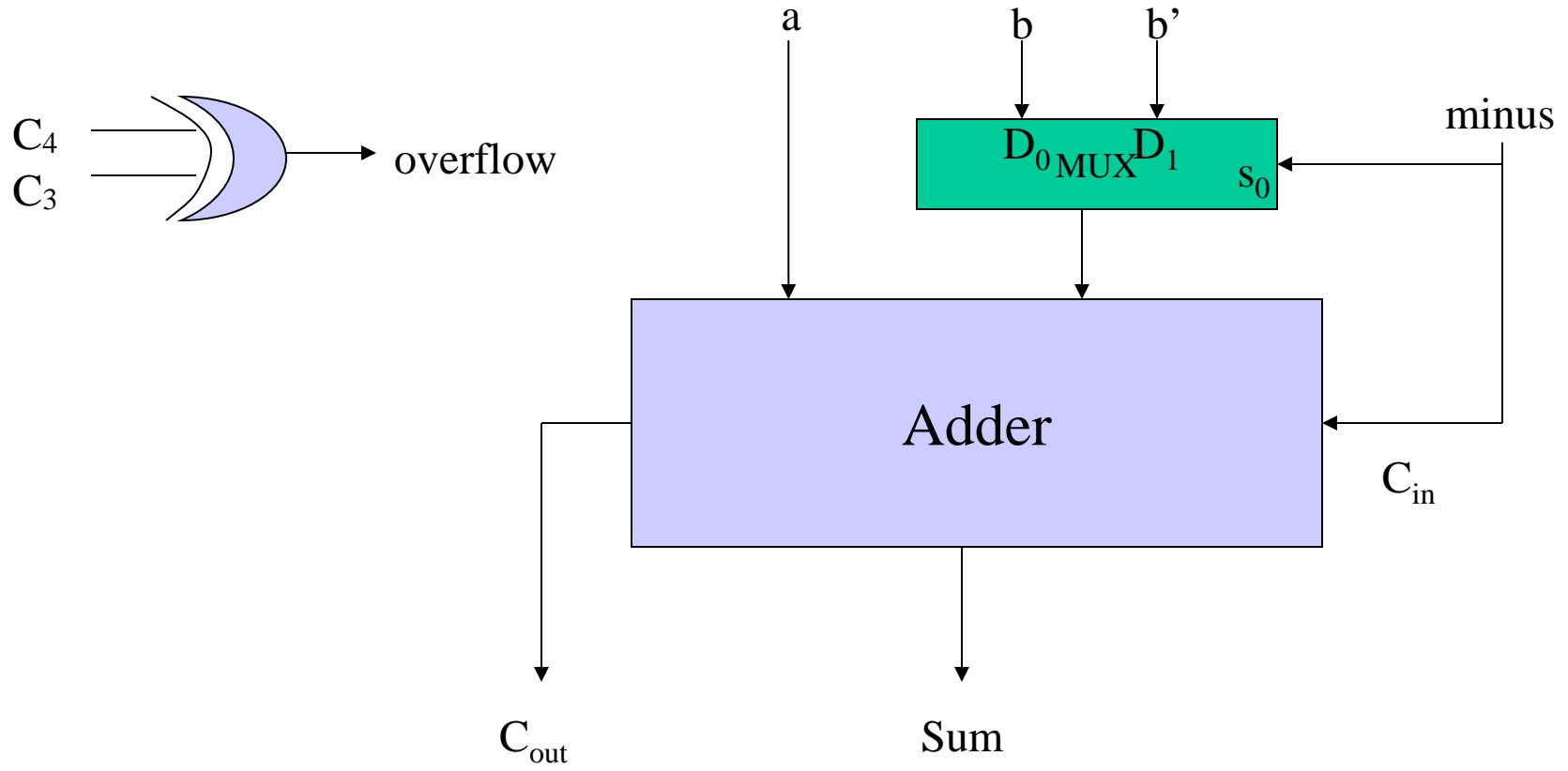
# Addition and Subtraction using 2's Complement



# 1-Bit Adders

## Half Adder

 


A	B	$C_{out}$	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

## Full Adder

 


$C_{in}$	A	B	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$


# Half Adder

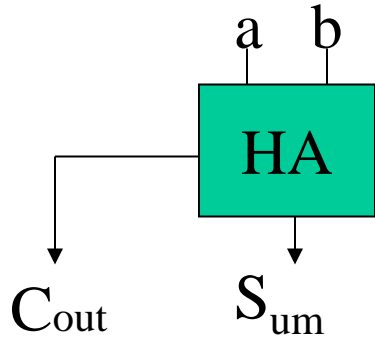


a	b	C <sub>out</sub>	S <sub>um</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S_{um} = ab' + a'b = a \oplus b$$


$$C_{out} = ab$$

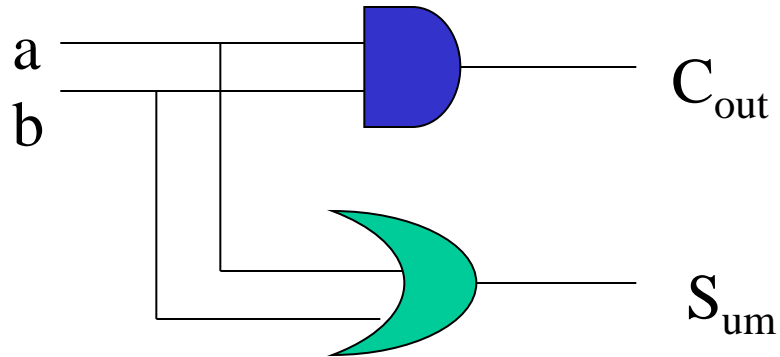

# Full Adder Composed of Half Adders

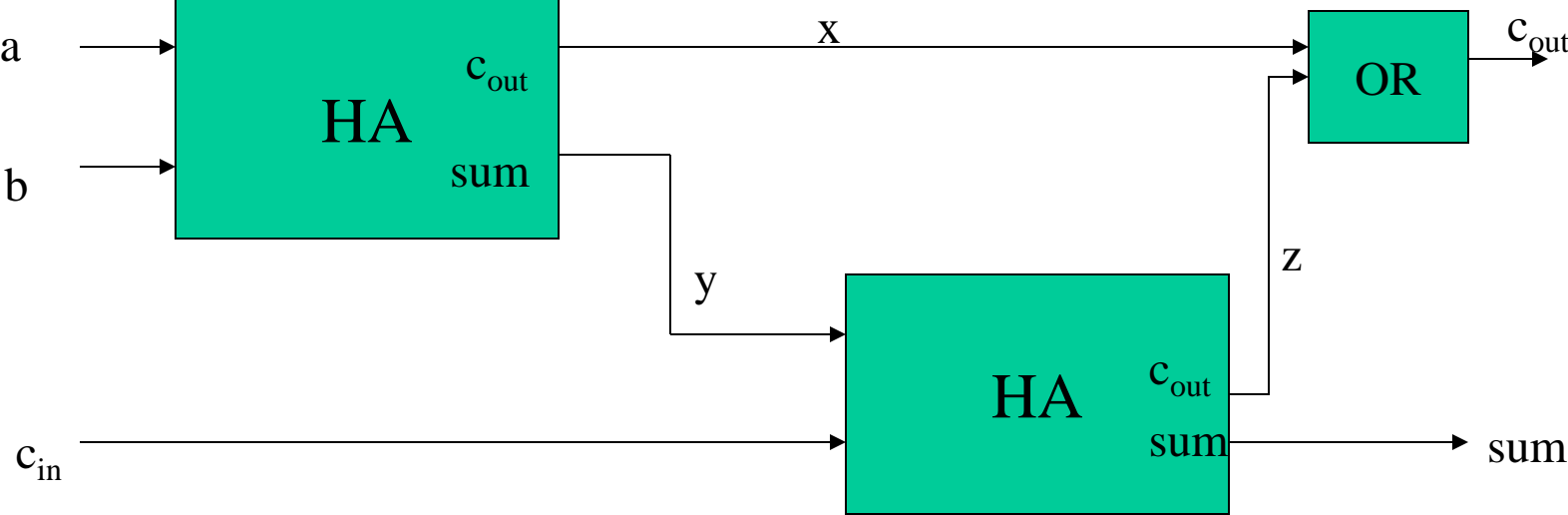

# Full Adder Composed of Half Adders

 


Id	a	b	$c_{in}$	x	y	z	$c_{out}$	$s_{um}$
0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	1
2	0	1	0	0	1	0	0	1
3	0	1	1	0	1	1	1	0
4	1	0	0	0	1	0	0	1
5	1	0	1	0	1	1	1	0
6	1	1	0	1	0	0	1	0
7	1	1	1	1	0	0	1	1

Id	x	z	$c_{out}$
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	-
 
# Adder


- Several types of carry propagate adders (CPAs) are:
  - Ripple-carry adders (slow)
  - Carry-lookahead adders (fast)
  - Prefix adders (faster)
- Carry-lookahead and prefix adders are faster for large adders but require more hardware.




 
# Ripple-Carry Adder

- Chain 1-bit adders together
- Carry ripples through entire chain
- Disadvantage: **slow**



# Ripple-Carry Adder Delay

- The delay of an  $N$ -bit ripple-carry adder is:

$$t_{\text{ripple}} = Nt_{FA}$$

where  $t_{FA}$  is the delay of a full adder

# Carry-Lookahead Adder

- Compress the logic levels of  $C_{\text{out}}$
- **Some definitions:**
  - Generate ( $G_i$ ) and propagate ( $P_i$ ) signals for each column:

- A column will generate a carry out if  $A_i$  AND  $B_i$  are both 1.

$$G_i = A_i B_i$$

- A column will propagate a carry in to the carry out if  $A_i$  OR  $B_i$  is 1.

$$P_i = A_i + B_i$$

- The carry out of a column ( $C_i$ ) is:

$$C_{i+1} = A_i B_i + (A_i + B_i) C_i = G_i + P_i C_i$$

# Carry Look Ahead Adder


$$C_1 = a_0b_0 + (a_0+b_0)c_0 = g_0 + p_0c_0$$

$$C_2 = a_1b_1 + (a_1+b_1)c_1 = g_1 + p_1c_1 = g_1 + p_1g_0 + p_1p_0c_0$$

$$C_3 = a_2b_2 + (a_2+b_2)c_2 = g_2 + p_2c_2 = g_2 + p_2g_1 + p_2p_1g_0 + p_2p_1p_0c_0$$

$$C_4 = a_3b_3 + (a_3+b_3)c_3 = g_3 + p_3c_3 = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0c_0$$



$$q_i = a_i b_i \quad p_i = a_i + b_i$$

 

# Carry-Lookahead Addition

- Step 1: compute *generate* ( $G$ ) and *propagate* ( $P$ ) signals for columns (single bits)
- Step 2: compute  $G$  and  $P$  for  $k$ -bit blocks
- Step 3:  $C_{in}$  propagates through each  $k$ -bit propagate/generate block

# 32-bit CLA with 4-bit blocks

  

# Carry-Lookahead Adder Delay

- Delay of an  $N$ -bit carry-lookahead adder with  $k$ -bit blocks:  $t_{CLA} = t_{pg} + t_{pg\_block} + (N/k - 1)t_{AND\_OR} + kt_{FA}$

where

- $t_{pg}$  : delay of the column generate and propagate gates
- $t_{pg\_block}$  : delay of the block generate and propagate gates
- $t_{AND\_OR}$  : delay from  $C_{in}$  to  $C_{out}$  of the final AND/OR gate in the  $k$ -bit CLA block
- An  $N$ -bit carry-lookahead adder is generally much faster than a ripple-carry adder for  $N > 16$

# Prefix Adder

- Computes the carry in ( $C_{i-1}$ ) for each of the columns as fast as possible and then computes the sum:

$$S_i = (A_i \oplus B_i) \oplus C_i$$

- Computes  $G$  and  $P$  for 1-bit, then 2-bit blocks, then 4-bit blocks, then 8-bit blocks, etc. until the carry in (generate signal) is known for each column
- Has  $\log_2 N$  stages



# Prefix Adder

- A carry in is produced by being either *generated* in a column or *propagated* from a previous column.
- Define column -1 to hold  $C_{in}$ , so  $G_{-1} = C_{in}, P_{-1} = 0$
- Then, the carry in to col.  $i$  = the carry out of col.  $i-1$ :

$$C_{i-1} = G_{i-1:-1}$$

$G_{i-1:-1}$  is the generate signal spanning columns  $i-1$  to  $-1$ .

There will be a carry out of column  $i-1$  ( $C_{i-1}$ ) if the block spanning columns  $i-1$  through  $-1$  generates a carry.

- Thus, we rewrite the sum equation:  $S_i = (A_i \oplus B_i) \oplus G_{i-1:-1}$
- **Goal:** Compute  $G_{0:-1}, G_{1:-1}, G_{2:-1}, G_{3:-1}, G_{4:-1}, G_{5:-1}, \dots$  (These are called the *prefixes*)

# Prefix Adder


- The generate and propagate signals for a block spanning bits  $i:j$  are:

$$G_{i:j} = G_{i:k} + P_{i:k} G_{k-1:j}$$





$$P_{i:j} = P_{i:k} P_{k-1:j}$$

- In words, these prefixes describe that:
  - A block will generate a carry if the upper part ( $i:k$ ) generates a carry or if the upper part propagates a carry generated in the lower part ( $k-1:j$ ).
  - A block will propagate a carry if both the upper and lower parts propagate the carry.

# Prefix Adder Schematic

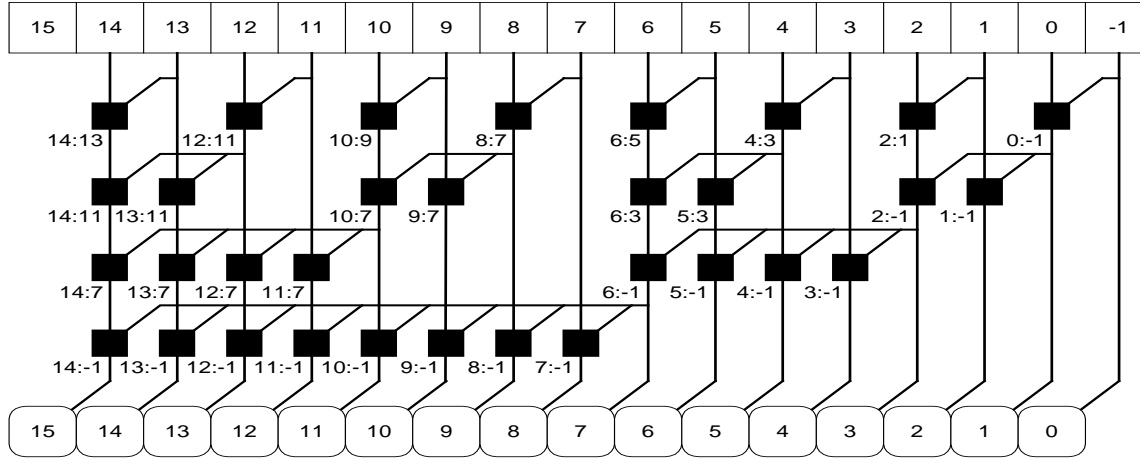

Legend

    

# Prefix Adder Delay

- The delay of an  $N$ -bit prefix adder is:

$$t_{PA} = t_{pg} + \log_2 N (t_{pg\_prefix}) + t_{XOR}$$

where

- $t_{pg}$  is the delay of the column generate and propagate gates (AND or OR gate)
- $t_{pg\_prefix}$  is the delay of the black prefix cell (AND-OR gate)

# Adder Delay Comparisons

- Compare the delay of 32-bit ripple-carry, carry-lookahead, and prefix adders. The carry-lookahead adder has 4-bit blocks. Assume that each two-input gate delay is 100 ps and the full adder delay is 300 ps.

# Adder Delay Comparisons

- Compare the delay of 32-bit ripple-carry, carry-lookahead, and prefix adders. The carry-lookahead adder has 4-bit blocks. Assume that each two-input gate delay is 100 ps and the full adder delay is 300 ps.


$$t_{\text{ripple}} = Nt_{FA} = 32(300 \text{ ps}) = 9.6 \text{ ns}$$

$$\begin{aligned} t_{CLA} &= t_{pg} + t_{pg\_block} + (N/k - 1)t_{AND\_OR} + kt_{FA} \\ &= [100 + 600 + (7)200 + 4(300)] \text{ ps} = 3.3 \text{ ns} \end{aligned}$$


$$\begin{aligned} t_{PA} &= t_{pg} + \log_2 N(t_{pg\_prefix}) + t_{XOR} \\ &= [100 + \log_2 32(200) + 100] \text{ ps} = 1.2 \text{ ns} \end{aligned}$$

# Comparator: Equality

## Symbol

 


## Implementation

 


# Comparator: Less Than

- Compare two numbers

 



# Arithmetic Logic Unit (ALU)

 


$F_{2:0}$	Function
000	A & B
001	A   B
010	A + B
011	not used
100	A & ~B
101	A   ~B
110	A - B
111	SLT





# Set Less Than (SLT) Example


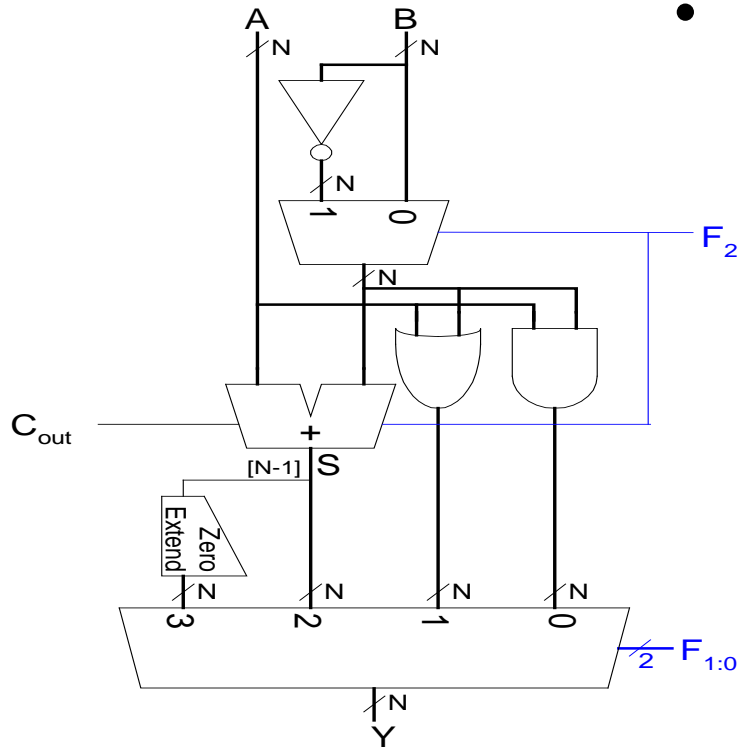


- Configure a 32-bit ALU for the set if less than (SLT) operation. Suppose  $A = 25$  and  $B = 32$ .
  - $F_2$  – A is less than B, so we expect Y to be the 32-bit representation of 1 (0x00000001).
  - For SLT,  $F_{2:0} = 111$ .
  - $F_2 = 1$  configures the adder unit as a subtracter. So  $25 - 32 = -7$ .
  - The two's complement representation of -7 has a 1 in the most significant bit, so  $S_{31} = 1$ .
  - With  $F_{1:0} = 11$ , the final multiplexer selects  $Y = S_{31}$  (zero extended) = 0x00000001.


# Shifters

- **Logical shifter:** shifts value to left or right and fills empty spaces with 0's
  - Ex:  $11001 \gg 2 = 00110$
  - Ex:  $11001 \ll 2 = 00100$
- **Arithmetic shifter:** same as logical shifter, but on right shift, fills empty spaces with the old most significant bit (msb).
  - Ex:  $11001 \ggg 2 = 11110$
  - Ex:  $11001 \lll 2 = 00100$
- **Rotator:** rotates bits in a circle, such that bits shifted off one end are shifted into the other end
  - Ex:  $11001 \text{ ROR } 2 = 01110$
  - Ex:  $11001 \text{ ROL } 2 = 00111$

# Shifter Design

  


# Shifter


 


$$\begin{aligned}
 y_i &= x_{i-1} \text{ if } E_n = 1, s = 1, \text{ and } d = L \\
 &= x_{i+1} \text{ if } E_n = 1, s = 1, \text{ and } d = R \\
 &= x_i \text{ if } E_n = 1, s = 0 \\
 &= 0 \text{ if } E_n = 0
 \end{aligned}$$

Can be implemented with a mux

 

# Barrel Shifter

 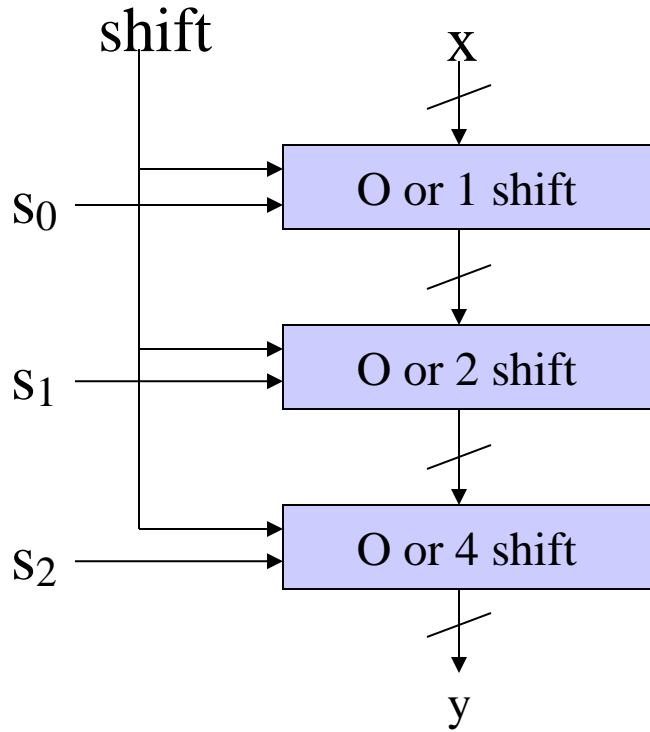



# Shifters as Multipliers and Dividers

- A left shift by  $N$  bits multiplies a number by  $2^N$ 
  - Ex:  $00001 \ll 2 = 00100$  ( $1 \times 2^2 = 4$ )
  - Ex:  $11101 \ll 2 = 10100$  ( $-3 \times 2^2 = -12$ )
- The arithmetic right shift by  $N$  divides a number by  $2^N$ 
  - Ex:  $01000 \ggg 2 = 00010$  ( $8 \div 2^2 = 2$ )
  - Ex:  $10000 \ggg 2 = 11100$  ( $-16 \div 2^2 = -4$ )

# Multipliers

- Steps of multiplication for both decimal and binary numbers:
  - Partial products are formed by multiplying a single digit of the multiplier with the entire multiplicand
  - Shifted partial products are summed to form the result

## Decimal

$$\begin{array}{r} 230 \\ \times 42 \\ \hline 460 \\ + 920 \\ \hline 9660 \end{array}$$

multiplicand  
multiplier  
partial  
products

result




$$230 \times 42 = 9660$$

## Binary

$$\begin{array}{r} 0101 \\ \times 0111 \\ \hline 0101 \\ 0101 \\ 0101 \\ + 0000 \\ \hline 0100011 \end{array}$$

$$5 \times 7 = 35$$

# 4 x 4 Multiplier

   

# Division Algorithm

- $Q = A/B$
- $R$ : remainder
- $D$ : difference

$$R = A$$

for  $i = N-1$  to 0

$$D = R - B$$

if  $D < 0$  then  $Q_i = 0, R' = R$       //  $R < B$

else                     $Q_i = 1, R' = D$       //  $R \geq B$

$$R = 2R'$$

# 4 x 4 Divider

