

# CSE 140 Lecture 14

## System Designs

CK Cheng

CSE Dept.

UC San Diego


# System Designs

- Introduction
- Components
- Spec
- Implementation

# Introduction

- Methodology
  - Approach with success stories.
  - Hierarchical designs with interface between the levels.
- Data Subsystem and Control Subsystem
  - For n-bit data, each operation takes n times or more in hardware complexity.
  - Data subsystem carries out the data operations and transports.
  - Control system sequences the data subsystem and itself.

# I. Introduction

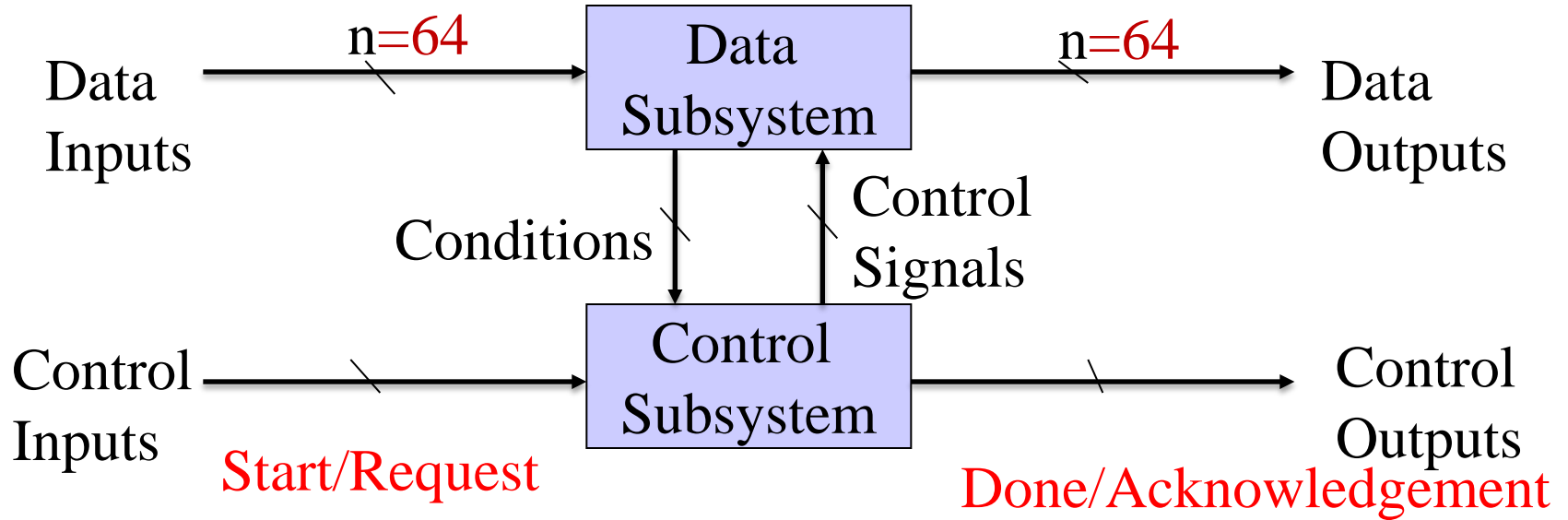

# Introduction

## Components

## Functions

Data  
Subsystem

Storage Modules  
Operators  
Interconnections

Data storage  
Data operations  
Data transport

Control  
Subsystem

Sequential machines

Control of data operations  
Control of data transports  
Control of the sequential system


# Data Subsystem Components

- Storage: Register, RAM, FIFO, LIFO, Counter, Shifter
- Operator: ALU, Floating Point Operators
- Interconnect: Wire, Buses, Crossbars

# Components: Storage Modules, Register

LD: Load


CLR: Clear

 

$$\begin{aligned} Q(t+1) &= (0, 0, \dots, 0) && \text{if } CLR = 1 \\ &= D && \text{if } LD = 1 \text{ and } CLR = 0 \\ &= Q(t) && \text{if } LD = 0 \text{ and } CLR = 0 \end{aligned}$$


# Storage Component: Registers, Array of Registers

Registers: If C then R  $\leftarrow$  D

 

Register Array: If C then R<sub>address</sub>  $\leftarrow$  D


Sharing connections and controls

 




# Storage Components: RAM, FIFO, LIFO

RAM

 


Size of RAM larger than registers  
Performance is slower


FIFO (First in first out)

 

LIFO (Last in first out:  
Stack)

 


# Modulo-n Counter

 

$$\begin{aligned} Q(t+1) &= (0, 0, \dots, 0) && \text{if CLR} = 1 \\ &= D && \text{if LD} = 1 \text{ and CLR} = 0 \\ &= (Q(t)+1) \bmod n && \text{if LD} = 0, \text{CNT} = 1 \text{ and CLR} = 0 \\ &= Q(t) && \text{if LD} = 0, \text{CNT} = 0 \text{ and CLR} = 0 \end{aligned}$$

$$\begin{aligned} \text{TC} &= 1 && \text{if } Q(t) = n-1 \text{ and CNT} = 1 \\ &= 0 && \text{otherwise} \end{aligned}$$

# Functional Modules

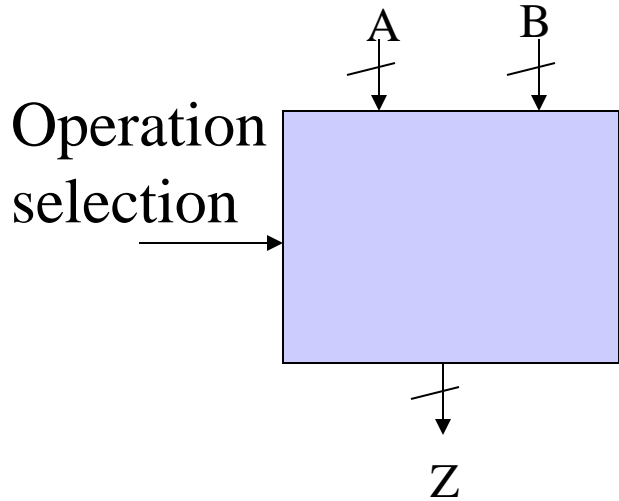

CASE Op-Sel Is

When F1,  $Z \leq A \text{ op1 } B$

When F2,  $Z \leq A \text{ op2 } B$

.

.

End CASE

Example:

CASE Op-Set Is

$Z \leq (A + B) \bmod 2^n$  if Op-Sel=addition,


$Z \leq (A - B) \bmod 2^n$  if Op-Sel=subtraction

End CASE


# Interconnect Modules (Wires and Switches)

- Single Lines
- Band of Wires
- Shared Buses
- Crossbar

 
## 1. Single line (shifting, time sharing)







## 2. Band of Wires (BUS)

 

## 3. Shared Bus

 


### Switches

    
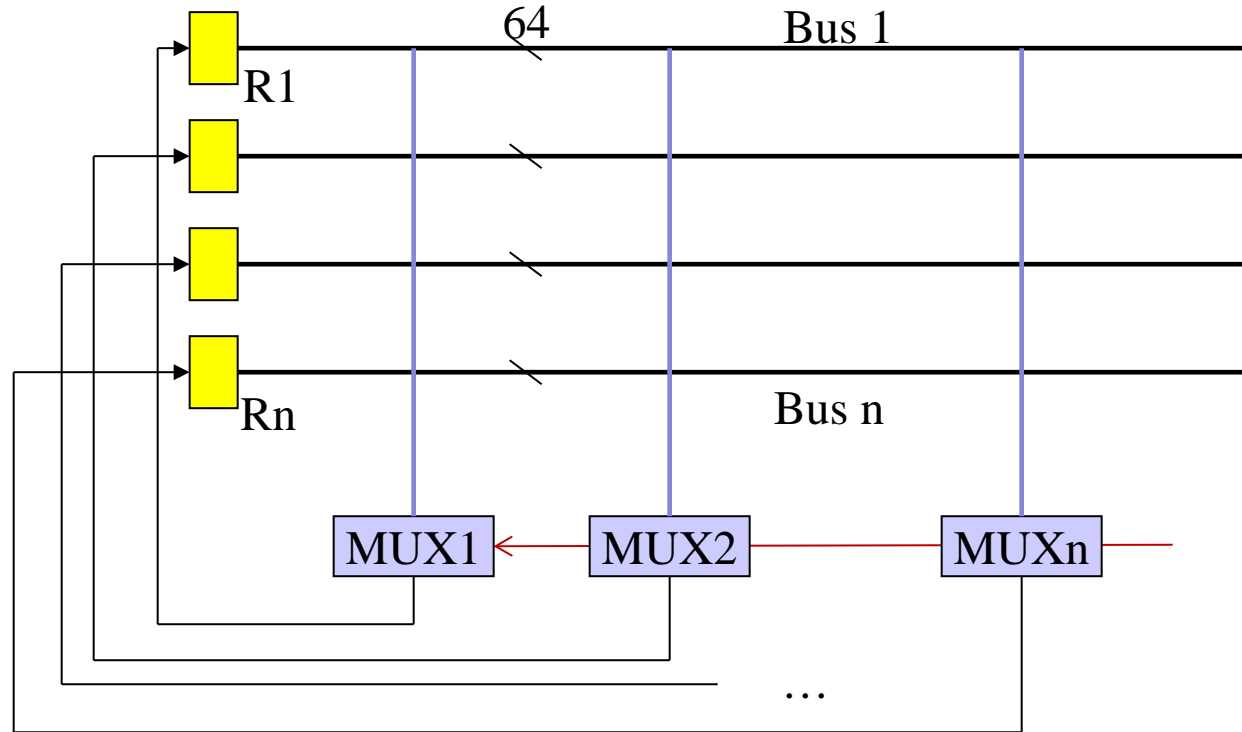
#### 4. Crossbar (Multiple buses running horizontally)

m simultaneous transfers are possible, but more expensive.



Program:

1. Objects (Registers, Outputs of combinational logic)
2. Operation (Logic, Add, Multiplication, DSP, and etc.)
3. Assignment
4. Sequencing

Example:

Signal S1, S2, R[15:0]:           FFs, Registers, wires


Z ← A + B:           Registers, Adder, Interconnect

R1 ← R2:           Registers and Interconnect


Begin, End:       Control

if ( ) then ( ), ENDIF: Control

 Ex. If C then  $R1 \leftarrow S1$   
 Else  $R2 \leftarrow S2$   
 Endif;



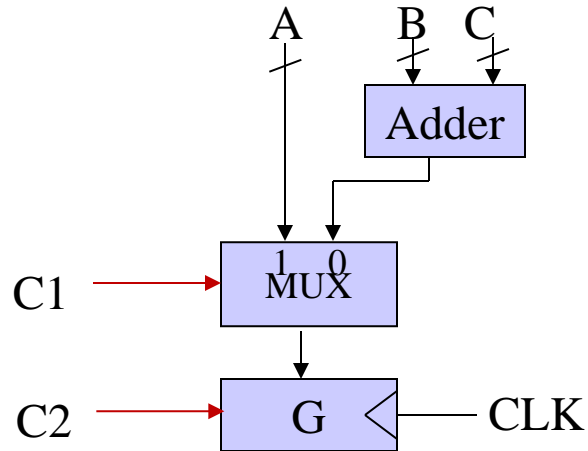If C1 then  $X \leftarrow A$   
 Else  $X \leftarrow B + C$   
 Endif  
 If C2 then  $G \leftarrow X$   
 Endif





# Implementation: Example

AddModule(X, Y, Z, start, done)

{ Input X[15:0], Y[15:0] type bit-vector,

start type boolean;

Local-Object A[15:0], B[15:0] type bit-vector;

Output Z[15:0] type bit-vector,

done type boolean;

S0: If start' goto S0 || done ← 1;


S1: A ← X || B ← Y || done ← 0;

S2: Z ← Add(A, B) || goto S0;

}

Exercise: Go through the handshaking, data subsystem and control subsystem designs.

# AddModule(X, Y, start, done)

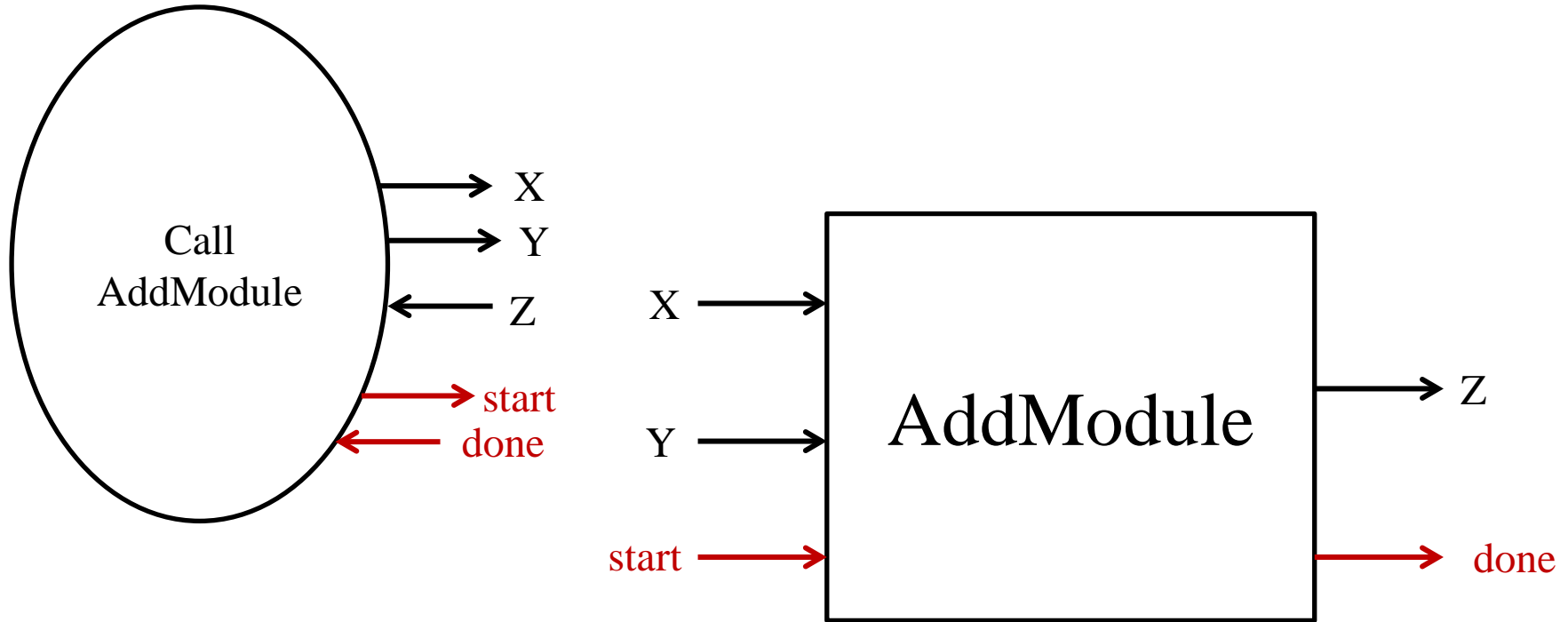

# Hand Shaking

