

CSE 140, Lecture 2
Combinational Logic
CK Cheng
CSE Dept.
UC San Diego

Combinational Logic Outlines

1. Introduction

1. Scope

2. Review of Boolean Algebra

3. Review: Laws/Theorems and Digital Logic


2. Specification

3. Synthesis

1.1 Combinational Logic: Scope

- Description
 - Language: e.g. C Programming, Verilog, VHDL
 - Boolean algebra
 - Truth table
- Design
 - Schematic Diagram
 - Inputs, Gates, Nets, Outputs
- Goal
 - Validity: correctness, turnaround time
 - Performance: power, timing, cost
 - Testability: yield, diagnosis, robustness

Scope: Boolean Algebra for Logic

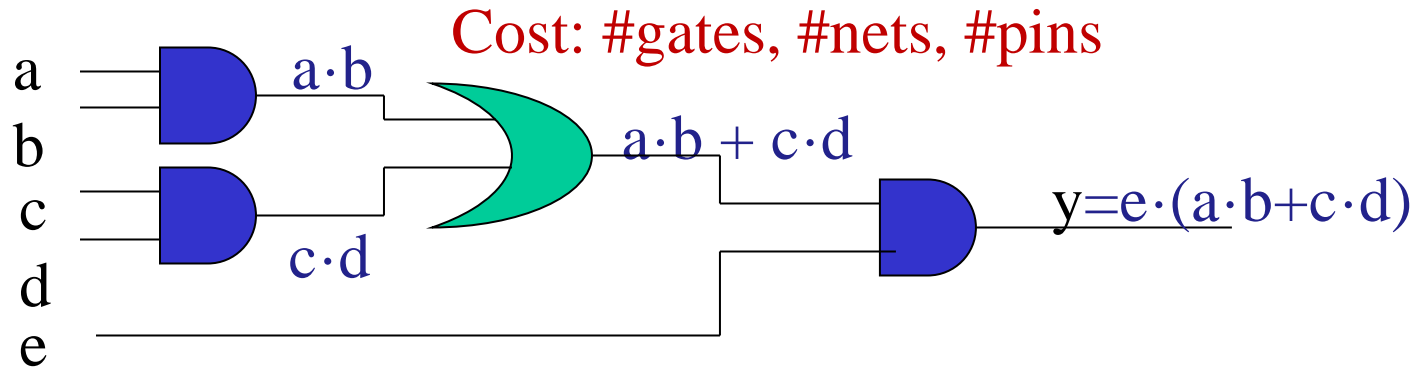

Schematic Diagram:

5 primary inputs

1 primary output

4 gates (3 ANDs, 1 OR)

9 signal nets

Boolean Algebra:

5 variables

1 expression

4 operators (3 ANDs, 1 OR)

5 literals

Scope: Boolean Algebra for Logic

Schematic Diagram:

5 primary inputs

4 components (gates)

9 signal nets

12 pins


A. #inputs

B. #gates

C. #nets

D. #pins

E. None

 

5 literals

4 operators

I. #operators

II. #literals + #operators

III. #literals + 2 #operators - 1

Schematic Diagram vs. Boolean Expression

- Boolean Expression: #literals, #operators
- Schematic Diagram: #gates, #nets, #pins
- One more example?

1.2 George Boole, 1815 - 1864


- Born to working class parents
- Taught himself mathematics and joined the faculty of Queen's College in Ireland.
- Wrote *An Investigation of the Laws of Thought* (1854)
- Introduced binary variables
- Introduced the three fundamental logic operations: AND, OR, and NOT



Scanned at the American
Institute of Physics

Switching Algebra

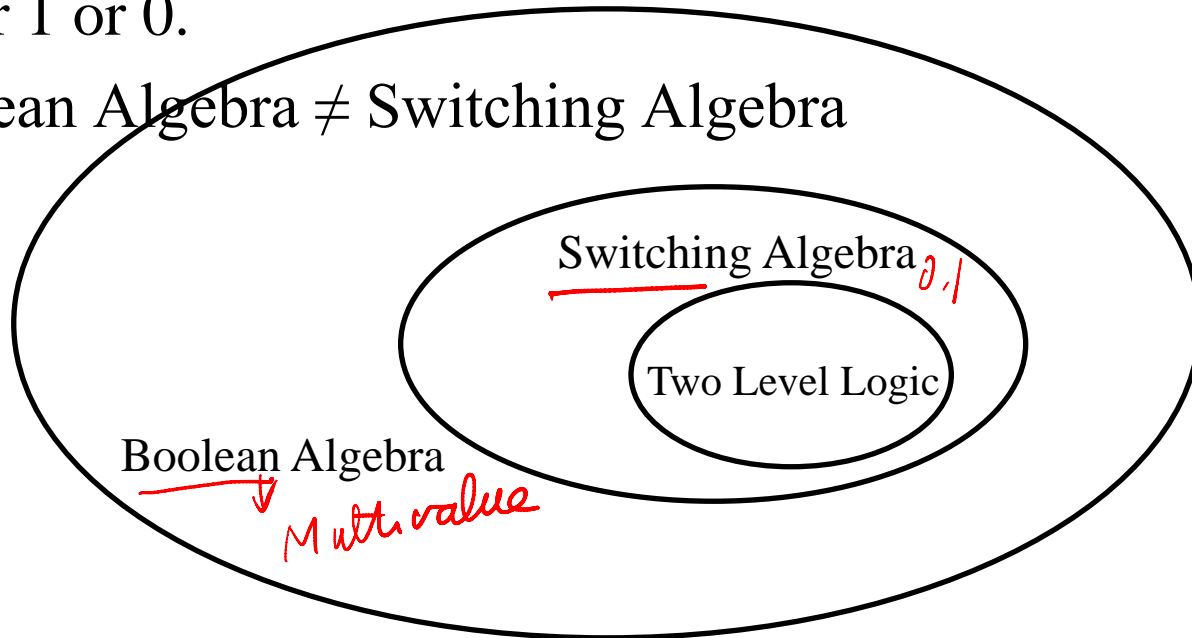- Boolean Algebra: multiple-valued logic, i.e. each variable have multiple values.
- Switching Algebra: binary logic, i.e. each variable can be either 1 or 0.
- Boolean Algebra \neq Switching Algebra



Scope: Binary Values

- Typically consider only two discrete values:
 - 1's and 0's
 - 1, TRUE, HIGH
 - 0, FALSE, LOW
- 1 and 0 can be represented by specific voltage levels, rotating gears, fluid levels, etc.
- Digital circuits usually depend on specific voltage levels to represent 1 and 0
- *Bit: Binary digit*

Switching Algebra


- Two Level Logic: Sum of products, or product of sums, e.g. $ab + a'c + a'b'$, $(a'+c)(a+b')(a+b+c')$
- Multiple Level Logic: Many layers of two level logic with some inverters, e.g. $((a+bc)'+ab')+b'c+c'd)bc+c'e$

Features of Digital Logic Design

- Multiple Outputs
- Don't care sets

Handy Tools:

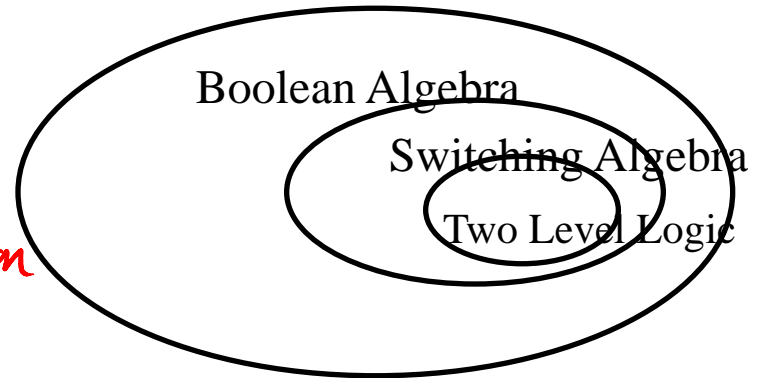- DeMorgan's Law: Complements } *Boolean*
- Consensus Theorem
- Shannon's Expansion } *0,1*
- Truth Table } *0,1 ⇒ Switching*
- Karnaugh Map (single output, two level logic) } *0,1*



Review of Boolean Algebra

Let B be a nonempty set with two 2-input operations, a 1-input operation $\bar{}$, and two distinct elements 0 and 1. Then B is called a Boolean algebra if the following axioms hold.

- Commutative laws: $a+b=b+a$, $a \cdot b=b \cdot a$
- Distributive laws: $a+(b \cdot c)=(a+b) \cdot (a+c)$,
 $a \cdot (b+c)=a \cdot b+a \cdot c$
- Identity laws: $a+0=a$, $a \cdot 1=a$
- Complement laws: $a+a'=1$, $a \cdot a'=0$

Duality
(0,1) (AND OR)
 $a \rightarrow a'$
Complement (one only one)



1.3 Boolean algebra and switching functions:

Operators and Digital Logic Gates

Two-input operator

AND (\wedge, \cdot)

AND		A	B	Y
		0	0	0
		0	1	0
		1	0	0
		1	1	1

  

0 dominates in AND



0 blocks the output

1 passes signal A

Two-input operator

OR ($\vee, +$)

OR		A	B	Y
		0	0	0
		0	1	1
		1	0	1
		1	1	1

  

1 dominates in OR

1 blocks the output

0 passes signal A

One-input operator

NOT (Complement, $\bar{}$)

NOT	A	Y
	0	1
	1	0

Review: Laws and Digital Logic

1. Identity

$$A * 1 = A$$

$$A + 1 = 1$$

$$A * 0 = 0$$

$$A + 0 = A$$



2. Complement

$$A + A' = 1$$



$$A * A' = 0$$

T8. Distributive Law

$$A(B+C) = AB + AC$$

  



$$A+BC = (A+B)(A+C)$$

  



Review: Laws and Digital Logic

T7. Associativity

$$(A+B) + C = A + (B+C)$$

  


$$(AB)C = A(BC)$$

  


DeMorgan's Theorem and Digital Logic

T12. DeMorgan's Theorem $(A+B)' = A'B'$ $(AB)' = A' + B'$

- $Y = (AB)' = A' + B'$

 


- $Y = (A + B)' = A'B'$

 

DeMorgan's Theorem: Bubble Pushing

 - Pushing bubbles backward (from the output) or forward (from the inputs) changes the body of the gate from AND to OR or vice versa.
- Pushing a bubble from the output back to the inputs puts bubbles on all gate inputs.



- Pushing bubbles on *all* gate inputs forward toward the output puts a bubble on the output and changes the gate body.

Consensus Theorem

- $AB+AC+B'C$

$$=AB+B'C$$

- $(A+B)(A+C)(B'+C)$

$$=(A+B)(B'+C)$$



The consensus of AB , $B'C$ is: ?

Exercise: to prove the reduction using

- (1) Venn Diagrams,
- (2) Boolean algebra,
- (3) Logic simulation and
- (4) Shannon's expansion

Consensus Theorem: Venn Diagrams

$$AB+AC+B'C : AB+B'C$$

  

Consensus Theorem: Boolean Algebra

$$\begin{aligned} & \bullet \underline{AB+AC+B'C} \\ & = AB+B'C \\ & AB+AC+B'C \\ & = AB+AC1+B'C \\ & = AB+AC(B+B')+B'C \\ & = AB+ABC+AB'C+B'C \\ & = AB(1+C)+(A+1)B'C \\ & = AB+B'C \end{aligned}$$

$$\begin{aligned} & \bullet (A+B)(A+C)(B'+C) \\ & = (A+B)(B'+C) \end{aligned}$$

$$\begin{aligned} f(a,b,c) &= Bf(A,0,c) + B'f(A,1,c) \\ &= \cancel{BA} + \cancel{B'C} \\ &= \underline{AB} + \underline{B'C} \end{aligned}$$

Consensus Theorem: Logic Simulation

$$f(A,B,C) = AB + AC + B'C$$

$$g(A,B,C) = AB + B'C$$

Index	A	B	C	AB	AC	B'C	f	g
0	0	0	0	0	0	0		
1	0	0	1	0	0	1		
2	0	1	0	0	0	0		
3	0	1	1	0	0	0		
4	1	0	0	0	0	0		
5	1	0	1	0	1	1		
6	1	1	0	1	0	0		
7	1	1	1	1	1	0		

Shannon's Expansion

- Shannon's expansion assumes a switching algebra system
- Divide a switching function into smaller functions
- Pick a variable x , partition the switching function into two cases: $x=1$ and $x=0$
 - $f(x,y,z,\dots) = xf(x=1,y,z,\dots) + x'f(x=0,y,z,\dots)$
- For example
 - $f(x) = xf(1) + x'f(0)$
 - $f(x,y) = xf(1,y) + x'f(0,y)$

Shannon's Expansion: Example

$$f(x,y,z)=xf(?,y,z)+x'f(?',y,z)$$

A. $?=0$

B. $?=1$.

$$f(x,y)=(x+f(?,y))(x'+f(?',y))$$

- A. $?=0$
- B. $?=1$.

Shannon's Expansion

- Decompose the switching function into minterms

$$f(x, y) = xf(1, y) + x'f(0, y)$$

$$= x(yf(1,1) + y'f(1,0)) + x'(y(f(0,1) + y'f(0,0)))$$

$$= xyf(1,1) + xy'f(1,0) + x'yf(0,1) + x'y'f(0,0).$$

- Decompose the switching function into maxterms

$$f(x, y) = (x' + f(1, y))(x + f(0, y))$$

$$= (x' + (y' + f(1,1))(y + f(1,0)))(x + (y' + f(0,1))(y + f(0,0)))$$

$$= (x' + y' + f(1,1))(x' + y + f(1,0))(x + y' + f(0,1))(x + y + f(0,0))$$

Shannon's Expansion: Example

Which term in $AB' + AC + BC$ can be deleted?

A. AB'

B. AC

C. BC

D. None of the above

Review Summary: Switching Algebra and Karnaugh Map

Shannon's expansion and consensus theorem are used for logic optimization

- Shannon's expansion divides the problem into smaller functions
- Consensus theorem finds common terms when we merge small functions
- Karnaugh map mimics the above two operations in two dimensional space as a visual aid.

Part I. Combinational Logic

II) Specification

1. Language

2. Boolean Algebra

Canonical Expression: Sum of minterms and
Product of maxterms

3. Truth Table

4. Incompletely Specified Function

II. Specification

Decimal Addition

$$\begin{array}{r} 5 \\ + 7 \\ \hline \end{array}$$

→ **1** 2 ←

Carry Sum

Binary Addition

$$\begin{array}{r} 1 \quad 1 \quad 1 \\ \quad 1 \quad 0 \quad 1 \\ + \quad 1 \quad 1 \quad 1 \\ \hline \end{array}$$

→ **1** 1 0 ←


Carryout Sums

← Carry bits
5
7
12

Binary Addition: Hardware

- Half Adder: Two inputs (a,b) and two outputs (carry, sum).
- Full Adder: Three inputs (a,b, c_{in}) and two outputs (carry, sum).

Half Adder

 

Truth Table

a	b	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Switching Function

Switching Expressions:

$$\text{Sum (a,b)} = a' \cdot b + a \cdot b'$$



$$\text{Carry (a, b)} = a \cdot b$$

Ex:


$$\text{Sum (0,0)} = 0' \cdot 0 + 0 \cdot 0' = 0 + 0 = 0$$

$$\text{Sum (0,1)} = 0' \cdot 1 + 0 \cdot 1' = 1 + 0 = 1$$
  
$$\text{Sum (1,1)} = 1' \cdot 1 + 1 \cdot 1' = 0 + 0 = 0$$



Full Adder

 

Truth Table

Id	a	b	c_{in}	carry	sum
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

Minterm and Maxterm

Id	a	b	c	carryout	
0	0	0	0	0	$a+b+c$
1	0	0	1	0	$a+b+c'$
2	0	1	0	0	$a+b'+c$
3	0	1	1	1	$a' b c$
4	1	0	0	0	$a'+b+c$
5	1	0	1	1	$a b' c$
6	1	1	0	1	$a b c'$
7	1	1	1	1	$a b c$

\swarrow
 maxterm

Minterms

$$f_1(a,b,c) = a'bc + ab'c + abc' + abc$$

$$a'bc = 1 \text{ iff } (a,b,c) = (0,1,1)$$

$$ab'c = 1 \text{ iff } (a,b,c) = (1,0,1)$$

$$abc' = 1 \text{ iff } (a,b,c) = (1,1,0)$$

$$abc = 1 \text{ iff } (a,b,c) = (1,1,1)$$

$$f_1(a,b,c) = 1 \text{ iff } (a,b,c) = (0,1,1), (1,0,1), (1,1,0), \text{ or } (1,1,1)$$

Ex: $f_1(1,0,1) = 1'01 + 10'1 + 101' + 101 = 1$

$$f_1(1,0,0) = 1'00 + 10'0 + 100' + 100 = 0$$

Maxterms

$$f_2(a,b,c) = (a+b+c)(a+b+c')(a+b'+c)(a'+b+c)$$

$$a + b + c = 0 \text{ iff } (a,b,c) = (0,0,0)$$

$$a + b + c' = 0 \text{ iff } (a,b,c) = (0,0,1)$$

$$a + b' + c = 0 \text{ iff } (a,b,c) = (0,1,0)$$

$$a' + b + c = 0 \text{ iff } (a,b,c) = (1,0,0)$$

$$f_2(a,b,c) = 0 \text{ iff } (a,b,c) = (0,0,0), (0,0,1), (0,1,0), (1,0,0)$$

$$\text{Ex: } f_2(1,0,1) = (1+0+1)(1+0+1')(1+0'+1)(1'+0+1) = 1$$

$$f_2(0,1,0) = (0+1+0)(0+1+0')(0+1'+0)(0'+1+0) = 0$$

$$f_1(a,b,c) = a'bc + ab'c + abc' + abc$$

$$f_2(a,b,c) = (a+b+c)(a+b+c')(a+b'+c)(a'+b+c)$$

$$f_1(a, b, c) = m_3 + m_5 + m_6 + m_7 = \Sigma m(3,5,6,7)$$

$$f_2(a, b, c) = M_0M_1M_2M_4 = \Pi M(0, 1, 2, 4)$$

iClicker: Does $f_1 = f_2$?

A. Yes

B. No.

The coverage of a single minterm. e.g. $m_4 = ab'c'$

Id	a	b	c_{in}	carry	minterm $_4 = ab'c'$
0	0	0	0	0	0
1	0	0	1	0	0
2	0	1	0	0	0
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	0

Only one row has a 1.

The coverage of a single maxterm. E.g. $M_4 = a'+b+c$

Id	a	b	c_{in}	carry	maxterm 4 = $a+b+c$
0	0	0	0	0	1
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	1
4	1	0	0	0	0
5	1	0	1	1	1
6	1	1	0	1	1
7	1	1	1	1	1

Only one row has a 0.

Incompletely Specified Function

Don't care set is important because it allows us to minimize the function

Id	a	b	f(a, b)
0	0	0	1
1	0	1	0
2	1	0	1
3	1	1	-

- 1) The input does not happen.
- 2) The input happens, but the output is ignored.

Examples:

- Decimal number 0... 9 uses 4 bits. (1,1,1,1) does not happen.
- Final carry out bit (output is ignored).

Incompletely Specified Function

Id	a	b	c	$g(a,b,c)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	-
3	0	1	1	1
4	1	0	0	1
5	1	0	1	-
6	1	1	0	0
7	1	1	1	1

$$\begin{aligned}
 g_1(a,b,c) &= a'b'c + a'bc + ab'b' + abc \\
 &= m_1 + m_3 + m_4 + m_7 \\
 &= \sum m(1,3,4,7)
 \end{aligned}$$

$$\begin{aligned}
 g_2(a,b,c) &= (a+b+c)(a'+b'+c) \\
 &= M_0 M_6 \\
 &= \prod M(0,6)
 \end{aligned}$$

Exercise: Does $g_1(a,b,c) = g_2(a,b,c)$?