

# CSE 140: Components and Design Techniques for Digital Systems

## Lecture 3: Incompletely Specified Functions and K Maps

CK Cheng

Dept. of Computer Science and Engineering  
University of California, San Diego

# Outlines

- Definitions
  - Minterms and Maxterms
  - Incompletely Specified Function
- Implementation: Boolean Algebra vs Map
- Karnaugh Maps: Two Dimensional Truth Table
  - 2-Variable Map
  - 3-Variable Map
  - Up to 6-Variable Map

# Definitions

- Literals  $x_i$  or  $x_i'$
- Product Term  $x_2 x_1' x_0'$
- Sum Term  $x_2 + x_1' + x_0$
- Minterm of  $n$  variables: A product of  $n$  literals in which every variable appears **exactly** once.
- Maxterm of  $n$  variables: A sum of  $n$  literals in which every variable appears **exactly** once.
- Adjacency: Two minterms are adjacent if they differ by only one variable.

# Definitions

- Minterm of  $n$  variables: A product of  $n$  literals in which every variable appears **exactly** once.
  - E.g. For function  $f(a,b,c,d,e)$ ,  $abcde$ ,  $a'b'c'de$  are minterms, while  $bcd$ ,  $a'bcd$  are not.
- Maxterm of  $n$  variables: A sum of  $n$  literals in which every variable appears **exactly** once.
- Adjacency: Two minterms are adjacent if they differ by only one variable.
  - E.g.  $abcde$  and  $a'bcde$  are adjacent, while  $a'b'cde$  and  $abc'd'e'$  are not

# iClicker

For two terms  $ab'c'd'$  and  $ab'cd'$ , are they adjacent?

A. Yes

B. No

Adjacency allows us to merge the terms to reduce the Boolean expression.

# Incompletely Specified Function

- Situations where the output of a switching function can be either 0 or 1 for a particular combination of inputs
- This is specified by a don't care in the truth table

Id	a	b	f(a, b)
0	0	0	1
1	0	1	0
2	1	0	1
3	1	1	X (don't care)

For example:

- 1) The input pattern does not happen.
- 2) The input pattern happens, but the output is ignored.

Example:

-Decimal number 0... 9 uses 4 bits. (1,1,1,1) does not happen.

How to completely specify the truth table in canonical form?

We have three types of output which divides the input space into three sets:

Onset  $\mathcal{F}$ : All the input conditions for which the output is 1

Offset  $\mathcal{R}$ : All the input conditions for which the output is 0

Don't care  $\mathcal{D}$ : All the input conditions for which the output is a 'don't care'

Example: The truth table on right has

$\mathcal{F}$  covers input pattern  $(a,b)=(1,0)$

$\mathcal{R}$  covers input patterns  $(a,b)=(0,0)$  and  $(1,1)$

$\mathcal{D}$  covers input pattern  $(a,b)=(0,1)$

**The union of  $\mathcal{F}$ ,  $\mathcal{R}$ ,  $\mathcal{D}$  is the whole set of all input patterns.**

Id	a	b	F(a,b)
0	0	0	0
1	0	1	X
2	1	0	1
3	1	1	0

# Reducing Incompletely Specified Functions

iClicker Q: Which of the following assignment would result in an implementation with the fewest gates?

Id	a	b	F(a,b)
0	0	0	0
1	0	1	0
2	1	0	1
3	1	1	X

- A.  $F(1,1)=1$
- B.  $F(1,1)=0$
- C. Neither A or B
- D. Both A and B



# Reducing Incompletely Specified Functions

Don't care set is important because it allows us to minimize the function

Id	a	b	F(a,b)
0	0	0	0
1	0	1	0
2	1	0	1
3	1	1	1

$$F(a,b)=a$$

# Implementation

- Specification → Schematic Diagram  
Net list,  
Switching expression
- Obj min cost → Search in solution space  
(max performance)
- Cost: wires, gates → Literals, product terms,  
sum terms

For two level logic (sum of products or product of sums), we want to minimize # of terms, and # of literals

# Implementation: Specification $\Rightarrow$ Logic Diagram

## Karnaugh Map: A 2-dimensional truth table

Flow 1:

1. Specification
2. Truth table
3. Sum of products (SOP) or product of sums(POS) canonical form
4. Reduced expression using Boolean algebra
5. Schematic diagram of two level logic

Flow 2:

1. Specification
2. Truth Table
3. Karnaugh Map (truth table in two dimensional space)
4. Reduce using K'Maps
5. Reduced expression (SOP or POS)
6. Schematic diagram of two level logic

# Truth Table vs. Karnaugh Map

2-variable function,  $f(A,B)$

ID	A	B	$f(A,B)$
0	0	0	$f(0,0)$
1	0	1	$f(0,1)$
2	1	0	$f(1,0)$
3	1	1	$f(1,1)$

	B=0	B=1
A=0	$f(0,0)$	$f(0,1)$
A=1	$f(1,0)$	$f(1,1)$

# Truth Table

An example of 2-variable function,  $f(A,B)$

ID	A	B	$f(A,B)$	minterm
0	0	0	0	
1	0	1	1	$A'B$
2	1	0	1	$AB'$
3	1	1	1	$AB$

Function can be represented by sum of minterms:

$$f(A,B) = A' B + AB' + AB$$

This is not optimal however!

We want to minimize the number of literals and terms.

To minimize the number of literals and terms.

We factor out common terms –

$$\begin{aligned} & A' B + AB' + AB \\ &= A' B + AB' + AB + AB \\ &= (A' + A)B + A(B' + B) = B + A \end{aligned}$$

Hence, we have

$$f(A,B) = A + B$$

# How can we guarantee the most reduced expression was reached?

- Boolean expressions can be minimized by combining terms
- K-maps minimize equations graphically

ID	A	B	f(A,B)
0	0	0	f(0,0)
1	0	1	f(0,1)
2	1	0	f(1,0)
3	1	1	f(1,1)

	B=0	B=1
A=0	$A'B'$	$A'B$
A=1	$AB'$	$AB$



# K-Map: Truth Table in 2 Dimensions

ID	A	B	f(A,B)
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	1

	B = 0	B = 1
A = 0	0 0	1 1
A = 1	2 1	3 1

# K-Map: Truth Table in 2 Dimensions

ID	A	B	f(A,B)
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	1

	B = 0	B = 1	
A = 0	0 0	1 1	←
A = 1	2 1	3 1	


$$f(A,B) = A + B$$

# Two Variable K-maps

Id	a	b	f (a, b)
0	0	0	f (0, 0)
1	0	1	f (0, 1)
2	1	0	f (1, 0)
3	1	1	f (1, 1)

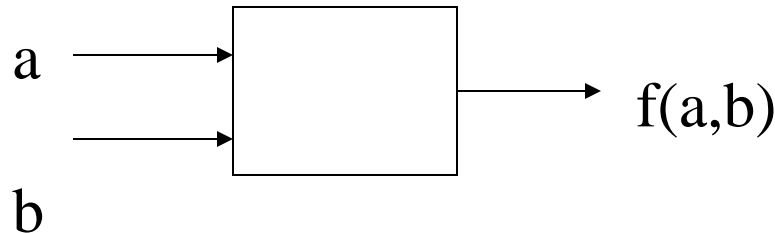
**# possible 2-variable functions:**

For 2 variables as inputs, we have  $4=2^2$  entries. Each entry can be 0 or 1. Thus we have  $16=2^4$  possible functions.


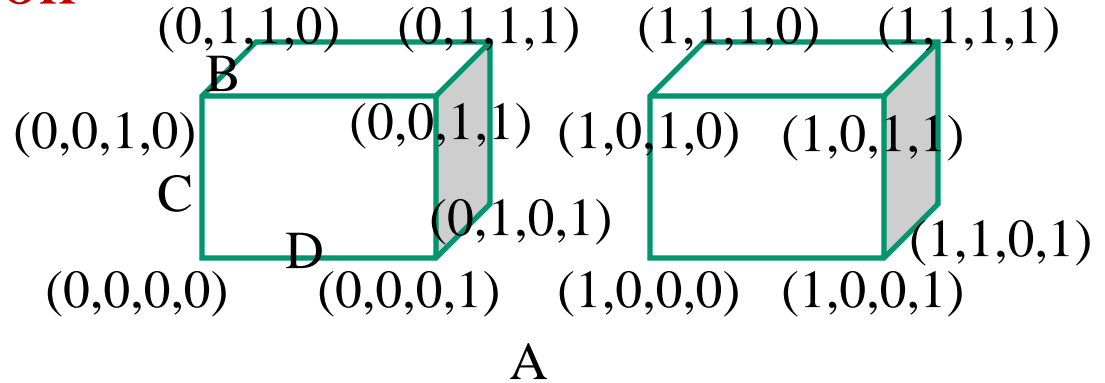
# Representation of k-Variable Func.

- Boolean Expression
- Truth Table
- Cube
- K Map
- Binary Decision Diagram




A cube of 4 variables: (A,B,C,D)

# Truth table

Id	a	b	c	f(a,b,c)
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	0

# Corresponding three variable K-map

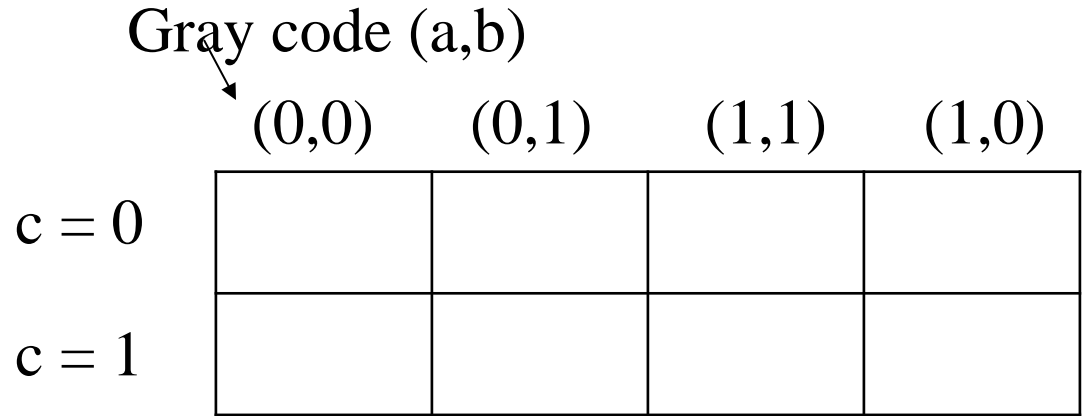

# Karnaugh Maps (K-Maps)

- K-maps minimize equations graphically
- Note that the label decides the order in the map

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	0	0	0

		AB			
		00	01	11	10
C	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
	1	$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

# K-map

- Circle 1's in adjacent squares
- Find rectangles which correspond to product terms in Boolean expression

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	0	0	0

$$y(A,B,C) = A' B' C' + A' B' C = A' B' (C' + C) = A' B'$$

# Another 3-Input truth table

Id	a	b	c	f(a,b,c)
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	X
7	1	1	1	1

# Corresponding K-map

	(0,0)	(0,1)	(1,1)	(1,0)
c = 0	<sup>0</sup> 0	<sup>2</sup> 1	<sup>6</sup> X	<sup>4</sup> 1
c = 1	<sup>1</sup> 0	<sup>3</sup> 0	<sup>7</sup> 1	<sup>5</sup> 1



# Another 3-Input truth table

Id	a	b	c	f(a,b,c)
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	X
7	1	1	1	1

# Corresponding K-map

		$b = 1$			
		(0,0)	(0,1)	(1,1)	(1,0)
$c = 0$		0 0	1 1	X X	1 1
$c = 1$		1 0	3 0	7 1	5 1
		$a = 1$			

$$f(a,b,c) = a + bc'$$

### 3 Input Truth table with Don't cares

Id	a	b	c	f (a,b,c,d)
0	0	0	0	1
1	0	0	1	1
2	0	1	0	X
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	0

### Corresponding K-map

	(0,0)	(0,1)	(1,1)	(1,0)
c = 0	0 1	2 X	6 0	4 1
c = 1	1 1	3 0	7 0	5 1

PIQ: In the above case the minimal Boolean expression is obtained when the don't care term is:

- A. Included i.e. Circled in with one or more minterms that evaluate to 1
- B. Excluded when grouping the minterms that evaluate to one

### 3 Input Truth table with Don't cares

Id	a	b	c	f(a,b,c,d)
0	0	0	0	1
1	0	0	1	1
2	0	1	0	X
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	0

### Corresponding K-map

	(0,0)	(0,1)	(1,1)	(1,0)
c = 0	0 1	2 X	6 0	4 1
c = 1	1 1	3 0	7 0	5 1

PIQ: In the above case the minimal Boolean expression is obtained when the don't care term is:

- A. Included i.e. Circled in with one or more minterms that evaluate to 1
- B. Excluded when grouping the minterms that evaluate to one

### 3 Input Truth table with Don't cares

Id	a	b	c	f(a,b,c,d)
0	0	0	0	1
1	0	0	1	1
2	0	1	0	X
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	0
7	1	1	1	0

### Corresponding K-map

		$b = 1$			
		(0,0)	(0,1)	(1,1)	(1,0)
$c = 0$		0 1	2 X	6 0	4 1
$c = 1$		1 1	3 0	7 0	5 1
		$a = 1$			

$$f(a,b,c) = b'$$

# Proof of Consensus Theorem using K Maps

Consensus Theorem:  $A' B + AC + BC = A' B + AC$

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Y C	AB			
	00	01	11	10
0	0	1	0	0
1	0	1	1	1

Y C	AB			
	00	01	11	10
0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
1	$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$