

# CSE 140: Components and Design Techniques for Digital Systems

## Lecture 7: Sequential Networks

CK Cheng

Dept. of Computer Science and Engineering

University of California, San Diego


# What is a sequential circuit?

“A circuit whose output depends on current inputs and past outputs”

“A circuit with **memory**”

Memory  $\Rightarrow$  Time

# Part II. Sequential Networks

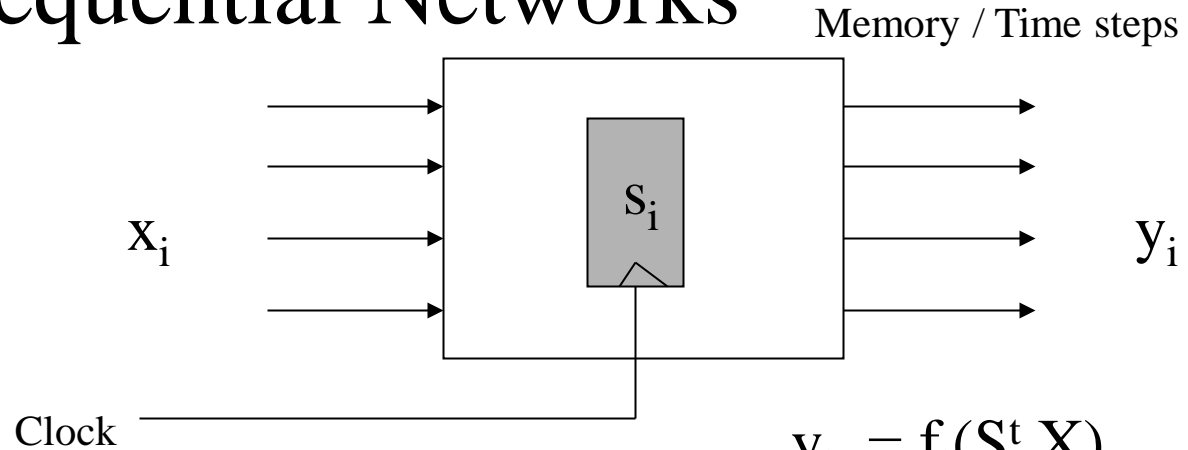

$$y_i = f_i(S^t, X)$$
$$s_i^{t+1} = g_i(S^t, X)$$

Memory: Flip flops

Specification: Finite State Machines

Implementation: Excitation Tables

Main Theme: Timing

Present time =  $t$  and next time =  $t+1$

Timing constraints to separate the present and next times.


# Sequential Networks

- Memory Components
  - Hierarchy of Memory
  - Basic Mechanism of Memory
  - Types of Flip-Flops
- Implementation
  - Finite State Machine

# Memory Hierarchy

- What are registers made of?

Flip-Flops, Latches


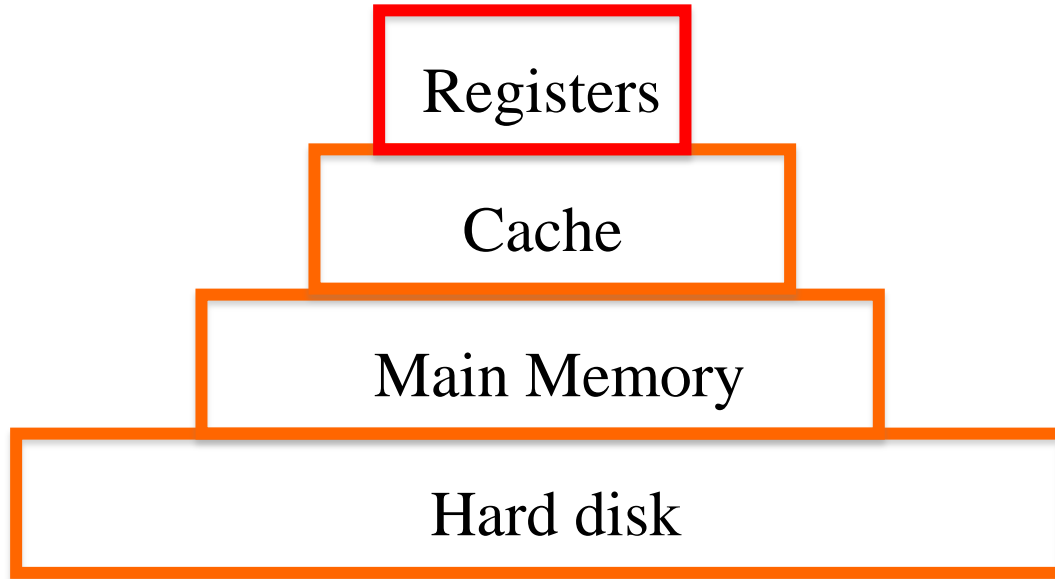


# The usage of a sequential machine

iClicker Question:

- A. Digital systems are implemented using sequential machines.
- B. Only a small subset of digital systems can be implemented using sequential machines.
- C. Sequential machines are too simple for complicated digital systems.



# Fundamental Memory Mechanism

  

# Memory Mechanism: Capacitive Load

- Fundamental building block of sequential circuits
- Two outputs:  $Q$ ,  $\bar{Q}$
- There is a feedback loop!
  - In a typical combinational logic, there is no feedback loop.


- No inputs

  


 
# Capacitive Loads

- Consider the two possible cases:
  - $Q = 0$ : then  $Q' = 1$  and  $Q = 0$  (consistent)
  - $Q = 1$ : then  $Q' = 0$  and  $Q = 1$  (consistent)
  - Bistable circuit stores 1 bit of state in the state variable,  $Q$  (or  $Q'$ )
  - Hold the value due to capacitive charges and feedback loop strengthening
- But there are **no inputs to control the state**



# iClicker

Q. Given a memory component made out of a loop of inverters, the number of inverters in the loop has to be

A. Even



B. Odd

# Flight attendant call button


- Flight attendant call button
  - Press call: light turns on
    - *Stays on* after button released
  - Press cancel: light turns off
  - Logic gate circuit to implement this?

- SR latch implementation

  
- Call=1 : sets Q to 1 and keeps it at 1
- Cancel=1 : resets Q to 0



1. Call button pressed – light turns on

 

 
2. Call button released – light *stays on*



3. Cancel button pressed – light turns off

# SR (Set/Reset) Latch


- SR Latch

 


- Consider the four possible cases:
  - $S = 1, R = 0$
  - $S = 0, R = 1$
  - $S = 0, R = 0$
  - $S = 1, R = 1$

# SR Latch Analysis

–  $S = 1, R = 0$ :

 


–  $S = 0, R = 1$ :

 

 
# SR Latch Analysis

–  $S = 1, R = 0$ : then  $Q = 1$  and  $\bar{Q} = 0$




 –  $S = 0, R = 1$ : then  $Q = 0$  and  $\bar{Q} = 1$




# SR Latch Analysis

–  $S = 1, R = 1$ :

 

# SR Latch Analysis



–  $S = 0, R = 0$ :

 




  
# SR Latch Analysis

–  $S = 0, R = 0$ : then  $Q = Q_{prev}$   
 $Q_{prev} = 0$



 –  $S = 1, R = 1$ : then  $Q = 0$  and  $Q = 0$



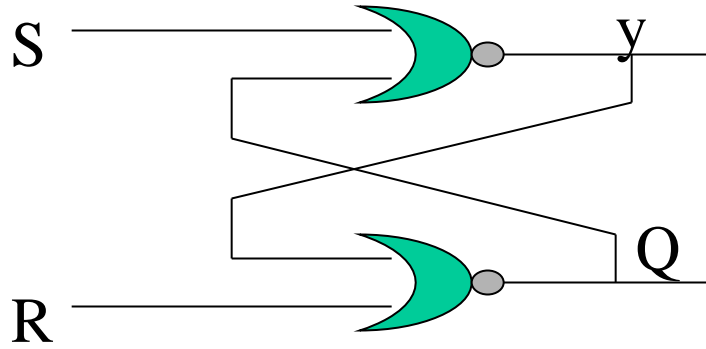


$$y = (S+Q)'$$

$$Q = (R+y)'$$

# SR Latch

SR F-F (Set-Reset)

 


Inputs: S, R


State: (Q, y)

| Id | Q(t) | y(t) | S | R | Q(t <sub>1</sub> ) | y(t <sub>1</sub> ) | Q(t <sub>2</sub> ) | y(t <sub>2</sub> ) | Q(t <sub>3</sub> ) | y(t <sub>3</sub> ) |
|----|------|------|---|---|--------------------|--------------------|--------------------|--------------------|--------------------|--------------------|
| 0  | 0    | 0    | 0 | 0 | 1                  | 1                  | 0                  | 0                  | 1                  | 1                  |
| 1  | 0    | 0    | 0 | 1 | 0                  | 1                  | 0                  | 1                  | 0                  | 1                  |
| 2  | 0    | 0    | 1 | 0 | 1                  | 0                  | 1                  | 0                  | 1                  | 0                  |
| 3  | 0    | 0    | 1 | 1 | 0                  | 0                  | 0                  | 0                  | 0                  | 0                  |
| 4  | 0    | 1    | 0 | 0 | 0                  | 1                  | 0                  | 1                  | 0                  | 1                  |
| 5  | 0    | 1    | 0 | 1 | 0                  | 1                  | 0                  | 1                  | 0                  | 1                  |
| 6  | 0    | 1    | 1 | 0 | 0                  | 0                  | 1                  | 0                  | 1                  | 0                  |
| 7  | 0    | 1    | 1 | 1 | 0                  | 0                  | 0                  | 0                  | 0                  | 0                  |
| 8  | 1    | 0    | 0 | 0 | 1                  | 0                  | 1                  | 0                  | 1                  | 0                  |
| 9  | 1    | 0    | 0 | 1 | 0                  | 0                  | 0                  | 1                  | 0                  | 1                  |
| 10 | 1    | 0    | 1 | 0 | 1                  | 0                  | 1                  | 0                  | 1                  | 0                  |
| 11 | 1    | 0    | 1 | 1 | 0                  | 0                  | 0                  | 0                  | 0                  | 0                  |
| 12 | 1    | 1    | 0 | 0 | 0                  | 0                  | 1                  | 1                  | 0                  | 0                  |
| 13 | 1    | 1    | 0 | 1 | 0                  | 0                  | 0                  | 1                  | 0                  | 1                  |
| 14 | 1    | 1    | 1 | 0 | 0                  | 0                  | 1                  | 0                  | 1                  | 0                  |
| 15 | 1    | 1    | 1 | 1 | 0                  | 0                  | 0                  | 0                  | 0                  | 0                  |

## State diagram

 

Present **Transition** Next

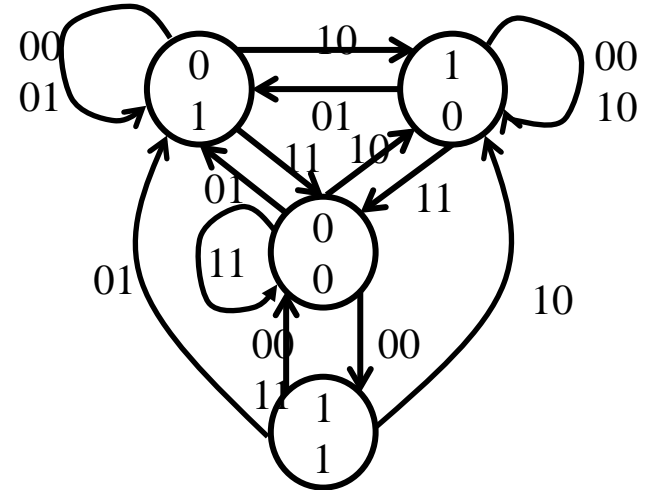

CASES:

SR=01,  $(Q,y) = (0,1)$

SR=10,  $(Q,y) = (1,0)$

SR=11,  $(Q,y) = (0,0)$


SR= 00 => if  $(Q,y) = (0,0)$  or  $(1,1)$ , the output keeps changing

Q. To avoid the SR latch output from toggling or behaving in an undefined way which input combinations should be avoided:

A.  $(S, R) = (0, 0)$



B.  $(S, R) = (1, 1)$

# SR Latch

 

  
# SR Latch Analysis

- $S = 0, R = 0$ : then  $Q = Q_{prev}$  and  $\bar{Q} = \bar{Q}_{prev}$  (**memory!**)



 - $S = 1, R = 1$ : then  $Q = 0$  and  $\bar{Q} = 0$  (**invalid state:  $Q \neq \text{NOT } \bar{Q}$** )



# CASES

SR=01:  $(Q,y) = (0,1)$

SR=10:  $(Q,y) = (1,0)$

SR=11:  $(Q,y) = (0,0)$

SR = 00: if  $(Q,y) = (0,0)$  or  $(1,1)$ , the output keeps changing

Solutions: Avoid the two cases

1) SR = (0,0),

2) SR = (1,1).

State table

|            |   | SR |    |    |    |
|------------|---|----|----|----|----|
|            |   | 00 | 01 | 10 | 11 |
| PS<br>Q(t) | 0 | 0  | 0  | 1  | -  |
|            | 1 | 1  | 0  | 1  | -  |

Characteristic Expression

$$Q(t+1) = S(t) + R'(t)Q(t)$$


Q(t+1) NS (next state)



# SR Latch Symbol

- SR stands for Set/Reset Latch
  - Stores one bit of state ( $Q$ )
- Control what value is being stored with  $S$ ,  $R$  inputs
  - **Set:** Make the output 1 ( $S = 1$ ,  $R = 0$ ,  $Q = 1$ )
  - **Reset:** Make the output 0 ( $S = 0$ ,  $R = 1$ ,  $Q = 0$ )

SR Latch  
Symbol

 


- **Must do something to avoid invalid state (when  $S = R = 1$ )**



# D Latch

- Two inputs:  $CLK$ ,  $D$ 
  - $CLK$ : controls *when* the output changes
  - $D$  (the data input): controls *what* the output changes to
- Function
  - When  $CLK = 1$ ,  $D$  passes through to  $Q$  (the latch is *transparent*)
  - When  $CLK = 0$ ,  $Q$  holds its previous value (the latch is *opaque*)
- Avoids invalid case when  $Q \neq \text{NOT } Q$


D Latch  
Symbol

 

# D Latch Internal Circuit

  


# D Latch Internal Circuit

 

| <i>CLK</i> | <i>D</i> | <i><math>\overline{D}</math></i> | <i>S</i> | <i>R</i> | <i>Q</i> | <i><math>\overline{Q}</math></i> |
|------------|----------|----------------------------------|----------|----------|----------|----------------------------------|
| 0          | X        |                                  |          |          |          |                                  |
| 1          | 0        |                                  |          |          |          |                                  |
| 1          | 1        |                                  |          |          |          |                                  |

# D Latch Internal Circuit

 


| $CLK$ | $D$ | $\overline{D}$ | $S$ | $R$ | $Q$        | $\overline{Q}$        |
|-------|-----|----------------|-----|-----|------------|-----------------------|
| 0     | X   | $\overline{X}$ | 0   | 0   | $Q_{prev}$ | $\overline{Q}_{prev}$ |
| 1     | 0   | 1              | 0   | 1   | 0          | 1                     |
| 1     | 1   | 0              | 1   | 0   | 1          | 0                     |


# D Flip-Flop

- Two inputs:  $CLK$ ,  $D$
- *Function*
  - The flip-flop “samples”  $D$  on the rising edge of  $CLK$ 
    - When  $CLK$  rises from 0 to 1,  $D$  passes through to  $Q$
    - Otherwise,  $Q$  holds its previous value
  - $Q$  changes only on the rising edge of  $CLK$
- A flip-flop is called an *edge-triggered* device because it is activated on the clock edge

D Flip-Flop Symbols

 


# D Flip-Flop Internal Circuit

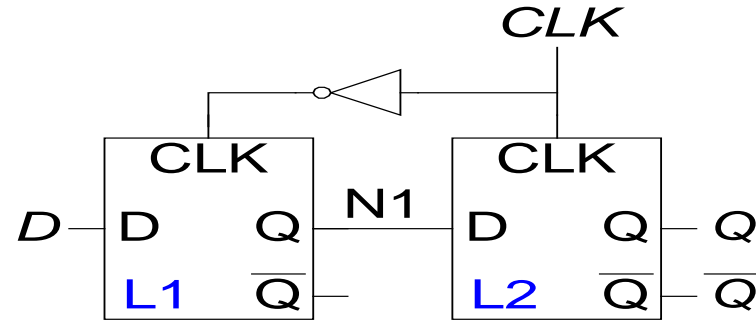



 
# D Flip-Flop Internal Circuit

- Two back-to-back latches (L1 and L2) controlled by complementary clocks
- When  $CLK = 0$ 
  - L1 is transparent, L2 is opaque
  - $D$  passes through to N1
- When  $CLK = 1$ 
  - L2 is transparent, L1 is opaque
  - N1 passes through to  $Q$
- Thus, on the edge of the clock (when  $CLK$  rises from 0 → 1)
  - $D$  passes through to  $Q$








# D Flip-Flop vs. D Latch

   


# D Flip-Flop vs. D Latch

   


# Latch and Flip-flop (two latches)

A latch can be considered as a door

 


CLK = 0, door is shut

 


CLK = 1, door is unlocked


A flip-flop is a two door entrance

 

CLK = 1


 


CLK = 0

 

CLK = 1

# D Flip-Flop (Delay)

  

| Id | D | Q(t) | Q(t+1) |
|----|---|------|--------|
| 0  | 0 | 0    | 0      |
| 1  | 0 | 1    | 0      |
| 2  | 1 | 0    | 1      |
| 3  | 1 | 1    | 1      |

State table

| PS \ D | 0 | 1 |
|--------|---|---|
| 0      | 0 | 1 |
| 1      | 0 | 1 |

← NS = Q(t+1)

Characteristic Expression:  $Q(t+1) = D(t)$


# iClicker

Can D flip-flip serve as a memory component?

A. Yes

B. No

# JK F-F

 


State table

| PS \ JK | 00 | 01 | 10 | 11 |
|---------|----|----|----|----|
| 0       | 0  | 0  | 1  | ?  |
| 1       | 1  | 0  | 1  | ?  |

$Q(t+1)$

# JK F-F

 

State table


| PS \ JK | 00 | 01 | 10 | 11 |
|---------|----|----|----|----|
| 0       | 0  | 0  | 1  | 1  |
| 1       | 1  | 0  | 1  | 0  |

Q(t+1)

Characteristic Expression

$$Q(t+1) = Q(t)K'(t) + Q'(t)J(t)$$

# T Flip-Flop (Toggle)

 

State table

| PS \ T | 0 | 1 |
|--------|---|---|
| 0      | 0 | 1 |
| 1      | 1 | 0 |


← Q(t+1)

Characteristic Expression

$$Q(t+1) = Q'(t)T(t) + Q(t)T'(t)$$


 
# Using a JK F-F to implement a D and T F-F




iClicker

What is the function of the above circuit?

- A. D F-F
- B. T F-F
- C. None of the above

 
# Using a JK F-F to implement a D and T F-F




T flip flop
 
# Rising vs. Falling Edge D Flip-Flop

The triangle means clock input, edge triggered



 Symbol for rising-edge triggered D flip-flop




Internal design:  
Just invert servant clock rather than master

Symbol for falling-edge triggered D flip-flop


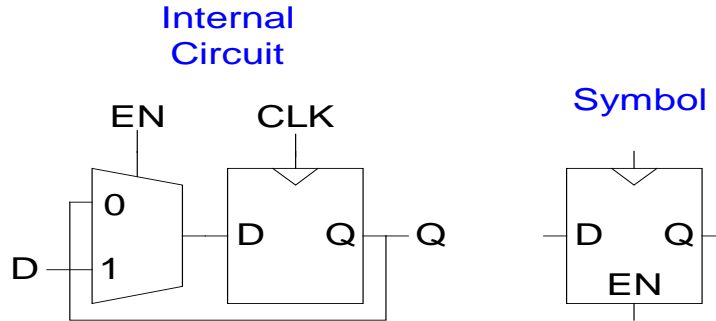
# Enabled D-FFs

- **Inputs:**  $CLK$ ,  $D$ ,  $EN$ 
  - The enable input ( $EN$ ) controls when new data ( $D$ ) is stored
- **Function**
  - $EN = 1$ :  $D$  passes through to  $Q$  on the clock edge
  - $EN = 0$ : the flip-flop retains its previous state



# Resettable Flip-Flops

## Symbols

- **Inputs:**  $CLK$ ,  $D$ ,  $Reset$

- **Function:**


- **$Reset = 1$ :**  $Q$  is forced to 0
- **$Reset = 0$ :** flip-flop behaves as ordinary D flip-flop

- Two types:



- **Synchronous:** resets at the clock edge only
- **Asynchronous:** resets immediately when  $Reset = 1$

- Asynchronously resettable flip-flop requires changing the internal circuitry of the flip-flop




 
- Synchronously resettable flip-flop circuit:



  - There are also synch/asynch settable FFs



# Bit Storage Overview

    


S=1 sets Q to 1, R=1 resets Q to 0. Problem: SR=11 yield undefined Q. We can design outside circuit so SR=11 never happens when C=1. Problem: avoiding SR=11 can be a burden.

SR can't be 11 if D is stable before and while C=1, and will be 11 for only a brief glitch even if D changes while C=1. \*Transition may cross many levels of latches.


Only loads D value present at rising clock edge, so values can't propagate to other flip-flops during same clock cycle. \*Transition happens between two level of flip-flops.
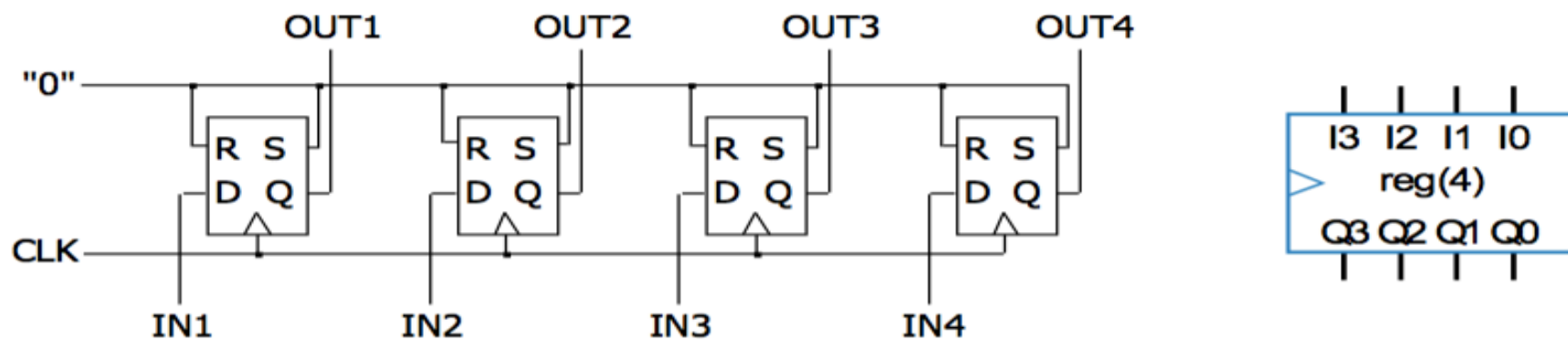
# Building blocks with FFs: Basic Register



# Shift register


- Holds & shifts samples of input

 


 
# Pattern Recognizer

- Combinational function of input samples



# Counters

- Sequences through a fixed set of patterns

