

CSE 140: Components and Design Techniques for Digital Systems

Lecture 9: Sequential Networks: Implementation

CK Cheng

Dept. of Computer Science and Engineering

University of California, San Diego



Implementation

- Format and Tool
- Procedure
- Excitation Tables
- Example

Canonical Form: Mealy and Moore Machines

Mealy Machine: $y_i(t) = f_i(X(t), S(t))$

Moore Machine: $y_i(t) = f_i(S(t))$

 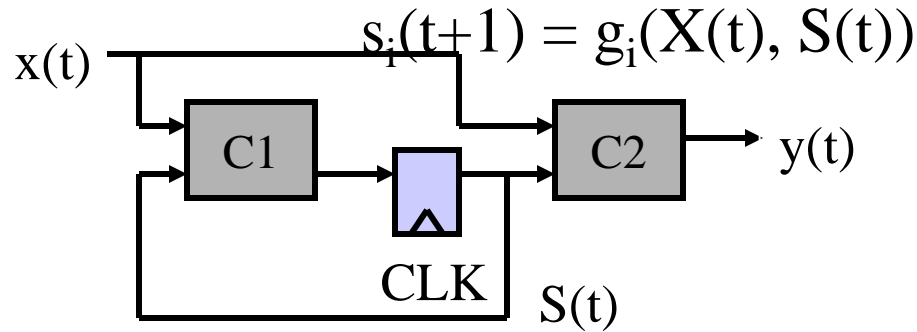

iClicker


In the logic diagram below, a D flip-flop has input x and output y .

A: $x=Q(t)$, $y=Q(t)$


B: $x=Q(t+1)$, $y=Q(t)$

C: $x=Q(t)$, $y=Q(t+1)$

D: None of the above

 

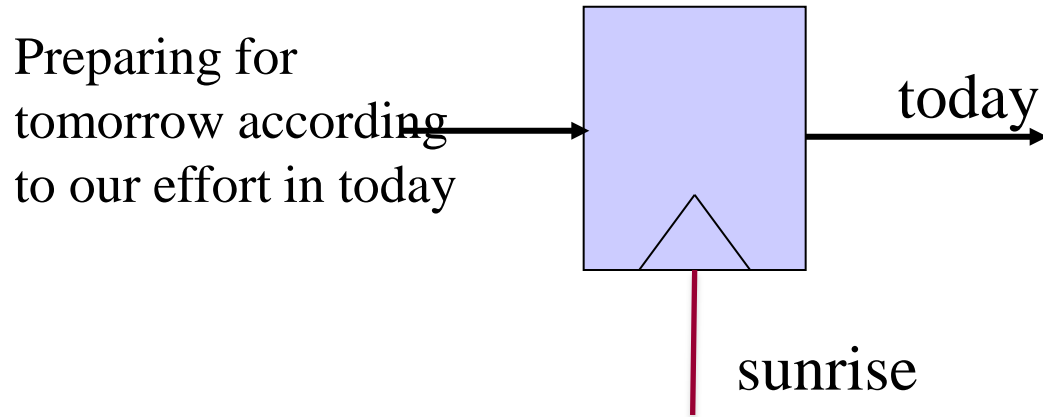Understanding Current State and Next State in a sequential circuit




Implementation Format

Canonical Form: Mealy & Moore machines

State Table \rightarrow Netlist


Tool: Excitation Table

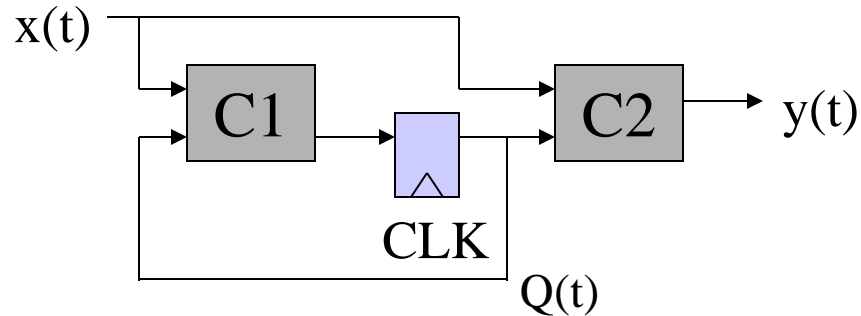

$$Q(t+1) = h(x(t), Q(t)) \quad \text{Circuit C1}$$

$$y(t) = f(x(t), Q(t)) \quad \text{Circuit C2}$$

Implementation Tool: Excitation Table

 

State Table

| id | x(t) | Q(t) | Q(t+1) |
|----|------|------|--------|
| 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |
| 2 | 0 | 0 | 1 |
| 3 | 1 | 1 | 0 |

Find D, T, (S R), (J K) to drive F-Fs


Implementation Tool: Excitation Table

State Table

| id | x(t) | Q(t) | Q(t+1) |
|----|------|------|--------|
| 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |
| 2 | 0 | 1 | 1 |
| 3 | 1 | 1 | 0 |

Excitation Table

| id | x(t) | Q(t) | T(t) | Q(t+1) |
|----|------|------|------|--------|
| 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 |
| 2 | 0 | 1 | 0 | 1 |
| 3 | 1 | 1 | 1 | 0 |

 


Example with T flip flop

Implementation Tool: Excitation Table

Implement combinational logic **C1**

 $D(t)$, $T(t)$, $(S(t) R(t))$, $(J(t) K(t))$ are functions of $(x, Q(t))$



Excitation Table

| id | $x(t)$ | $Q(t)$ | $T(t)$ | $Q(t+1)$ |
|----|--------|--------|--------|----------|
| 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 |
| 2 | 0 | 1 | 0 | 1 |
| 3 | 1 | 1 | 1 | 0 |

Implementation: Procedure

State Table \Rightarrow Excitation Table

Problem: Given a state table, we have

$$\text{NS: } Q(t+1) = h(x(t), Q(t))$$

We find $D, T, (S R), (J K)$ to drive F-Fs from $Q(t)$ to $Q(t+1)$.

Excitation Table: The setting of

$$D(t), T(t), (S(t) R(t)), (J(t) K(t)) \text{ to drive } Q(t) \text{ to } Q(t+1).$$

We implement combinational logic **C1**

$$D(t), T(t), (S(t) R(t)), (J(t) K(t)) \text{ are functions of } (x, Q(t)).$$

Implementation: Procedure

State Table \Rightarrow Excitation Table

Problem: Given a state table, we have

$$\text{NS: } Q(t+1) = h(x(t), Q(t))$$

We find $D, T, (S \ R), (J \ K)$ to drive F-Fs from $Q(t)$ to $Q(t+1)$.

Excitation Table: The setting of

$D(t), T(t), (S(t) \ R(t)), (J(t) \ K(t))$ to drive $Q(t)$ to $Q(t+1)$.

We implement combinational logic **C1**

$D(t), T(t), (S(t) \ R(t)), (J(t) \ K(t))$ are functions of $(x, Q(t))$.

Implementation: Procedure

F-F State Table \Leftrightarrow F-F Excitation Table

| | |
|------------|---------------|
| | DTSRJK |
| PS Q(t) | NS Q(t+1) |

| | |
|------------|---------------|
| | NS Q(t+1) |
| PS Q(t) | DTSRJK |

- D F-F

- $D(t) = e_D(Q(t+1), Q(t))$

- T F-F

- $T(t) = e_T(Q(t+1), Q(t))$

- SR F-F

- $S(t) = e_S(Q(t+1), Q(t))$

- $R(t) = e_R(Q(t+1), Q(t))$

- JK F-F

- $J(t) = e_J(Q(t+1), Q(t))$

- $K(t) = e_K(Q(t+1), Q(t))$

Excitation Table

State table of JK F-F:

| | | | | | | |
|------|---|----|----|----|----|--------|
| | | JK | | | | |
| | | 00 | 01 | 10 | 11 | |
| Q(t) | 0 | 0 | 0 | 1 | 1 | Q(t+1) |
| 1 | 1 | 1 | 0 | 1 | 0 | |

Excitation table of JK F-F:

| | | | | | |
|------|---|----|----|--------|---|
| | | NS | | Q(t+1) | |
| | | 0 | 1 | 0 | 1 |
| PS | 0 | 0- | 1- | | |
| Q(t) | 1 | -1 | -0 | | |
| | | | | JK | |

If Q(t) is 1, and Q(t+1) is 0, then JK needs to be -1.

Excitation Tables and State Tables

Excitation Tables:

SR

| | | | |
|------|---------|--------|---|
| | | Q(t+1) | |
| | PS \ NS | 0 | 1 |
| | 0 | 0- 10 | |
| Q(t) | 1 | 01 -0 | |

T

| | | | |
|------|---------|--------|---|
| | | Q(t+1) | |
| | PS \ NS | 0 | 1 |
| | 0 | 0 1 | |
| Q(t) | 1 | 1 0 | |

State Tables:

SR

| | | | | | |
|------|---------|---------|----|----|----|
| | | Q(t+1) | | | |
| | PS \ SR | 00 | 01 | 10 | 11 |
| | 0 | 0 0 1 - | | | |
| Q(t) | 1 | 1 0 1 - | | | |

T

| | | | |
|------|--------|--------|---|
| | | Q(t+1) | |
| | PS \ T | 0 | 1 |
| | 0 | 0 1 | |
| Q(t) | 1 | 1 0 | |

Excitation Tables and State Tables

Excitation Tables:

JK

| | | Q(t+1) | |
|------|----|--------|-------|
| | | 0 | 1 |
| Q(t) | PS | 0- 1- | |
| | NS | 1 | -1 -0 |

D

| | | Q(t+1) | |
|------|----|--------|---|
| | | 0 | 1 |
| Q(t) | PS | 0 | 1 |
| | NS | 0 | 1 |

State Tables:

JK

| | | Q(t+1) | | | |
|------|----|--------|----|----|----|
| | | 00 | 01 | 10 | 11 |
| Q(t) | PS | 0 | 0 | 1 | 1 |
| | JK | 1 | 1 | 0 | 1 |

D


| | | Q(t+1) | |
|------|----|--------|---|
| | | 0 | 1 |
| Q(t) | PS | 0 | 1 |
| | D | 0 | 1 |

Implementation: Procedure

1. State table: $y(t) = f(Q(t), x(t))$, $Q(t+1) = h(x(t), Q(t))$
2. Excitation table of F-Fs:
 - $D(t) = e_D(Q(t+1), Q(t))$;
 - $T(t) = e_T(Q(t+1), Q(t))$;
 - (S, R), or (J, K)
3. From 1 & 2, we derive excitation table of the system
 - $D(t) = g_D(x(t), Q(t)) = e_D(h(x(t), Q(t)), Q(t))$;
 - $T(t) = g_T(x(t), Q(t)) = e_T(h(x(t), Q(t)), Q(t))$;
 - (S, R) or (J, K).
4. Use K-map to derive optional combinational logic implementation.
 - $D(t) = g_D(x(t), Q(t))$
 - $T(t) = g_T(x(t), Q(t))$
 - $y(t) = f(x(t), Q(t))$

Implementation: Example

Implement a JK F-F with a T F-F

 

Implement a JK F-F: $Q(t+1) = h(J(t), K(t), Q(t)) = J(t)Q'(t) + K'(t)Q(t)$

JK

| PS \ JK | 00 | 01 | 10 | 11 |
|---------|----|----|----|----|
| 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 0 |

Example: Implement a JK flip-flop using a T flip-flop

Excitation Table of T Flip-Flop $T(t) = Q(t) \oplus Q(t+1)$

| | | | | |
|----|---|----|---|---|
| | | NS | | |
| | | 0 | 1 | |
| PS | 0 | 0 | 1 | |
| | 1 | 1 | 0 | T |

Excitation Table of the Design

| id | J(t) | K(t) | Q(t) | Q(t+1) | T(t) |
|----|------|------|------|--------|------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 |
| 2 | 0 | 1 | 0 | 0 | 0 |
| 3 | 0 | 1 | 1 | 0 | 1 |
| 4 | 1 | 0 | 0 | 1 | 1 |
| 5 | 1 | 0 | 1 | 1 | 0 |
| 6 | 1 | 1 | 0 | 1 | 1 |
| 7 | 1 | 1 | 1 | 0 | 1 |


$$T(t) = Q(t) \text{ XOR } (J(t)Q'(t) + K'(t)Q(t))$$

Example: Implement a JK flip-flop using a T flip-flop

T(J,K,Q):

| | | | | |
|------|---|---|---|---|
| | K | | | |
| | 0 | 0 | 1 | 1 |
| Q(t) | 0 | 1 | 1 | 0 |
| | J | | | |

$$T = K(t)Q(t) + J(t)Q'(t)$$

 


iClicker

Given a flip-flop, the relation of its state table and excitation table is

 - A. One to one
- B. One to many
- C. Many to one
- D. Many to many
- E. None of the above


Let's implement our free running 2-bit counter using T-flip flops



State Table

| PS | Next state |
|-------|------------|
| S_0 | S_1 |
| S_1 | S_2 |
| S_2 | S_3 |
| S_3 | S_0 |

 Let's implement our free running 2-bit counter using T-flip flops



State Table

| | |
|-------|-------|
| S_0 | S_1 |
| S_1 | S_2 |
| S_2 | S_3 |
| S_3 | S_0 |

State Table with Assigned Encoding

| Current | Next |
|---------|------|
| 0 0 | 01 |
| 0 1 | 10 |
| 1 0 | 11 |
| 1 1 | 00 |

Let's implement our free running 2-bit counter using T-flip flops

Excitation table

| id | $Q_1(t)$ | $Q_0(t)$ | $T_1(t)$ | $T_0(t)$ | $Q_1(t+1)$ | $Q_0(t+1)$ |
|----|----------|----------|----------|----------|------------|------------|
| 0 | 0 | 0 | | | 0 | 1 |
| 1 | 0 | 1 | | | 1 | 0 |
| 2 | 1 | 0 | | | 1 | 1 |
| 3 | 1 | 1 | | | 0 | 0 |

Let's implement our free running 2-bit counter using T-flip flops

Excitation table

| id | $Q_1(t)$ | $Q_0(t)$ | $T_1(t)$ | $T_0(t)$ | $Q_1(t+1)$ | $Q_0(t+1)$ |
|----|----------|----------|----------|----------|------------|------------|
| 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| 2 | 1 | 0 | 0 | 1 | 1 | 1 |
| 3 | 1 | 1 | 1 | 1 | 0 | 0 |

Let's implement our free running 2-bit counter using T-flip flops

Excitation table

| id | $Q_1(t)$ | $Q_0(t)$ | $T_1(t)$ | $T_0(t)$ | $Q_1(t+1)$ | $Q_0(t+1)$ |
|----|----------|----------|----------|----------|------------|------------|
| 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| 2 | 1 | 0 | 0 | 1 | 1 | 1 |
| 3 | 1 | 1 | 1 | 1 | 0 | 0 |

$$T_0(t) =$$

$$T_1(t) =$$

$$Q_0(t+1) = T_0(t) Q'_0(t) + T'_0(t) Q_0(t)$$

$$Q_1(t+1) = T_1(t) Q'_1(t) + T'_1(t) Q_1(t)$$

Let's implement our free running 2-bit counter using T-flip flops


Excitation table

| id | $Q_1(t)$ | $Q_0(t)$ | $T_1(t)$ | $T_0(t)$ | $Q_1(t+1)$ | $Q_0(t+1)$ |
|----|----------|----------|----------|----------|------------|------------|
| 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| 2 | 1 | 0 | 0 | 1 | 1 | 1 |
| 3 | 1 | 1 | 1 | 1 | 0 | 0 |

$$T_0(t) = 1$$

$$T_1(t) = Q_0(t)$$

Free running counter with T flip flops

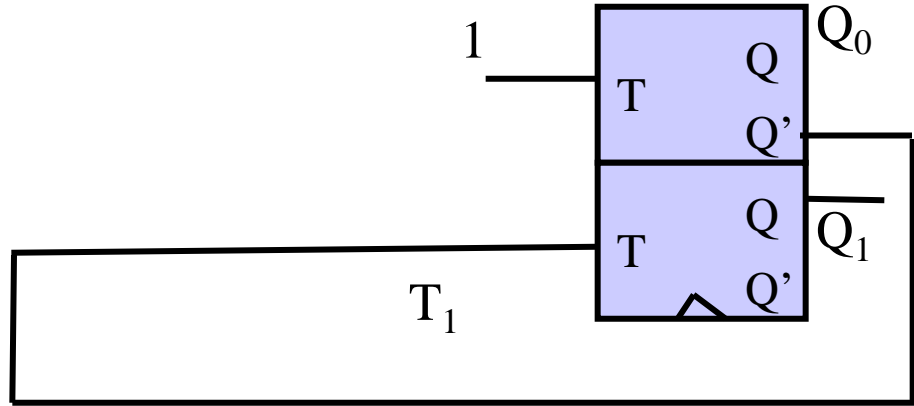

$$T_0(t) = 1$$

$$T_1(t) = Q_0(t)$$

Summary: Implementation

- Set up canonical form
 - Mealy or Moore machine
- Identify the next states
 - state diagram \Leftrightarrow state table
 - state assignment
- Derive excitation table
 - Inputs of flip flops
- Design the combinational logic
 - don't care set utilization