

Quiz 1


Name: _____
GTID: _____

1. Design an ALU that performs the following operations. Please show the block diagram of the ALU first and then implement the ALU with Verilog. A and B are 8-bits 2's complement signed values:

A + B
A - B
- A
! A
A & B
A | B
A ^ B
A >> 1


Answer:

```
module Alu (sel, A, B, Cout, Z);  
  
    input        [2:0] sel;  
    input signed [7:0] A, B;  
    output reg   Cout;  
    output reg   [7:0] Z;  
  
    always @(sel, A, B)  
    begin  
        case(sel)  
            3'b000: {Cout, Z}    <= A + B;  
            3'b001: {Cout, Z}    <= A - B;  
            3'b010: Z            <= ~A + 1;  
            3'b011: Z            <= ~A;  
            3'b100: Z            <= A & B;  
            3'b101: Z            <= A | B;  
            3'b110: Z            <= A ^ B;  
            3'b111: Z            <= A >> 1;  
        endcase  
    end  
endmodule
```

 

2. Please design a circuit that detects the 1011 sequence. Show the state machine and implement the sequence detector in Verilog.

Answer:

 

```

module detector(clk, rst, x, z);

    input clk;
    input rst;
    input x;
    output z;

    reg [2:0] state;

    parameter start      = 3'b000;
    parameter got1       = 3'b001;
    parameter got10      = 3'b010;
    parameter got101     = 3'b011;
    parameter got1011    = 3'b100;

    always @(posedge clk)
    begin
        if(rst)
            begin
                state <= start;
            end
        else
            begin
                case (state)
                    start: begin
                        if(x) state <= got1;
                        else state <= start;
                    end
                    got1: begin
                        if(x) state <= got1;
                        else state <= got10;
                    end
                    got10: begin
                        if(x) state <= got101;
                        else state <= start;
                    end
                    got101: begin
                        if(x) state <= got1011;
                        else state <= got10;
                    end
                    got1011: begin
                        if(x) state <= got1;
                        else state <= got10;
                    end
                endcase
            end
        end
        assign z = (state == got1011);
    endmodule
  
```

3. Write Verilog code to implement an SRAM memory containing 512 entries. Each entry is a 32-bit value. The reads and writes are synchronized with the positive edge of the clock. Your design should include the following inputs and outputs:

- Data_in
- Data_out
- Address
- Rw_enable
- Clk

Answer:

```
module sram(Clk, Rw_enable, Address, Data_in, Data_out);

    parameter        BIT_WIDTH = 32;
    parameter        ADDR_SIZE = 9;

    input            Clk;
    input            Rw_enable;
    input            [ADDR_SIZE-1:0] Address;
    input            [BIT_WIDTH-1:0] Data_in;
    output reg       [BIT_WIDTH-1:0] Data_out;

    reg              [BIT_WIDTH-1:0] mem [0:(1<<ADDR_SIZE)-1];

    always @(posedge Clk)
    begin
        if(Rw_enable) // write
        begin
            mem[Address] <= Data_in;
        end
        else // read
        begin
            Data_out <= mem[Address];
        end
    end
endmodule
```